

# Phase-Locked Loops

Ching-Yuan Yang



National Chung-Hsing University  
Department of Electrical Engineering


## Overview

- Main Readings
  - B. Razavi, Chapter 15 of *Design of Analog CMOS Integrated Circuit*, 2002.
  - Cicero S. Vaucher, Chapter 2 of *Architectures for RF Frequency Synthesizers*, 2002
  - Dean Banerjee, *PLL Performance, Simulation, and Design*.
- Outline
  - Simple Phase-Locked Loops
  - Charge-Pump Phase-Locked Loops
  - Nonideal Effects in PLLs
  - Jitter/Noise in PLLs
  - Applications of PLLs
  - Behavior Simulation


# Simple Phase-Locked Loops

## Why phase-lock ?


### - Jitter Suppression

 


### - Skew Reduction

 


### - Frequency Synthesis

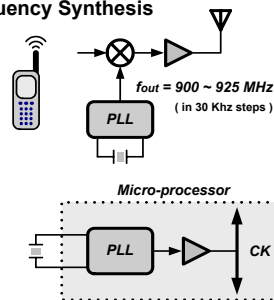

### - Clock Recovery

 

## What is PLL ?

 

- Operates on excess phase of  $x(t)$  and  $y(t)$ .
- Feedback system with PD as an error amplifier.
- “Locked” when phase difference between input and output is constant with time.


## History of PLL

- First PLL: 1932 by de Bellesize, Coherent communication
- First PLL IC: 1965, purely analog (Linear PLL)
- First Digital PLL: around 1970 (using Digital Phase Detector)
- All Digital PLL: Digital Filters, NCO (Numerically Controlled Oscillator), ...
- Software PLL: Using DSP
- 1990s: Most of the PLL is Charge Pump PLL

## Terminology

- Locking  
When VCO output is in phase as well as in frequency with the reference input signal
- Lock Range  
Input frequency range over which the loop can maintain locking
- Capture Range  
Input frequency range onto which the loop can lock
- Free Running Frequency  
VCO running frequency when no input applied
- Acquisition Time: Pull-in time + Settling time  
Time required for the PLL to lock itself on to the reference clock
- Phase Offset or Phase Error (Steady State)  
When PLL is locked, the phase difference between input and output


## Phase detector

 


- A phase detector is a circuit whose average output,  $\overline{V_{out}}$ , is linearly proportional to the phase difference,  $\Delta\phi$ , between its two inputs.
- In the ideal case, the relationship between  $\overline{V_{out}}$  and  $\Delta\phi$  is linear, crossing the origin for  $\Delta\phi = 0$ .
- The operation of phase detectors is similar to that of differential amplifiers in that both sense the *difference* between the two inputs, generating a proportional output.
- Gain  $K_{PD}$ : the slope of the line, is expressed in V/rad.
 
## Phase detector : Multiplier



- Phase Detector using Analog Multiplier
- Gilbert multiplier
  - ❑ Output voltage dependent on the input signal amplitudes
  - ❑ Narrow linear range (Narrow lock range)
  - ❑ Cannot discriminate frequency difference


 
$$\overline{V_d} = V_{dm} \sin(\theta_e) + V_{offset}$$








## Phase detector : XOR

  

$$V_{out} = 2 \cdot V_0 \cdot \frac{\Delta\phi}{2\pi} = \frac{V_0}{\pi} \cdot \Delta\phi$$

     
$$K_{PD} = \frac{V_0}{\pi} \text{ independent of the input frequency}$$



## Phase detector : XOR (cont'd)

- When locked, the phase difference is 90 degree
- Output voltage *independent* on the input signal amplitudes
- Output voltage *dependent* on the input duty cycles
- Narrow linear range (Narrow lock range)  $\Rightarrow \pm \pi/2$
- Cannot discriminate frequency difference
- Use for Data/Clock Recovery PLL: input noise dominant
  - Hybrid PLL (Analog PLL + Digital PLL)
- *No Dead Zone*

## Voltage-controlled oscillators (VCOs)

 


An ideal VCO is a circuit whose output frequency is a linear function of its control voltage:

$$\omega_{out} = \omega_0 + K_{VCO} V_{cont}$$


- $\omega_0$  represents the intercept corresponding to  $V_{cont} = 0$ .
- $K_{VCO}$  denotes the *gain* or *sensitivity* of the circuit (expressed in rad/s/V).
- The achievable range,  $\omega_2 - \omega_1$ , is called the *tuning range*.

## Basic PLL topology

- Two waveforms with a skew

 

 - Change of VCO frequency to eliminate the skew



PLL ICs

1-12

Ching-Yuan Yang / EE, NCHU

## Discussion

- To vary the phase, we *must* vary the frequency and allow the integration


$$\phi = \int (\omega_0 + K_{VCO} V_{cont}) dt \quad \text{to take place.}$$

⇒ Phase alignment can be achieved only by a (temporary) frequency change.

- The output phase of a VCO can be aligned with the phase of a reference if
  - the frequency of the VCO is changed momentarily,
  - a phase detector is used to determine when the VCO and reference signals are aligned.
- Phase locking* is a task of aligning the output phase of the VCO with the phase of the reference.

 
## Basic PLL topology (cont'd)

- Feedback loop comparing input and output phases



- The PD compares the phases of  $V_{out}$  and  $V_{in}$ , generating an error that varies the VCO frequency until the phases are aligned, i.e., the loop is locked.
- The topology must be modified because
  - the PD output,  $V_{PD}$ , consists of a dc component (desirable) and high frequency components (undesirable),
  - the control voltage of the oscillator must remain quiet in the steady state, i.e., the PD output must be filtered.

- Simple PLL

 


- A low-pass filter is interposed between the PD and the VCO, suppressing the high-frequency components of the PD output and presenting the dc level to the oscillator.
- The feedback loop compares the phases of the input and output. If the loop gain is large enough, the difference between the input phase,  $\phi_{in}$ , and the output phase,  $\phi_{out}$ , falls to a small value in the steady state, providing phase alignment
- Phase lock condition:  $\phi_{out} - \phi_{in}$  is constant and preferably small.

$$\frac{d\phi_{out}}{dt} - \frac{d\phi_{in}}{dt} = 0 \quad \Leftrightarrow \quad \omega_{out} = \omega_{in}$$

When locked, a PLL produces an output that has a small phase error with respect to the input but exactly the same frequency.



## PLL waveforms in locked condition

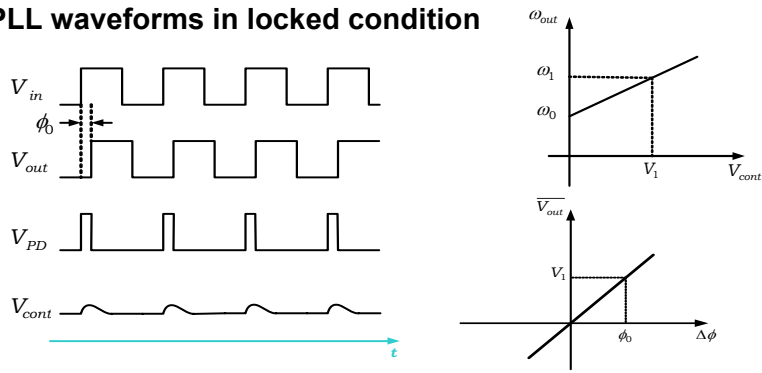

- If the input and output frequencies are equal to  $\omega_1$ , then the required oscillator control voltage is unique  $V_1$ . Since  $\omega_{out} = \omega_0 + K_{VCO} V_{cont}$  and , we can write


$$V_1 = \frac{\omega_1 - \omega_0}{K_{VCO}} \quad \text{and} \quad \phi_0 = \frac{V_1}{K_{PD}} = \frac{\omega_1 - \omega_0}{K_{PD} K_{VCO}}$$

- It reveals two important points:
  - ▢ as the input frequency of the PLL varies, so does the phase error,
  - ▢ to minimize the phase error,  $K_{PD} K_{VCO}$  must be maximized.

 
## PLL waveforms in locked condition (cont'd)

- Nonlinear PD


If the frequency is high enough ( $= \omega_X$ ) to mandate  $V_{cont} = V_0$ , then the PD must operate at the peak of its characteristic. However, the PD gain drops to zero here and feedback loop fails. Thus, the circuit cannot lock if  $\omega_{in} = \omega_X$ .



 - Drift of data with respect to clock in the presence of small frequency error





- Frequency-locked loop


 


The frequency detector (FD) would suffer from a finite difference between  $\omega_{in}$  and  $\omega_{out}$  due to various mismatches and other nonidealities.


## Response of a PLL to a phase step

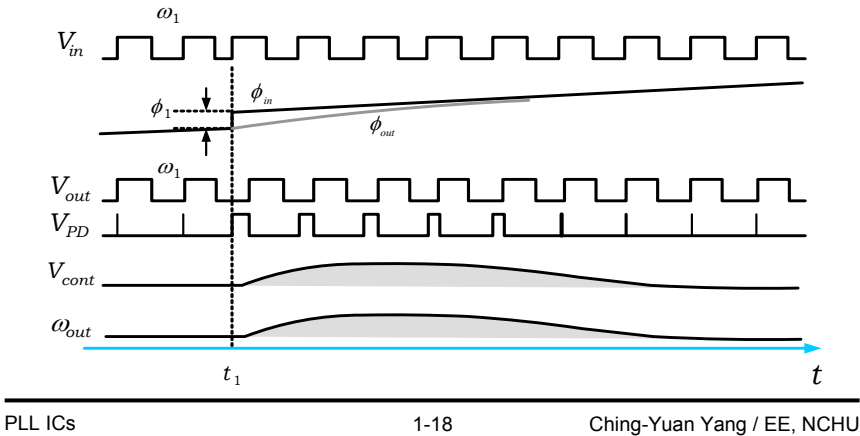 

## Response of a PLL to a frequency step

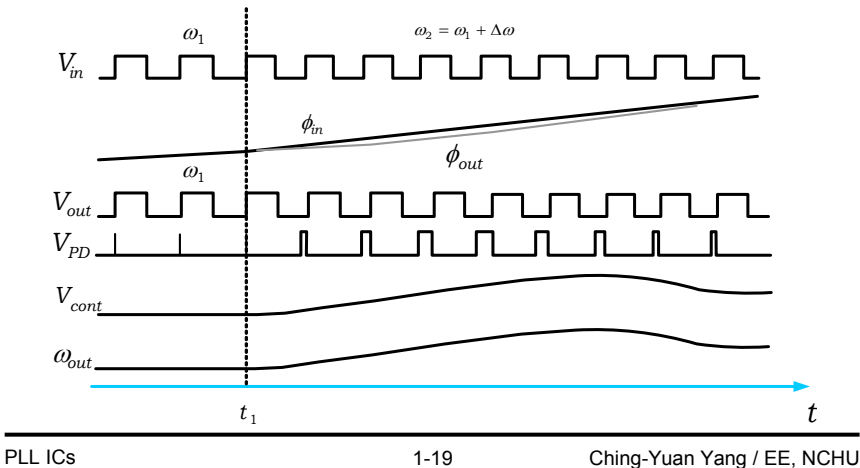 


## Example of phase step response

 

- The control voltage of the oscillator can serve as a suitable test point in analysis of PLLs.  
While it is difficult to measure the time variations of phase and frequency,  $V_{cont} (= V_{LPF})$  can be readily monitored in simulations and measurements.
- The state of the loop:
  - At  $t = t_2$ , the output frequency is equal to its final value but the loop continues the transient because the phase error deviates from the required value.
  - At  $t = t_3$ , the phase error is equal to its final value but the output frequency is not.
 For the loop to settle, both the phase and the frequency must settle to proper values.

## Linear model of type I PLL

 

- The open-loop transfer function is given by

$$H(s)|_{\text{open}} = \frac{\phi_{\text{out}}(s)}{\phi_{\text{in}}(s)}|_{\text{open}} = K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$

revealing the poles at  $s = -\omega_{LPF}$  and  $s = 0$ .

Since the loop gain contains a pole at the origin, the system is called "type I."

- Owing to the pole at the origin, the loop gain goes to infinity as  $s$  approaches to zero. Thus, the PLL ensures that the change in  $\phi_{\text{out}}$  is exactly equal the change in  $\phi_{\text{in}}$  as  $s$  goes to zero

- The closed-loop transfer function can be written as

$$H(s)|_{\text{close}} = \frac{\phi_{\text{out}}(s)}{\phi_{\text{in}}(s)}|_{\text{close}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}^2} + s + K_{PD}K_{VCO}} = \frac{\omega_{\text{out}}(s)}{\omega_{\text{in}}(s)}$$

If  $s \rightarrow 0$ ,  $H(s) \rightarrow 1$  because the infinite loop gain.

Since the loop gain contains a pole at the origin, the system is called "type I."

- Since a change in  $\omega_{\text{out}}$  must be accompanied by a

change in  $V_{\text{cont}}$ , we have  $H(s) = K_{VCO} \cdot \frac{V_{\text{cont}}(s)}{\omega_{\text{in}}(s)}$

The response of  $V_{\text{cont}}$  to variations in  $\omega_{\text{in}}$  indeed yields the response of the close-loop system.

## Linear model of type I PLL (cont'd)

- 2<sup>nd</sup> order transfer function: 
$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

where natural frequency  $\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}}$  and damping ratio  $\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$

- The two poles of the closed-loop system are given by

$$s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2} = (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$$

➤ If  $\zeta > 1$ , the system is overdamped.

➤ If  $\zeta < 1$ , the pole are complex, the system is underdamped and the response to an input frequency step  $\omega_{in} = \Delta\omega u(t)$  is equal to


$$\omega_{out} = \left[ 1 - \frac{1}{\sqrt{1 - \zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1 - \zeta^2} t + \theta) \right] \Delta\omega u(t)$$

where  $\omega_{out}$  denotes the change in the output frequency

$$\text{and } \theta = \sin^{-1} \sqrt{1 - \zeta^2}$$

The step response contains a sinusoidal component

 with a frequency  $\sqrt{1 - \zeta^2}$  that decays with a time constant  $(\zeta\omega_n)^{-1}$ .




## Linear model of type I PLL (cont'd)

- Settling speed of PLLs: The exponential decay determines how fast the output approaches its final value, implying that  $\zeta\omega_n$  must be maximized. For the type I PLL,

$$\text{we have } \zeta\omega_n = \frac{1}{2}\omega_{LPF}$$

□ It reveals a critical trade-off between the settling speed and the ripple on the VCO control line: the lower  $\omega_{LPF}$  the greater the suppression of the high-frequency components produced by the PD but the longer the settling time constant.

- Underdamped response:

 

□ 900 MHz PLL:

$$\omega_{LPF} = 2\pi \cdot (20 \text{ KHz}),$$

$$f_{out} = 901 \text{ MHz} \rightarrow 901.2 \text{ MHz},$$


how long does the PLL output frequency take to settle within 100Hz of its final value?

In the worst case, we have


$$e^{-\zeta\omega_n t_s} \approx \frac{100 \text{ Hz}}{200 \text{ KHz}} \Rightarrow t_s = 0.12 \text{ ms}$$

## Linear model of type I PLL (cont'd)

- Bode plots

 


- Root locus

 


## Charge-Pump Phase-Locked Loops

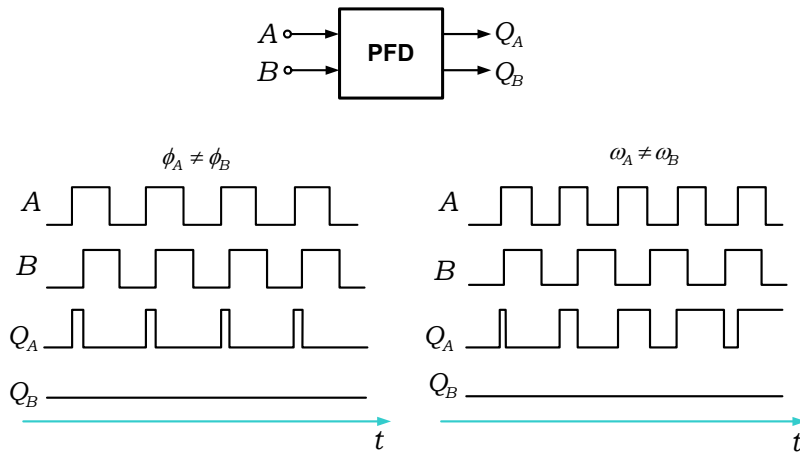
## Conceptual operation of a phase-frequency detector (PFD)




## Phase detector : PFD – three-state PD

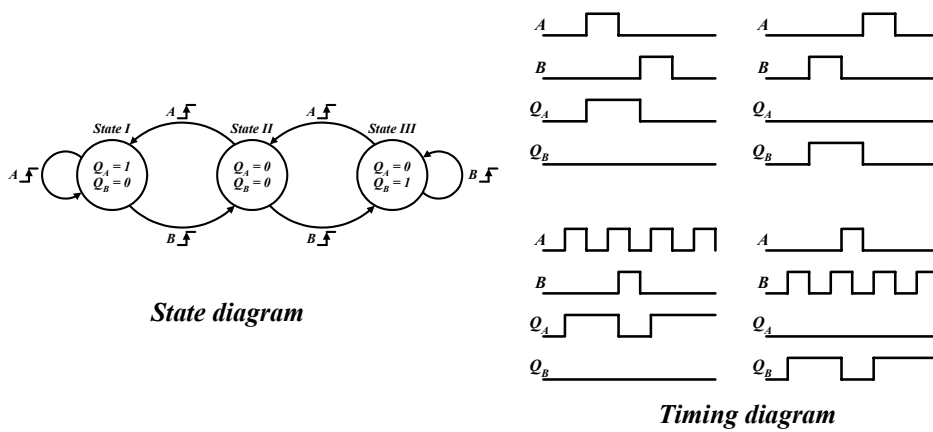


## - Implementation of PFD

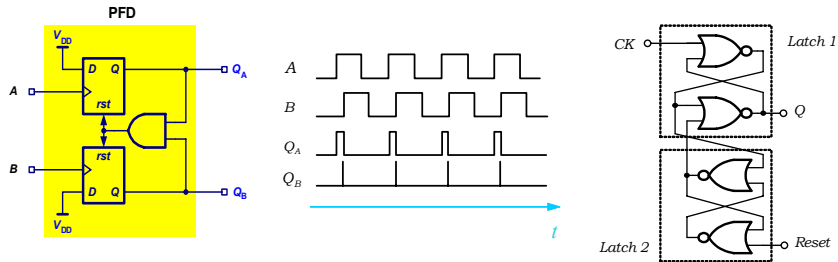

Input-output characteristic:

 


PFD followed by low-pass filters:

 


## - Phase detector : PFD

- When locked, the phase difference is 0 degree
- Output voltage *independent* on the input signal amplitudes
- Output voltage *independent* on the input duty cycles
- Wide linear range (Wide lock range)  $\Rightarrow \pm 2\pi$
- Discriminate frequency difference
- Use carefully for Data/Clock Recovery PLL
  - Hybrid PLL (Analog PLL + Digital PLL)
- *Dead Zone problem*
  - Due to finite gate delay
  - Introduce large jitter or poor phase noise
 
## - The width of the narrow reset pulses




## - Dynamic CMOS PFD

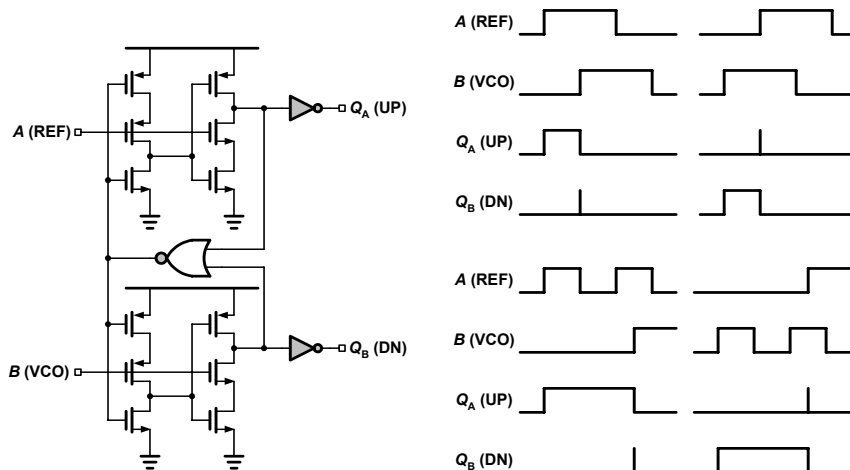



## Charge-pump PLL

 

### Why charge pump PLL ?


#### ● Advantages

- ❑ No active component for zero steady state phase error
- ❑ Large frequency and phase capture range
- ❑ Digital output (full CMOS swing)
- ❑ Simple and robust design
- ❑ Discrete time analysis


#### ● Disadvantages

- ❑ Slow comparing with analog PLL
- ❑ May create dead zone problem
- ❑ Noisy

## PFD with charge pump

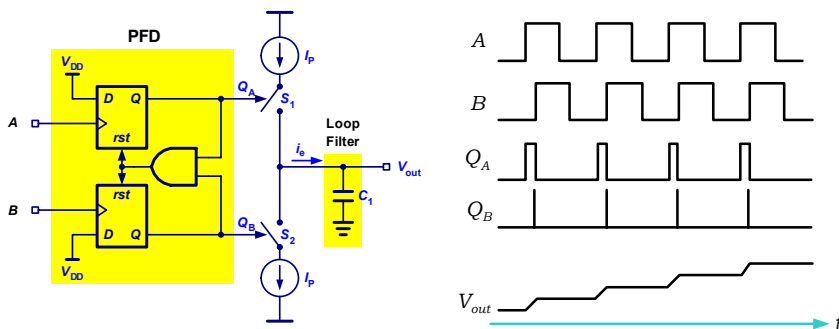


## Simple charge-pump PLL (Type II PLL)

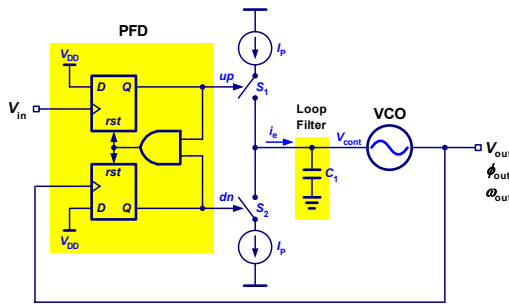


### Operation

- ① When the loop is turned on,  $\omega_{out}$  may be far from  $\omega_{in}$ , and the PFD and the charge pump vary the control voltage such that  $\omega_{out}$  approaches to  $\omega_{in}$ .
  - ② When  $\omega_{out}$  and  $\omega_{in}$  are sufficiently close, the PFD operates as a phase detector, performing phase lock.
- ③ The loop locks when the phase difference drops to zero and the charge pump remains relatively idle.
    - If  $V_{cont}$  remains constant for a long time, the VCO frequency and phase begin to drift. The PFD then detects the phase difference, producing a corrective pulse on  $up$  and  $dn$  that adjusts the VCO frequency through the charge pump and the filter.
    - Since phase comparison is performed in every cycle, the VCO phase and frequency cannot drift substantially.
  - In locked condition, the gain of the PFD/CP combination is infinite, i.e., a nonzero (deterministic) difference between  $\phi_{in}$  and  $\phi_{out}$  leads to indefinite charge buildup on  $C_1$ . Therefore, the input phase error must be exactly zero.

## Linearity of PFD/CP/LPF combination

 

### Step response:

 

- The system is not linear in the strict sense.

We approximate a discrete-time system by a continuous-time model.


- Approximated by a ramp,  $\Delta\phi = \phi_0 u(t)$

$$V_{out}(t) = \frac{I_P}{2\pi C_1} t \cdot \phi_0 u(t)$$

$$\Rightarrow \text{transfer function } \frac{V_{out}}{\Delta\phi}(s) = \frac{I_P}{2\pi C_1} \cdot \frac{1}{s}$$

- It contains a pole at the origin.
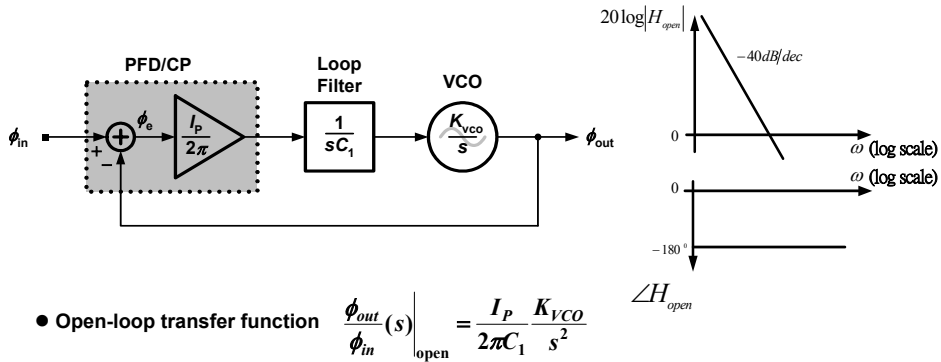
## Linear model of simple charge-pump PLL




Since the loop gain has two poles at the origin, this topology is called a “type II” PLL.

• Closed-loop transfer function 
$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_1}}{s^2 + \frac{I_P K_{VCO}}{2\pi C_1}}$$

It contains two imaginary poles at  $s_{1,2} = \pm j\sqrt{I_P K_{VCO} / (2\pi C_1)}$  and is unstable.

## Addition of zero to charge-pump PLL

 


• Open-loop transfer function  $\left. \frac{\phi_{out}}{\phi_{in}}(s) \right|_{open} = \frac{I_P}{2\pi} \left( R_1 + \frac{1}{C_1 s} \right) \frac{K_{VCO}}{s} \Rightarrow \text{a zero at } s_z = -1/(R_1 C_1).$

• Closed-loop transfer function 
$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_1} (R_1 C_1 s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_1 s + \frac{I_P}{2\pi C_1} K_{VCO}}$$

$\Rightarrow \omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_1}}, \quad \zeta = \frac{R_1}{2} \sqrt{\frac{I_P C_1 K_{VCO}}{2\pi}} \quad \text{and decay time constant } \frac{1}{\zeta \omega_n} = \frac{4\pi}{R_1 I_1 K_{VCO}}$
 
## Stability degradation of charge-pump PLL



## Stability limit and overload limit

In fact, the elegant way to determine the stability limit in the charge pump PLL is to linearize a set of difference equations, to transform it into the  $z$ -domain, and to apply the stability criterion on it.

- Normalize PLL parameters:

- ① the normalized loop gain  $K_N = I_p R_1 K_{vco} T / 2\pi$
- ② the normalized loop filter  $\tau_{1N} = R_1 C_1 / T$
- ③ the normalized natural frequency  $F_N = f_n / f_i = f_n T$


$$\Rightarrow F_N = \frac{1}{2\pi} \sqrt{\frac{K_N}{\tau_{1N}}} \quad \zeta = \frac{\sqrt{K_N \tau_{1N}}}{2}$$

Stability limit condition:


$$K_N < \frac{2}{1 + \frac{1}{2\tau_{1N}}} \quad \Rightarrow \quad F_N < \frac{\sqrt{1 + \zeta^2} - \zeta}{\pi}$$

VCO overload limit:
 
$$V_{cont} = \frac{f_i}{K_{vco}} - I_p R_1 > 0 \quad \Rightarrow \quad K_N < 1 \quad \Rightarrow \quad F_N < \frac{1}{4\pi\zeta}$$



## Compensated type II PLL

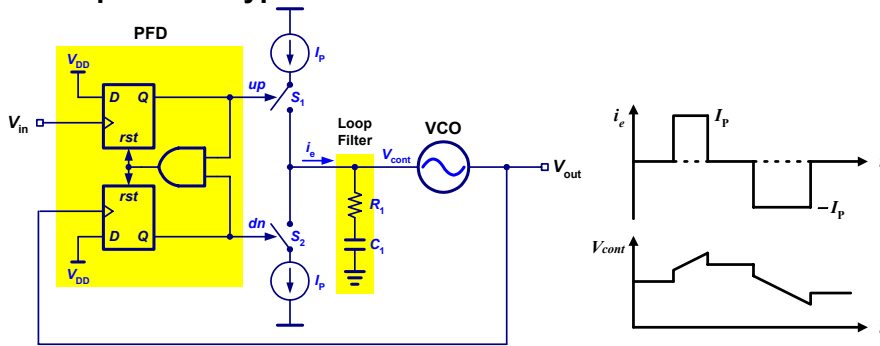

Critical drawback :


- In the charge pump drives the series combination of  $R_p$  and  $C_p$ , each time a current is injected into the loop filter, the control voltage experiences a large jump.
- In lock condition, the mismatches between  $I_1$  and  $I_2$  and charge injection and clock feedthrough of  $S_1$  and  $S_2$  introduce voltage jumps in  $V_{cont}$ .

⇒ The resulting ripple severely disturbs the VCO, corrupting the output phase.

## Design flow of 2<sup>nd</sup>-order PLLs

- 1 Determine  $K_{VCO}$ .
- 2 Choose the natural frequency  $\omega_n$  to be about or less than one-tenth of the input frequency.
- 3 Select  $I_p$ , to meet the reasonable trade-off between the value the filter components (i.e., chip area) and the pump current.
- 4 Set the damping factor  $\zeta$  to be 0.707.
- 5 Calculate  $R_p$  and  $C_p$ .

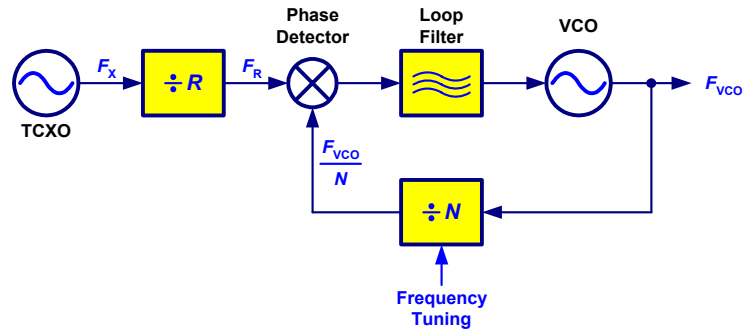
## PLL frequency synthesizer using dividers



TCXO: Temperature Compensated  
Crystal Oscillator  
VCO: Voltage Controlled Oscillator

*In the locked state:*  
 $F_{vco} = N \times F_R, N \in \mathbb{N}$   
 $F_{vco} / N = F_x / R = F_R$
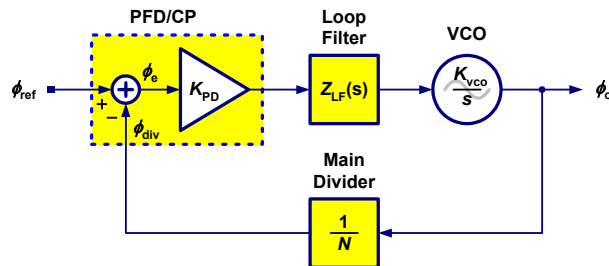
## Linear model of 3<sup>rd</sup>-order PLLs with 2<sup>nd</sup>-order loop filter



PLL phase transfer functions:


Forward-loop gain  $G(s) = \frac{\theta_o}{\theta_e} = \frac{K_{PD} Z_{LF}(s) K_{vco}}{s}$

Reverse-loop gain  $\beta(s) = \frac{\theta_{div}}{\theta_o} = \frac{1}{N}$

Open-loop gain  $\beta(s)G(s) = \frac{\theta_{div}}{\theta_e} = \frac{K_{PD} Z_{LF}(s) K_{vco}}{Ns}$

Closed-loop gain  $\frac{\theta_o}{\theta_{ref}} = \frac{G(s)}{1 + \beta(s)G(s)}$

## - 2<sup>nd</sup>-order passive filter

 


(Addition of  $C_2$  to reduce ripple on the control line.)

$$Z_{LF}(s) = \frac{k}{s} \cdot \frac{1+s\tau_z}{1+s\tau_p} = \frac{k}{s} \cdot \frac{1+s\tau_z}{1+s\tau_z/b}$$

$$Z_{LF1}(s) = \frac{1+sR_1C_1}{s^2R_1C_1C_2+s(C_1+C_2)} = \frac{1+s\tau_z}{s(C_1+C_2)(1+s\tau_p)}$$

Parameters	Loop Filter 1	Loop Filter 2
$\tau_z$	$R_1 C_1$	$R_1 (C_1 + C_2)$
$\tau_p$	$R_1 \left( \frac{C_1 C_2}{C_1 + C_2} \right)$	$R_1 C_2$
$k$	$\left( \frac{b-1}{b} \right) \cdot \frac{1}{C_1}$	$\frac{1}{C_1}$
$b = \frac{\tau_z}{\tau_p}$	$1 + \frac{C_1}{C_2}$	$1 + \frac{C_1}{C_2}$

 


$$Z_{LF2}(s) = \frac{1+sR_1(C_1+C_2)}{sC_1(1+sR_1C_2)}$$

## - Open-loop bandwidth $\omega_c$ and phase margin $\phi_m$

Open-loop gain  $\beta(s)G(s) = \frac{\theta_{div}}{\theta_e} = \frac{K_{PD}Z_{LF}(s)K_{VCO}}{Ns} = \frac{I_P \cdot K_{VCO} \cdot k}{2\pi \cdot N \cdot s^2} \cdot \frac{1+s\tau_z}{1+s\tau_p}$

$$\Rightarrow \beta(s)G(s)|_{s=j\omega} = -\frac{I_P \cdot K_{VCO} \cdot k}{2\pi \cdot N \cdot \omega^2} \cdot \frac{1+j\omega\tau_z}{1+j\omega\tau_p}$$
 
$$\phi(\omega) = \tan^{-1}(\omega \cdot \tau_z) - \tan^{-1}(\omega \cdot \tau_p) + 180^\circ$$



$$\phi_{m,max}: \frac{d\phi}{d\omega} = \frac{\tau_z}{1+(\omega \cdot \tau_z)^2} - \frac{\tau_p}{1+(\omega \cdot \tau_p)^2} = 0$$

$$\Rightarrow \omega_c = \frac{1}{\sqrt{\tau_z \cdot \tau_p}}$$

$$\text{and } \phi_{m,max} = \tan^{-1}\left(\frac{\tau_z - \tau_p}{2\sqrt{\tau_z \cdot \tau_p}}\right) = \tan^{-1}\left(\frac{b-1}{2\sqrt{b}}\right)$$

- If the loop bandwidth  $\omega_c$  and the phase margin  $\phi_m$  are specified, we have

$$b = \frac{1}{\left(-\tan \phi_m + \frac{1}{\cos \phi_m}\right)^2}$$

and  $\tau_z = \frac{\sqrt{b}}{\omega_c}$   $\tau_p = \frac{1}{\sqrt{b} \cdot \omega_c}$

For loop filter 1:

$$\omega_c = \frac{I_p K_{vco}}{2\pi \cdot N} R_1 \frac{b-1}{b} = \frac{I_p K_{vco}}{2\pi \cdot N} R_1 \frac{C_1}{C_1 + C_2}$$

$$R_1 = \frac{2\pi \cdot N \cdot \omega_c}{I_p \cdot K_{vco}} \frac{b}{b-1}$$

$$C_1 = \frac{\tau_z}{R_1} \text{ and } C_2 = \frac{1}{R_1} \cdot \frac{\tau_z \tau_p}{\tau_z - \tau_p}$$

For loop filter 2:


$$\omega_c = \frac{I_p K_{vco}}{2\pi \cdot N} R_1 \frac{b}{b-1} = \frac{I_p K_{vco}}{2\pi \cdot N} R_1 \frac{C_1 + C_2}{C_1}$$

$$R_1 = \frac{2\pi \cdot N \cdot \omega_c}{I_p \cdot K_{vco}} \frac{b-1}{b}$$

$$C_1 = \frac{\tau_z - \tau_p}{R_1} \text{ and } C_2 = \frac{\tau_p}{R_1}$$

$\phi_m$	$b$	sqrt( $b$ )
20°	2.04	1.42
30°	3.00	1.73
40°	4.59	2.14
45°	5.82	2.41
50°	7.55	2.74
55°	10.06	3.17
60°	13.93	3.73
70°	32.16	5.67
80°	130.64	11.43


## Active loop filter implementation

 

The active loop filter is often used when the charge-pump output can not directly provide the required voltage range for tuning of the VCO. Such voltages are incompatible with charge-pumps built in standard IC technologies, so that a (partly external) active loop filter is then used to isolate the charge-pump output from the VCO tuning input, and to generate the high tuning voltages.



## Multi-path charge-pump filter

 

$$i_{e1} = I_{p1} \times \frac{\theta_e}{2\pi} \quad i_{e2} = I_{p2} \times \frac{\theta_e}{2\pi}$$

The loop filter transfer function is

$$\frac{V_{cont}(s)}{\theta_e(s)} = K_{pd} Z_{LF}(s) = \frac{I_{p1}}{2\pi} \frac{1}{C_a} + \frac{I_{p1}}{2\pi} \left( R_b \parallel \frac{1}{sC_b} \right)$$

$$= \frac{I_{p1}}{2\pi \cdot sC_a} \cdot \frac{sC_b \left( C_b + C_a \frac{I_{p2}}{I_{p1}} \right) + 1}{sR_bC_b + 1}$$

$$\Rightarrow \frac{1}{\omega_z} = R_b \left( C_b + C_a \frac{I_{p2}}{I_{p1}} \right) \approx R_b C_a \frac{I_{p2}}{I_{p1}}$$


$$\frac{1}{\omega_p} = R_b C_b$$

$$\omega_c \approx \frac{I_{p1} \cdot K_{vco}}{2\pi \cdot N \cdot C_a \cdot \omega_z} = \frac{K_{vco}}{2\pi \cdot N} \cdot I_{p2} \cdot R_b$$

J. Craninckx, IEEE JSSC, Dec. 1998

## Nonideal Effects in PLLs

## PFD and charge-pump filter

 


Owing to the finite risetime and falltime resulting from the capacitance seen at the nodes, the pulse may not find enough time to reach a logical high level, failing to turn on the charge pump switches.

- For  $|\Delta\phi| < \phi_0$ , the charge pump injects no current.
- The loop gain drops to zero and the output phase is not locked.
- The PFD/CP suffers from a dead zone equal to  $\pm\phi_0$  around  $\Delta\phi = 0$ .

⇒ Jitter resulting from the dead zone

## Reference spurs

 


- Periodic disturbance of VCO control line due to charge pump activity:

$$i_e(t) = \underbrace{I_p \delta_{cp}}_{DC} + \underbrace{2 I_p \delta_{cp} \sum_{n=1}^{\infty} \cos(2\pi n f_{ref} t)}_{\text{Spectral components}}$$

- Main effects which generate reference spurious breakthrough:
  - leakage current in the loop filter,
  - skew between  $up$  and  $down$  ( $dn$ ) signals,
  - mismatch in the charge  $up$  and  $down$  current sources,
  - Charge sharing.

## - Effect of leakage current

 

- Sources of leakage currents:
  - the capacitor of loop filter,
  - the input of VCO,
  - the charge-pump output,
  - the input biasing current of the op-amp, when active loop filter configuration is used.
- The duty cycle of the charge-pump output is

$$\bar{i}_e = I_P \delta_{cp} = I_{leak} \Rightarrow \delta_{cp} = \frac{I_{leak}}{I_P}$$

- The amplitude of charge-pump output:

$$i_e(t) = I_{leak} + 2I_{leak} \sum_{n=1}^{\infty} \cos(2\pi n f_{ref} t)$$

- ① The spectral component are twice the value of  $I_{leak}$ .
- ② Not dependent on the nominal charge-pump current  $I_P$ .

- Link the leakage current to the magnitude of the spurious components at the output of the VCO:

$$V_{ripple}(n \cdot f_{ref}) = 2I_{leak} |Z_{LF}(j2\pi n f_{ref})|$$

- Phase deviation

$$\theta_p(n \cdot f_{ref}) = \frac{\Delta f(n \cdot f_{ref})}{n \cdot f_{ref}} = \frac{V_{ripple}(n \cdot f_{ref}) K_{vco}}{n \cdot f_{ref}} = \frac{2I_{leak} |Z_{LF}(j2\pi n f_{ref})| K_{vco}}{n \cdot f_{ref}}$$

- ① Each of baseband modulation frequencies  $n \cdot f_{ref}$  generates two RF spurious signals at offset frequencies  $\pm n \cdot f_{ref}$  from the carrier  $f_{LO}$ .
- ② The amplitude of each spurious signal

$$A_{SP}(f_{LO} \pm n \cdot f_{ref}) = A_{LO} \frac{\theta_p(n \cdot f_{ref})}{2} = A_{LO} \frac{I_{leak} |Z_{LF}(j2\pi n f_{ref})| K_{vco}}{n \cdot f_{ref}}$$


$$\Rightarrow \frac{A_{SP}(f_{LO} \pm n \cdot f_{ref})}{A_{LO}} = \frac{I_{leak} |Z_{LF}(j2\pi n f_{ref})| K_{vco}}{n \cdot f_{ref}}$$

$$\Rightarrow \left[ \frac{A_{SP}}{A_{LO}} \right]_{dBc} = 20 \log \frac{\theta(n \cdot f_{ref})}{2} = 20 \log \frac{I_{leak} |Z_{LF}(j2\pi n f_{ref})| K_{vco}}{n \cdot f_{ref}} \text{ [dBc]}$$


The relative amplitude of the spurious signal is *not* dependent on the value of loop bandwidth or on the nominal charge-pump current  $I_P$ .

Theoretically, if  $I_{leak} = 0$  there are *no* reference spurs in the output.
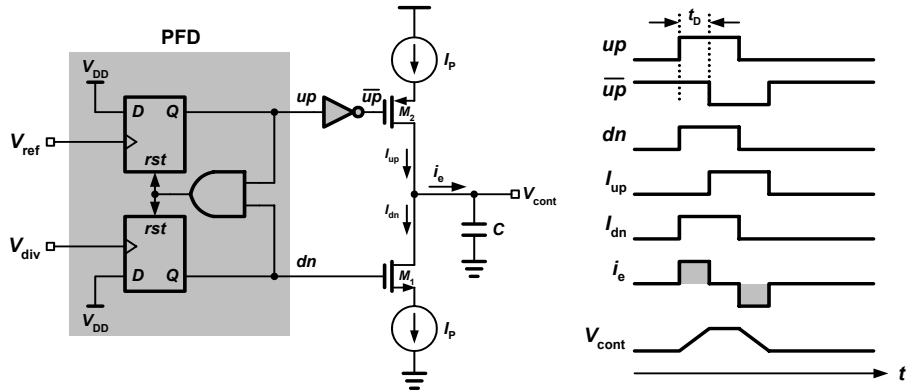
## - Effect of skew between *up* and *down* signals


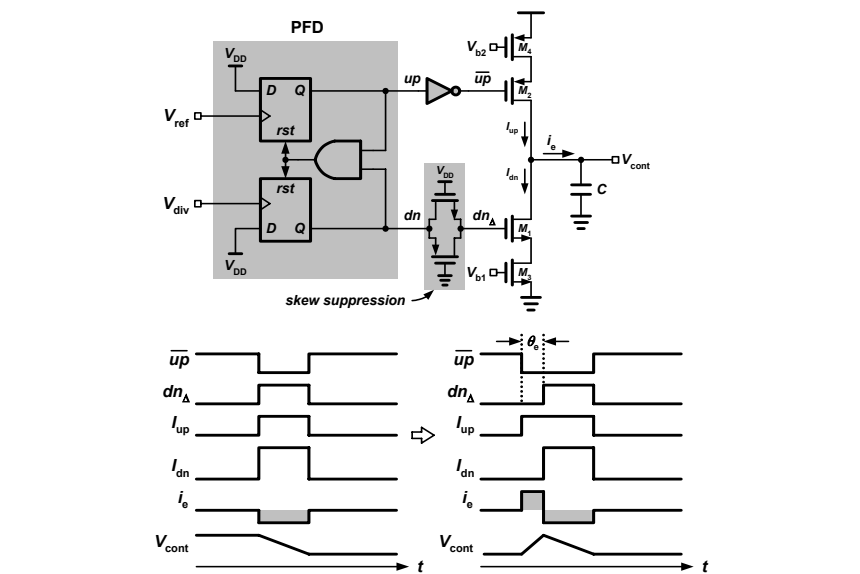
## - Effect of mismatch in the charge-pump current sources




## - Effect of mismatch in the charge-pump current sources

- For the loop to remain locked, the average value of  $V_{cont}$  must remain constant. The PLL therefore creates a phase error between the input and the output such that the net current injected by the charge pump in every cycle is zero.
  - ⇒ The control voltage still experiences a periodic ripple .
  - ⇒ Owing to the low output impedance of short-channel MOSFETs, the current mismatch *varies* with the output voltage.
  - ⇒ The clock feedthrough and charge injection mismatch between  $M_1$  and  $M_2$  further increases both the phase error and the ripple.
- The magnitude of the spectral components of the ripple voltage due to current-source mismatch can be found

$$V_{mismatch}(n \cdot f_{ref}) = I_{out}(n \cdot f_{ref}) \cdot |Z_{LF}(j2\pi n f_{ref})|$$


$$\Rightarrow \left[ \frac{A_{sp}(n \cdot f_{ref})}{A_{LO}} \right]_{dBc} = 20 \log \frac{I_{out}(n \cdot f_{ref}) |Z_{LF}(j2\pi n f_{ref})| K_{vco}}{2 \cdot n \cdot f_{ref}}$$

## - Effect of charge sharing

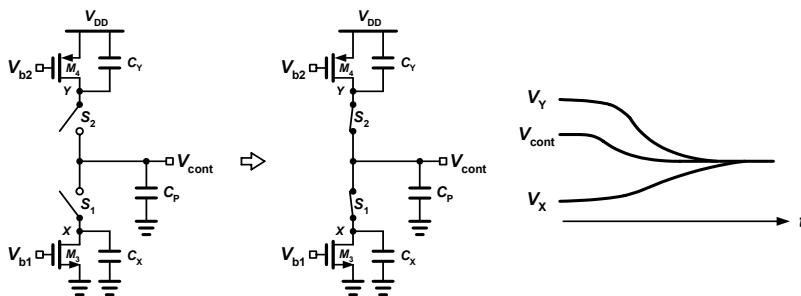

- Charge sharing between  $C_p$  and capacitances at X and Y:
  - $S_1$  and  $S_2$  are off, allowing  $M_3$  to discharge X to ground and  $M_4$  to charge Y to  $V_{DD}$ .
  - At the next phase comparison instant, both  $S_1$  and  $S_2$  turn on,  $V_X$  rises,  $V_Y$  falls, and  $V_X \approx V_Y \approx V_{cont}$ .
- If the phase error is zero and  $I_{D3} = |I_{D3}|$ , does  $V_{cont}$  remain constant after the switches turn on? Even if  $C_X = C_Y$ , the change in  $V_X$  is not equal to that in  $V_Y$ .


## - Effect of charge sharing

 

- Bootstrapping  $X$  and  $Y$  to minimize charge sharing:
  - When  $S_1$  and  $S_2$  turn off,  $S_3$  and  $S_4$  turn on, allowing the unity-gain amplifier to hold nodes  $X$  and  $Y$  at a potential equal to  $V_{cont}$ .
  - At the next phase comparison instant,  $S_1$  and  $S_2$  turn on,  $S_3$  and  $S_4$  turn off, and  $V_X$  and  $V_Y$  begin with a value equal to  $V_{cont}$ .
- The ideal is to “pin”  $V_X$  and  $V_Y$  to  $V_{cont}$  after phase comparison is finished. Thus, no charge sharing occurs between  $C_p$  and the capacitances at  $X$  and  $Y$ .

## Jitter/Noise in PLLs


## Jitter in PLLs

 

## Jitter in PLLs (cont'd)

**Slow-jitter waveform**

**Fast-jitter waveform**

 

- Effect of input jitter

$$\frac{\phi_{out}}{\phi_{in}}(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



$$\frac{\phi_{out}}{\phi_{in}}(s) = \frac{\omega_n^2(1 + s\tau_z)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

⇒ *Low-pass* characteristic. Slow jitter at the input propagates to the output unattenuated but fast jitter does not.

- Effect of VCO jitter


$$\frac{\phi_{out}}{\phi_{in}}(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

  ⇒ *High-pass* characteristic. Slow jitter components generated by the VCO are suppressed but fast jitter components are not.


 
## Jitter in PLLs (cont'd)


Transfer functions of jitter from input and VCO to the output




- Effect of VCO jitter:
  - If  $\phi_{VCO}$  changes slowly (e.g., the oscillation period drifts with temperature), then the comparison with  $\phi_{in} = 0$  (i.e., a perfectly periodic signal) generates a slowly varying error that propagates through the LPF and adjusts the VCO frequency, thereby counteracting the change in  $\phi_{VCO}$ .
  - If  $\phi_{VCO}$  varies rapidly, (e.g., high-frequency noise modulates the oscillation period), then the error produced by the phase detector is heavily attenuated by the poles in the loop, failing to correct for the change.
- In summary, depending on the application and environment, one or both sources may be significant, requiring an optimum choice of the loop bandwidth.
 
## Noise in PLLs

- Phase noise  $\phi_n(t) \Rightarrow x(t) = A \cos(\omega_c t + \phi_n(t))$   
If the input signal or the building blocks of a PLL exhibit noise, then the output signal will also suffer from noise.
- Phase noise at input


 
$$\frac{\phi_{out}(s)}{\phi_{in}} = \frac{\omega_n^2(1 + s/\omega_z)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$





 
## Noise in PLLs (cont'd)


- Phase noise of VCO

$$\frac{\phi_{out}}{\phi_{VCO}}(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



The VCO phase noise experiences a high-pass transfer function as it appears at the output of a PLL. Thus, increasing the bandwidth of the PLL can lower the contribution of the VCO phase noise.

## Noise sources of the PLL

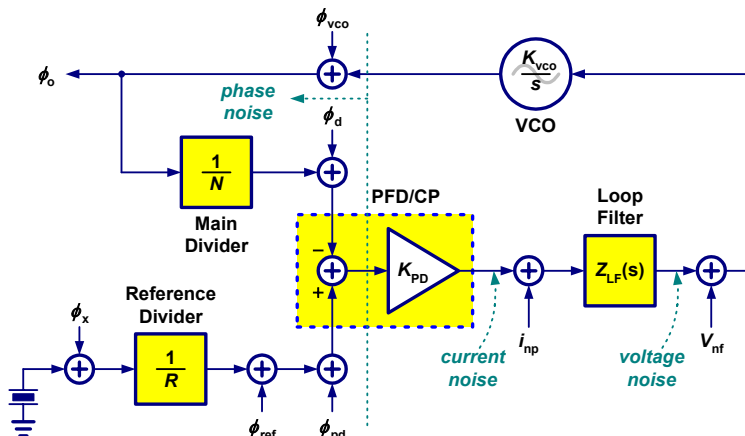

The rms phase noise power density of the loop's output signal is denoted  $\phi_o(f_m)$ .


The output phase noise power density:

$$\phi_o^2(f_m) = \phi_{oLP}^2(f_m) + \phi_{oHP}^2(f_m)$$

Low-pass transfer function

High-pass transfer function

## - Phase noise

 

$$v(t) = V_s \sin(2\pi f_o t + \theta_n(t))$$

The phase noise  $\zeta(f_m)$ , usually in dBc, is the ratio of the single-sideband (SSB) power in a 1-Hz band width  $f_m$  Hz away from the carrier to the total signal power, i.e.,

$$\zeta(f_m) \equiv \frac{P_s}{P_{ssb}}$$

Let  $S_{\theta_n}(f)$  be the power spectral density of  $\theta_n(t)$  in frequency domain, it can be

shown that  $S_{\theta_n}(f_m) \approx 2\zeta(f_m)$  and  $\overline{\theta_n^2} = \int_0^\infty S_{\theta_n}(f) df$

## - Phase noise originated from dividers, PFD/CP and crystal reference sources

- $\phi_d(f_m)$ ,  $\phi_{ref}(f_m)$  and  $\phi_{pd}(f_m)$  to  $\phi_o(f_m)$ :  $H_{LP}(s) = N \frac{G(s)}{1+G(s)} = N \cdot H(s)$  (Low pass)

with open-loop transfer function  $G(s) = \frac{\theta_{Div}(s)}{\theta_{ref}(s)} = K_{pd} Z_{LF}(s) \frac{K_{vco}}{s} \frac{1}{N}$


and closed-loop transfer function  $H(s) = \frac{\phi_{Div}(s)}{\phi_{ref}(s)} = \frac{G(s)}{1+G(s)} = \frac{K_{pd} Z_{LF}(s) K_{vco} / N}{s + K_{pd} Z_{LF}(s) K_{vco} / N}$

$$\Rightarrow \phi_{oLP}^2(f_m) = N^2 |H(j2\pi f_m)|^2 \left( \phi_d^2(f_m) + \phi_{ref}^2(f_m) + \phi_{pd}^2(f_m) + \frac{i_{np}^2(f_m)}{K_{pd}^2} + \frac{\phi_x^2(f_m)}{R^2} \right)$$

where  $\phi_{eq}^2(f_m) \equiv \phi_d^2(f_m) + \phi_{ref}^2(f_m) + \phi_{pd}^2(f_m) + \frac{i_{np}^2(f_m)}{K_{pd}^2} + \frac{\phi_x^2(f_m)}{R^2}$

$\Rightarrow$  The equivalent synthesizer phase noise floor at the input of the phase detector.

$$\Rightarrow \phi_{oLP}^2(f_m) = N^2 |H(j2\pi f_m)|^2 \phi_{eq}^2(f_m)$$

 

## - Phase noise due to loop filter and free-running VCO phase noise

- Oscillator:  $\phi_{vco}^2(f_m) \approx \frac{Fk_B T}{P_{rf}} \left[ 1 + \left( \frac{f_{vco}}{2Q_l f_m} \right)^2 \right] \left( 1 + \frac{f_k}{f_m} \right) \text{ rad}^2 / \text{Hz}$

where  $F$  is a noise factor,  $k_B = 1.37 \times 10^{-23} \text{ J/K}$  (Boltzmann constant),  
 $T$  is the absolute temperature,  $P_{rf}$  is the power of the oscillator signal,  
 $f_{vco}$  is the output frequency of the oscillator,  
 $Q_l$  is the loaded quality factor of the tuning circuit,  
 $f_m$  is the offset frequency from the frequency  $f_{vco}$ , and  
 $f_k$  is the offset frequency which delimits the 9dB/octave dependency of the phase noise power density on the offset frequency ( $\Rightarrow \phi_{vco}^2 \propto 1/f_m^3$ ).

Assume  $f_k \approx 0$  and  $f_m$  is small,  $\phi_{vco}^2(f_m) \approx \frac{Fk_B T}{4P_{rf}} \frac{1}{Q_l^2} \frac{f_{vco}^2}{f_m^2} \text{ rad}^2 / \text{Hz}$

$\Rightarrow -6\text{dB/oct}$  dependency on  $f_m$ .

$\Rightarrow \phi_{vco}^2(f_m)$  as a function of the phase noise power density at an offset frequency  $f_r$ :

$$\phi_{vco}^2(f_m) = \phi_{vco}^2(f_r) \frac{f_r^2}{f_m^2} \quad \text{VCO noise floor power density}$$

$\Rightarrow$  **Exact function:**  $\phi_{vco}^2(f_m) = \phi_{vco}^2(f_r) \frac{f_r^2}{f_m^2} \left( 1 + \frac{f_k}{f_m} \right) + \phi_{vco,nf}^2$


## - Phase noise due to loop filter and free-running VCO phase noise

- Loop filter: Thermal noise voltage originated in the loop filter resistor causes unintended phase modulation of the VCO.

$$\phi_{lf}^2(f_m) = v_{nf}^2(f_m) \frac{K_{vco}^2}{f_m^2} \text{ rad}^2 / \text{Hz}$$

- Influence of the loop: The influence of the feedback loop on the free-running VCO phase noise power density  $\phi_{vco}^2(f_m)$  and on the open-loop phase noise power density generated by the loop filter elements  $\phi_{lf}^2(f_m)$  is expressed with the transfer function  $T_{HP}(s)$ ,


$$T_{HP}(s) = \frac{1}{1 + G(s)} \quad (\text{High pass})$$
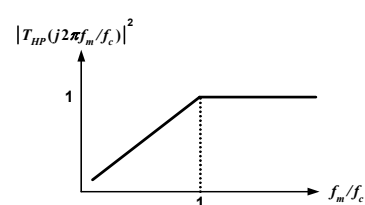
$$\Rightarrow \phi_{oHP}^2(f_m) = |T_{HP}(j2\pi f_m)|^2 (\phi_{vco}^2(f_m) + \phi_{lf}^2(f_m))$$


## - Total phase noise at the output of the PLL

- Total phase noise noise power spectral density:

$$\phi_o^2(f_m) = \underbrace{N^2 \phi_{eq}^2(f_m) \cdot |H(j2\pi f_m)|^2}_{\text{(Low pass)}} + \underbrace{(\phi_{vco}^2(f_m) + \phi_{lf}^2(f_m)) \cdot |T_{HP}(j2\pi f_m)|^2}_{\text{(High pass)}} \quad \text{rad}^2 / \text{Hz}$$

 

## - General bandwidth requirements

- Low PLL System Jitter
  - ⇒ Wide Loop Bandwidth
- Large Input Jitter Reduction
  - ⇒ Narrow Loop Bandwidth
- Fast Locking
  - ⇒ Wide Loop Bandwidth
- Phase Fluctuation Tracking
  - ⇒ Adaptive Loop Bandwidth Control
- There are Trade-offs: No single good solution for All

## Spectral purity & design of PLL loop filter

- Consideration:

- Decrease  $I_p$  to acceptable level in order to decrease the power dissipation and to simplify the design of the charge-pump circuitry.
- The impedance level of the loop filter should be maximized, for the chip-area of fully integrated loop filters to be minimized.

Note: high impedance level  $\Rightarrow$  small  $C_1$  and  $C_2$ , large  $R_1$ , and small  $I_p$ .

$\Rightarrow$  a higher noise contribution from the filter.

- Spurious reference breakthrough:

- Effect of leakage currents

$$\left| Z_{LF}(j2\pi f_{ref}) \right| < \frac{n \cdot f_{ref}}{I_{leak} \cdot K_{vco}} 10^{\frac{Max.spurious}{20}} \quad (\text{the worst case situation})$$

$$(f_c \ll f_{ref}) \quad \left| Z_{LF}(j2\pi f_{ref}) \right| \approx \frac{1}{2\pi f_{ref} C_2} \quad \Rightarrow \quad C_{2,min} = \frac{I_{leak} \cdot K_{vco}}{2\pi \cdot n \cdot f_{ref}^2} 10^{\frac{Max.spurious}{20}}$$

$$\text{● Effect of charge-pump current mismatch} \quad C_{2,min} = \frac{I_{out}(f_{ref}) \cdot K_{vco}}{4\pi \cdot n \cdot f_{ref}^2} 10^{\frac{Max.spurious}{20}}$$

- Phase noise contribution from the loop filter resistor

$$v_{nf}^2(f_m) = \left( \frac{b-1}{b} \right)^2 \cdot \frac{4k_B TR_1}{|1 + j2\pi f_m \tau_p|^2}$$

$$\Rightarrow \phi_{lf}^2(f_m) = v_{nf}^2(f_m) \frac{K_{vco}^2}{f_m^2} = \left( \frac{b-1}{b} \right)^2 \cdot \frac{4k_B TR_1}{|1 + j2\pi f_m \tau_p|^2} \cdot \frac{K_{vco}^2}{f_m^2}$$

Define  $\alpha_{lf}(f_m) \equiv \frac{\phi_{lf}^2(f_m)}{\phi_{vco}^2(f_m)} = \left( \frac{b-1}{b} \right)^2 \cdot \frac{4k_B TR_1 K_{vco}^2}{\phi_{vco}^2(f_r) f_r^2} \cdot \frac{1}{|1 + j2\pi f_m \tau_p|^2}$  where  $\phi_{vco}^2(f_m) = \phi_{vco}^2(f_r) \frac{f_r^2}{f_m^2}$


$$\Rightarrow \alpha_{lf}(f_m) = \alpha_{lf,dc} \cdot \frac{1}{|1 + j2\pi f_m \tau_p|^2} \quad \text{with} \quad \alpha_{lf,dc} = \left( \frac{b-1}{b} \right)^2 \cdot \frac{4k_B TR_1 K_{vco}^2}{\phi_{vco}^2(f_r) f_r^2}$$

Maximum value of  $R_1$ :

$$R_{1,max} = \alpha_{lf,dc} \left( \frac{b}{b-1} \right)^2 \cdot \frac{\phi_{vco}^2(f_r) f_r^2}{4k_B TK_{vco}^2}$$

A smaller value than  $R_{1,max}$  for the loop filter resistor obviously leads to a smaller  $\alpha_{lf,dc}$ , which is always an acceptable situation from the point of view of phase noise performance.
 
## More attenuation of unwanted spurs with the 3<sup>rd</sup>-order filter



$$Z_{LF1}(s) = \frac{1 + s\tau_z}{s(C_1 + C_2)(1 + s\tau_p)}$$

$$Z_{LF}(s) = \frac{Z_{LF1}(s) \cdot \left(\frac{1}{sC_3}\right)}{Z_{LF1}(s) + R_3 + \frac{1}{sC_3}}$$

Assume  $C_2 \geq 10C_3$ , we have

The added attenuation from the low-pass filter:

$$ATTEN = 20 \log[(2\pi f_{ref} \tau_{p3})^2 + 1]$$

where  $\tau_{p3} = R_3 C_3$

(low-pass pole)

$$\Rightarrow \tau_{p3} = \frac{\sqrt{10^{\frac{ATTEN}{20}} - 1}}{2\pi f_{ref}}$$

$$\tau_z = \frac{1}{\omega_c^2 \cdot (\tau_p + \tau_{p3})}$$

$$\omega_c = \frac{\tan \phi_m \cdot (\tau_p + \tau_{p3})}{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}} \cdot \left( \sqrt{1 + \frac{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}}{(\tan \phi_m \cdot (\tau_p + \tau_{p3}))^2}} - 1 \right)$$

$$\Rightarrow C_2 = \frac{\tau_p}{\tau_z} \cdot \frac{K_{pd} \cdot K_{vco}}{\omega_c^2 \cdot N} \cdot \left( \frac{(1 + \omega_c^2 \cdot \tau_z^2)}{(1 + \omega_c^2 \cdot \tau_p^2)(1 + \omega_c^2 \cdot \tau_{p3}^2)} \right)^{\frac{1}{2}}$$

$$C_1 = C_2 \cdot \left( \frac{\tau_z}{\tau_p} - 1 \right) \quad \text{and} \quad R_1 = \frac{\tau_z}{C_1} \quad (\text{similar to the 2<sup>nd</sup>-order filter})$$

## - Derivation of $\omega_c$

The impedance of the loop filter:  $Z_{LF}(s) = \frac{Z_{LF1}(s) \cdot \left(\frac{1}{sC_3}\right)}{Z_{LF1}(s) + R_3 + \frac{1}{sC_3}}$  and  $Z_{LF1}(s) = \frac{1 + s\tau_z}{s(C_1 + C_2)(1 + s\tau_p)}$

Knowing that  $C_2 \geq 10C_3$  and  $\tau_{p3} = R_3 C_3$

$$\text{Open-loop gain: } \beta(s)G(s) \Big|_{s=j\omega} = -\frac{K_{PD} \cdot K_{VCO}}{\omega^2 \cdot C_1 \cdot N} \cdot \frac{1 + j\omega\tau_z}{1 + j\omega\tau_p} \cdot \frac{\tau_p}{\tau_z} \cdot \frac{1}{1 + j\omega\tau_{p3}}$$

$$\phi(\omega) = \tan^{-1}(\omega \cdot \tau_z) - \tan^{-1}(\omega \cdot \tau_p) - \tan^{-1}(\omega \cdot \tau_{p3}) + 180^\circ \quad \dots (A)$$

Assume  $\omega_z < \omega < \omega_p < \omega_{p3}$ , we have

$$\phi_{m,\max}: \frac{d\phi}{d\omega} = \frac{\tau_z}{1 + (\omega \cdot \tau_z)^2} - \frac{\tau_p}{1 + (\omega \cdot \tau_p)^2} - \frac{\tau_{p3}}{1 + (\omega \cdot \tau_{p3})^2} = 0$$


$$\Rightarrow \frac{\tau_z}{(\omega \cdot \tau_z)^2} - \tau_p - \tau_{p3} \approx 0 \quad \Rightarrow \quad \tau_z = \frac{1}{\omega^2(\tau_p + \tau_{p3})} \quad \dots (B)$$

$$\text{Substituting (B) into (A) gives } \tan \phi = \frac{-\omega \cdot (\tau_p + \tau_{p3}) - \frac{\omega \cdot \tau_p \tau_{p3}}{\tau_p + \tau_{p3}} + \frac{1}{\omega \cdot (\tau_p + \tau_{p3})}}{2 - \omega^2 \cdot \tau_p \tau_{p3}}$$

$$\Rightarrow \omega^2 + \omega \frac{2 \tan \phi}{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}} - \frac{1}{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}} = 0$$

$$\text{Taking the negative root } \Rightarrow \omega_c = \frac{\tan \phi_m \cdot (\tau_p + \tau_{p3})}{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}} \cdot \left( \sqrt{1 + \frac{(\tau_p + \tau_{p3})^2 + \tau_p \tau_{p3}}{(\tan \phi_m \cdot (\tau_p + \tau_{p3}))^2}} - 1 \right)$$

## PLL block diagram

 


- Noise transfer function:

$$\frac{\theta_o}{\theta_n} = \frac{s}{s + 2\pi f_L}$$

where the loop bandwidth  $f_L$  is determined by  $K_d$ ,  $K_v$  and  $F(s)$ .


- $\theta_n$  can be represented by integrated white noise giving a  $1/f^2$  power spectral density (psd).

## PLL output phase noise psd

 


- $\theta_n$  : open-loop phase noise psd (integrated white noise)
- $\theta_o$  : closed-loop phase noise psd (lowpass due to shaping by loop)
 
## Measured phase noise: frequency domain



## Measured phase noise: time domain

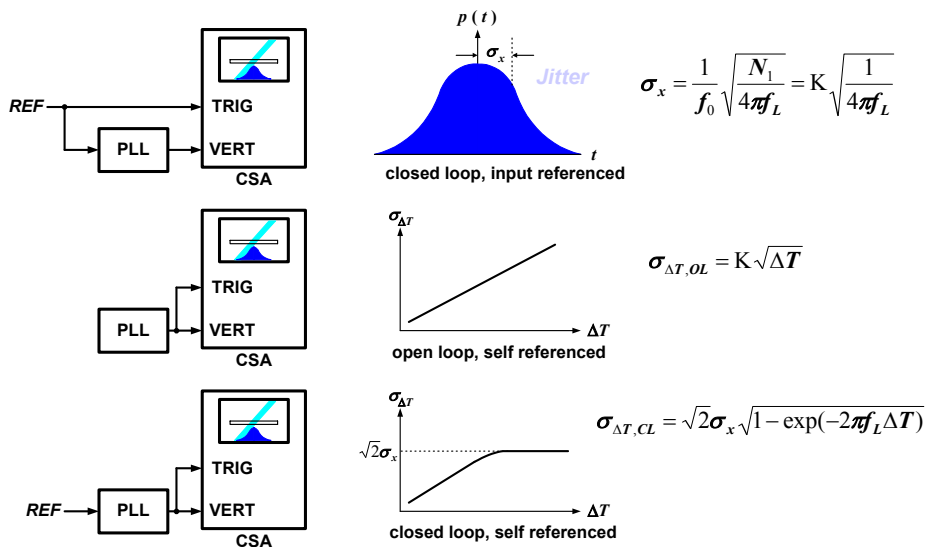



## Design example

- A VCO with center frequency of  $f_0 = 622$  MHz and phase noise  $-106$  dBc at a 1-MHz offset is to be used in a PLL. Assuming the VCO is the dominant source of jitter, what is the required loop bandwidth  $f_L$  to realize a jitter of  $\sigma_x = 10$  ps rms?

⊗ Determine  $N_1$ :

$$\text{Phase noise @ } f_{os} = 10 \log (N_1/f_{os}^2)$$


$$-106 \text{ dBc} = 10 \log (N_1/(1\text{MHz})^2) \Rightarrow N_1 = 25.1 \text{ Hz}$$

⊗ Find  $f_L$ :

$$\text{Jitter } \sigma_x = \frac{1}{f_0} \sqrt{\frac{N_1}{4\pi f_L}}$$


$$\Rightarrow f_L = 51.6 \text{ kHz}$$
 
## Equivalent model for the phase noise of a VCO



- VCO acts as an ideal integrator.
- The input source,  $n_0(s)$ , has white and  $1/f$  noise portions that will generate the  $1/f^2$  and  $1/f^3$  regions in the output spectrum. The output source,  $n_1(s)$ , models the noise floor.
 
## Typical phase noise and timing jitter of a free running VCO



### ● Output power spectrum

$$S_{\Phi_{out}}(\omega) = \left| \frac{K_V}{j\omega} \right|^2 S_n(\omega) + \frac{N_1}{2} = \frac{K_V^2 N_0}{2\omega^2} \left( 1 + \frac{\omega_1/f^3}{\omega} \right) + \frac{N_1}{2}$$

where  $N_{0,1}/2$  are the double-sideband power spectral densities of the input and output white noise sources,  $n_{0,1}(s)$ , and  $\omega_1/f^3$  is the  $1/f$  noise corner of the input behavior noise source,  $n_0(s)$ , that is equal to the  $1/f^3$  noise corner of the VCO.


### ● In the time domain, the uncertainties in the transition times accumulate continuously, increasing the timing jitter of the oscillator.

⊗ Uncorrelated part:  $\sigma_\tau = \kappa\sqrt{\tau}$  where  $\sigma_\tau$  is the rms jitter  $\tau$  seconds after the reference, and  $\kappa$  is the proportionality constant.

⊗ Correlated part: the magnitudes add directly resulting in an additional region with a slope of one.


## Phase noise and jitter in 1st order loops
 
### ● Assuming a noiseless input and assuming the VCO noise is dominated by its $1/f^2$ noise




## Phase noise and jitter in 1st order loops

- Ideal VCO and noisy input

 
 
$$\frac{\Phi_{out}(s)}{\Phi_{in}(s)} = \frac{K_D K_V}{K_D K_V + s} = \frac{1}{1 + s/\omega_{loop}} \Rightarrow S_{\Phi_{out}}(\omega) = \frac{\alpha}{\omega^2} \frac{\omega_{loop}^2}{\omega_{loop}^2 + \omega^2} \text{ if } S_{\Phi_{in}}(\omega) = \frac{\alpha}{\omega^2}$$




PLL ICs

1-84


Ching-Yuan Yang / EE, NCHU
 
## Phase noise and jitter in 1st order loops

- PLL with large VCO noise (e.g. clock generators, frequency synthesizers)



 - PLL with large input reference noise (e.g. clock recovery)




PLL ICs

1-85

Ching-Yuan Yang / EE, NCHU


## Phase noise in higher-order loops

- Charge-pump PLL

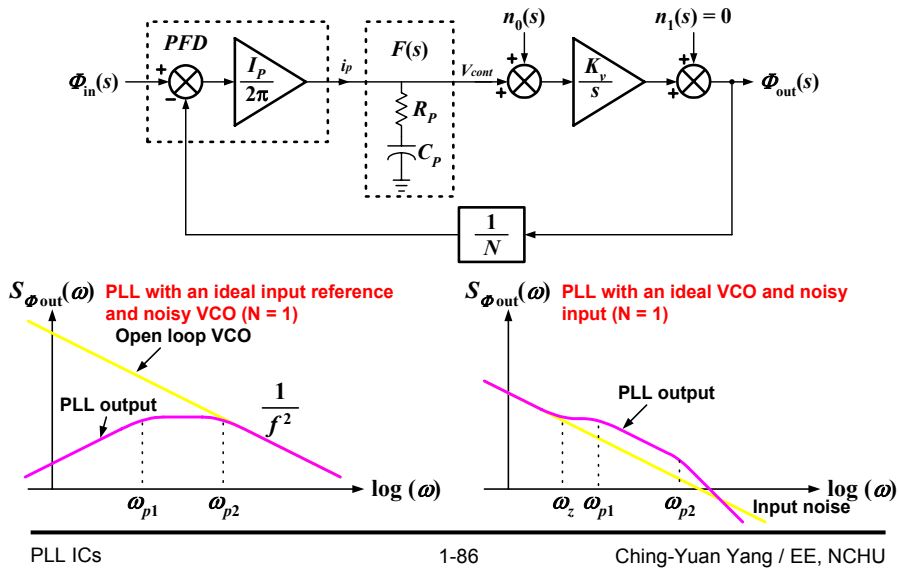


## Phase noise in higher-order loops

- PLL with  $N = 1$

 


- PLL with  $N$

 

The effect of an *ideal* frequency divider is to increase the phase noise of the input by a factor of  $20 \log(N)$
 
## Noise contribution of the frequency divider


- Equivalent model for frequency divider noise



- ⊗ The divider's noise usually appears as directly at the input of the PD and experiences the same transfer function as the noise on the input terminal.
- ⊗ Digital dividers usually have a large white noise floor at their output. If the divider is implemented using active devices with large  $1/f$  noise, it may even swamp the noise of the reference completely.
- ⊗ Due to the resonant nature, analog regenerative and injection-locked dividers are generally less noisy than the digital synchronous and asynchronous counterparts.


## Applications of PLLs

## Delay-locked loops

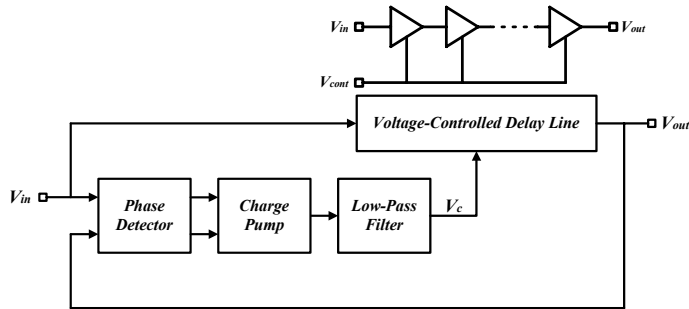

- Delay line much less noisy than VCOs.
- First-order system (for first-order LPF), thus very stable.
- But input and output frequencies must be equal.

## Transfer function of DLL

 

Transfer function of PD/CP/LPF

$$\frac{V_{cont}}{\Delta\phi}(s) = \frac{I_P}{2\pi} \left[ \left( R_p + \frac{1}{C_p s} \right) \left( \frac{1}{C_2 s} \right) \right] = \frac{I_P}{2\pi} \frac{R_p C_p s + 1}{(R_p C_p C_2 s + C_p + C_2) s}$$

Close-loop transfer function


$$\left. \frac{\phi_{out}}{\phi_{in}}(s) \right|_{closed} = \frac{\frac{I_P K_{VCDL}}{2\pi} (R_p C_p s + 1)}{R_p C_p C_2 s^2 + \left[ C_p + C_2 + \frac{I_P K_{VCDL} R_p C_p}{2\pi} \right] s + \frac{I_P K_{VCDL}}{2\pi}}$$

Discussion


- The closed-loop transfer can be used to determine how  $\phi_{out}$  settles if  $\phi_{in}$  experiences a change.  $\Rightarrow \omega_n, \zeta$
- In practice  $R_p$  may not be need because the loop contains only one pole at the origin.

## Skew reduction

- Skew between data and buffered clock

 


- Use of a PLL to eliminate skew

 

 
## Data Recovery (Jitter reduction)

- Retiming data with D flipflop driven by a low-noise clock



- ❑ Random binary signals experience jitter because
  - crosstalk on the chip and in the package,
  - package parasitics,
  - additive electronic noise of devices, etc.
- ❑ The idea is to resample the midpoint of each bit by a D flipflop that is driven by a low-noise clock.
- ❑ Clock recovery circuit (CRC): The CRC produces the clock from the data. Employing phase locking with a relatively narrow loop bandwidth, the CRC minimizes the effect of the input jitter on the recovered clock.

## Frequency multiplication

 


- When the loop is locked,  $\omega_F = \omega_{in}$ , and hence  $\omega_{out} = M \cdot \omega_{in}$ . The divide ratio of  $M$  is called the “modulus.”
- Frequency multiplication also amplifies the input phase noise. For example, the magnitude of phase noise components within the  $-3\text{dB}$  bandwidth of the PLL is multiplied by a factor of approximately  $M$ .

## Phase-Locked Loops

### Behavior Simulation


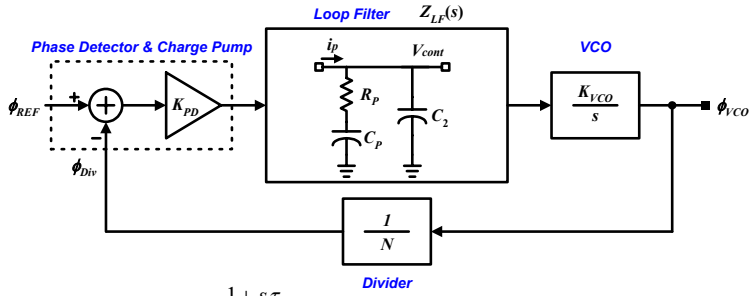
## Linear model of 3<sup>rd</sup>-order PLLs



**Loop filter:**  $Z_{LF}(s) = \frac{1 + s\tau_z}{s(C_p + C_2)(1 + s\tau_p)}$  with  $\tau_z = R_p C_p$  and  $\tau_p = R_p(C_p^{-1} + C_2^{-1})^{-1}$ .


**Open-loop transfer function:**  $GH(s) = \frac{I_p \cdot K_{VCO}}{2\pi \cdot N} \cdot \frac{1 + s\tau_z}{s^2(C_p + C_2) \cdot (1 + s\tau_p)}$

$\Rightarrow$  **Crossover frequency**  $\omega_c \approx \frac{I_p \cdot R_p \cdot K_{VCO}}{2\pi \cdot N} \cdot \frac{C_p}{C_p + C_2}$

**Gain margin**  $GH(s)|_{s=j\omega} = -\frac{I_p K_{VCO}}{2\pi \cdot N} \cdot \frac{(1 + j\omega\tau_z)}{\omega^2(C_p + C_2) \cdot (1 + j\omega\tau_p)}$

**Phase margin**  $\phi(\omega) = 180^\circ + \tan^{-1}(\omega\tau_z) - \tan^{-1}(\omega\tau_p)$
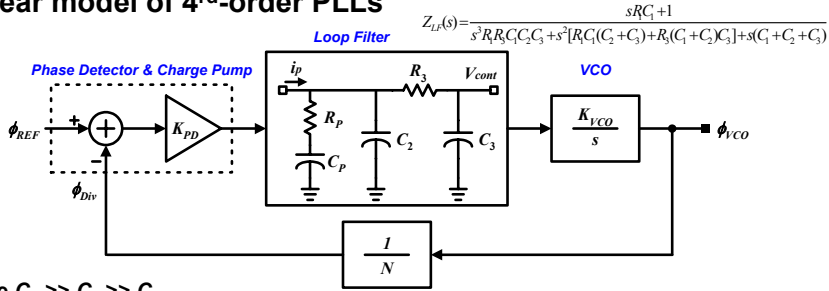
## Linear model of 4<sup>rd</sup>-order PLLs



Assume  $C_p \gg C_2 \gg C_3$ ,

**Loop filter:**  $Z_{LF}(s) \approx \frac{1 + s\tau_z}{sC_p(1 + s\tau_{p1})(1 + s\tau_{p2})}$  with  $\tau_z = R_p C_p$ ,  $\tau_{p1} = R_1 C_2$  and  $\tau_{p2} = R_3 C_3$ .


**Open-loop transfer function:**  $GH(s) \approx \frac{I_p \cdot K_{VCO}}{2\pi \cdot N} \cdot \frac{1 + s\tau_z}{s^2 C_p \cdot (1 + s\tau_{p1}) \cdot (1 + s\tau_{p2})}$

$\Rightarrow$  **Crossover frequency**  $\omega_c \approx \frac{I_p \cdot R_p \cdot K_{VCO}}{2\pi \cdot N}$

**Gain margin**  $GH(s)|_{s=j\omega} \approx -\frac{I_p K_{VCO}}{2\pi \cdot N} \cdot \frac{(1 + j\omega\tau_z)}{\omega^2 C_p \cdot (1 + j\omega\tau_{p1}) \cdot (1 + j\omega\tau_{p2})}$

**Phase margin**  $\phi(\omega) \approx 180^\circ + \tan^{-1}(\omega\tau_z) - \tan^{-1}(\omega\tau_{p1}) - \tan^{-1}(\omega\tau_{p2})$
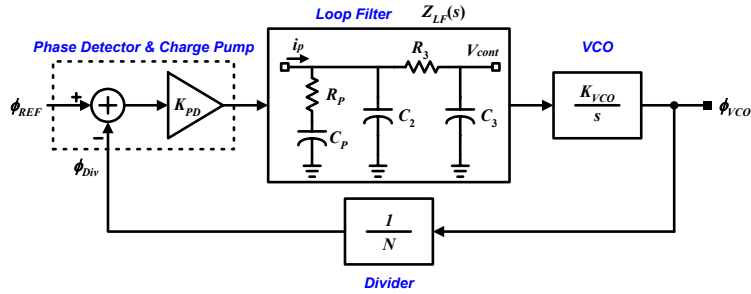
## Linear model of 4<sup>rd</sup>-order PLLs



Design the extra pole  $\omega_{p2}$  on the top of  $\omega_{p1}$  by taking  $\tau_{p2} = \tau_{p1}$ .


$$\Rightarrow \tau_{p2} = R_3 \cdot C_3 = (\lambda R_3) \cdot (C_3 / \lambda) \text{ with } \lambda > 10.$$

$$\Rightarrow \text{Crossover frequency } \omega_c \approx \frac{I_p \cdot R_p \cdot K_{VCO}}{2\pi \cdot N}$$

$$\text{Gain margin } GH(s)|_{s=j\omega} \approx -\frac{I_p K_{VCO}}{2\pi \cdot N} \cdot \frac{(1 + j\omega\tau_z)}{\omega^2 C_p \cdot (1 + j\omega\tau_{p1})^2}$$

$$\text{Phase margin } \phi(\omega) \approx 180^\circ + \tan^{-1}(\omega\tau_z) - 2 \tan^{-1}(\omega\tau_{p1})$$

 
## Bode diagram of 3<sup>rd</sup>-order and 4<sup>th</sup>-order PLLs



Choose  $\omega_c = 2\pi \times 200$  Krad/s and  $\gamma = 5$

$$\Rightarrow N = 50, K_v = 50 \text{ MHz/V}, I_p = 100 \mu\text{A}, R_1 = 13.4 \text{ K}\Omega, C_1 = 237 \text{ pF}, C_2 = 16 \text{ pF}, \text{ and } \lambda = 12.$$
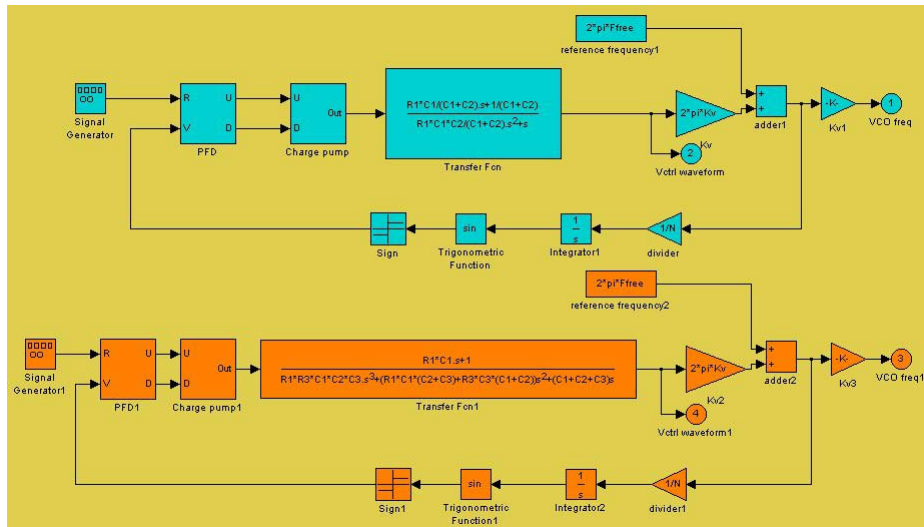
## Simulink behavior simulation of 3<sup>rd</sup>-order and 4<sup>rd</sup>-order PLLs



PLL ICs

1-100

Ching-Yuan Yang / EE, NCHU

## Transient of 3<sup>rd</sup>-order and 4<sup>rd</sup>-order PLLs

$f_{REF} = 20 \text{ MHz}$

$f_{VCO}: 900 \rightarrow 1000 \text{ MHz}$



PLL ICs

1-101

Ching-Yuan Yang / EE, NCHU