
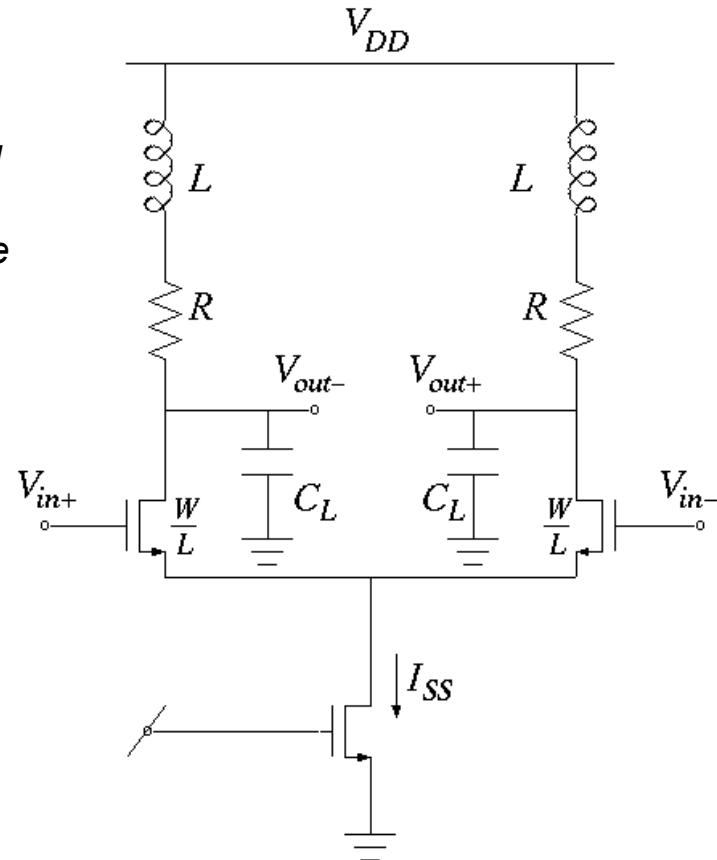


Shunt-Peaking (1)

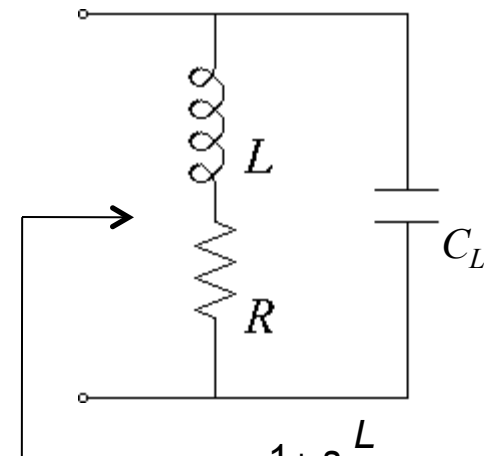
By connecting an inductor in series with the load resistor (series connection in shunt with output), more current is used, for a longer time, to charge the load capacitance.



Properties of Shunt-Peaking


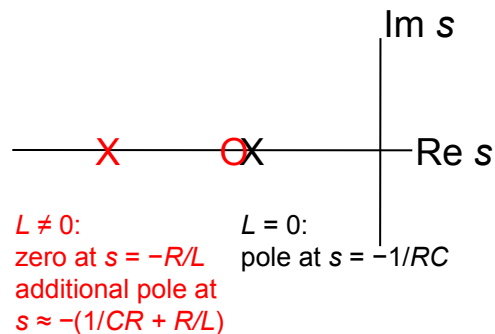
$$Z(s) = R \cdot \frac{1 + s \frac{L}{R}}{1 + sC_L R + s^2 LC_L}$$



Frequency response:

$$Z(j\omega) = R \cdot \frac{1 + j\omega \frac{L}{R}}{(1 - \omega^2 LC_L) + j\omega C_L R}$$

Resonant frequency:


$$\omega_r^2 = \frac{1}{LC_L} \left(1 - \frac{C_L R^2}{L} \right)$$

No resonance for $\frac{L}{C_L R^2} < 1$

Shunt-Peaking -- AC Response


$$C_L = 38 \text{ fF}$$
$$R = 400 \, \Omega$$

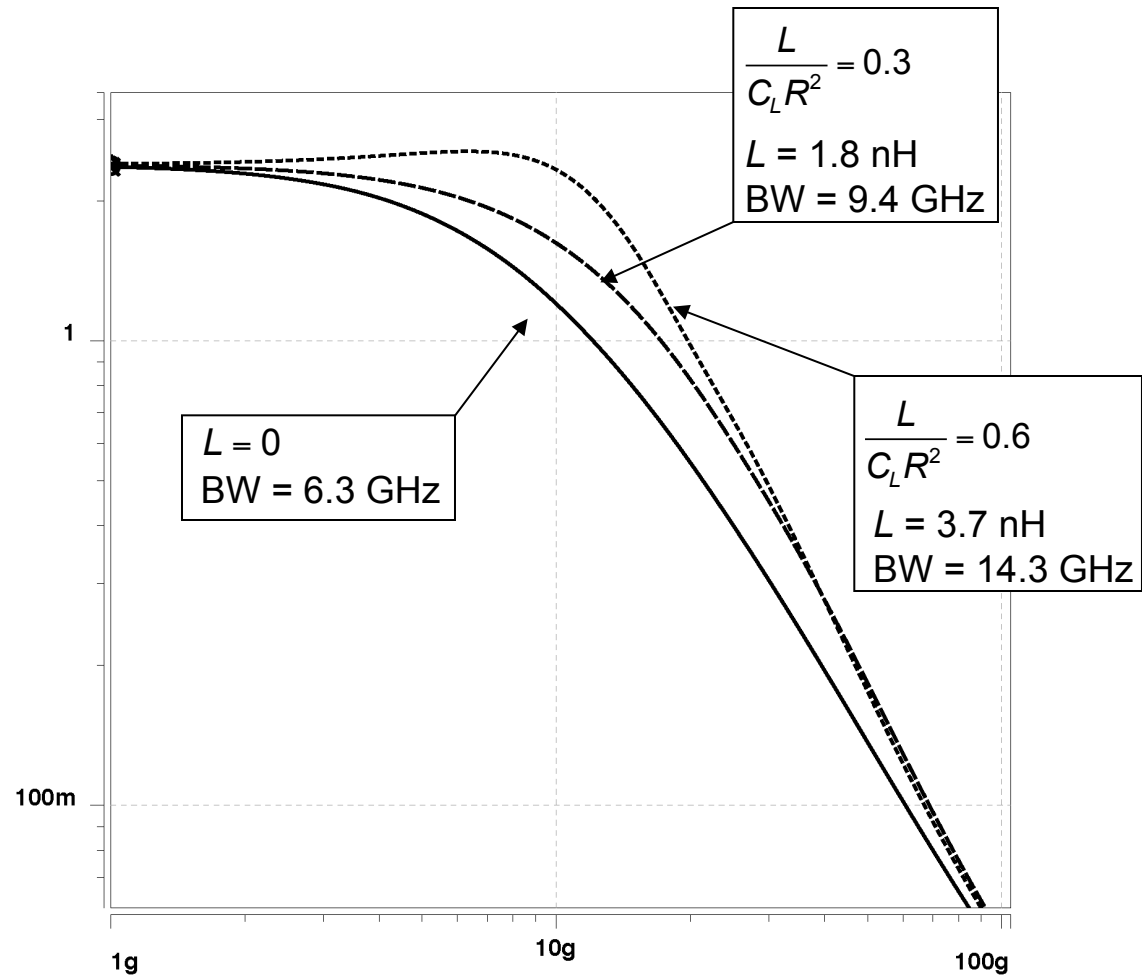*Use of shunt-peaking
increases small-signal bandwidth*




Shunt Peaking – Transient Response (1)

Step Response:

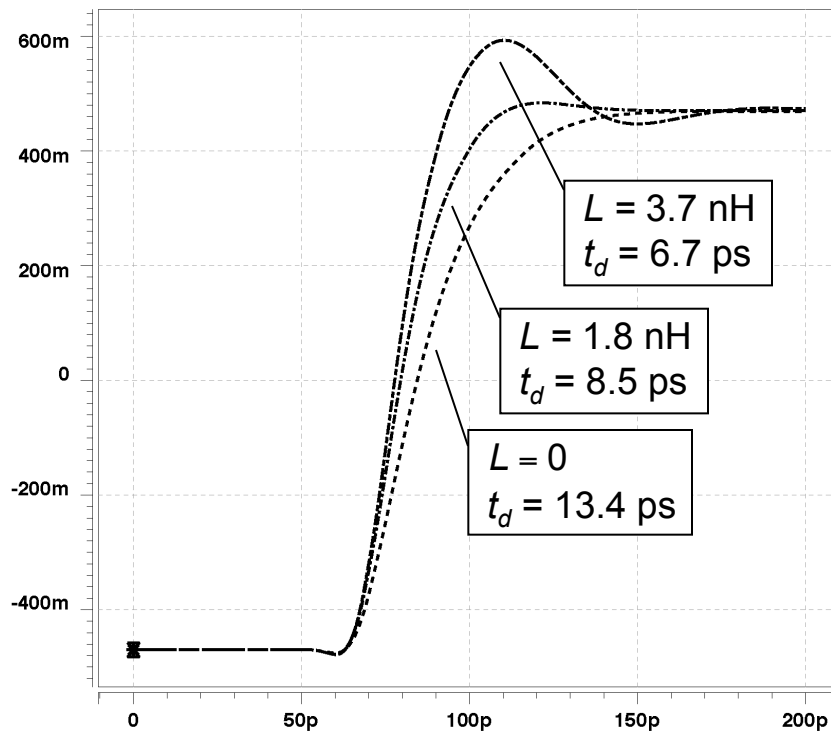

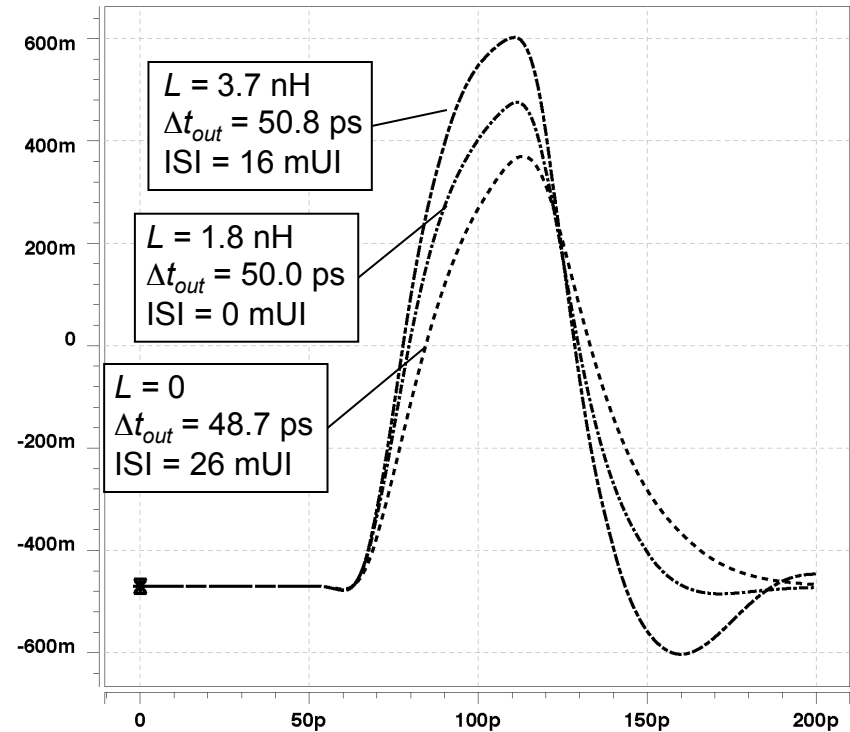
Pulse Response ($\Delta t_{in} = 50 \text{ ps}$):



Other Advantages of Shunt-Peaking

- CML load is passive & linear
- Can be shown to be very robust in the presence of parasitic series resistance and shunt capacitance $\Rightarrow$ inductors can be placed far away from other CML circuit elements.

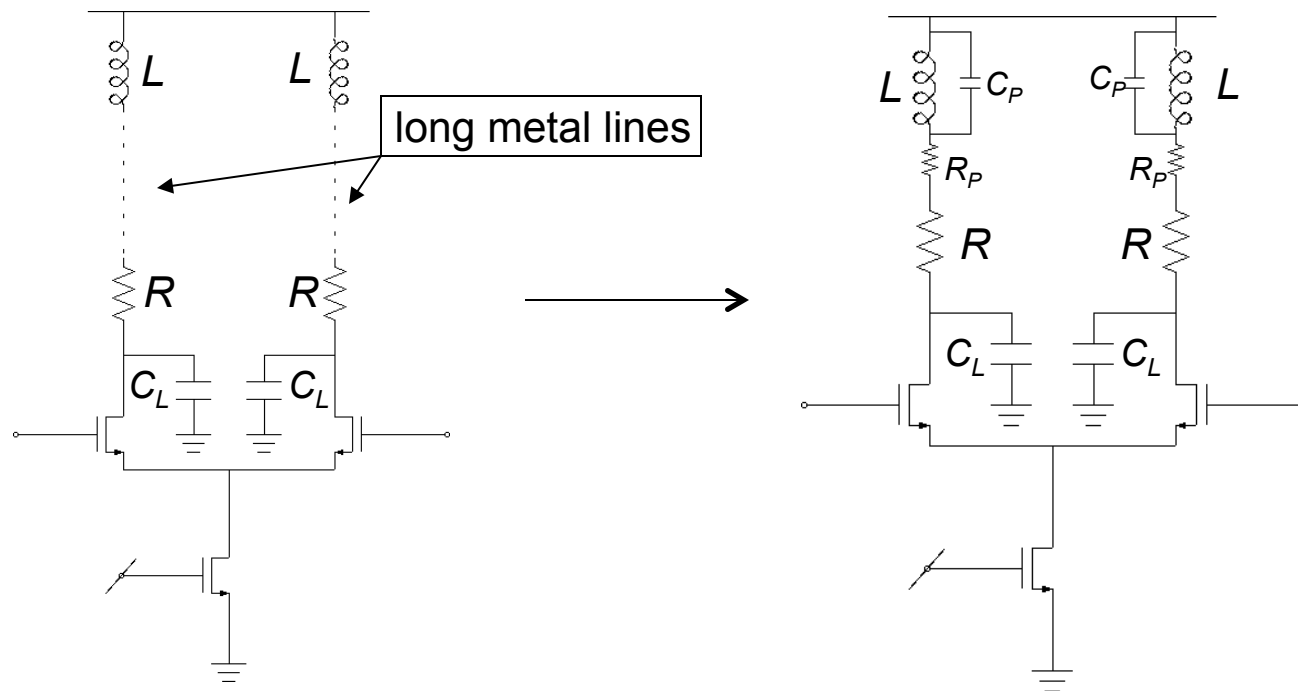
Effect of Shunt-Peaking Inductor Parasitics (1)



- Series resistance R_P simply adds to R
- Shunt capacitance C_P resonates with L ...


Effect of Shunt-Peaking Inductor Parasitics (2)

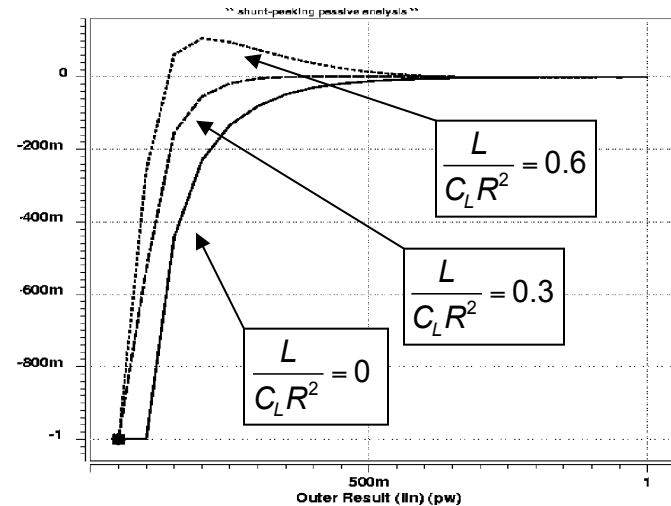ISI (UI) vs. input pulse width
 $C_P = 0$



Moderate amount of parasitic capacitance has similar effect to slightly larger inductor.

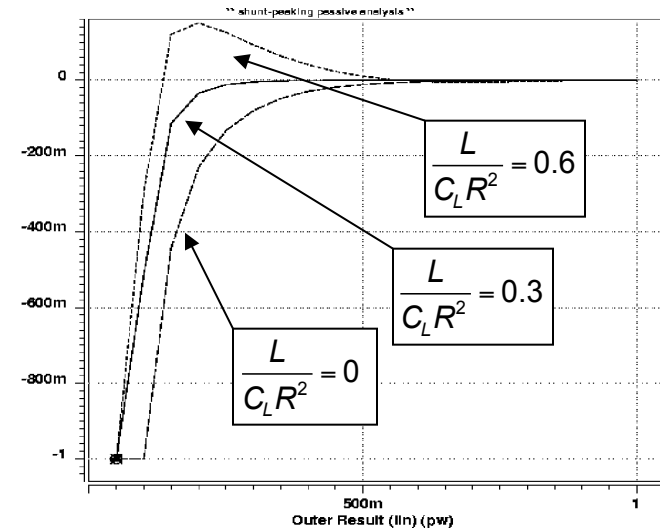
ISI (UI) vs. input pulse width
 $C_P = 0.2C_L$



Disadvantages of using passive inductors:

- Consume huge die area
- Difficult to design & model


Multi-layer Inductors (1)

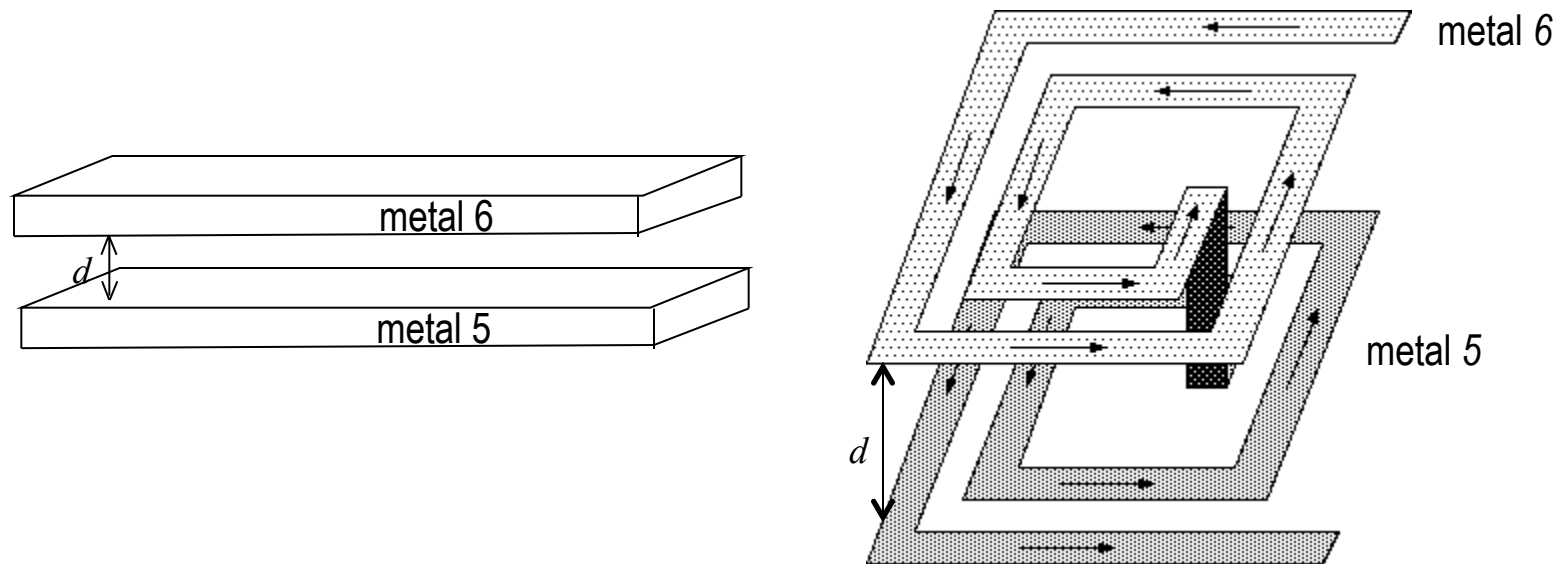

Distance d between two metal layers is much smaller than lateral distances (e.g., w , l , s)

Multi-layer Inductors (2)

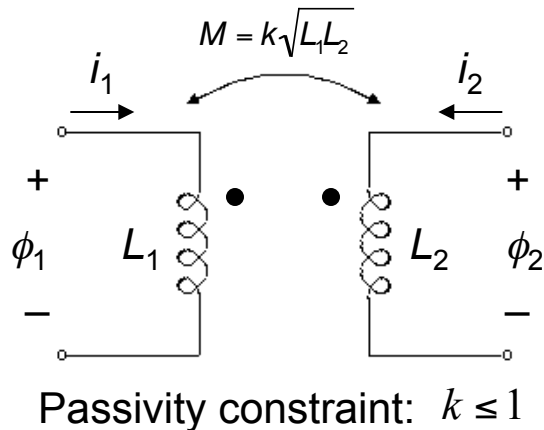
2-port representation of coupled inductors:



$$\begin{pmatrix} \phi_1 \\ \phi_2 \end{pmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

For metal geometries close to each other, k is close to unity.

series connection of coupled inductors:

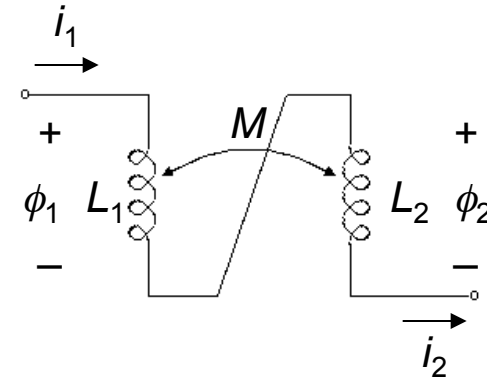

$$\phi_{\text{series}} = \phi_1 + \phi_2 = (L_1 + M)i_1 + (L_2 + M)i_2$$

$$i_{\text{series}} = i_1 = i_2$$

$$\Rightarrow L_{\text{series}} = \frac{\phi_{\text{series}}}{i_{\text{series}}} = L_1 + L_2 + 2M$$

For $L_1 = L_2 = L$, we have: $L_{\text{series}} = 2L + 2M = 2L(1 + k) \approx 4L$

In general, for n layers we have: $L_{\text{series}} \approx n^2 L$


Multi-layer inductors are more appropriate for shunt-peaking than resonant structures due to additional contact resistance.

Multi-layer Inductors (3)

Effective Capacitance:

$$L_{\text{effective}} \approx 4L$$
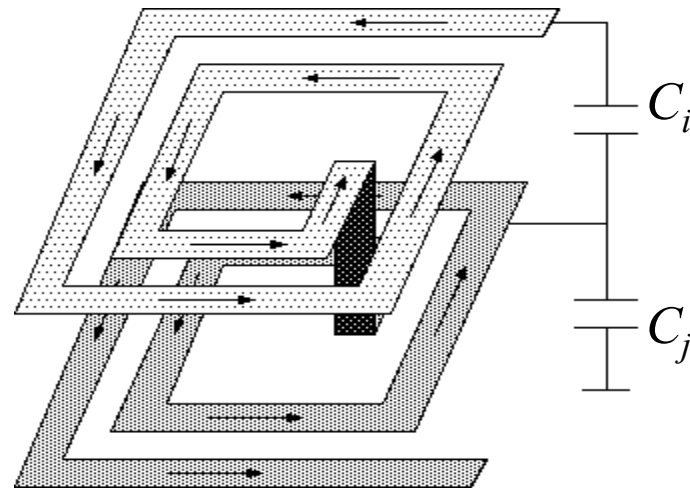
$$C_{\text{effective}} \approx \frac{1}{3}C_i + \frac{1}{12}C_j$$



For more details, see:


A. Zolfaghari, A. Chan & B. Razavi, "Stacked inductors and transformers in CMOS technology,"

IEEE Journal of Solid-State Circuits, vol. 36, April 2001, pp. 620-628.




Multi-layer Inductors (4)

Area comparison:

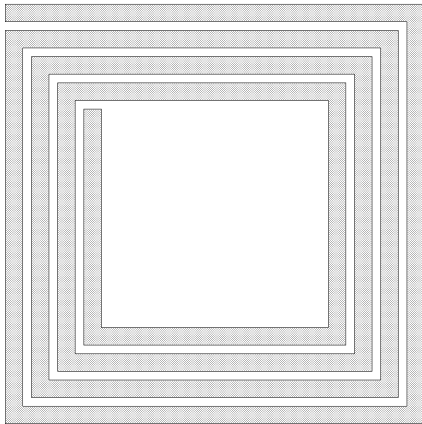metal 6 only
 $100\mu \times 100\mu$
 $w = 4; s = 2; n = 4$
 $L = 2.0 \text{ nH}$
 $R = 6.9 \Omega$




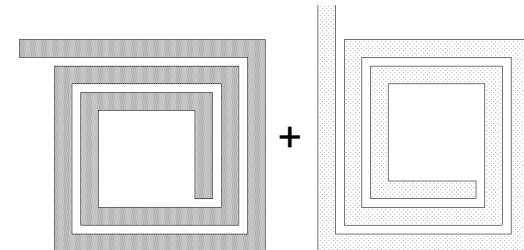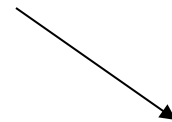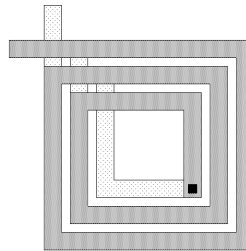metal 6 over metal 4
 $46\mu \times 46\mu$
 $w = 4; s = 2; n = 2.5$
 $L = 2.0 \text{ nH}$
 $R = 12.5 \Omega$



Active Inductors (1)


Ideal gyrator:

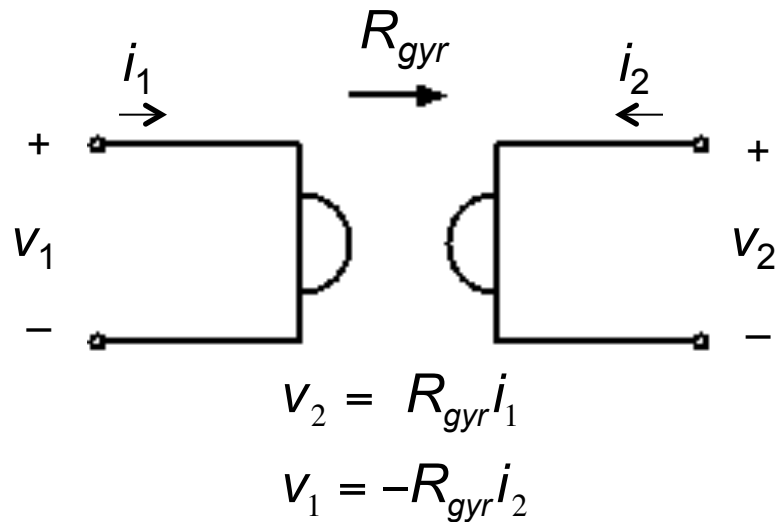

Matrix representation (Z-parameters):

$$\begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{bmatrix} 0 & -R_{gyr} \\ R_{gyr} & 0 \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$


Impedance inversion:

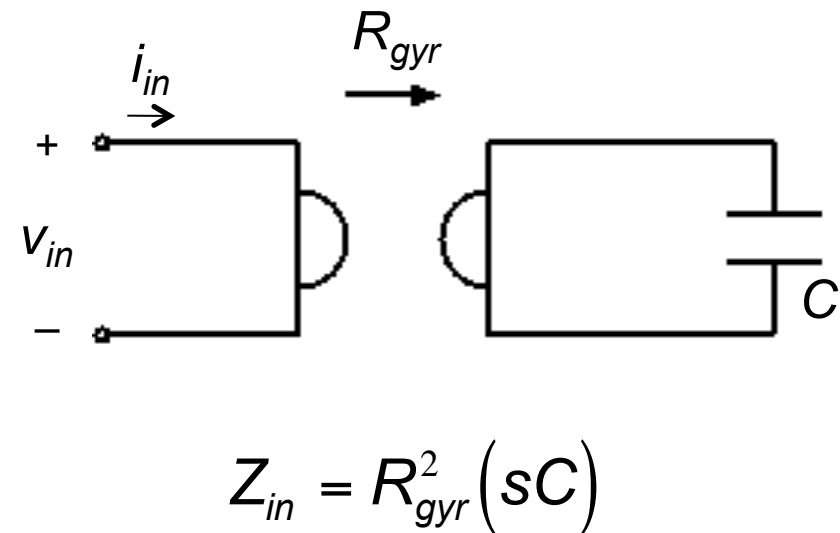

Port 1 exhibits inductance when port 2 is connected to a capacitance.

Active Inductors (2)

Consider common-drain configuration:

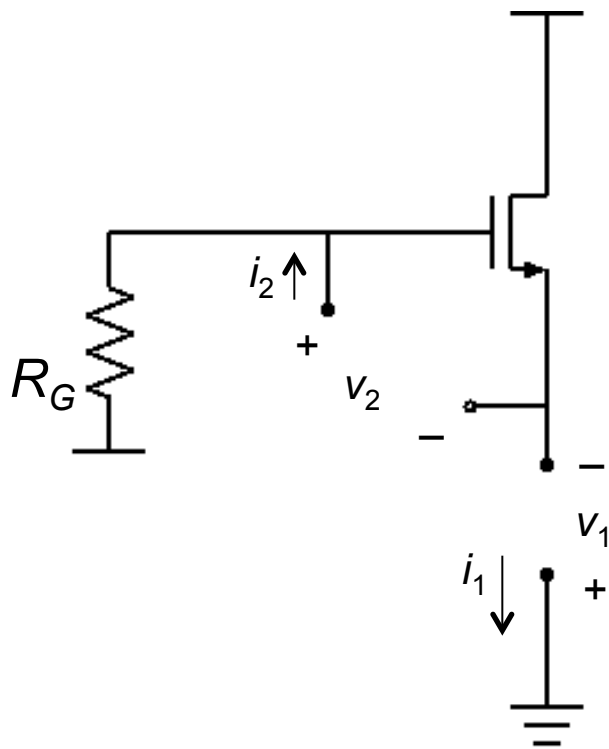

i_1 applied with port 2 open-circuited:

$$v_2 = \frac{1}{g_m} i_1$$

i_2 applied with port 1 open-circuited:


$$v_1 = -\left(R_G - \frac{1}{g_m}\right) i_2 \quad (\text{Assume } R_G g_m > 1)$$

Complete Z-parameters (lossy/active gyrator):

$$\begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{bmatrix} 1/g_m & -(R_G - 1/g_m) \\ 1/g_m & 1/g_m \end{bmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$


Active Inductors (3)

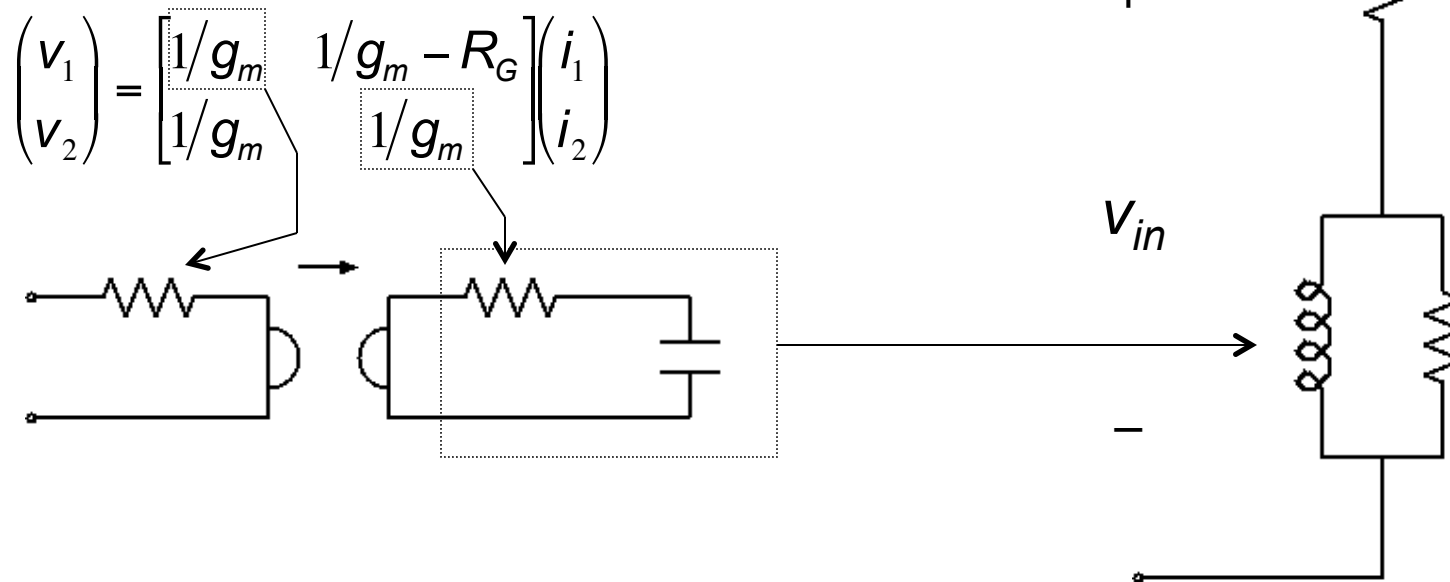Interpretation of non-ideal matrix entries:



Active Inductors (4)

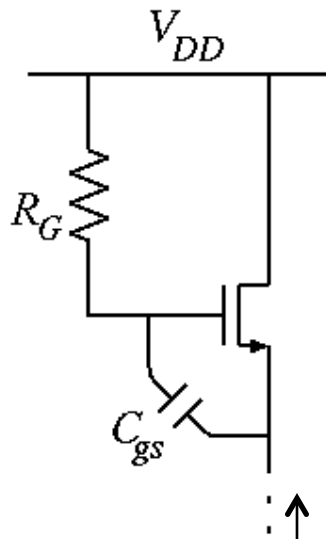Impedance at port 1 with port 2 terminated with transistor C_{gs} :




At low frequencies (C_{gs} open) $\Rightarrow Z_{source} = 1/g_m$


At high frequencies (C_{gs} short) $\Rightarrow Z_{source} = R_G$

$$Z_{source} = \frac{1}{g_m} \left[\frac{1 + sC_{gs}R_G}{1 + sC_{gs}/g_m} \right]$$


Active Inductors (5)

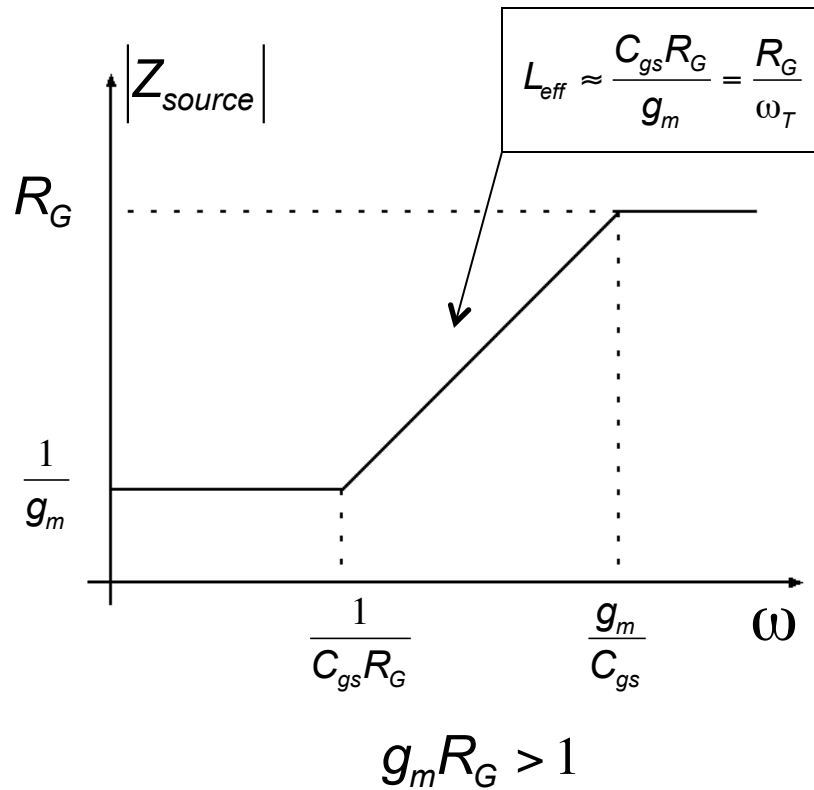

Equivalent circuit:

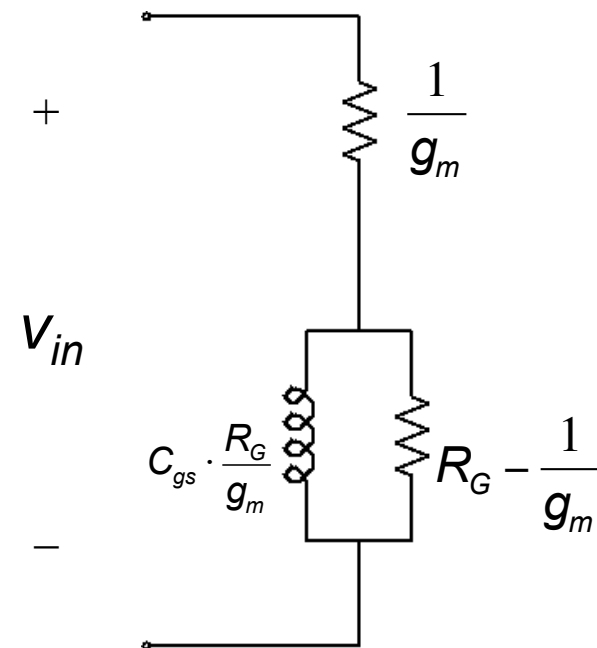

CML Buffer with Active Inductor Load

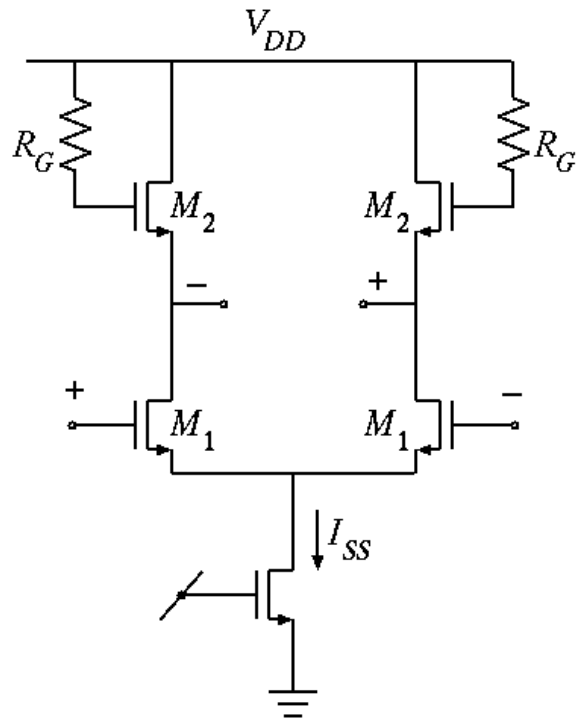

$$\left(\frac{W}{L}\right)_1 = \frac{4}{0.18} \quad \left(\frac{W}{L}\right)_2 = \frac{2.5}{0.18}$$

$$I_{SS} = 400 \mu\text{A}$$

Low-frequency gain:

$$A_v = \frac{g_{m1}}{g_{m2}} = \sqrt{\frac{W_1}{W_2}}$$



For shunt peaking:

$$L \approx 0.3 C_L R^2$$




$$\frac{C_{gs} R_G}{g_{m2}} = 0.3 \frac{C_L}{g_{m2}^2} \longrightarrow g_{m2} R_G = 0.3 \frac{C_L}{C_{gs}}$$

Active Inductor AC Response

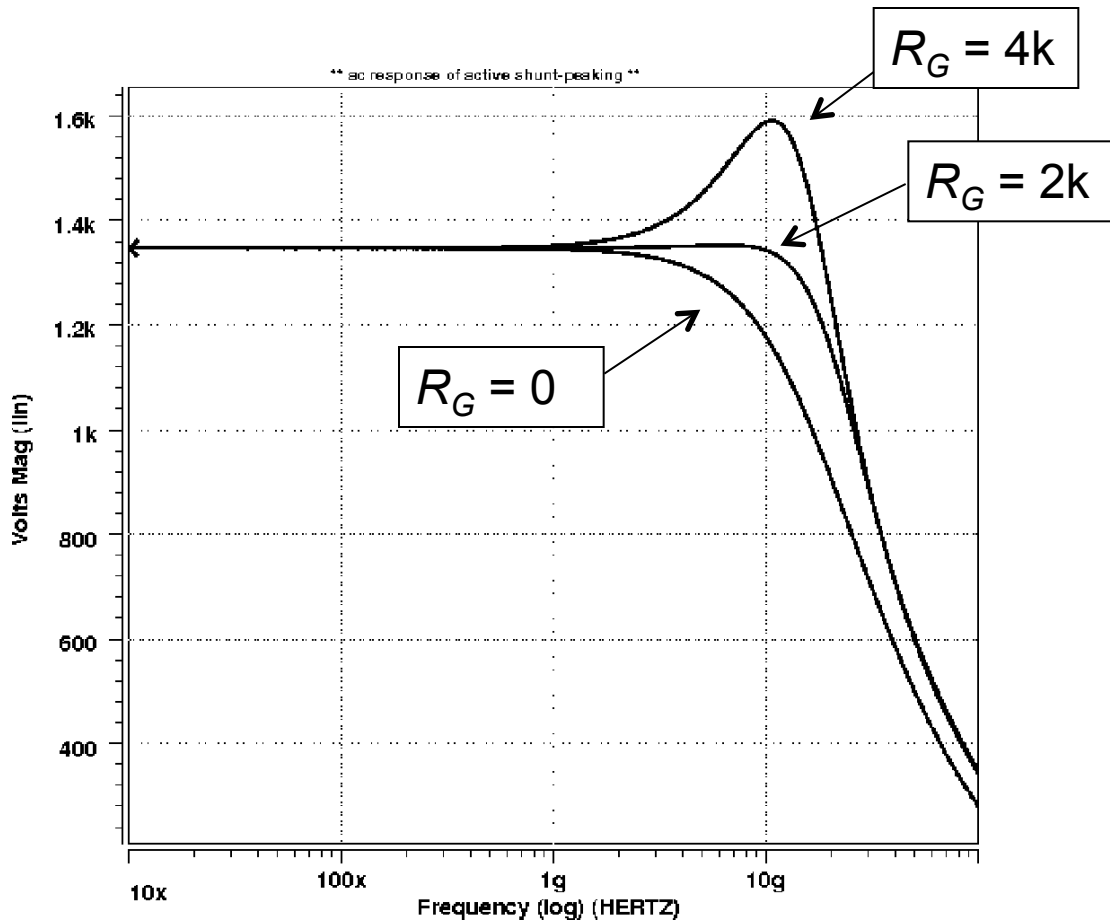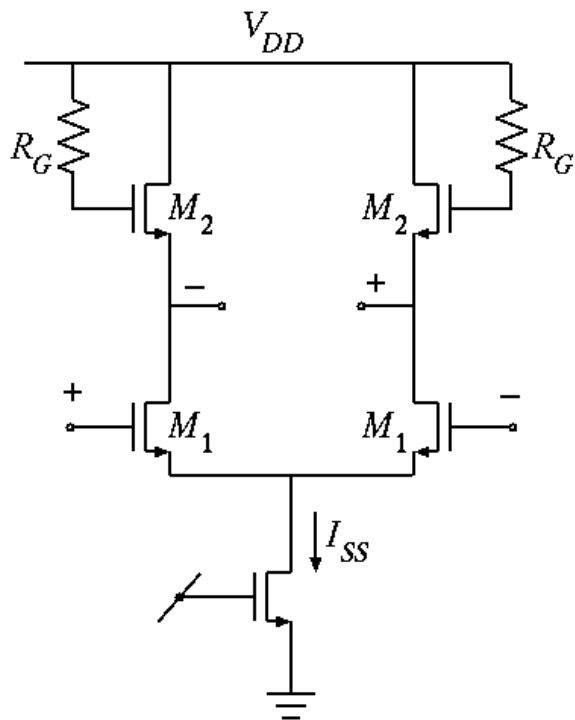


Active Inductor Transient Response (1)


Differential signals:

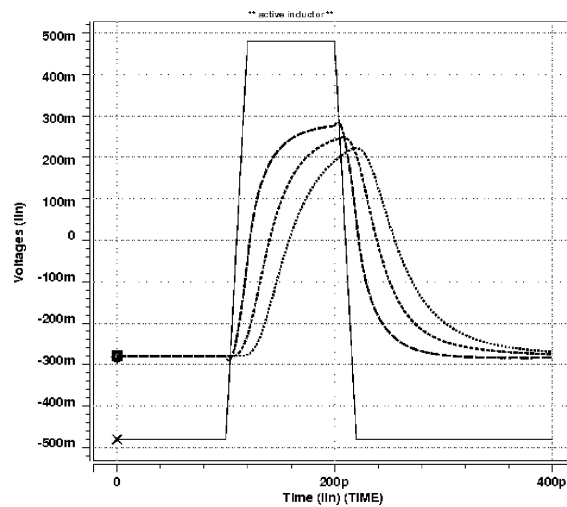

$R_G = 0$
PW = 97ps

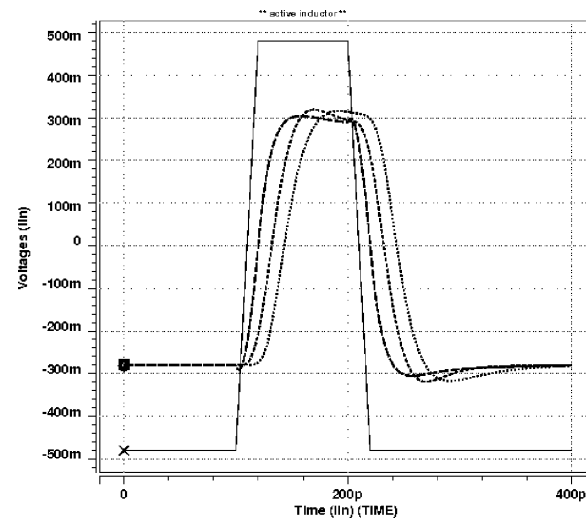

$R_G = 5k$
PW = 100 ps


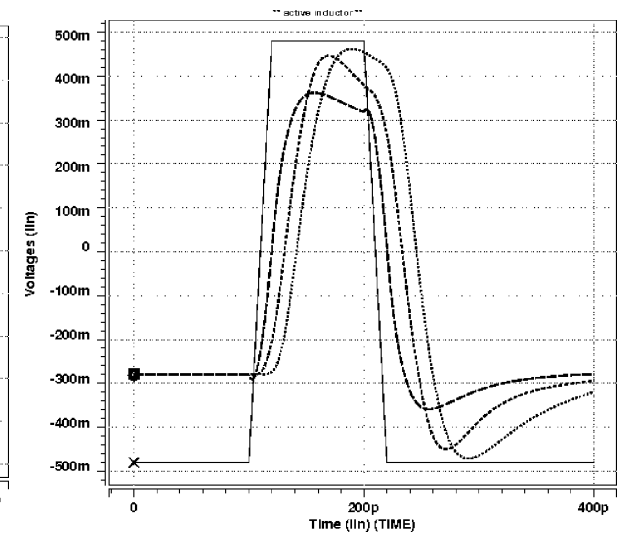


$R_G = 10k$
PW = 104 ps

Active Inductor Transient Response (2)



Single-ended signals:

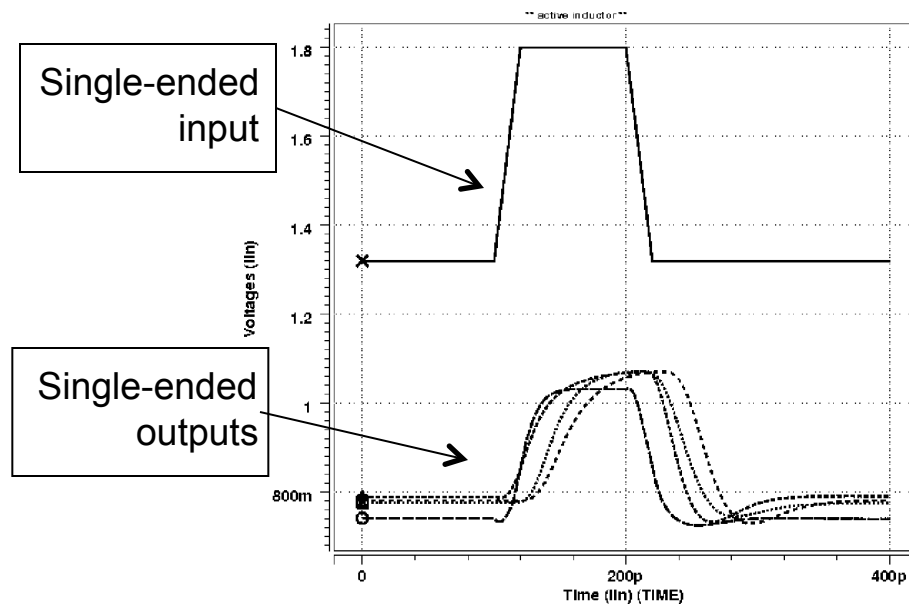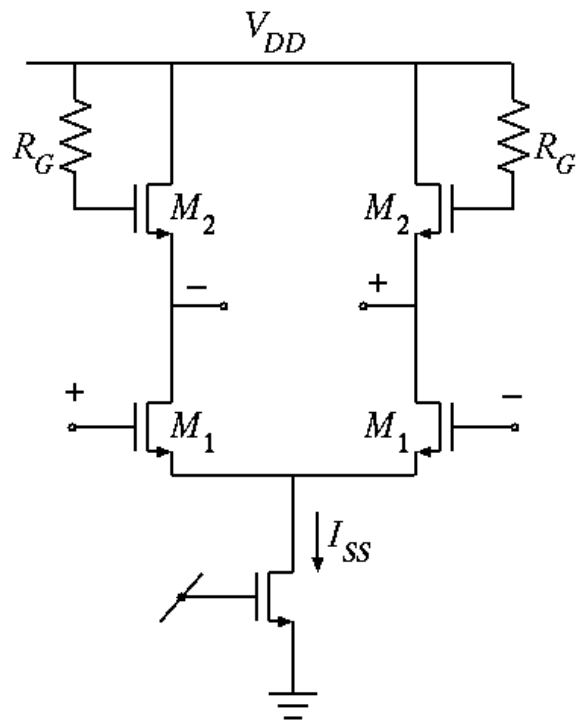Problem: n-channel load shifts output by V_t .
 $V_{sb} > 0$; body effects exacerbates this effect..




Active Inductor Alternate Topology

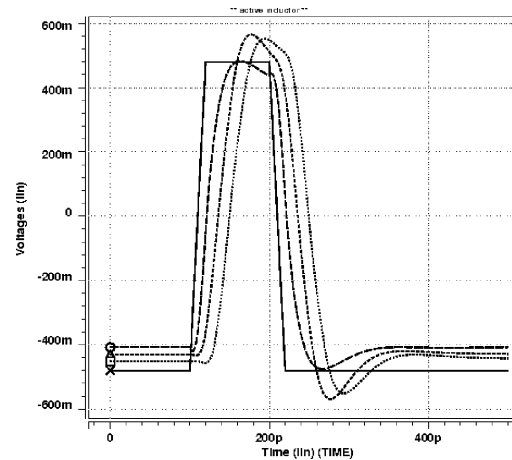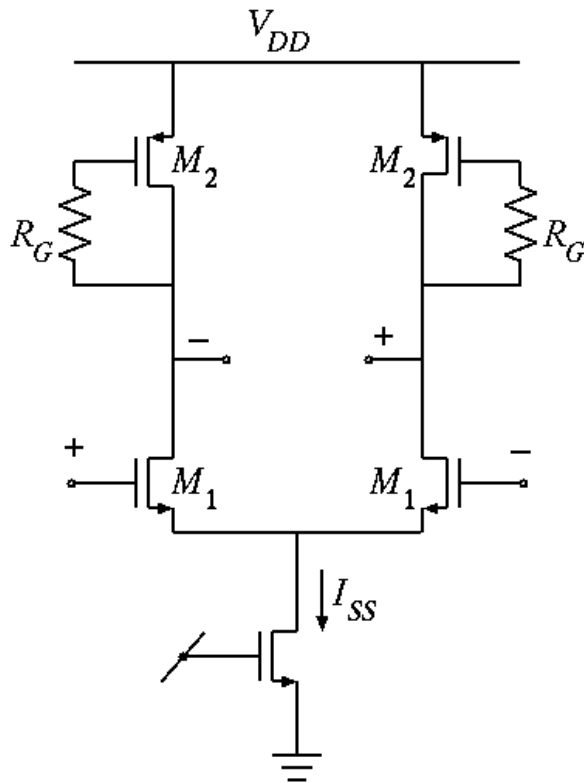Alternate topology:
p-channel load exhibits lower V_t
($V_{bs} = 0$)



differential

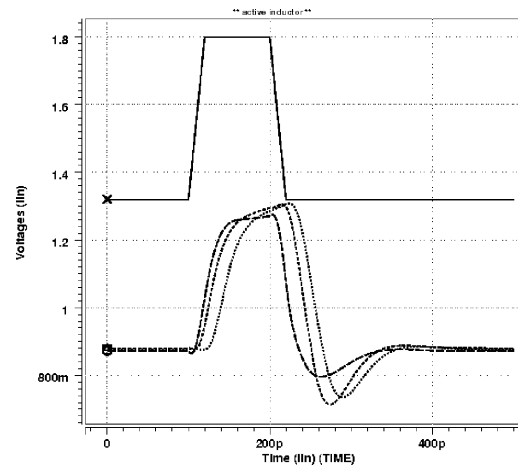

single-ended