

Dynamic-Offset Cancellation Techniques in CMOS

Kofi Makinwa

Electronic Instrumentation Laboratory

Delft University of Technology

Delft, The Netherlands

email: k.makinwa@ieee.org





Motivation

- Many analog circuits e.g. opamps, integrators, comparators, ADC and DAC stages etc. require amplifiers with offsets in the **microvolt** range
- Also, many sensors (e.g. thermopiles, bridges, hall-effect sensors etc.) output DC signals that need to be processed with **microvolt** precision
- However, the offset of native CMOS amplifiers is typically in the **millivolt** range
- This tutorial will focus on **dynamic** offset-cancellation (DOC) techniques, with which offset can be reduced to the **microvolt** level.

Outline

- Differential amplifiers
 - Offset and $1/f$ noise
- Trimming
- Dynamic Offset Cancellation
 - Auto-zeroing
 - Chopping
- Design of a CMOS temperature sensor
- Summary
- References

What is Offset?

  


- When the input of a REAL amplifier is shorted, $V_{out} \neq 0$!
- The **offset** V_{os} is the input voltage required to make $V_{out} = 0$. It is typically in the range $100\mu\text{V}$ to 10mV .
- Note: In CMOS, input currents are usually negligible.

Amplifier Behaviour Near DC

Characterized by

 - Offset
- Drift
- $1/f$ (flicker) noise
- Thermal noise
- $1/f$ corner frequency
- Errors due to finite CMRR and PSRR




Differential Amplifiers

Differential amplifiers are often used to amplify DC signals.

Their balanced structure is

 - Nominally offset free
- Rejects common-mode and power supply interference
- Easily realized in both CMOS and bipolar technologies



Offset in Differential Amplifiers

Component mismatch


e.g. $R_1 \neq R_2$, $M_1 \neq M_2 \Rightarrow$ **offset**

Mismatch is mainly due to

- Doping variations
- Lithographic errors
- Packaging & local stress

All things being equal

 - Bipolar $\Rightarrow V_{os} \sim 0.1\text{mV}$
- CMOS $\Rightarrow V_{os}$ is 10 -100x worse!



What to Do?

Offset and $1/f$ noise are part of life!

But we can reduce offset “enough” by

1. Using “large” devices and good layout¹ \Rightarrow 1mV
2. Trimming \Rightarrow 100 μ V
3. Dynamic offset-cancellation (DOC) techniques \Rightarrow 1 μ V

DOC techniques also

- Reduce drift and $1/f$ noise
- Improve PSRR and CMRR

Trimming

- Low circuit complexity
- Minimal effect on circuit bandwidth
- Requires a memory element, e.g.
 - Fusible links (Zener diodes)
 - Laser-trimmed resistors
 - Floating gate MOSFETs
 - PROM
- Requires test infrastructure
- Does not reduce drift or $1/f$ noise
- Poorly defined temp. dependence of MOSFETs
⇒ offset after trimming $> 100\mu\text{V}$ over temp.

Dynamic Offset Cancellation (DOC)

Two basic ideas²

1. Measure the offset somehow and then subtract it from the input signal \Rightarrow Auto-zeroing
2. Modulate the offset away from DC and then filter it out \Rightarrow Chopping

DOC Techniques

Auto-zeroing

Discrete time

Sample offset,
then subtract.

Chopping

Continuous time

Modulate offset
away from DC,
then filter.


Switches required \Rightarrow CMOS or BiCMOS

DOC Techniques vs. Trimming

- + reduction of offset and $1/f$ noise
- + excellent stability (over temperature, time, supply and common-mode voltages)
- + no additional costs for testing

- possible bandwidth reduction
- increased circuit complexity
- aliasing & intermodulation issues


Auto-zero Principle (1)

 

Auto-zero phase

- S_1, S_2 closed, S_3 open $\Rightarrow V_{out} = V_{os}$
 \Rightarrow offset stored on C_{az}
- Amplifier is unavailable


Auto-zero Principle (2)

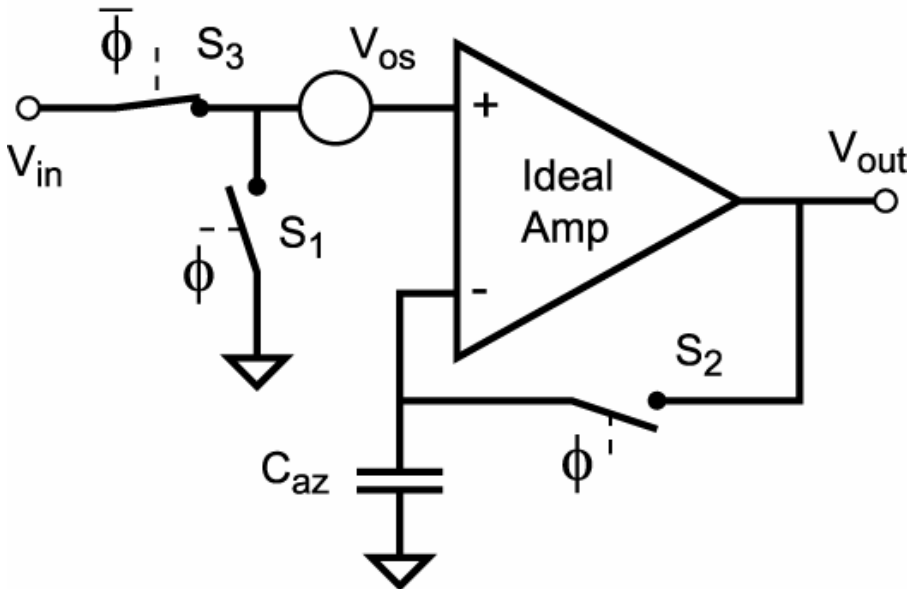

Amplification phase:

- S_1, S_2 open, S_3 closed $\Rightarrow V_{in}$ is amplified
- *Finite* voltage gain $A \Rightarrow$ error in sampled offset \Rightarrow input-referred residual offset $V_{res} = V_{os}/(A+1)$
- Charge injection is also a problem ...

Charge Injection (1)

 


Consists of two components

1. Channel charge, $Q_{ch} = WLC_{ox}(V_{GS} - V_t)$
2. Charge in the overlap capacitance between the gate and the source/drain \Rightarrow clock feed-through

Problematic when a MOSFET switches **OFF**.

Charge Injection (2)


 


Error voltage ΔV_{inj} depends on many factors^{3,4}


- Source voltage and impedance
- Transistor area (WL)
- Clock amplitude & slew rate
- Value of C_{az} (larger values \Rightarrow smaller errors)
- In a $0.7\mu\text{m}$ process, minimum size NMOS switch, 2.5V step & 10pF $\Rightarrow \Delta V_{inj} \sim 250\mu\text{V}$

Mitigating Charge Injection (CI)

  - Use differential topologies
 - ⇒ common-mode CI
 - ⇒ 1st order cancellation
- Use minimum size switches (subject to noise & BW requirements)
- For single-ended topologies dummy switches help^{3,4}
- **But** area of main switch will be ~2x minimum size ⇒ more CI ⇒ limited benefit




Sampling the offset: kT/C noise

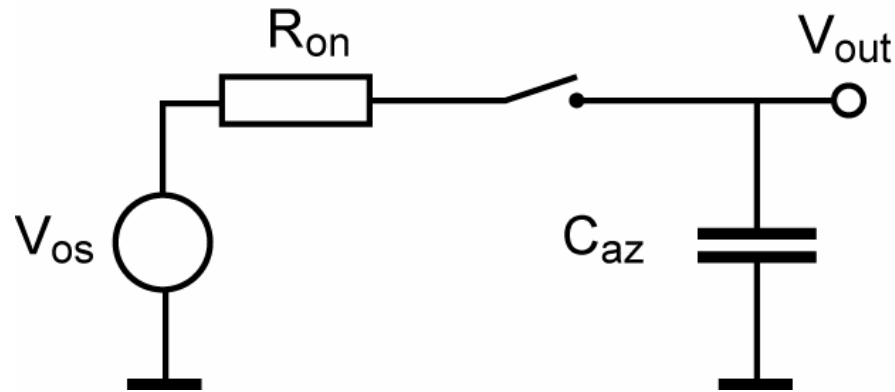

- Thermal noise of R_{on} is filtered by C_{az}
- When the switch is opened the instantaneous noise voltage is held on C_{az}
- Total noise power = kT/C_{az} (10pF @ 300K \Rightarrow 20.3 μ V)
- Large capacitance \Rightarrow accurate sampling of V_{os}


Reducing Capacitor Size (1)

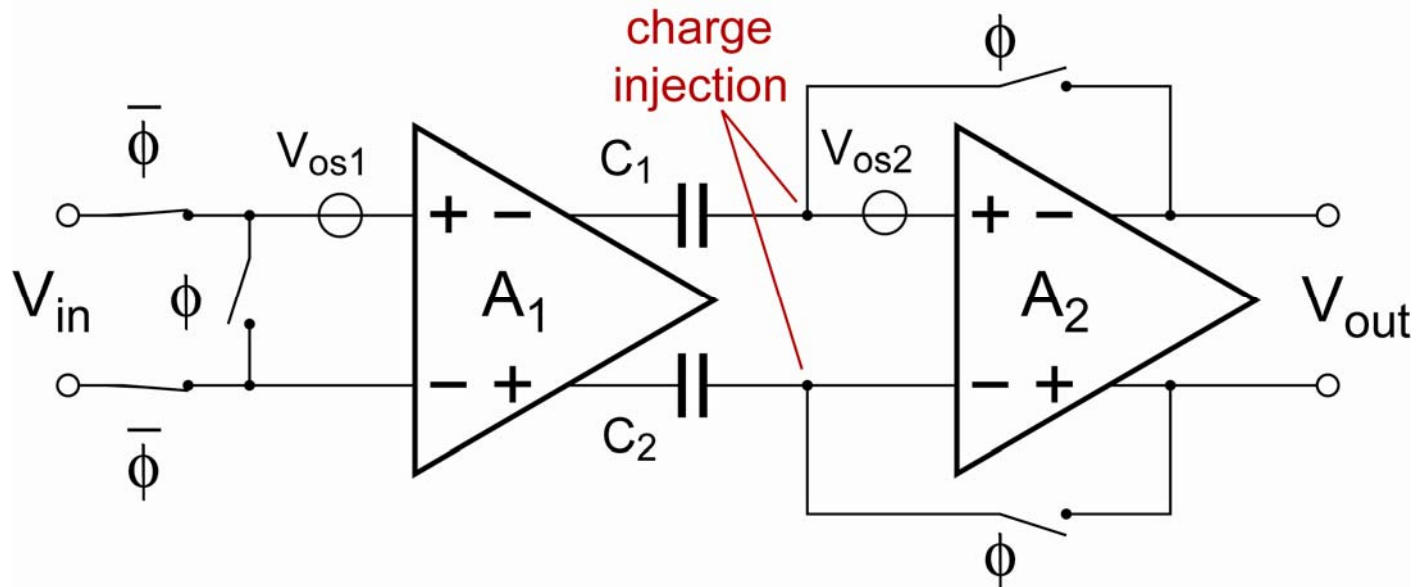

$$V_{res} = V_{os2}/(A_1 A_2) + \Delta V_{inj}/A_1$$

- Offset of 1st amplifier is cancelled^{5,6}
- Gain of 1st amplifier reduces offset of 2nd amplifier
- **But** too much gain \Rightarrow clipping!
- Also reduces kT/C noise and charge injection errors
 \Rightarrow Sampling capacitors can be smaller

Reducing Capacitor Size (2)

 

Amplifier with an auxiliary input^{7,8}

- $V_{res} \sim V_{os1}/(gm_2 R) + V_{os2}/(gm_1 R) + \Delta V_{inj}(gm_2/gm_1)$
- Large R and $gm_2 \ll gm_1 \Rightarrow$ low-offset and reduced kT/C noise and charge injection errors

\Rightarrow Sampling capacitors can be smaller

Residual Offset of Auto-zeroing

Determined by

- Charge injection
- Leakage on C_{az}
- Finite amplifier gain

In practice

- Minimum size switches
- C_{az} as large as possible (sometimes external)
- Multi-stage amplifier topologies

Results in residual offsets of 1-10 μ V

Residual Noise of Auto-zeroing (1)

$$V_{n,az}(f) = V_n(f) * (1 - H(f))$$


$H(f)$ is the frequency response of the S&H

$H(f) = \text{sinc}(\pi f/f_s) \Rightarrow$ LPF


$\Rightarrow 1 - H(f)$ is a HPF

\Rightarrow reduction of both offset and $1/f$ noise

 \Rightarrow but thermal noise will be (under) sampled





Residual Noise of Auto-zeroing (2)

 


- **Noise** bandwidth $B > f_s$ (due to settling considerations) \Rightarrow input noise will be folded back (aliased) to DC
- The result is then LP filtered by the $\text{sinc}(\pi f/f_s)$ function

Residual Noise of Auto-zeroing (3)

 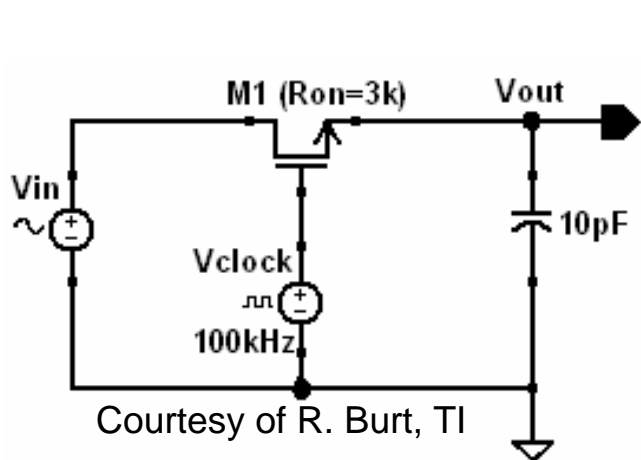

- S&H with 100kHz clock & 50% duty-cycle
- Noise aliasing \Rightarrow factor of 6 increase in LF noise!
- Notches at multiples of $2f_{\text{clock}}$ due to 50% duty cycle²
- Sampled noise spectrum obtained with Spectre RF^{9,10}


Residual Noise of Auto-zeroing (4)

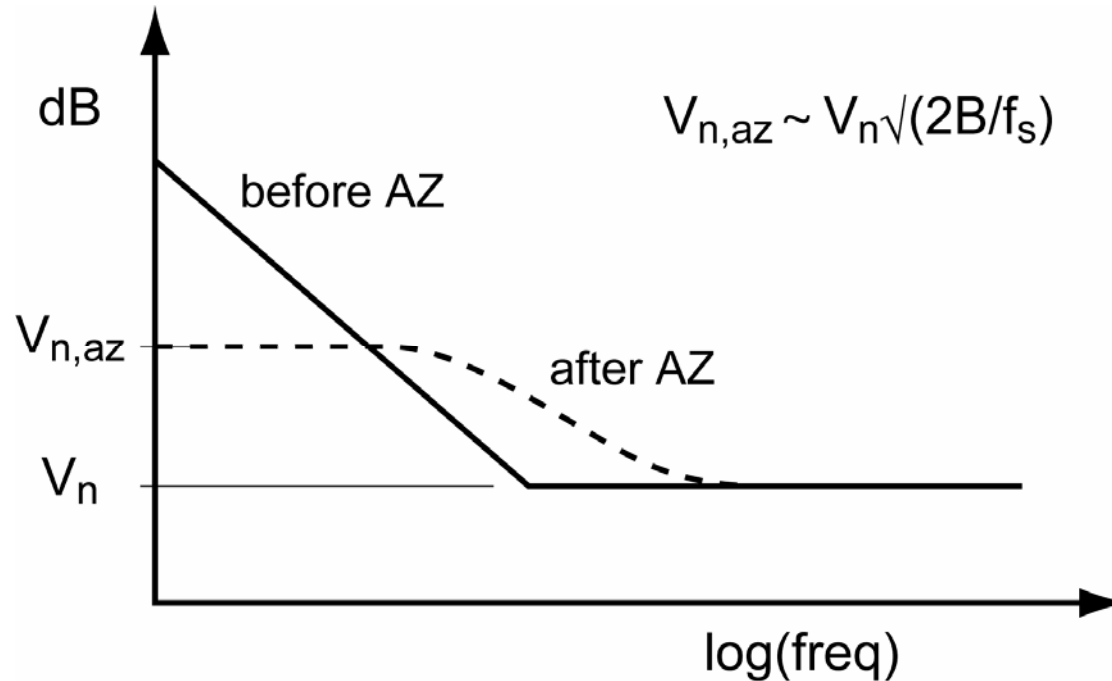

- Detailed analysis² \Rightarrow significant reduction of $1/f$ noise **IF** $f_s \gg 1/f$ corner frequency
- Noise aliasing \Rightarrow LF power increased by the under-sampling factor (USF) = $2B/f_s \Rightarrow$ factor 3 to 6 in volts

Ping-Pong Amplifier

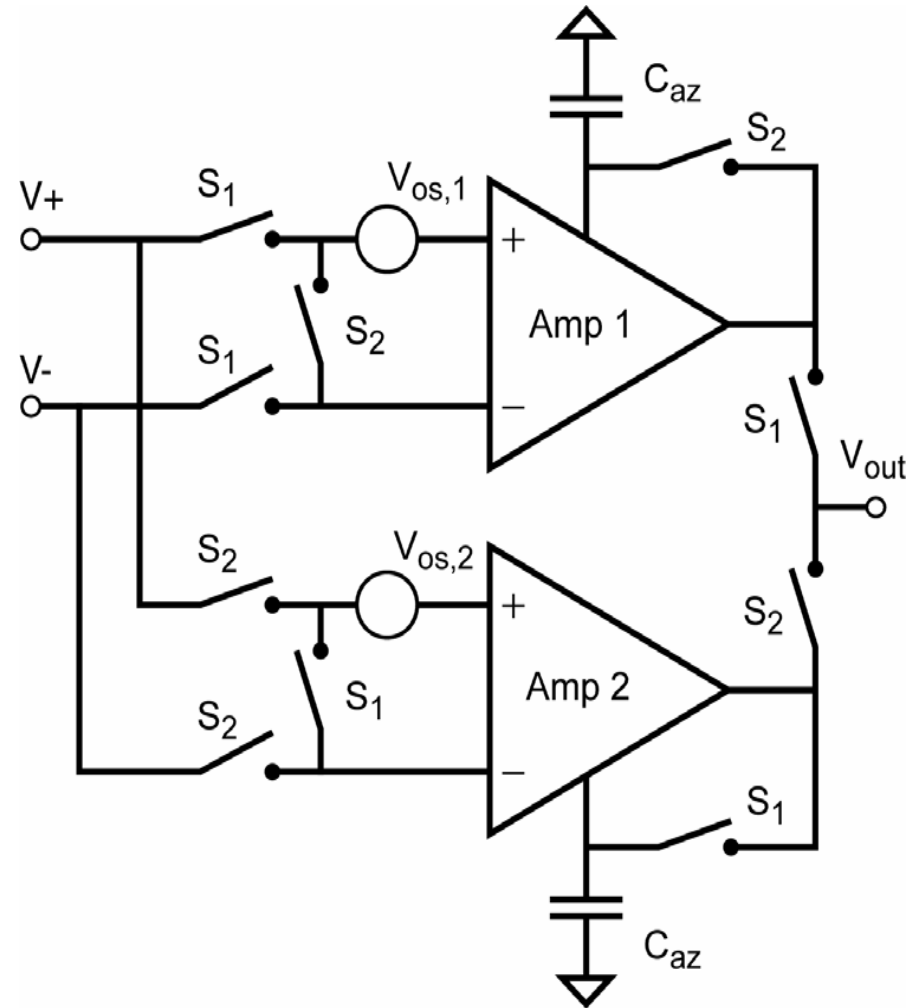
- Input signal “bounced” between two auto-zeroed amplifiers^{11,12}
- Output V_{out} is then a quasi-continuous signal
- But switching spikes limit performance
- Randomized switching reduces spikes¹³



Offset Stabilization (OS)

Negative feedback
⇒ offset visible at input


High bandwidth
main amplifier

 


Low bandwidth, low offset compensating amplifier
⇒ Auto-zeroed or chopped

AZ Offset-Stabilized Amplifier

 - Auto-zeroed nulling amp cancels the offset of main amplifier^{14,15}
- Continuous output and less spikes
- But poor overload performance, i.e. when $V_+ - V_- > V_{os}$
- Amplifier cannot be used as a comparator




System-level Auto-zeroing

 


- Phase 1: $V_1 = A(V_{os} + V_{in})$
 - Phase 2: $V_2 = AV_{os}$
- $\Rightarrow (V_1 - V_2) = AV_{in}$
- Offset stored in the digital domain
 - Widely used in instrumentation & measurement systems

Correlated Double Sampling (CDS)

 

- Sometimes only a signal **difference** is required e.g. in image sensors
- Phase 1: $V_1 = A(V_{in1} + V_{os})$
- Phase 2: $V_2 = A(V_{in2} + V_{os})$
- $\Rightarrow (V_1 - V_2) = A(V_{in1} - V_{in2})$
- To maximize suppression of $1/f$ noise, the interval $t_1 - t_2$, should be as short as possible

The 3 Signal Method

 

- Phase 1: $V_1 = A(V_{os} + V_{in})$
- Phase 2: $V_2 = A(V_{os} + V_{ref})$
- Phase 3: $V_3 = AV_{os}$


$$\Rightarrow V_{in} = V_{ref}(V_1 - V_3)/(V_2 - V_3)$$

Requires a known reference voltage
and a microprocessor to perform the division

Auto-Zeroing: Summary

- Offsets in the range of 1-10 μ V can be achieved
- No loss of bandwidth with appropriate amplifier topologies (ping-pong, offset-stabilization)
- Sampled data technique \Rightarrow kT/C noise is an issue
- Noise aliasing will occur \Rightarrow increased LF noise
- DOC technique of choice in sampled-data systems e.g. switched-capacitor filters, ADCs etc.


Chopping Principle

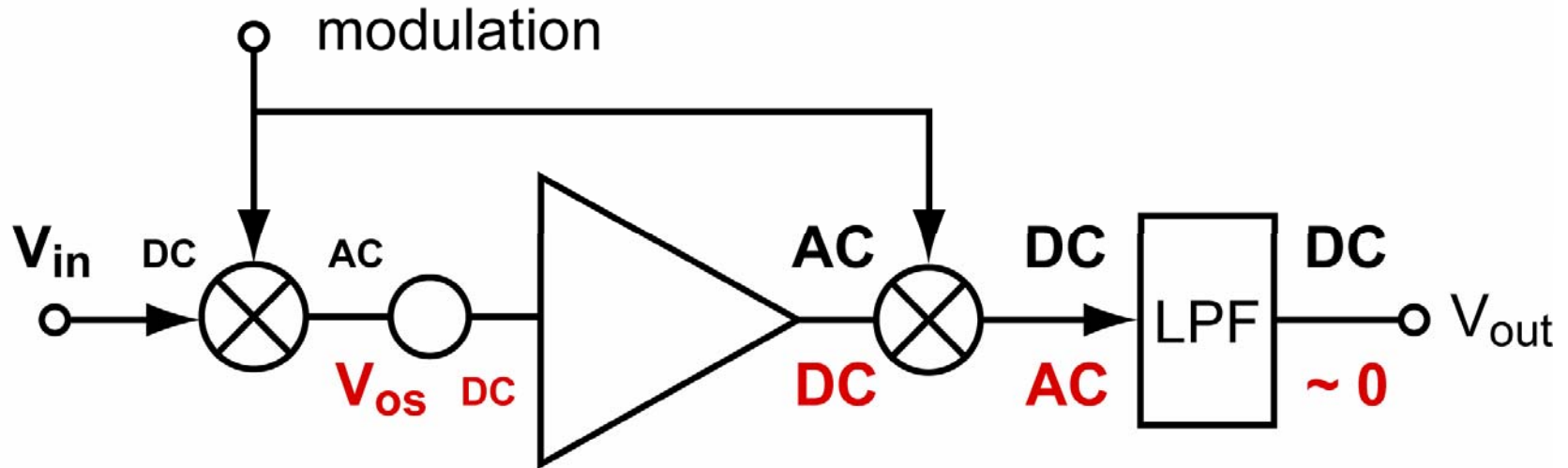

Signal is modulated, amplified and then demodulated¹⁶


- + Output signal is continuously available
- Low-pass filter required

Square-wave Modulation

 


- Easily generated modulating signal
- Modulator is a simple polarity-reversing switch
- Switches are easily realized in CMOS

Chopping in the Time Domain

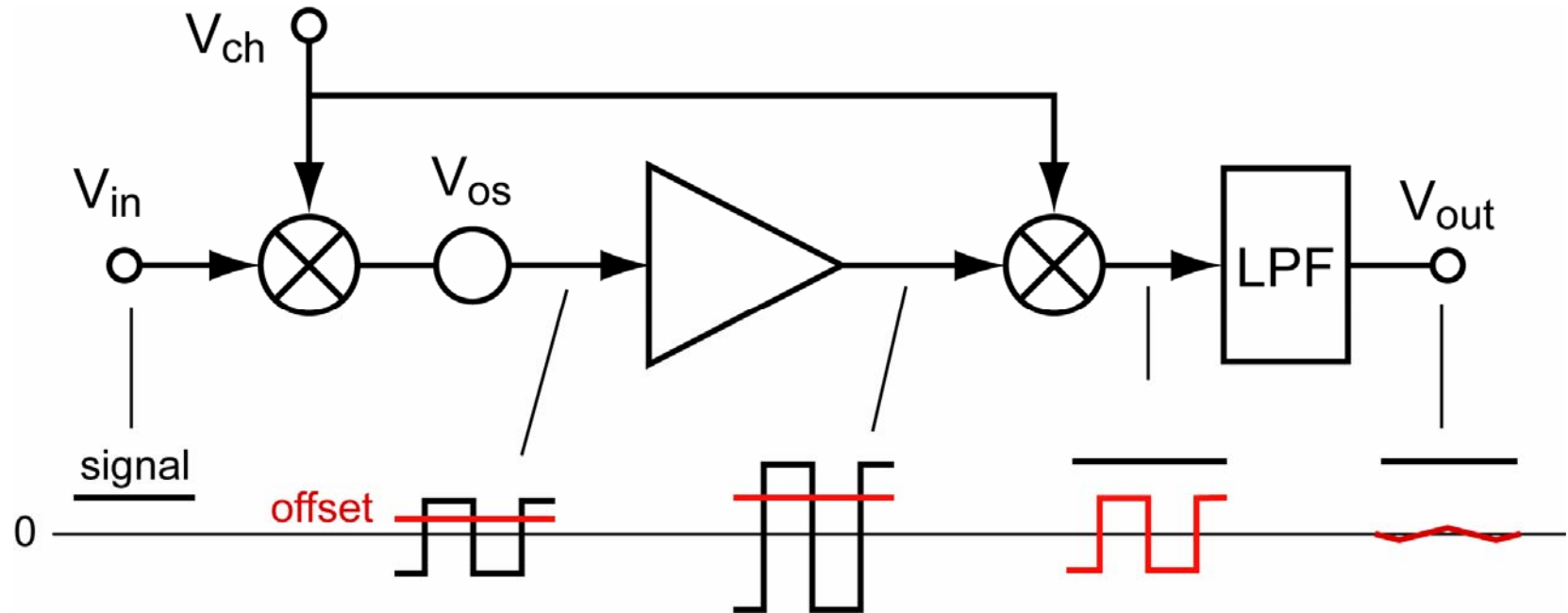


- $V_{res} = 0$ **IF** duty-cycle of V_{ch} is exactly 50% \Rightarrow flip-flop
- If $V_{os} = 10\text{mV}$ & $f_{ch} = 50\text{kHz}$, then 1ns skew $\Rightarrow V_{res} = 1\mu\text{V}$

Chopping in the Frequency Domain

 


Residual Noise of Chopping

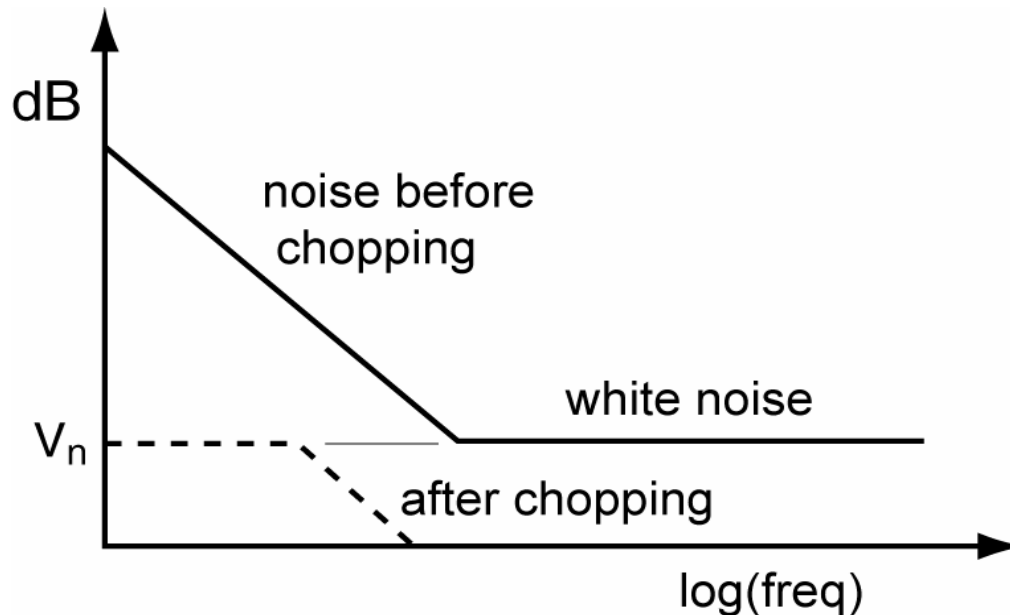


- $1/f$ noise is **completely** removed
IF $f_{ch} > 1/f$ corner frequency
- Significantly better than auto-zeroing!

Bandwidth & Gain Accuracy

 


- Limited BW \Rightarrow lower effective gain A_{eff}
and chopping artifacts at even harmonics of f_{ch}
- $A_{\text{eff}} = A (1 - 4\tau/T_{\text{ch}})$ for a 1st order LP filter,
where $\text{BW} = 1/2\pi\tau$ and $\tau \ll T_{\text{ch}}$
- $T_{\text{ch}}/\tau = 40 \Rightarrow \text{BW} = 6.4f_{\text{ch}} \Rightarrow 10\%$ gain error!

Chopper Opamp with Feedback

 


- Feedback resistors \Rightarrow Accurate gain^{17,18}
- To suppress V_{os2} , A_1 should have high gain
- Miller capacitors C_m also suppress ripple
- Minimum ripple \Rightarrow high chopping frequencies

Residual Offset of Chopping (1)

 

- Due to mismatched charge injection and clock feed-through at the input chopper^{19,20}
- Causes a typical offset of 1-10 μ V
- Input spikes \Rightarrow bias current (typically 50pA)

Residual Offset of Chopping (2)

 

- Residual offset² = $2f_{\text{ch}} V_{\text{spike}} \tau$
- Spike shape (τ) depends on source impedance e.g. feedback resistors around an opamp

Design Considerations

Input chopper


- Use minimum size switches
- Good layout \Rightarrow symmetric, balanced clock coupling
- Ensure that switches “see” equal impedances
- Use a flip-flop to ensure an exact 50% duty-cycle

Chopping frequency f_{ch}

- Higher than $1/f$ noise corner frequency
- Not **too** high, as the residual offset increases with f_{ch}

Amplifier BW $\gg f_{ch}$ to minimize gain errors

Band-Pass Filtering

 


Courtesy of C. Hagleitner, IBM


- Spike spectrum is “whiter” than that of modulated signal
⇒ BP filter will reduce **relative** spike amplitude^{19,21,22}
- Clock frequency tracks BP filter's center frequency
⇒ low Q filter, $Q \sim 5$
- Residual offset $\sim 0.5\mu\text{V}$!

Delayed Demodulation

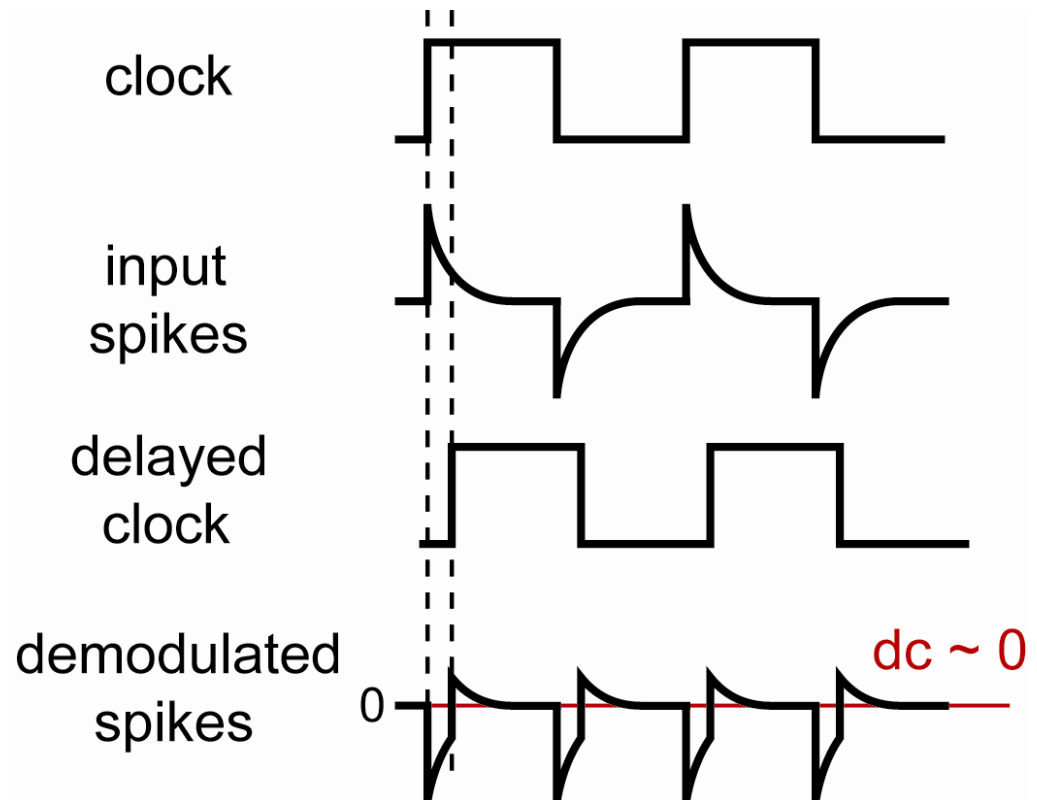- Optimal delay
 $\sim 0.7\tau_{\text{spike}}$
- Tricky timing!
- Solution: clock and spikes delayed by identical amplifiers²³
- Residual offset $\sim 1\mu\text{V}$




Nested Chopping

 


- Inner HF chopper removes $1/f$ noise
- Outer LF chopper removes residual offset^{24,25}
- Residual offset $\sim 100\text{nV}$, but reduced bandwidth
- Note: input choppers should not be merged!

Dead-Banding

 

- During dead-band amplifiers output is tri-stated^{26,27,28}
- Residual offset $\sim 200\text{nV}$!
- BUT loss of gain and aliasing due to S&H action
 \Rightarrow slightly worse noise performance

Precision V-I Converter

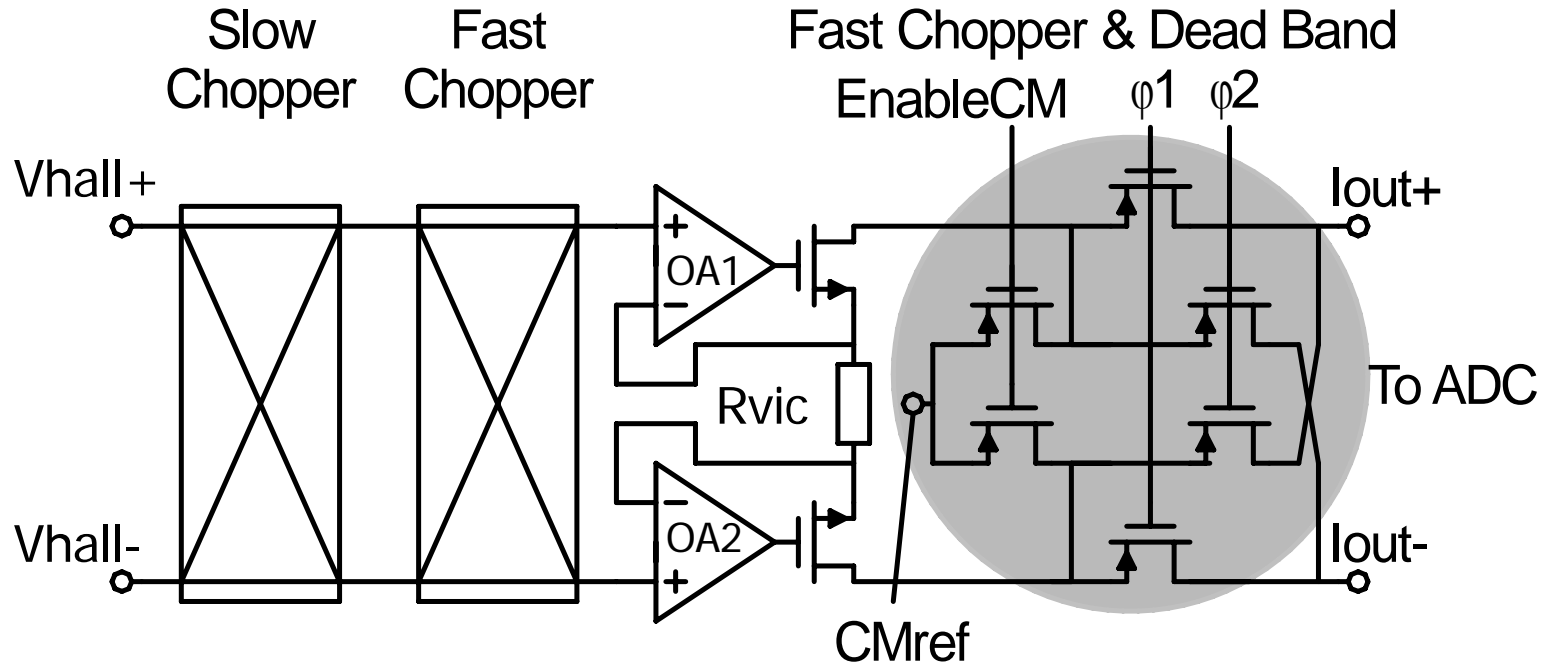


- Front-end of a magnetic field sensor²⁹ with $< 50\text{nV}$ offset!
- Fast output chopper implements dead-bands
- During dead-bands, output current flows into a CM node
- Slow output chopper implemented in ADC

Dealing with Spikes: Overview

- BP Filtering: $\sim 0.5\mu\text{V}$ offset, complex clock timing
- Delayed demodulation: $\sim 1\mu\text{V}$ offset, complex clock timing
- Dead-banding: $\sim 200\text{nV}$ offset, wide BW
- Nested chopping: $\sim 100\text{nV}$ offset, but limited BW

Last two techniques represent best compromise between offset magnitude and circuit complexity


Chopping Artifacts

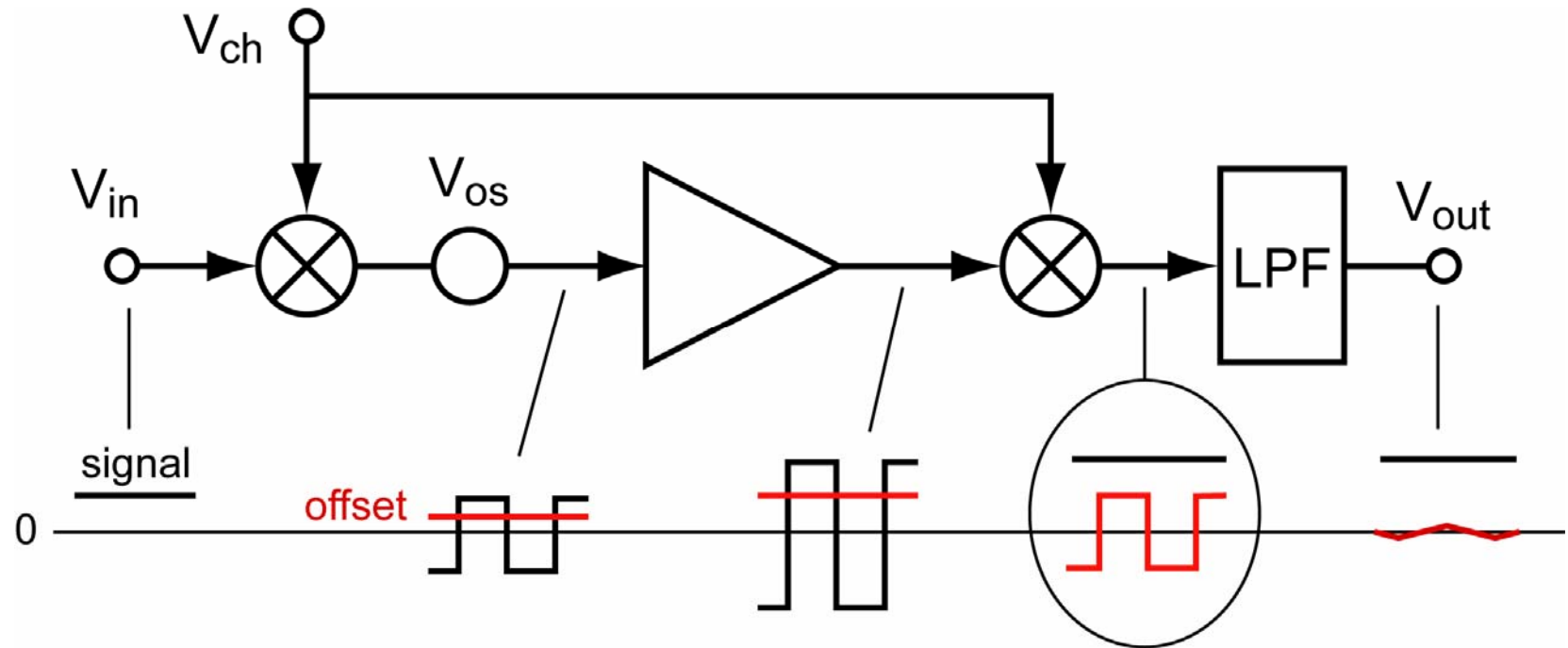

Modulated offset \Rightarrow chopping artifacts


- Can be removed by a low-pass filter
- BUT analog filters with low cut-off frequencies are difficult to realize on chip

Auto-zeroing and Chopping

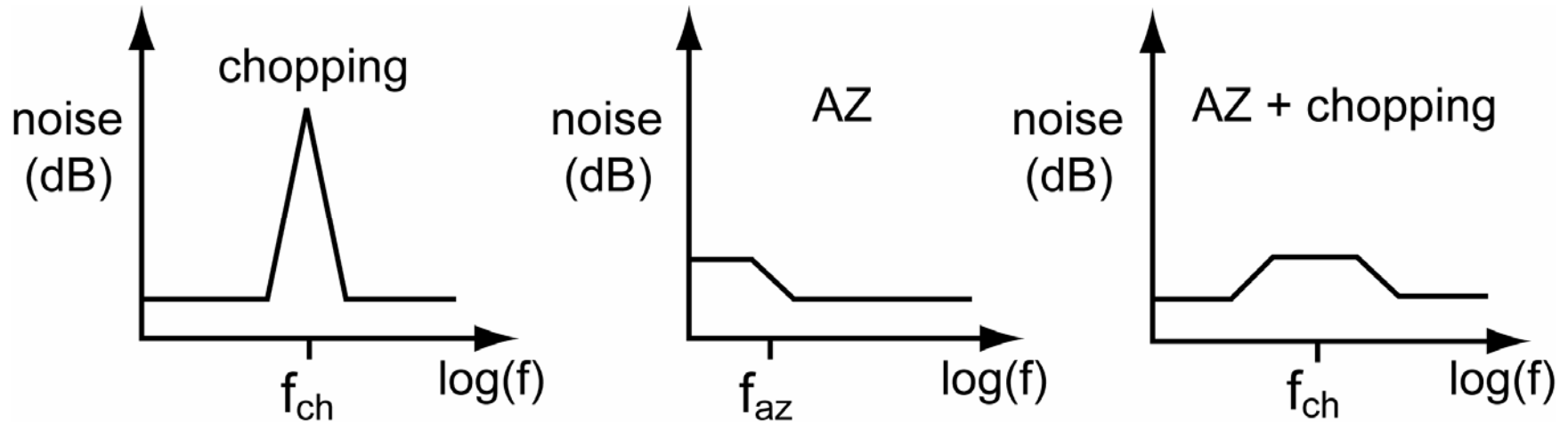


- Significantly improves LF noise performance^{30,31,42}
- Much less artifacts than with chopping alone
- 3 μV offset & 20nV/ $\sqrt{\text{Hz}}$ demonstrated in a ping-pong amplifier³⁰
- Choosing $f_{ch} = 2f_{az} \Rightarrow$ aliased noise has notch at DC

AC Coupling

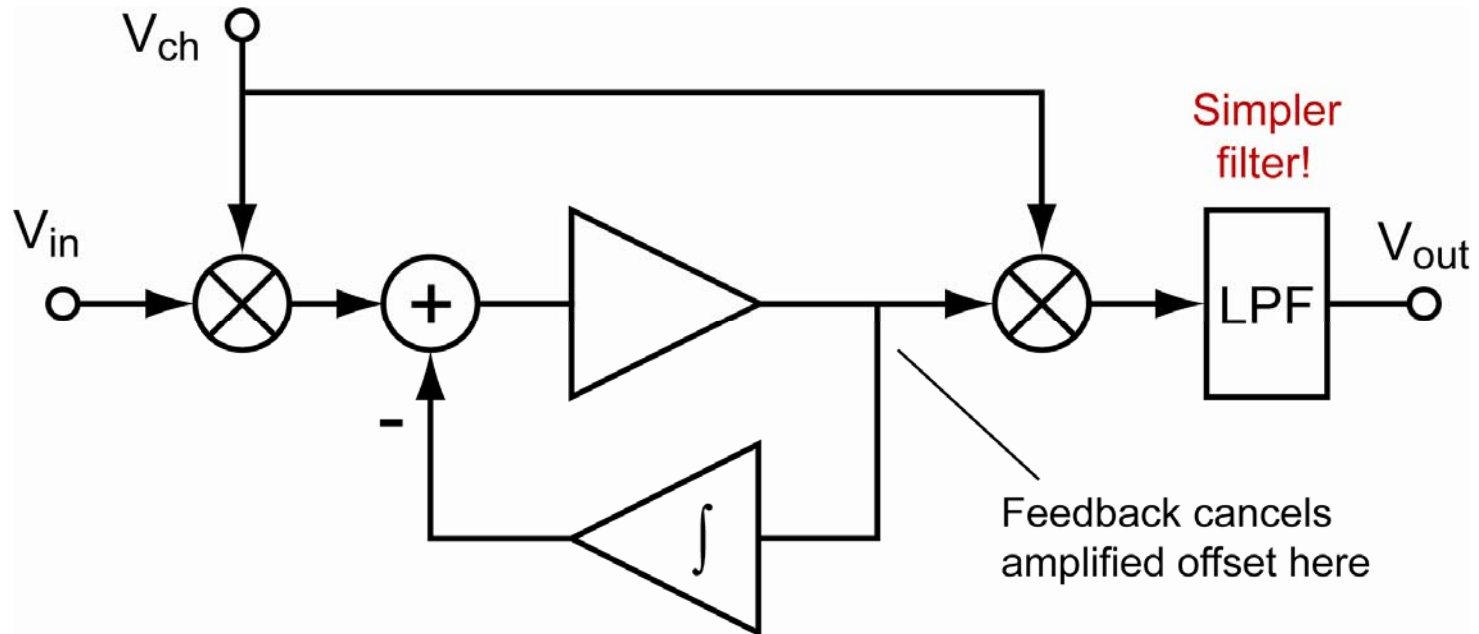


- AC coupling will block the amplifier's offset
- Alternatively, DC “servo” loop (shown) *inside* the choppers will also suppress the amplifier's offset^{32,33}
- Note: DC servo loop *outside* the choppers results in a low-noise amplifier with a HPF characteristic^{33,34}

Switched Capacitor Filter (1)

 

- Chopped offset is integrated & the triangular ripple is then sampled at the zero-crossings³⁵
- SC filter essentially eliminates residual ripple
- Filter introduces delay and a (small) noise penalty


Switched Capacitor Filter (2)

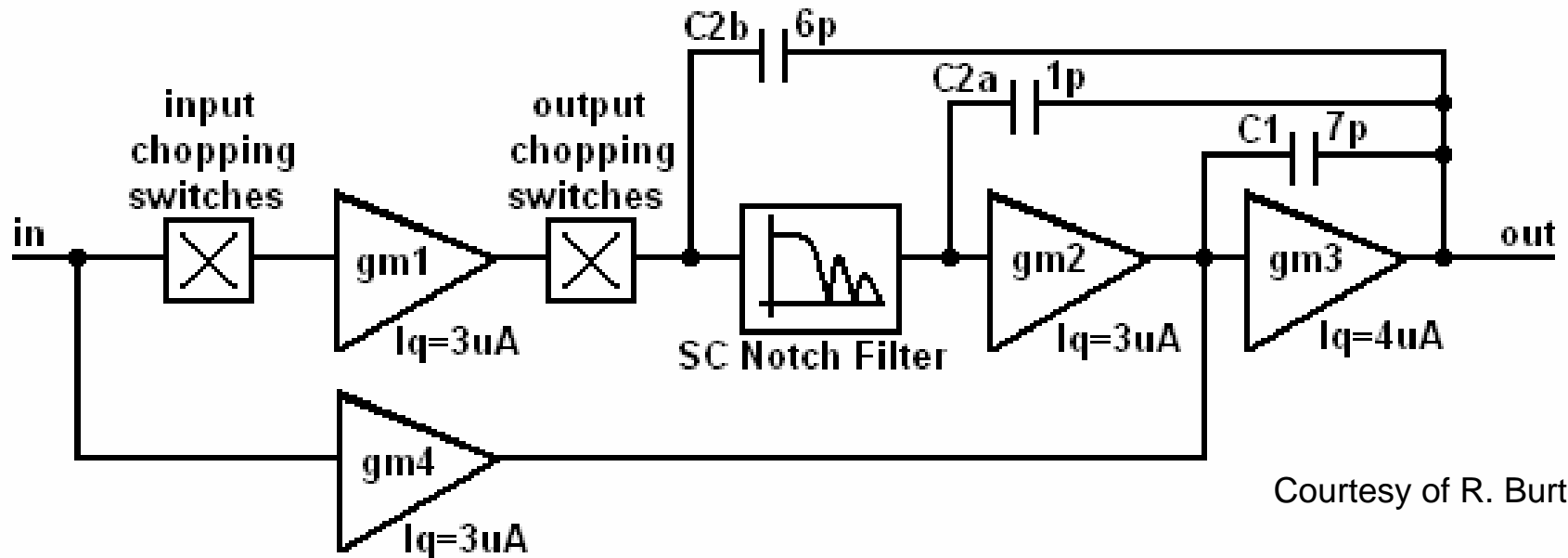

Courtesy of R. Burt, TI

- SC filters have been used in **true** chopper-stabilized opamps^{9,36}
- Note: gm4 is not chopped $\Rightarrow V_{res} > V_{os4} A_{gm4} / (A_{gm1} A_{gm2})$
- Filter delay incorporated into a multi-path nested Miller compensation scheme

Digital Filtering

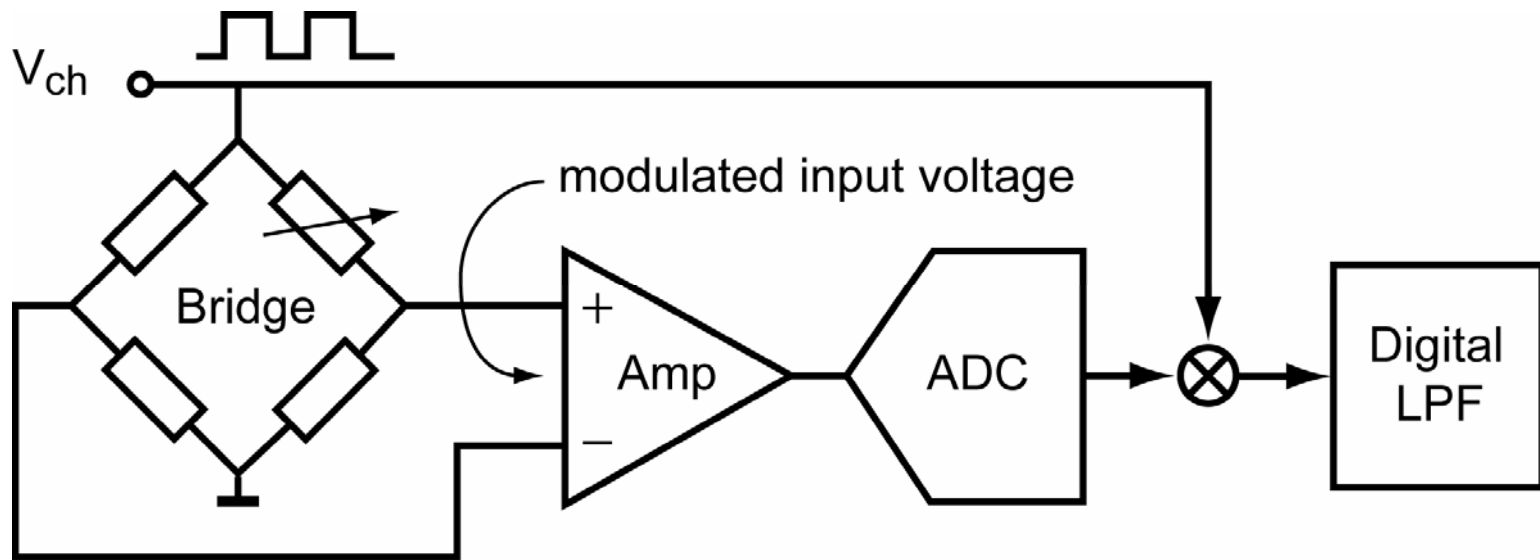

- Chopped signal is digitized
- Demodulation is done digitally^{25,37}
- Chopper artifacts are removed by a digital LPF
e.g. a sinc filter with notches at f_{ch}

Dealing with Artifacts: Overview

Reduce the amplifier's initial offset

- Auto-zeroing and chopping: increased noise
- DC servo: still requires some analog filtering
- Switched capacitor filtering

Digital Filtering

- Very low cut-off frequencies can be realized
- Decimation filter of a $\Sigma\Delta$ ADC can be used to remove chopper artifacts \Rightarrow no extra overhead

Chopping: Summary

- Offsets in the range of 50nV-10 μ V can be achieved
- Fundamental loss of bandwidth (unless offset-stabilized topologies can be used)
- Eliminates $1/f$ noise, noise floor set by thermal noise
- DOC technique of choice when noise or offset performance is paramount e.g. in biomedical amplifiers, low-power opamps, smart sensors etc.

State-of-the-Art Opamps



Type	Offset (max)	Noise (0 - 10Hz)	DOC Freq. (kHz)	I _{sy} (max, μ A)	Typ. GBW (MHz)	Technique
LTC2050	3 μ V	1.5 μ V	7.5	1200	3.0	AZ-OS
AD8571 ¹³	10 μ V	1.0 μ V	2 – 4	1075	1.0	Randomized AZ-PP
AD8628 ³⁰	10 μ V	0.6 μ V	7.5/15	1000	2.5	CH & AZ-PP
MAX4238 ³⁹	3.5 μ V	1.5 μ V	10 – 15	850	1.0	Randomized CH-OS
OPA333 ⁹	10 μ V	1.1 μ V	100	28	0.35	CH-OS
CS3001 ³⁸	10 μ V	0.125 μ V	200	2800	5.0*	CH-OS

*Conditionally stable

Design of a CMOS Temp. Sensor^{40,41}

- Why CMOS 'smart' temperature sensors?
 - + digital interface
 - + low cost
- But accuracy is a problem!
Only $\pm 2.0^{\circ}\text{C}$ from -55°C to 125°C
- By comparison: class-A Pt100
achieves $\pm 0.5^{\circ}\text{C}$ in the same temp. range
- Goal: $\pm 0.1^{\circ}\text{C}$ from -55°C to 125°C
with single temperature calibration only

Operating Principle

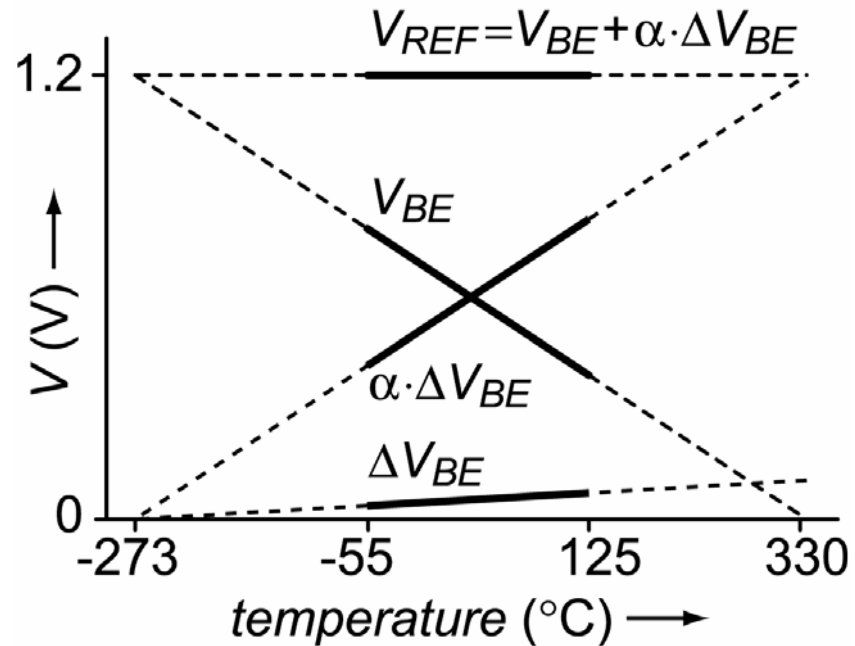 


- Substrate PNPs generate:

ΔV_{BE} proportional to absolute temp. (PTAT)

V_{BE} complementary to absolute temp. (CTAT)


- Ratiometric measurement:
$$\mu = \frac{V_{TEMP}}{V_{REF}} = \frac{\alpha \cdot \Delta V_{BE}}{V_{BE} + \alpha \cdot \Delta V_{BE}}$$

Block Diagram

 

- $\Sigma\Delta$ modulator produces bitstream bs whose average is representation of temperature
- Offset in ΔV_{BE} read-out results in errors of $\sim 10^\circ\text{C}/\text{mV}$
 \Rightarrow offset $\ll 10\mu\text{V}$ required for error $\ll 0.1^\circ\text{C}$
- Spread of V_{BE} and bias-current ratio are mitigated by trimming and DEM respectively^{40,41}
- Bitstream is filtered and scaled by decimation filter to produce binary reading in $^\circ\text{C}$


Charge Balancing in $\Sigma\Delta$

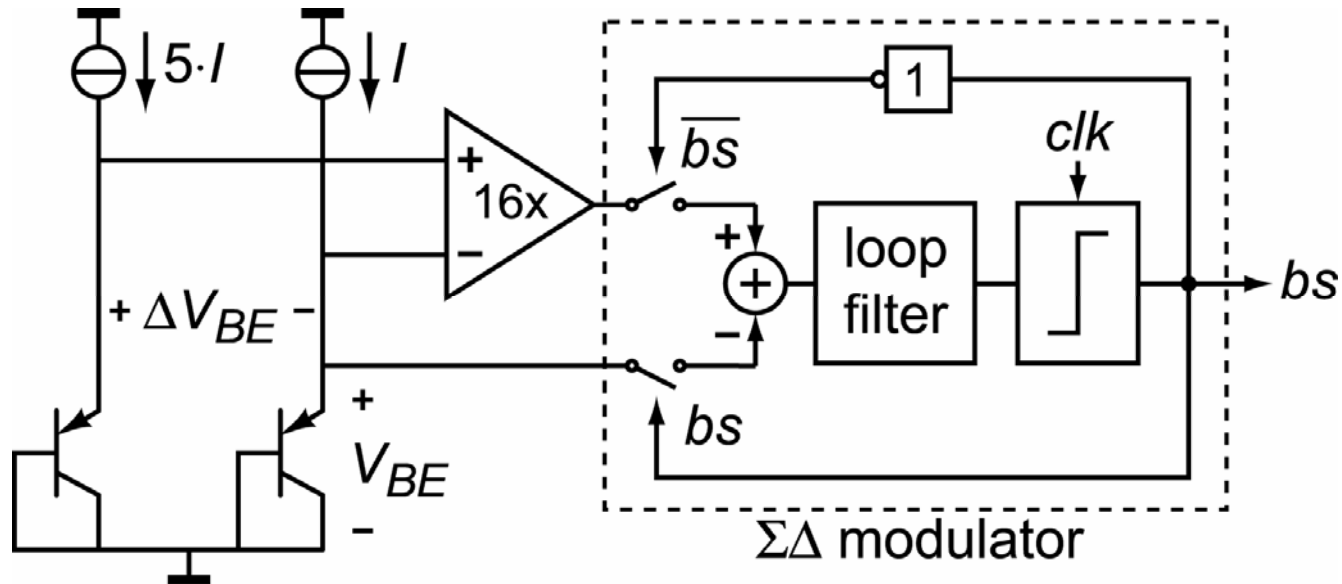

- Every clock cycle, either $16 \cdot \Delta V_{BE}$ ($bs=0$) or $-V_{BE}$ ($bs=1$) is input to the loopfilter
- Resulting bitstream average μ :


$$\mu \cdot V_{BE} = (1 - \mu) \cdot 16 \cdot \Delta V_{BE} \Rightarrow \mu = \frac{16 \cdot \Delta V_{BE}}{V_{BE} + 16 \cdot \Delta V_{BE}} = \frac{16 \cdot \Delta V_{BE}}{V_{REF}}$$

Switched-Capacitor 1st Integrator

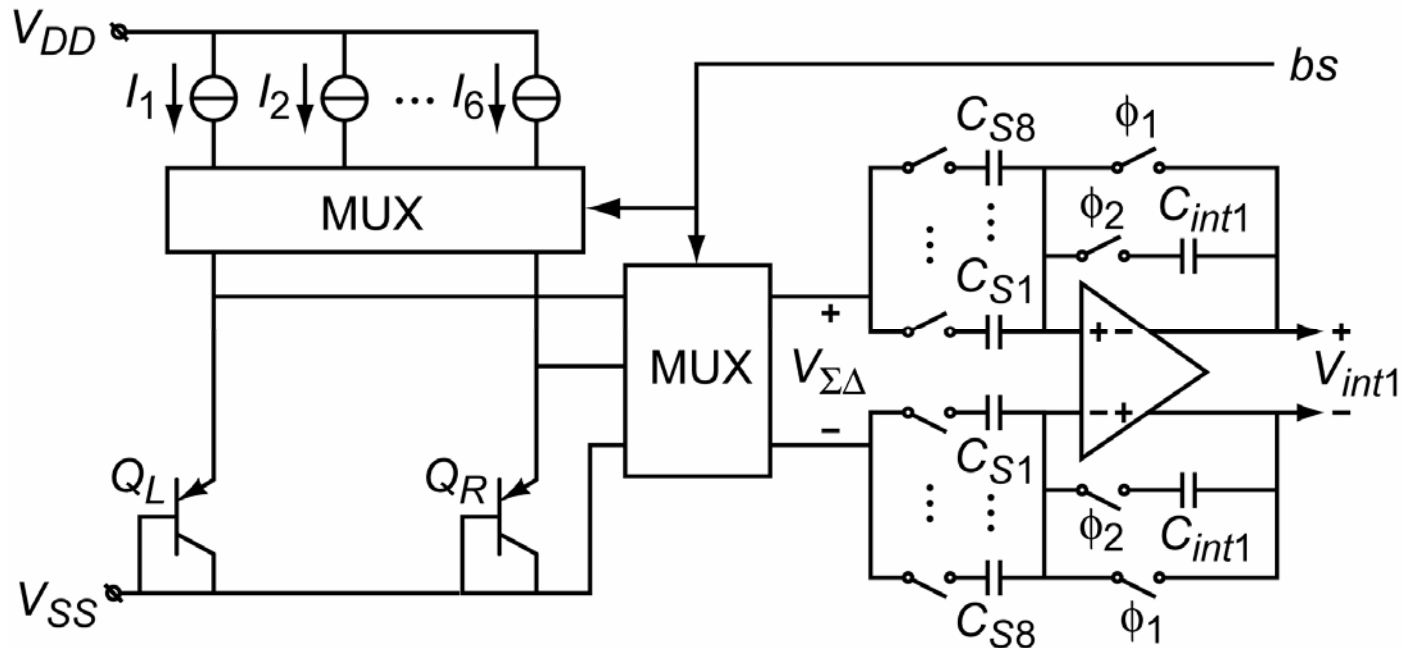


- PNPs Q_L and Q_R generate ΔV_{BE} ($bs=0$) or V_{BE} ($bs=1$)
- $C_{S1}-C_{S8} \Rightarrow$ gain of 1 or 16 (with 2 integration cycles)
- Correlated double-sampling (CDS) used to sample ΔV_{BE} or V_{BE} **and** cancel opamp's offset and $1/f$ noise

ΔV_{BE} Sampling ($bs=0$)

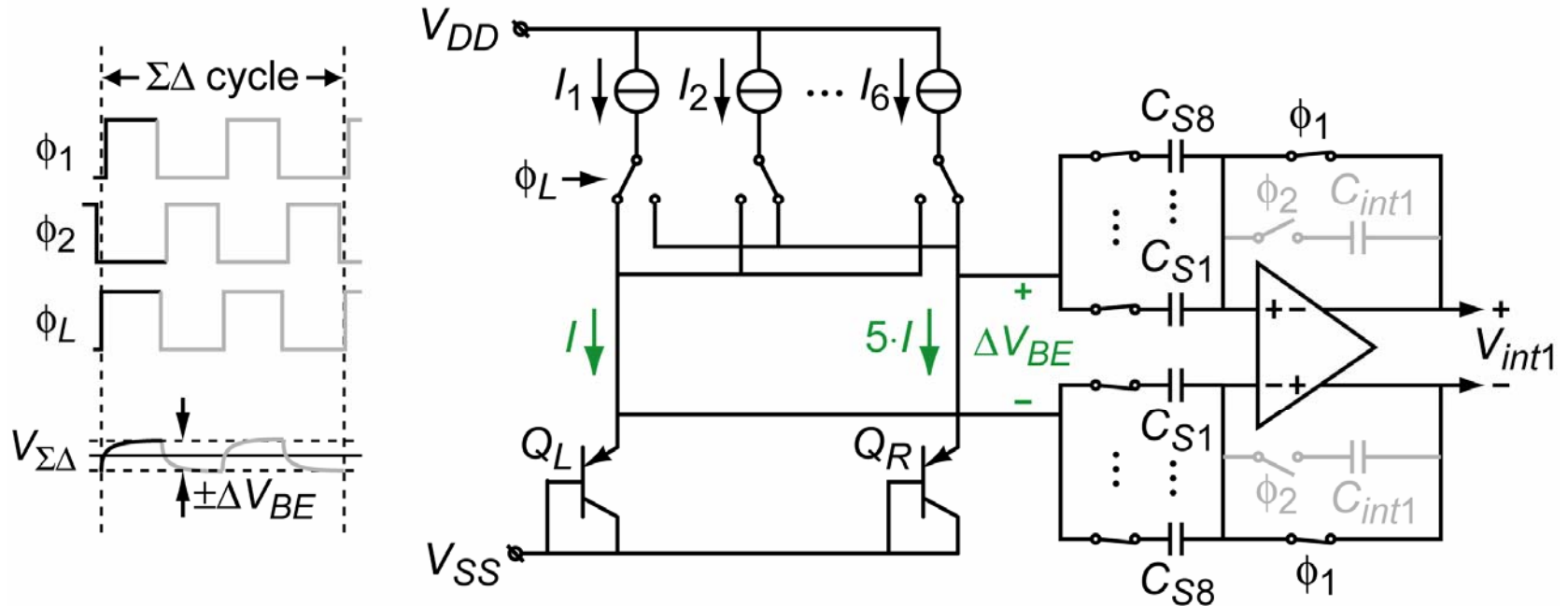


- PNPs biased at 1:5 current ratio
- $\Delta V_{BE,RL}$ **and** offset sampled on 8 sampling capacitors
- Minimum size NMOS switches + 5pF caps
 \Rightarrow residual offset $\sim 10\mu V \Rightarrow$ too high

ΔV_{BE} Integration ($bs=0$)

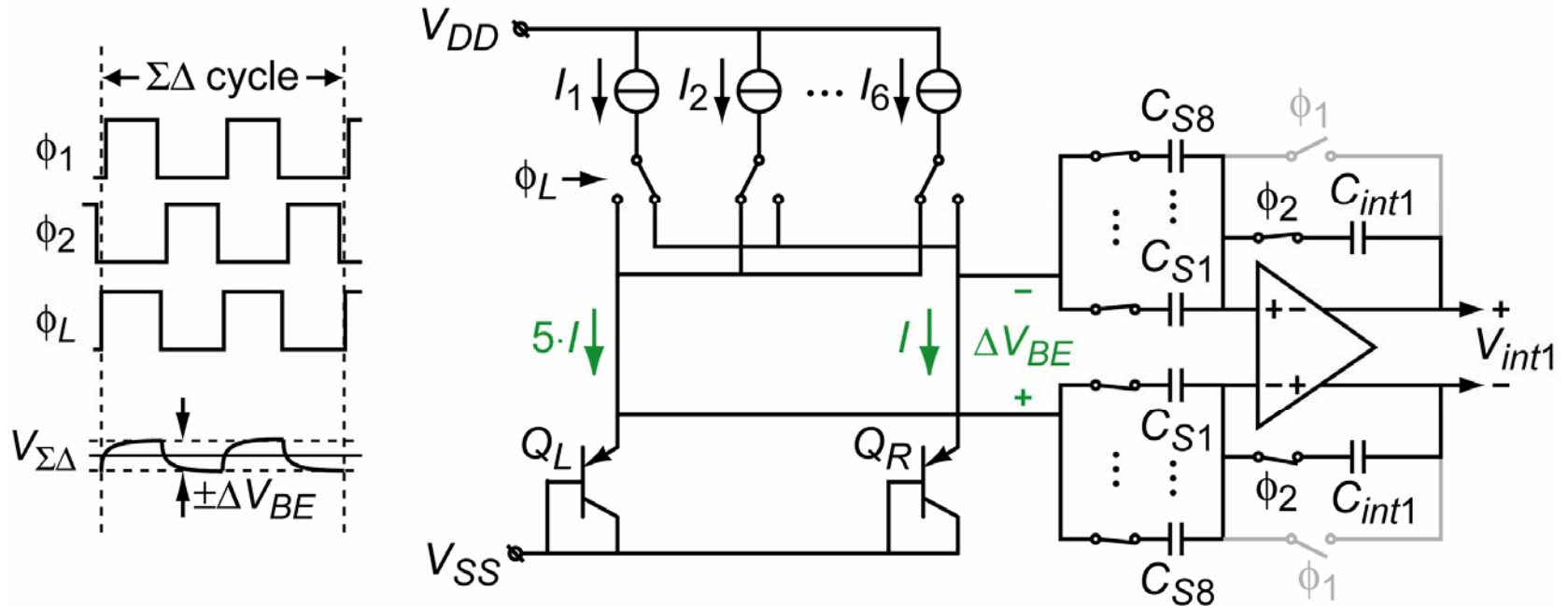


- Bias currents are swapped
 \Rightarrow integrated charge: $8 \cdot C_S \cdot (\Delta V_{BE,RL} + \Delta V_{BE,LR})$
- 2 integration cycles in 1 $\Sigma\Delta$ cycle
 \Rightarrow total charge: $16 \cdot C_S \cdot (\Delta V_{BE,RL} + \Delta V_{BE,LR})$

V_{BE} Sampling ($bs=1$)

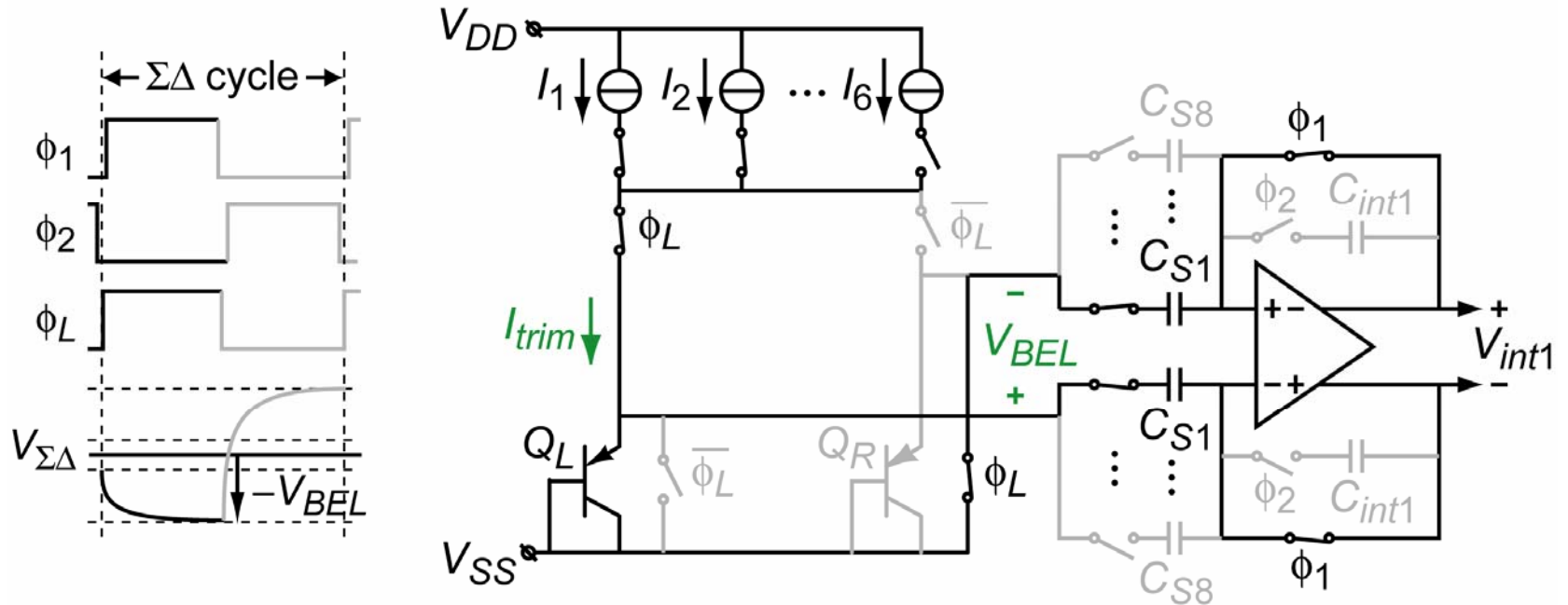


- Q_L biased at programmable current I_{trim}
- $-V_{BE}$ and offset sampled on 1 sampling capacitor

V_{BE} Integration ($bs=1$)

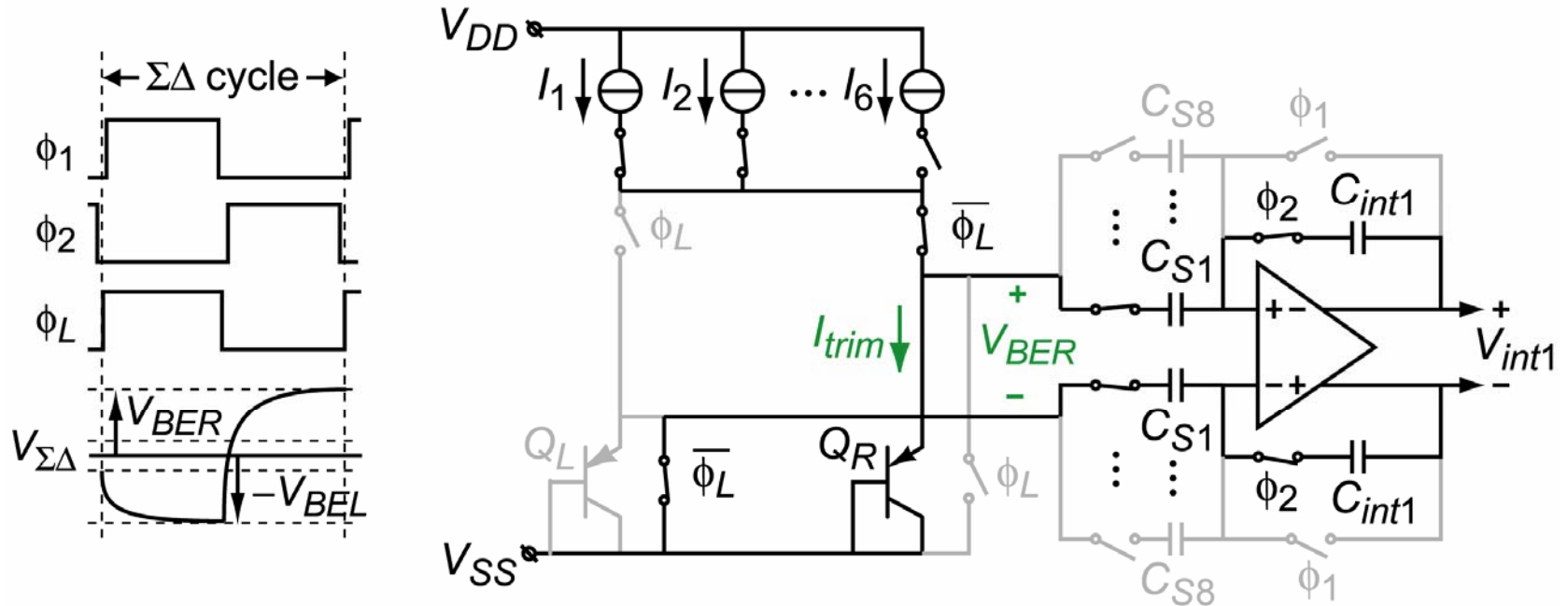


- I_{trim} swapped to Q_R
 \Rightarrow total charge: $C_S \cdot (V_{BEL} + V_{BER})$
- compare with $16 \cdot C_S \cdot (\Delta V_{BE,RL} + \Delta V_{BE,LR})$
 \Rightarrow effective 16x gain for ΔV_{BE}

Chopped $\Sigma\Delta$ Modulator

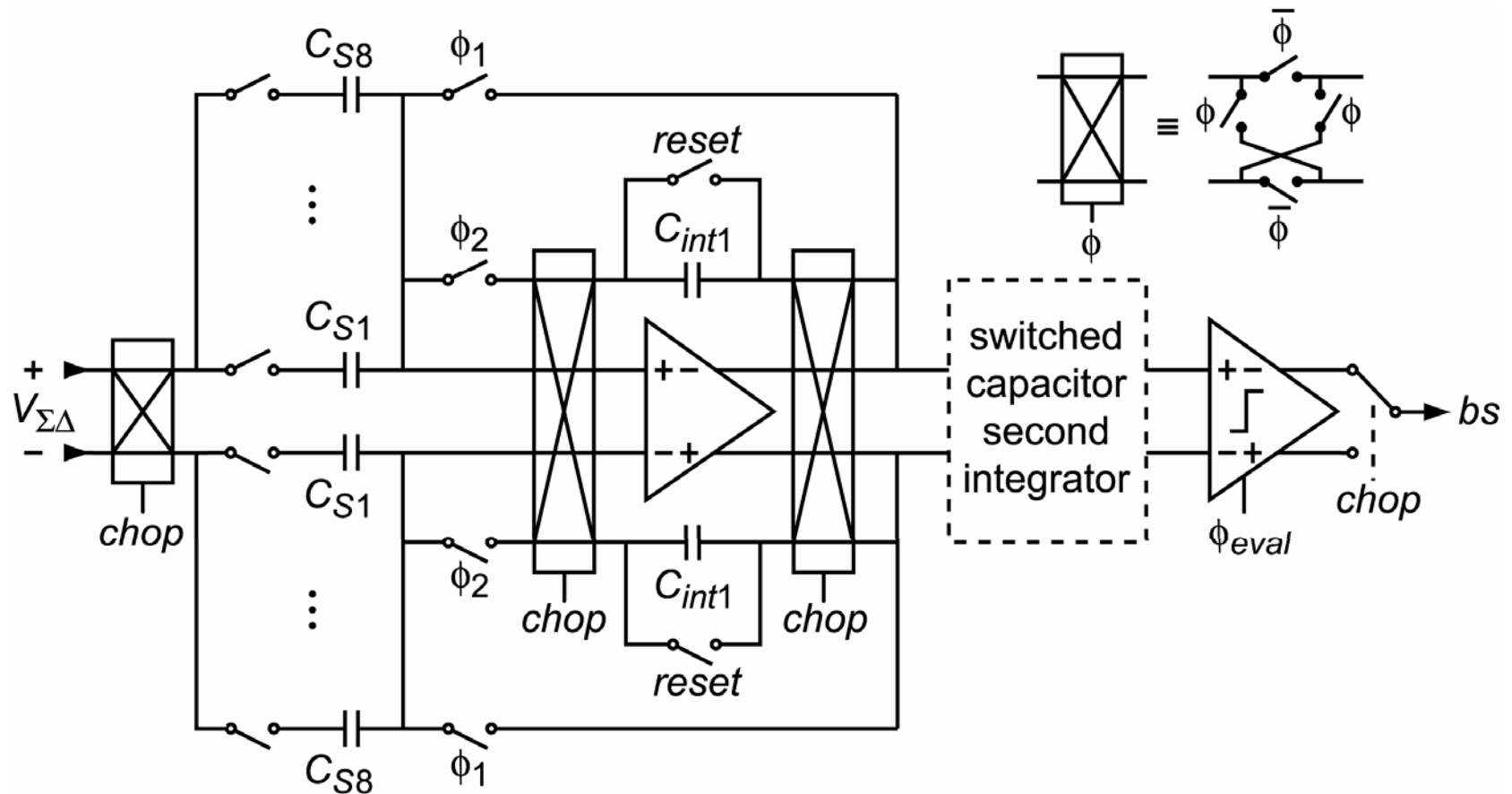


Offset after CDS $> 10\mu\text{V} \Rightarrow$ input, output **and** modulator state are chopped 2x per conversion \Rightarrow sub- μV offset

Chip Micrograph

 

- 4.5mm² in 0.7μm CMOS
- Off-chip decimation filter removes chopper residuals
- Supply voltage: 2.5..5.5V
- Supply current: 75μA

Measurement Results

 

24 samples
from 1 batch

Inaccuracy ($\pm 3\sigma$)
after trimming
at 30°C:

$\pm 0.03^\circ\text{C}$ 30°C
 $\pm 0.1^\circ\text{C}$ -55..125°C

World's most
accurate CMOS
temp sensor!

Summary

- Offset and $1/f$ are part of life!
- Trimming
 - reduces offset but not $1/f$ noise
 - no loss of bandwidth
- Auto-zeroing
 - Reduces $1/f$ noise, but sampling \Rightarrow noise aliasing
 - Indirect loss of bandwidth
- Chopping
 - eliminates $1/f$ noise
 - Direct loss of bandwidth
- Nested DOC techniques \Rightarrow sub-microvolt offset



INSTITUTE OF ELECTRICAL AND ELECTRONICS ENGINEERS

ISSCC

UNIVERSITY OF PENNSYLVANIA