 
 

Analog Front-End Design for Gb/s Wireline Receivers

Elad Alon
elad@eecs.berkeley.edu




Dept. of Electrical Engineering
and Computer Sciences
University of California, Berkeley

Importance of Wireline Links



 - Wireline I/O performance and power increasingly critical differentiators
 - Chassis can contain tens of 1000's of these links




Images from eetimes.com

The High-Speed Wireline Challenge


- Deliver as much throughput as possible
 - Multiple Tb/s for the whole chip

- Using as little power as possible
 - $\sim 1\text{pJ/bit}$ or less

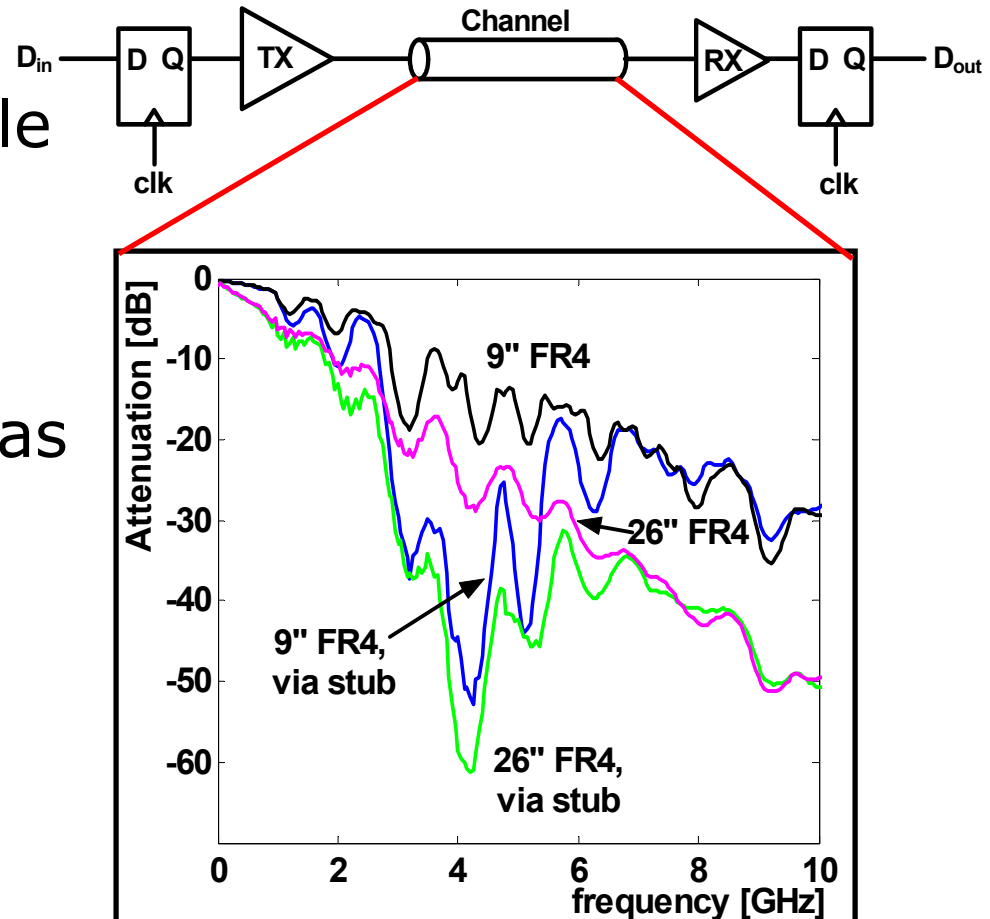- While dealing with “badness” of the channels



Focus of this Tutorial: RX

 

- By definition, TX knows the data, RX doesn't
 - Tends to place more stringent constraints on RX circuit design
- RX impedance levels tend to be higher – more efficient to implement signal processing there
- Knowledge of RX design techniques maps directly to TX design too

Tutorial Outline

- RX AFE Basics
- RX AFE Circuits & Power Analysis
- Practical Issues and Common Gotchas
- Key Lessons

Tutorial Outline

- RX AFE Basics


- Basic AFE requirements
- RX Equalizers

- RX AFE Circuits & Power Analysis

- Practical Issues and Common Gotchas

- Key Lessons



Most Basic RX

 

- Most basic RX really is “just” a comparator
 - Converts potentially small, analog voltages on the “wire” into digital levels

- What can go wrong?

Key Constraint: Bit Error Rate

 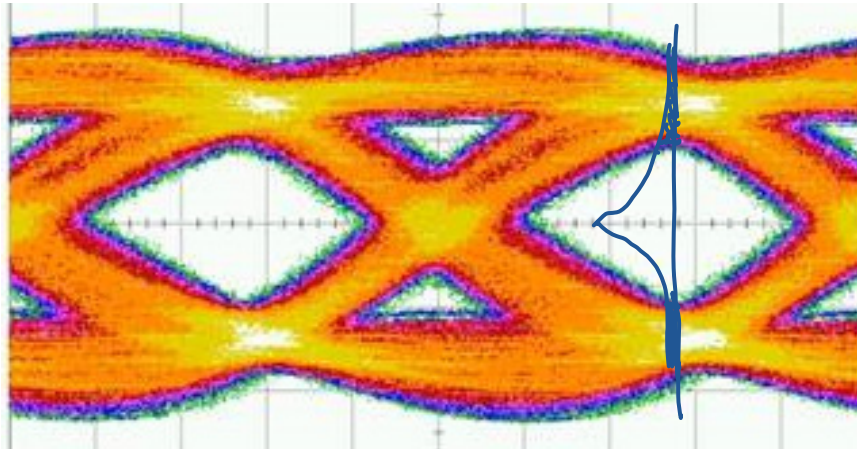

□ BER = Bit Error Rate

■ Average # of wrong received bits / total transmitted bits

□ Simplified example:
(voltage only)


$$BER = \frac{1}{2} \operatorname{erfc} \left(\frac{V_{in,ampl} - V_{off}}{\sqrt{2}\sigma_{noise}} \right)$$

□ BER = 10^{-12} : $(V_{in,ampl} - V_{off}) = 7\sigma_n$


□ BER = 10^{-20} : $(V_{in,ampl} - V_{off}) = 9.25\sigma_n$

Noise Not the Only Source of Errors: ISI

 - ISI: Inter-Symbol Interference
- Channel is band-limited
 - I.e., dispersive (low pass)
 - Short TX pulses get spread out
 - Low latency
- Also get reflections
 - Z mismatches, connectors, etc.
 - Longer latency




Equalization

 

- Basic goal is to “flatten” channel response
 - I.e., in time domain, get back our nice clean pulse


More Complete RX AFE

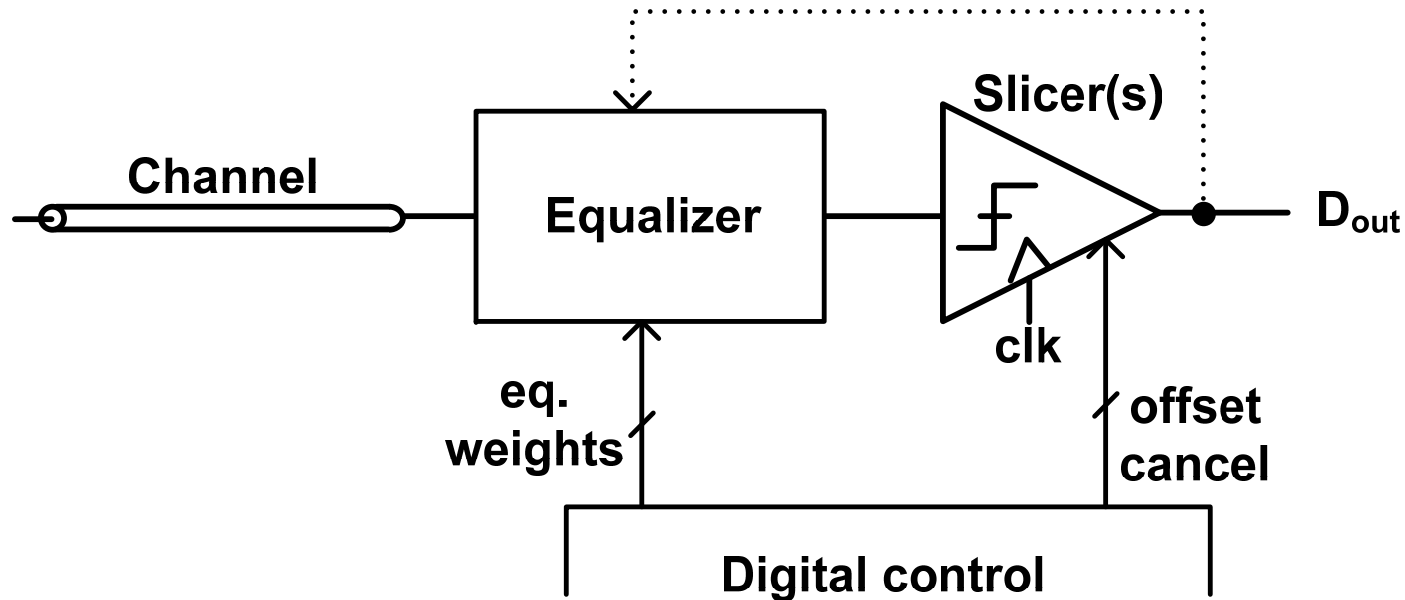

- Let's look at the types of equalizers we will need
 - Note that equalization is also often done on TX
 - But equalization burden is increasingly moving to RX

Continuous Time Linear Equalizer (CTLE)

 
- Basic idea: build an analog circuit that approximates the inverse of the channel



- Can't (and don't need to) exactly invert – **finite gain @ high f**
 - CTLE bandwidth set by data-rate: typically $\sim 2/3 * (1/T_{bit})$


CTLE Implementation, Limitations (1)

 - Often implemented using implicit or explicit negative feedback:




- Low-pass filter usually built out of R's and C's
 - Easy & efficient way to implement large time constants
 - Most effective with small # of poles & zeros
- May be hard to match complicated channels
 - Usually combined with a discrete-time equalizer

CTLE Implementation, Limitations (2)

 


LPF


 


- Implication of feedback:
 - Equalization is actually achieved by throwing away gain at DC...

CTLE

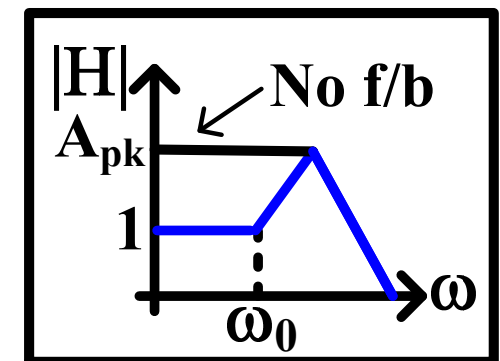

The Fundamental Issue: Noise

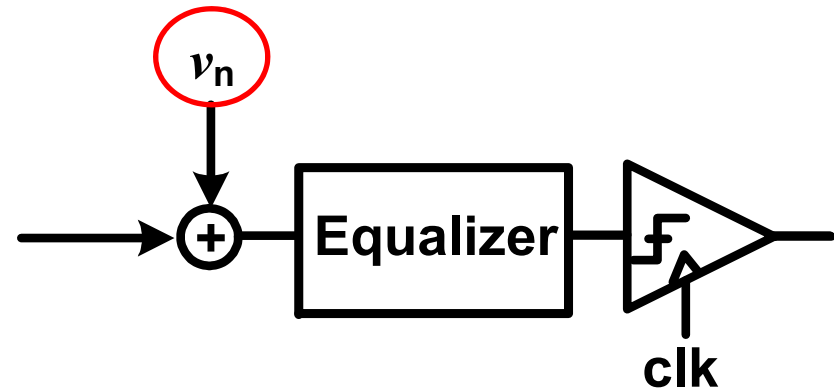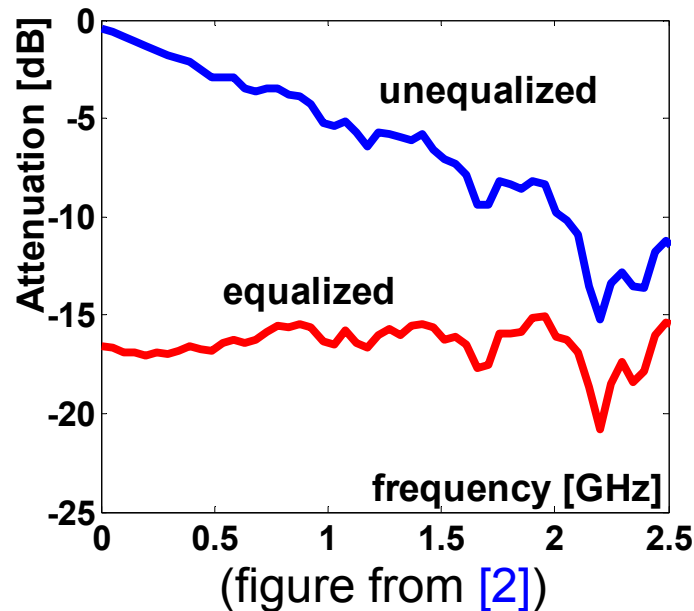


- Linear equalizers can eliminate ISI
 - But increase magnitude of noise (and high- f crosstalk) relative to signal
- Particularly bad on channels with notches
 - Equalizer needs large atten./gain



Good News: There is Another Way

- Once you know which bit was transmitted
 - You also know exactly what ISI that bit will cause

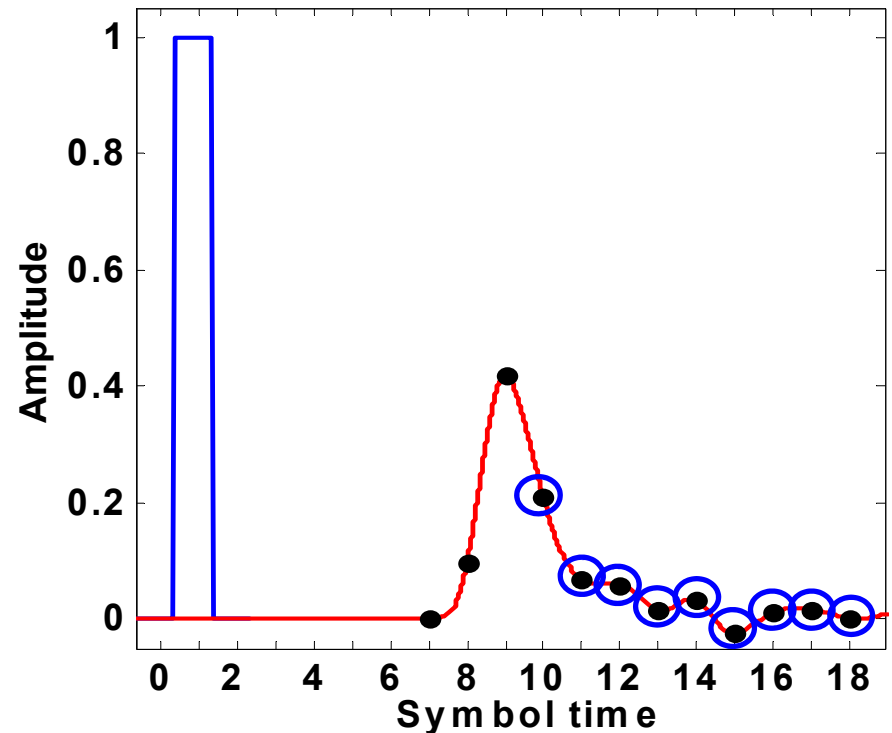- Why not directly cancel the ISI you know is coming?




Decision Feedback Equalization

 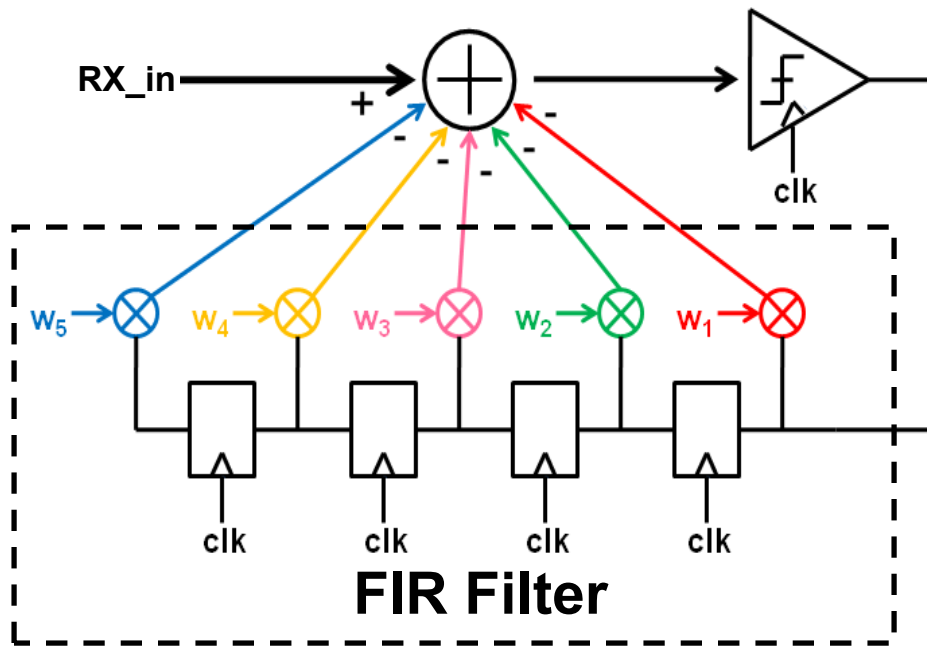


- Key advantage: no noise penalty
 - Feedback is based on "perfect" digital bits
 - ISI subtracted based on those bits

Key Constraint: Timing

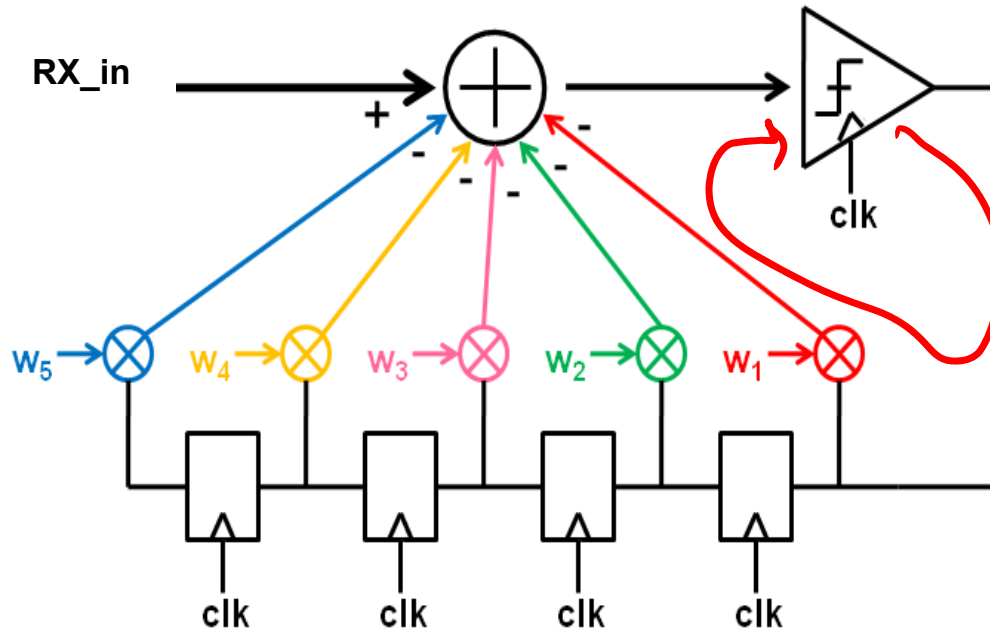

- Need to do all of the following in **at most $1 T_{\text{bit}}$** :
 - Resolve the (small) input voltage
 - Scale the bit by the coefficient
 - Sum the new analog value

Complete Signal Chain

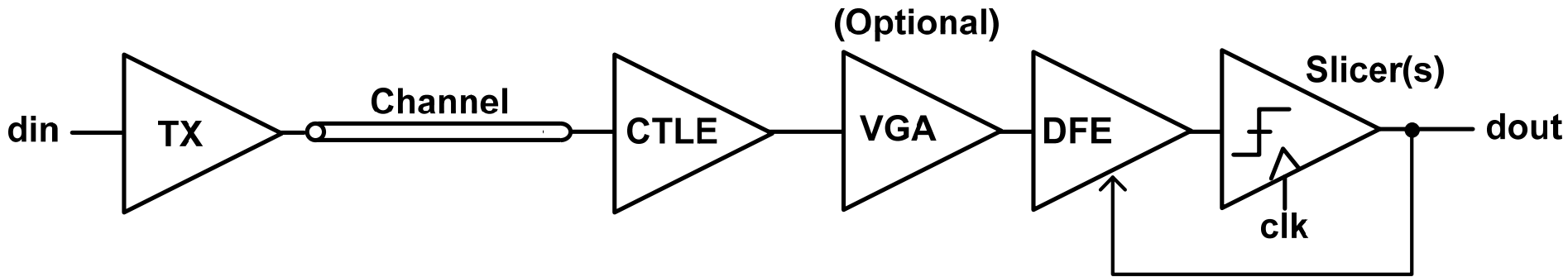

- VGA sometimes included to ensure DFE processes its input linearly
 - So that a linear FIR filter can be used to cancel the ISI
 - More later

Tutorial Outline

RX AFE Basics

RX AFE Circuits & Power Analysis

- Comparator

- CTLE




- VGA

- DFE


Practical Issues and Common Gotchas

Key Lessons

Comparator Circuit Design

   

Comparator Power Consumption

 


- Comparator core and latch typically just like digital gates:

$$P_{core,latch} = C_{sw,tot} V_{DD}^2 f_{clk}$$

- Let's look more carefully at preamp power

Preamp Power Consumption (1)

- Single-ended equiv. circuit:

 

- Reminder and definition:

$$\frac{g_m}{C_{self} + C_L} = A_V \omega_{bw}$$


$$C_{self} = \gamma \frac{g_m}{\omega_T}$$

- So:

$$g_m = \frac{A_V \omega_{bw} C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)}$$

Preamp Power Consumption (2)

- Single-ended equiv. circuit:

 

$$g_m = \frac{A_V \omega_{bw} C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)}$$



$$V^* \equiv \frac{I_D}{g_m} \text{ (diff. pair)}$$


$$I_{bias} = \frac{A_V \omega_{bw} V^* C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)}$$

- Typical 20Gb/s numbers in 65nm:

- $A_V = 2$, $\omega_{bw} = 80\text{Grps}$, $V^* = 200\text{mV}$, $C_L = 10\text{fF}$, $\omega_T = 400\text{Grps}$
- **$I_{bias} = 533\mu\text{A}$**

CTLE Circuit Design

 - Most common design: source-degenerated
 - Excellent linearity – more later



- At system level, really only care about:
 - ω_{zero} ← set by channel pole(s)
 - ω_{bw} ← CTLE BW (data-rate)
 - A_{pk} ← peak gain
 - A_{DC} ← DC gain

CTLE Design Equations (Simplified)

System	Circuit
$A_{pk} = g_m R_L$	$g_m = A_{pk} \omega_{bw} C_L$
$\omega_{bw} = \frac{1}{R_L C_L}$	$R_L = \frac{1}{\omega_{bw} C_L}$
$\frac{A_{pk}}{A_{DC}} = (1 + g_m R_s)$	$R_s = \left(\frac{A_{pk}}{A_{DC}} - 1 \right) \frac{1}{g_m}$
$\omega_{zero} = \frac{1}{R_s C_s}$	$C_s = \frac{g_m}{\omega_{zero}} \frac{A_{DC}}{(A_{pk} - A_{DC})}$

CTLE Power Consumption


- Identical equation as preamp:

$$I_{bias} = \frac{A_{pk} \omega_{bw} V^* C_L}{1 - A_{pk} \omega_{bw} / (\omega_T / \gamma)}$$



- (Remember, CTLE is just an amplifier with gain reduced at low frequencies)

VGA Implementation and Power

 - Many possible implementations
- Source degeneration again attractive:
 - Better linearity when gain is low
 - (Ideally) no extra loading on signal path
- Equation for power once again identical to preamp
 - Set by max. achievable gain





DFE Implementation (1)

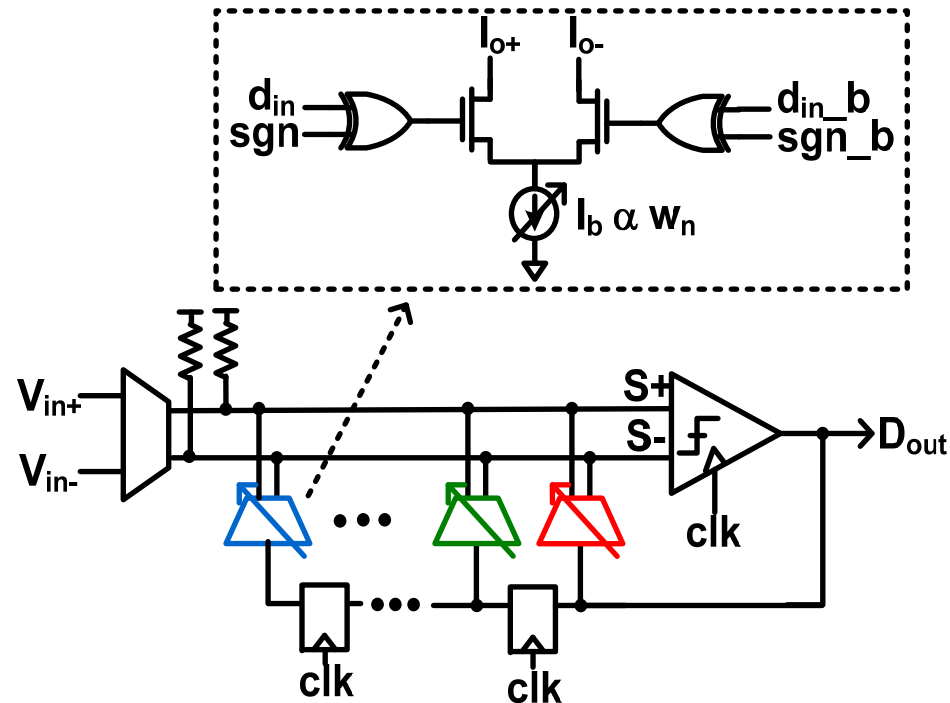 

- Mixed-signal FIR filter:
 - Digital delay
 - Analog scaling/summation

DFE Implementation (2)

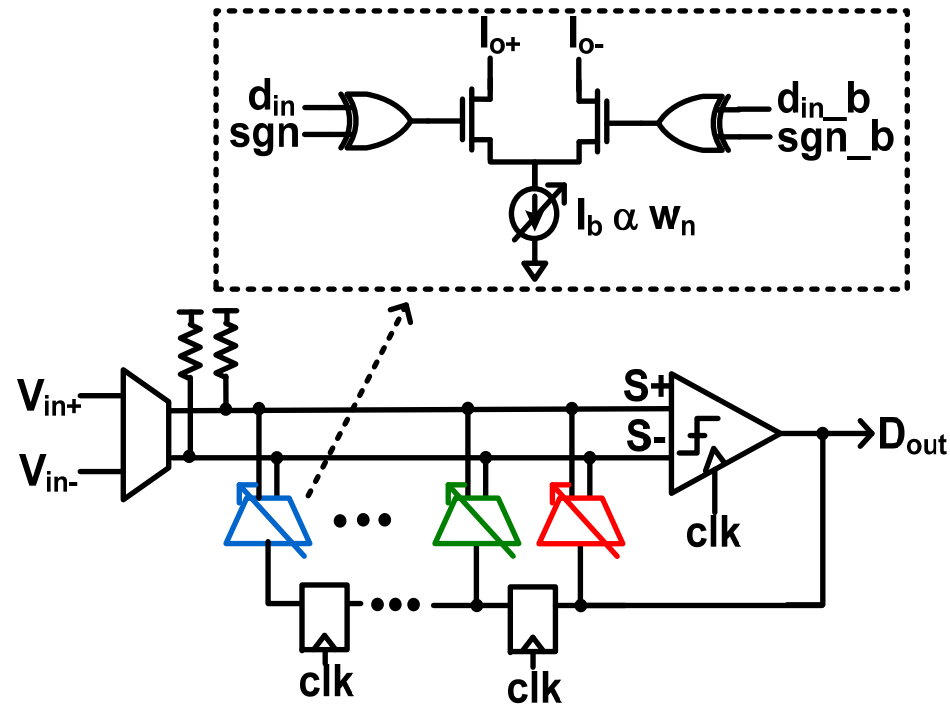 

- Design driven by feedback latency constraint
 - Summer output must settle within one bit time

DFE Summer Design


- Key constraint:

$$t_{\text{dig_fb}} + t_{\text{ana_settle}} = T_{\text{bit}}$$

- Need some N_{τ} of settling:

$$\tau_{\text{sum}} = (T_{\text{bit}} - t_{\text{dig_fb}}) / N_{\tau}$$

 
- Typically want $\sim 4\tau$ for $\sim 98\%$ settling




A Reminder: Self-Loading

$$I_{bias} = \frac{A_V \omega_{bw} V^* C_L}{1 - A_V \omega_{bw} / (\omega_T / \gamma)}$$

 - Creates bandwidth limit
 - No matter how much power you spend
- DFE has increased “self-loading” due to taps...



DFE Summer Power Consumption

 

□ Definition:


$$M_{DFE} = \frac{V_{out,tap}}{V_{out,cursor}} = \frac{I_{tap}}{g_m V_{cursor}}$$

□ Assuming same biasing for tap & cursor devices (see [4]):


$$I_{DFE,cursor} = \frac{A_v V^* C_L N_\tau / (T_{bit} - t_{dig})}{1 - \left(1 + \frac{2M_{DFE} V_{cursor}}{V^*} \right) \frac{A_v N_\tau / (T_{bit} - t_{dig})}{(\omega_T / \gamma)}}$$

Implication

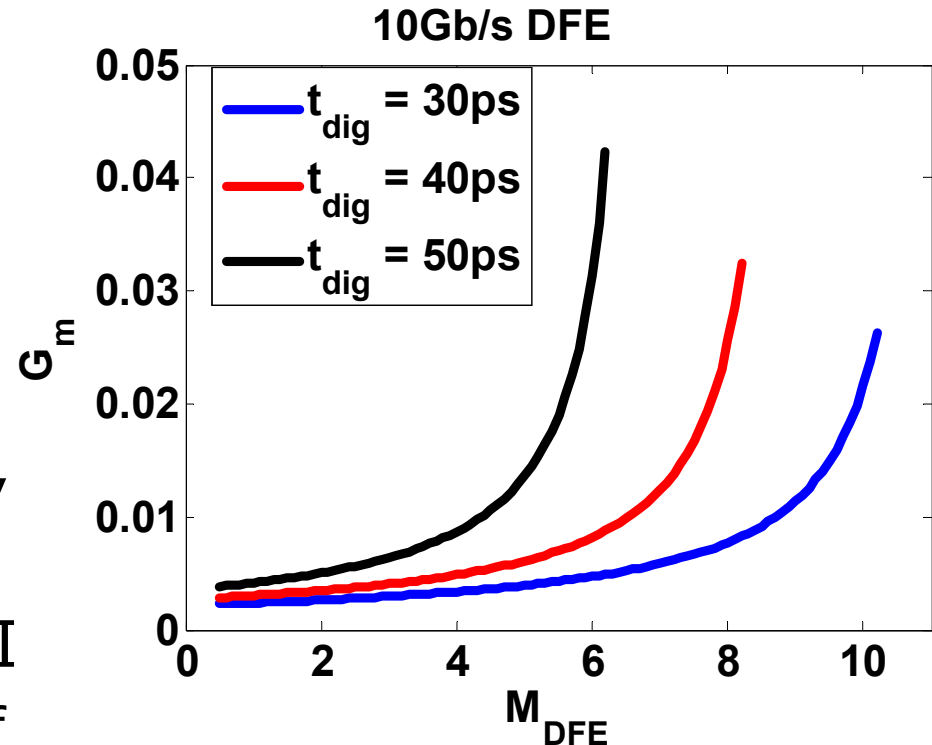
- There is a maximum M_{DFE} you can achieve
- Don't forget that every tap has to handle worst-case possible ISI
 - Implies max. number of taps (in given tech.)
- What if you need more taps/larger M_{DFE} ?



Current Integrating Summer^[5]

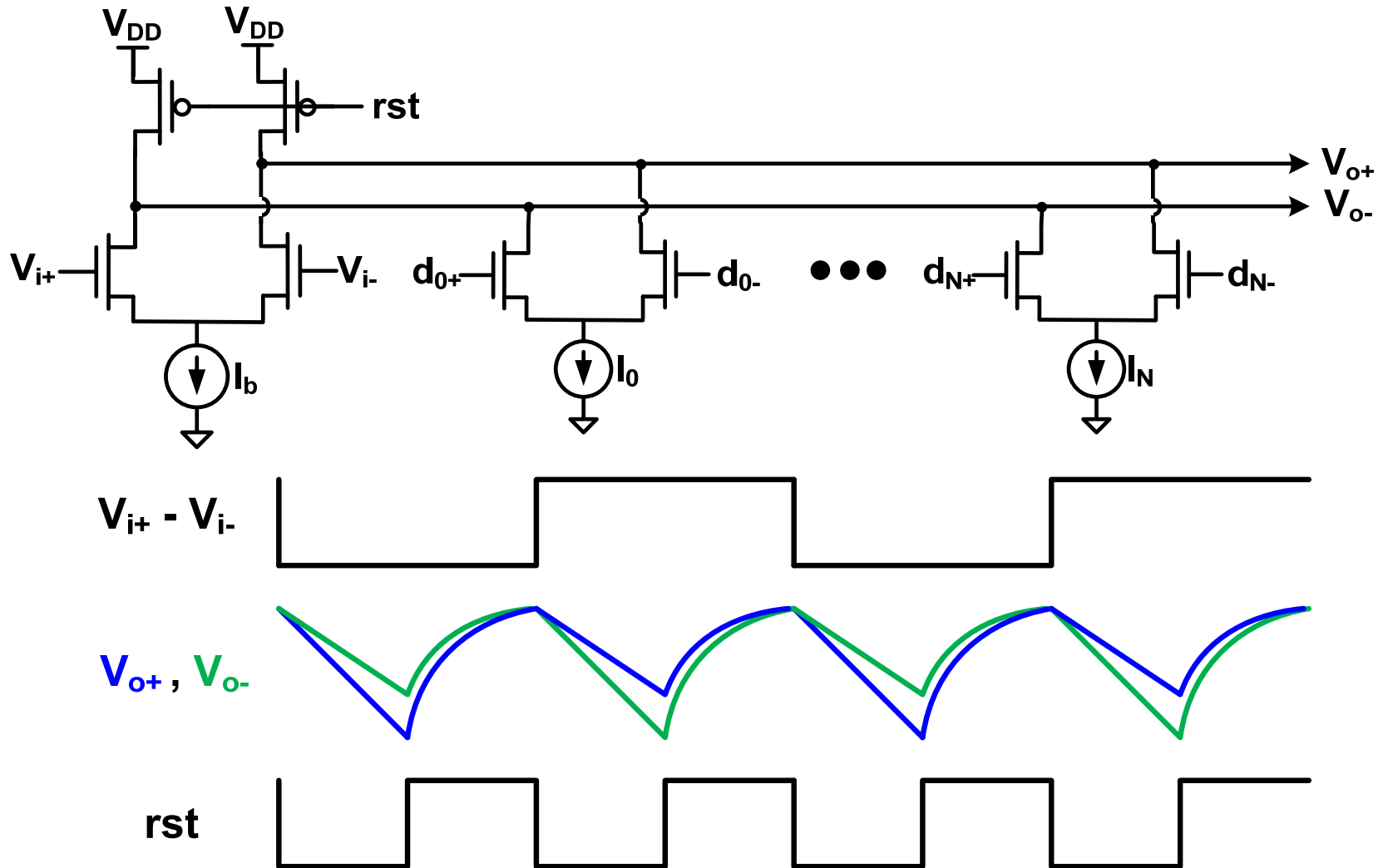

Why Current Integration Helps

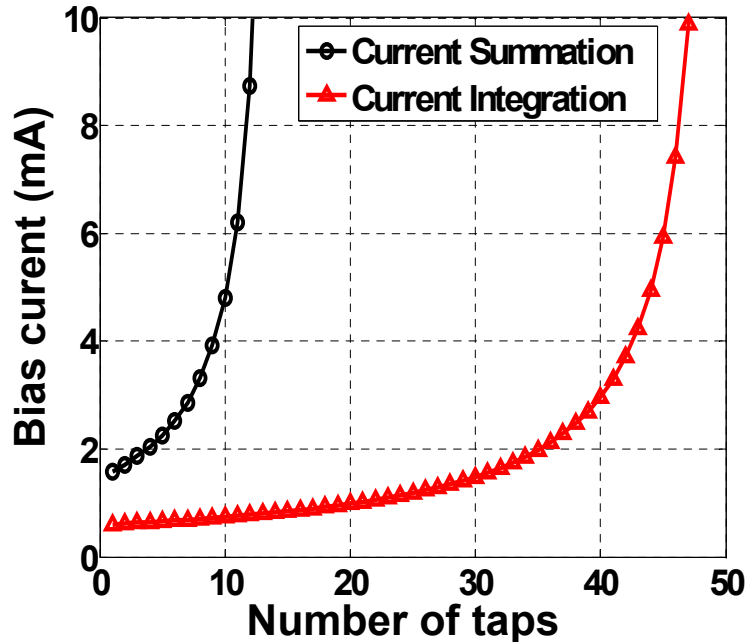

- Maximizes load impedance
 - ISI eliminated by resetting

- Power/number of taps improved by N_τ :

$$I_{DFE, cursor} = \frac{A_v V^* C_L / (T_{bit} - t_{dig})}{1 - \left(1 + \frac{2M_{DFE} V_{cursor}}{V^*} \right) \frac{A_v / (T_{bit} - t_{dig})}{(\omega_T / \gamma)}}$$

Example DFE Power Numbers

- 20Gb/s 10-tap DFE in 65nm (same process/bias as preamp example)
 - $M_{DFE} = 2.5$, $V_{cursor} = 75\text{mV}$, $t_{dig} = 25\text{ps}$,
 $A_V = 1$, $C_L = 30\text{fF}$

- Current integration summer power: $\sim 337\mu\text{A}$

- Digital power (flip-flops, XORs, etc.): $\sim 2\text{mA}$ w/1V V_{DD}
 - Typically $\sim 10\text{fF}$ switching cap/tap


Tutorial Outline

- RX AFE Basics
- RX AFE Circuits & Power Analysis
- Practical Issues and Common Gotchas
- Key Lessons

Comparator Offset Cancellation

- Never fight offset with sizing
 - 4X penalty in capacitance and hence power for 2X reduction in offset

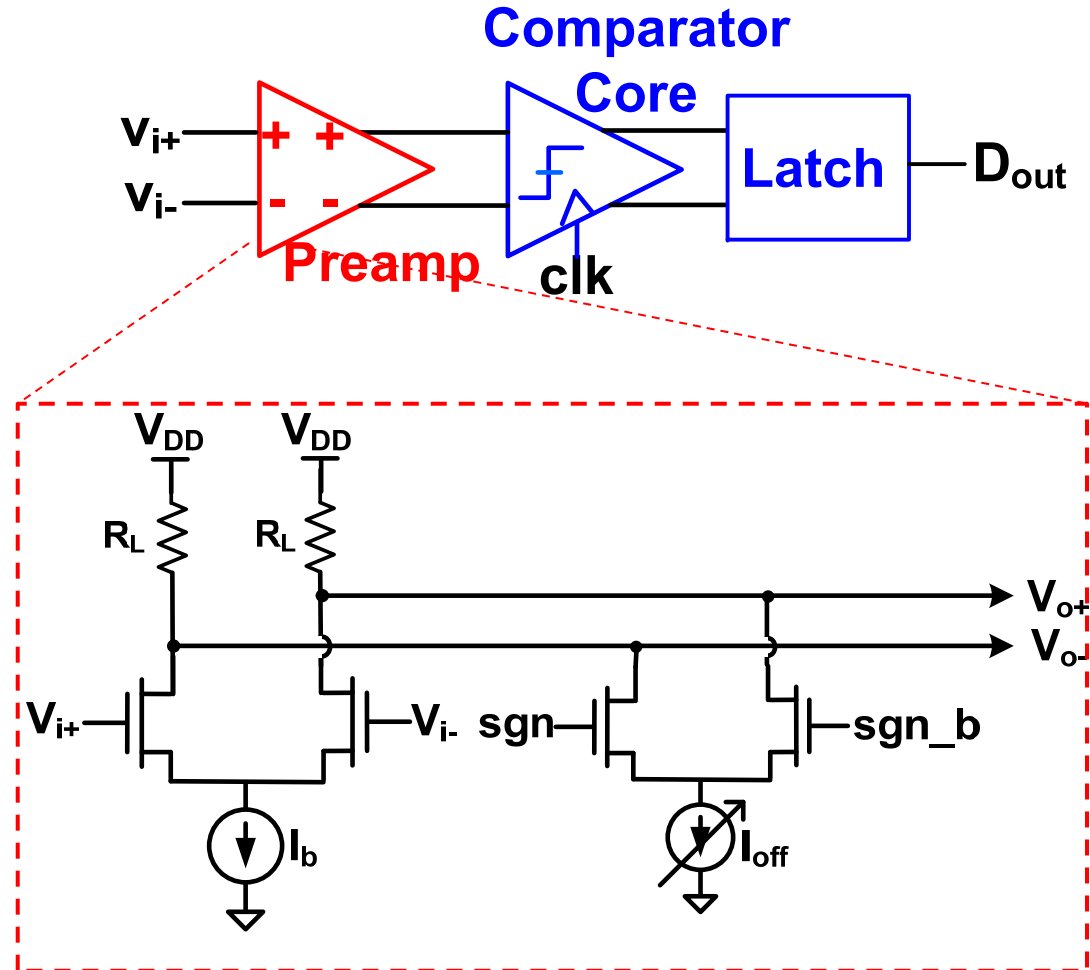- Preamp is a convenient point to cancel offset
 - Keeps cancellation DAC parasitics off of the signal path




CTLE Design Issues (1)

Cause:

- Finite input device r_o

Effects:

 - Couples source and drain dynamics
- Makes precise setting of poles/zeros more difficult




CTLE Design Issues (2)

Cause:


- Tail device r_o , C_{par}

Effects:

 - r_o limits maximum A_{pk}/A_{DC}
- C_{par} limits maximum ω_p
 - I.e., pole @ source associated with ω_{zero}




DFE Design: Closing the First Tap

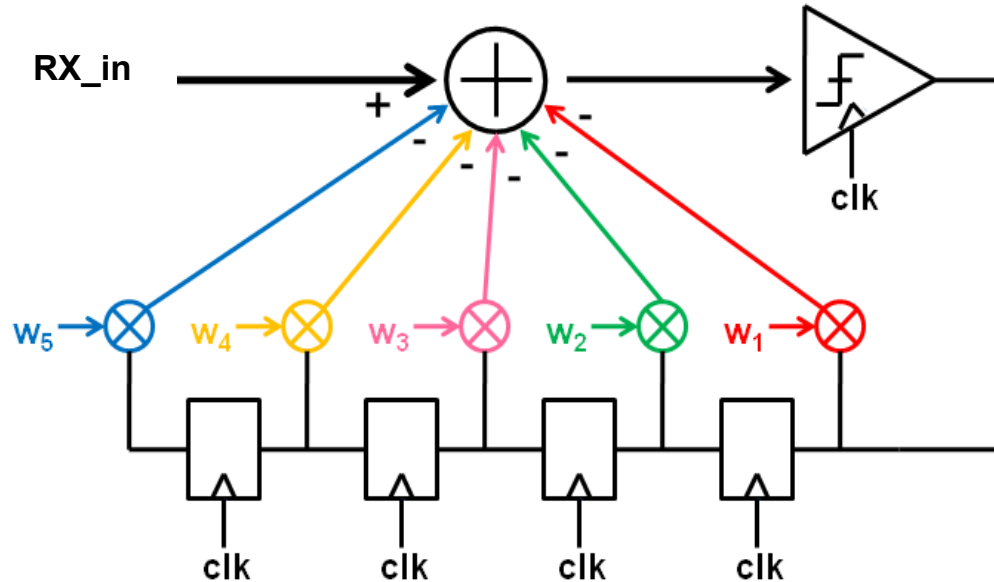


- First tap timing often the most challenging
 - Other taps already have digital inputs
 - First tap must resolve/amplify small analog input signal
 - Larger “ t_{dig} ”

Option 1: Split Summation^[6]

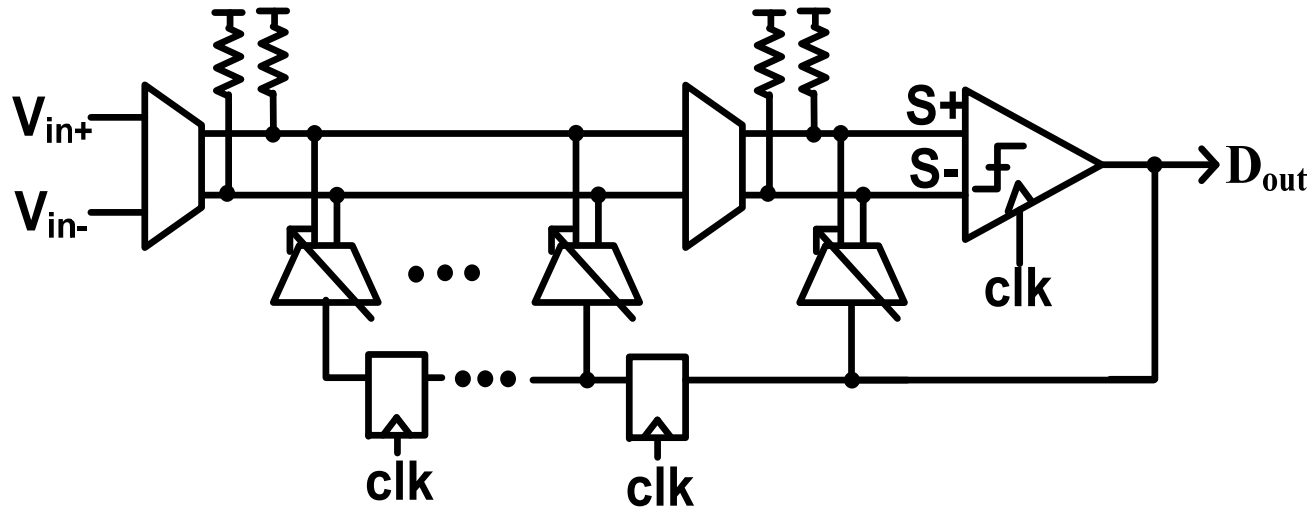


- Faster summer (less self-loading) for 1st tap
- Watch out for non-linearity
 - First summer (later taps) may distort the signal

Option 2: Loop Unrolling^[7]

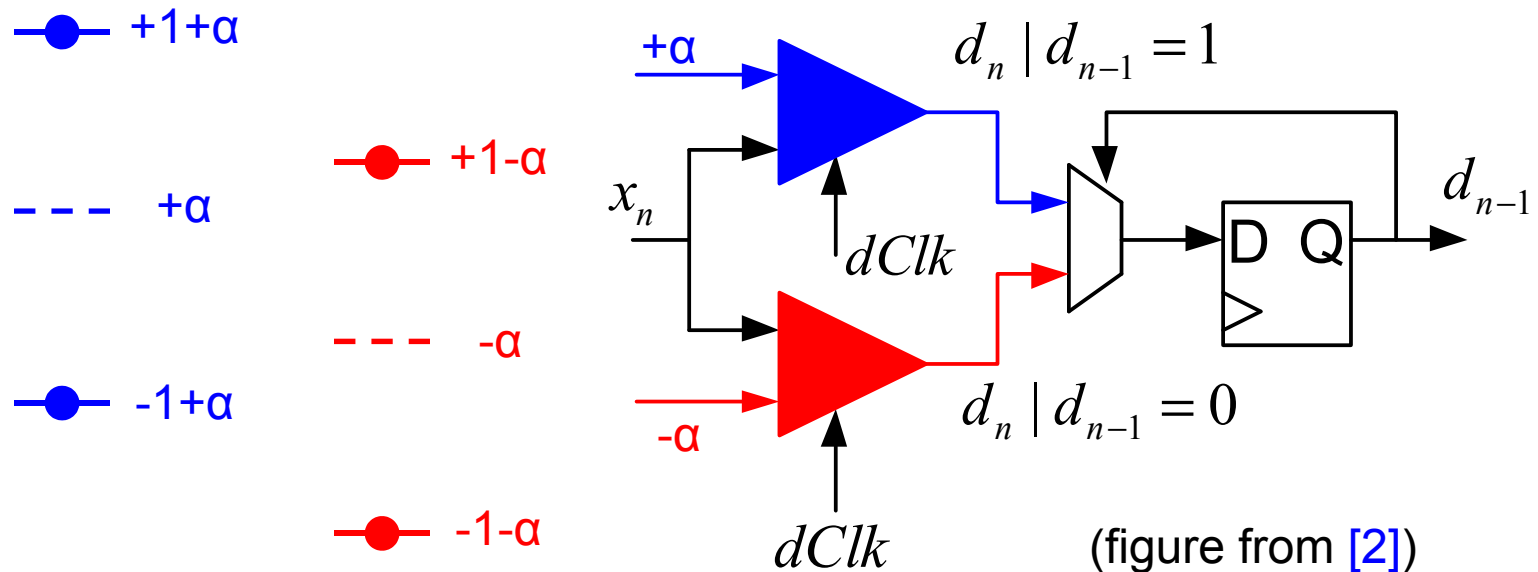

- ❑ Pushes feedback loop into digital domain
- ❑ Watch out for later taps (if there are any) though
 - MUX adds extra latency



Option 3: All CML Design^[8]

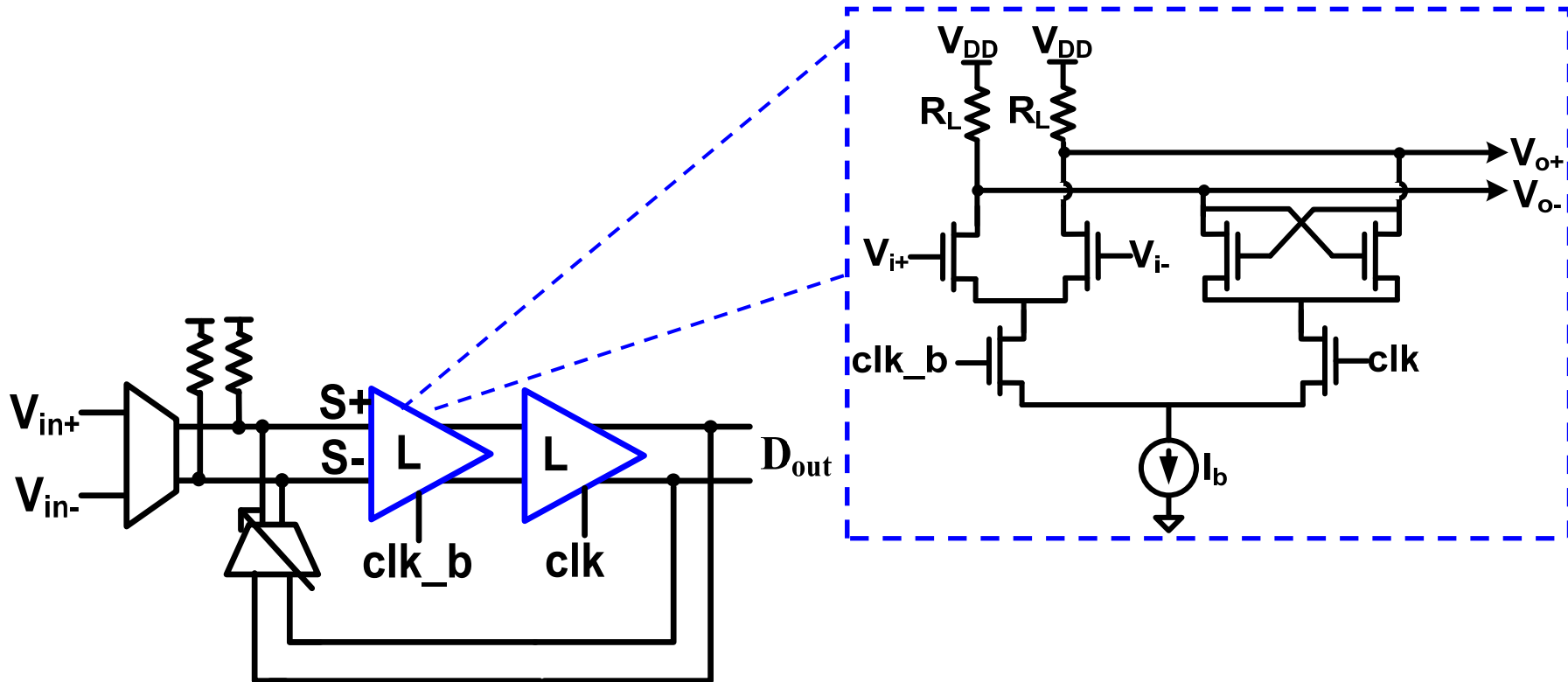


- ❑ Reduces required comparator gain
- ❑ [9] demonstrated over 20Gb/s in 65nm CMOS

DFE Physical Design

 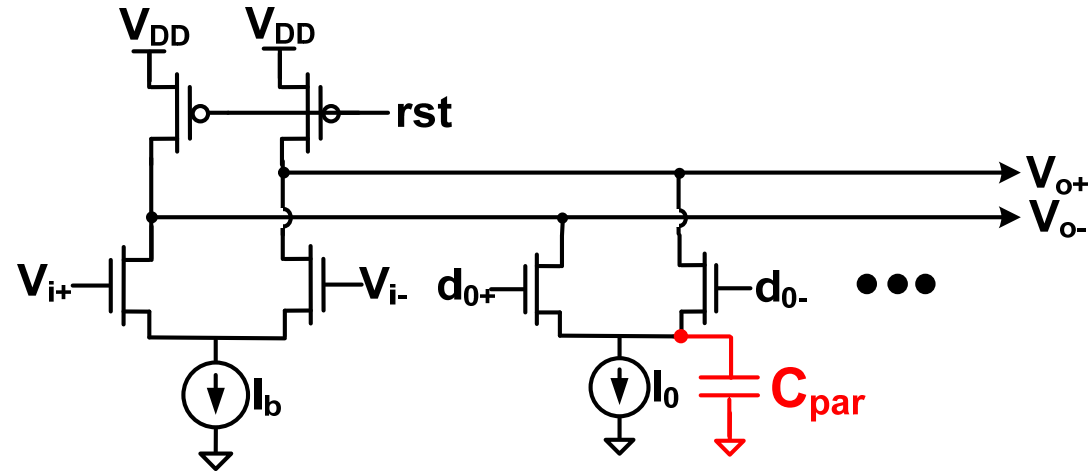- Tap DACs must be high resolution, hence large
- Don't want DACs to increase size (cap) of signal path
 - DACs placed far away
- Result: large C_{par} ...







Impact of Tap Tail Capacitance

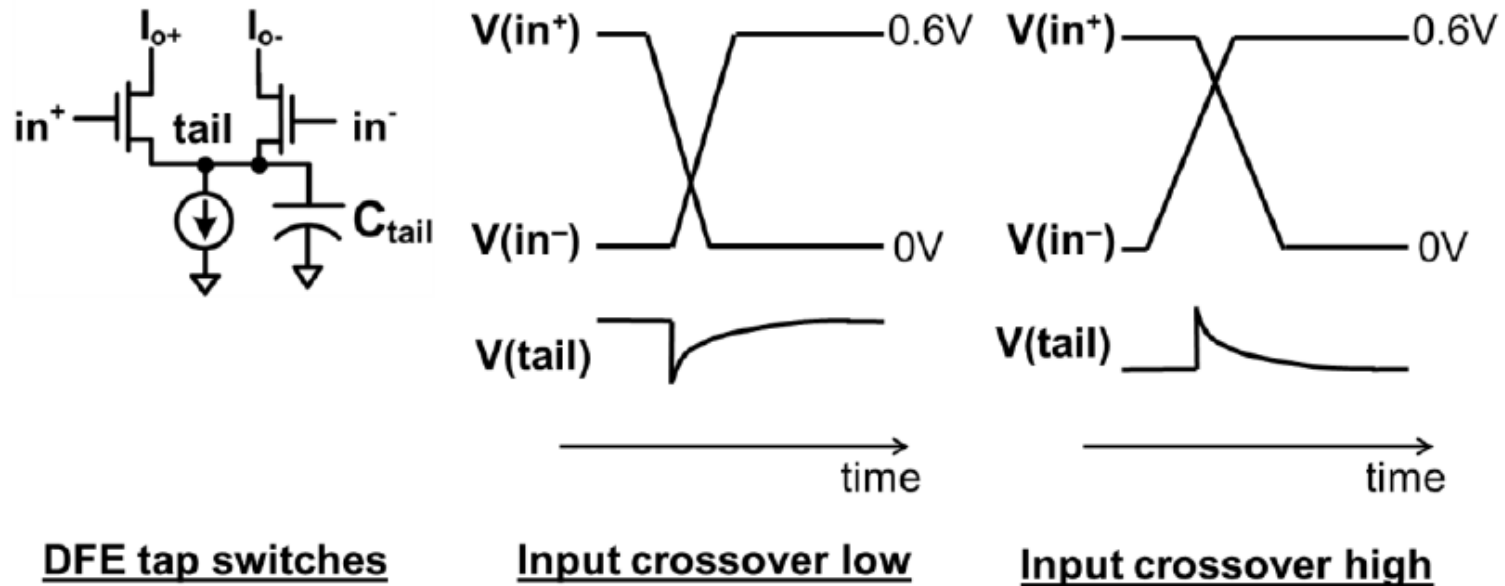

- ❑ Leads to signal-dependent glitches in DFE response
- ❑ Good news: adaptation can & will correct these errors^[4]

Complete Signal Path: Linearity

   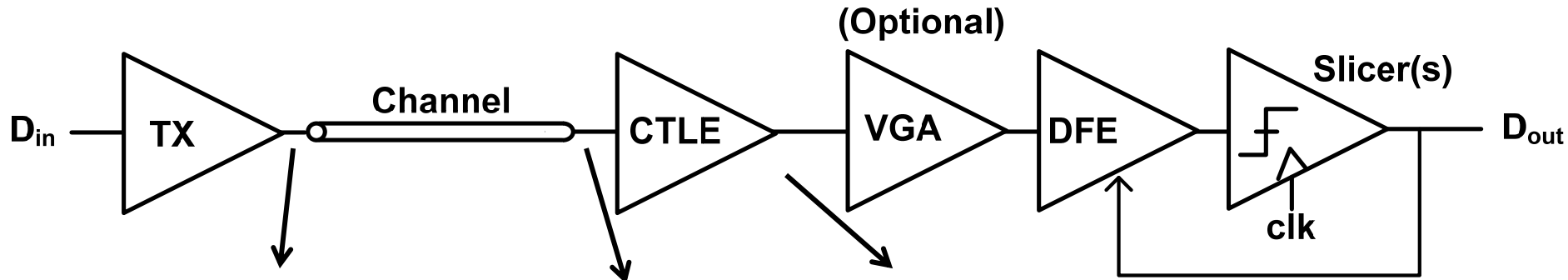

- Ordering of components on RX matters
 - Especially in systems with large TX swing
- CTLE should always be **first**
 - Reduces dynamic range caused by ISI

Tutorial Outline

- RX AFE Basics
- RX AFE Circuits & Power Analysis
- Practical Issues and Common Gotchas
- Key Lessons

Key Take-Home Lessons (1)

- Receiver AFE circuit power easy to predict
 - Calculate power early and often – feed back to system design

- Analog circuits themselves can be very low power
 - Even for many taps (DFE)
 - Power often dominated by large number of high-speed digital structures (flops)

Key Take-Home Lessons (2)

- Minimize dynamic range on the high-speed signal path
 - Watch out for block ordering
 - Keep DACs for e.g. offset cancellation, channel adaptation off the signal path

- Think about the whole system!
 - Often opportunities to save power by moving functionality/problems from one place to another

ISSCC 2014 Papers to Check Out

- Papers 2.1, 26.1: Front-end design issues within state-of-the-art 20 - 28Gb/s transceivers
- Papers 2.4, 2.5: Extremely energy-efficient 16-25Gb/s front-ends based on current-integration and charge domain techniques

Acknowledgements

- These slides include material from:
 - Prof. Vladimir Stojanovic (UC Berkeley)
 - Jared Zerbe (Apple)
 - Prof. Borivoje Nikolic (UC Berkeley)

Selected References

- [1] J. Zerbe et al., "Equalization and Clock Recovery for a 2.5 – 10Gb/s 2-PAM/4-PAM Backplane Transceiver Cell," *IEEE JSSC*, Dec. 2003
- [2] V. Stojanovic et al., "Modeling, Analysis, and Design of High-Speed Links," Ph.D. thesis, Stanford University, Dec. 2004.
- [3] S. Shekhar et al., "Design Considerations for Low-Power Receiver Front-End in High-Speed Data Links," *IEEE CICC*, Sept. 2013
- [4] C. Thakkar et. Al, "A 10Gb/s 45mW Adaptive 60GHz Baseband in 65nm CMOS," *IEEE JSSC*, Apr. 2012
- [5] M. Park et. al., "A 7Gb/s 9.3mW 2-Tap Current-Integrating DFE Receiver," *IEEE ISSCC*, Feb. 2007
- [6] B. Leibowitz, et al., "A 7.5Gb/s 10-Tap DFE Receiver with First Tap Partial Response, Spectrally Gated Adaptation, and 2nd-Order Data-Filtered CDR," *IEEE ISSCC*, Feb. 2007
- [7] K. K. Parhi, "High-speed architectures for algorithms with quantizer loops," *IEEE ISCAS*, May 1990
- [8] H. Wang et al., "A 21-Gb/s 87-mW transceiver with FFE/DFE/linear equalizer in 65-nm CMOS technology ," *IEEE JSSC*, Apr. 2010