

Pipelined A/D Converters


February 9th, 2006
San Francisco

Bang-Sup Song, Professor
Electrical and Computer Engineering
University of California, San Diego


Outline

- Introduction to pipelined architectures
- MDAC-based pipelined ADC
- High-resolution techniques
- Other variations of pipelined ADC
- Circuit design issues
 - Sampling nonlinearity
 - Dynamic comparator
 - Opamp design
- Conclusions

ADC Resolution vs. Speed

 

Nyquist-Rate ADC Family

 


- Averaging, **pipelining**, and time-interleaving are common techniques for all.


Design Solutions

What to do	How to do
To save # of preamps	Interpolation
To save # of comparators	Folding
To save # of both	Subranging
To reduce preamp offsets	Averaging
To speed up conversion	Interleaving
To speed up subranging	Pipelining
To improve linearity	Calibration


Flash vs. Subranging

 

 Save # of preamps and comparators, but need coarse comparator time.




Pipelined ADC Architecture

 


- S/H in every stage using non-overlapping 2-phase clocks.
- ADC should work between the sampling and amplification phases.
- More time for residue amplification than in subranging.

2b Pipelined Stage Example

 


2b Pipelined Residues

 

Capacitor-Array MDAC


(Song, JSSC, Dec. 1990)

 

- Capacitor-array MDAC replaces S/H, DAC, and residue amp.
- Capacitor array can be either binary or thermometer coded.


MDAC Operation

- Sample V_{in} during ϕ_1 .

 


- Amplify residue during ϕ_2 .

 
$$V_o = 2^N \left(V_{in} - \sum_{i=1}^N b_i \frac{2^{i-1}}{2^N} V_{ref} \right)$$



Restore Subtracted V_{ref} Digitally

 


Three Residue Errors

 


- Subtracted analog V_{ref} 's are not accurate.
- Errors should be smaller than the following-stage resolution.
- If over-ranged, ADC error can be recovered.

Digital Correction

(Lewis, JSSC, Mar. 1992)

 


@A	@B	@C	@D
00	01	10	11
10	00	11	01
010	010	111	111


 


Digital output increases monotonically across any digital transitions.

Digital Correction for 4b ADC


 


MDAC for Degenerate 1.5b Case

  


Multiply-by-2 ($2V_{in} -/+ V_{ref}$) circuit using 2 capacitors.

General Tri-Level MDAC Example

  

Issues in Pipelined ADC

 


1
kT/C,
Clock Jitter*,
Switch Nonlinearity*,
Opamp Nonlinearity

* For input S/H only.

2
Metastability,
Latch Time,
Latch Hysteresis,
Preamp Offset

3
Capacitor Matching,
Opamp Settling,
Finite Opamp Gain,
Opamp Nonlinearity


Nonlinearity Error Source

 


- Mismatch between analog and digital steps makes DNL.

Digital Correction vs. Calibration

Segment
Error
 $V_{step} - V_{ref}$

 

No
Segment
Error

 


Digital Correction:
Move segment up
by V_{ref} digitally.


Digital Calibration:
Move segment up
by V_{step} digitally.

INL for Three Cases


Capacitor Mismatch

 


Low Opamp Gain

 

Opamp Gain Nonlinearity

 


High-Resolution Techniques

 

Digital Calibration Concept

(Lee, JSSC, Dec. 1992)

 



1

Measure
segment errors.





2

Accumulate them
for code errors.

  


3


Subtract
errors digitally.

  


MDAC Capacitor Error

 


Residue Output

 

Transfer Function

 


After Calibration

 

- Move segments up or down by code error amounts.


MDAC Capacitor Error Measurement

 


- Measure αV_{ref} , βV_{ref} , γV_{ref} by injecting V_{ref} into each caps.
- These are segment errors. Accumulate them to get code errors.

MDAC Gain Error


Mismatch α , and/or finite opamp gain.

 


Residue Output

 

Transfer Function

 


After Calibration

 

- Discontinuity is corrected by shifting segments up/down like capacitor error.

MDAC Gain Error Measurement

 


- Finite opamp gain A_o error can be measured together with capacitor mismatch error.
- Output may exceed V_{ref} .

What If Output Exceeds V_{ref} ?


- Use a radix smaller than 2 to contain output within V_{ref} .
(Karanikolas, JSSC, Dec. '93)
- Split capacitors into two and limit output swing to $V_{ref}/2$, and add two half V_{ref} errors to get the whole V_{ref} error.
(Moon, TCAS-II, Feb. '97)
- Extend the output range to cover more than V_{ref} .
- Use V_{cal} which is $< V_{ref}$, and digitally subtract it, but need to know V_{cal} to a certain accuracy.
- Initialize with $-V_{cal}$, and measure $V_{ref} - V_{cal}$.

MDAC Gain Nonlinearity


Nonlinear opamp gain.

 


Residue Output

 

Transfer Function

 

After Calibration

 


- Discontinuity is corrected like capacitor and gain errors,
but residual nonlinearity remains.

Embedding Measurement in Background

- Retiring → Retire hardware for calibration.
(Shouwenaars, JSSC, Dec. 1988, Ingino, JSSC, Dec. 1998,
Choe, JSSC, Dec. 2000)
- Skip and Fill → Skip normal cycles randomly for error measurement
and fill in missing data point by interpolation.
(Moon, TCAS-II, Feb. 1997)
- Q-Based → Steal cycles for calibration by operating S/H faster than
the normal operation. (Blecker, ESSIRC 2000)
- Code Density → Estimate errors from output code density.
(Murmann, ISSCC 2003)
- Dithering or Shuffling → PN scrambling of errors and digital correlation
and cancellation.
(Ming, ISSCC 2000, Galton, TCAS-II, Mar. 2000)

Background Nonlinearity Measurement


(Murmann, ISSCC 2003)

 

- Random comparator threshold jump generates two residue curves with constant vertical gap.
- Gain nonlinearity makes $h_1 < h_2$. The difference is measured by code density, and nonlinearity is fitted with a polynomial.


Background Calibration by Dithering

(Ming, ISSCC 2000)

 


- Measure dither with slow but accurate $\Delta\Sigma$ ADC, and compare it with quantized dither to measure the gain error.
- Adjust V_{ref} to match with the subrange.
- Signal range is reduced for dithering.


1.5b MDAC Stage Modified for Dithering

 


 
- Split reference injection to keep the signal range.



Example of Calibration by Dithering

 


1.5b/stage ADC Calibrated by Dithering

  


Technology	0.18 μ CMOS
Resolution	15b
Speed	20MS/s
Supply	1.8V
Reference	1.4V/0.4V
DNL/INL	0.4LSB/1.3LSB
Peak SNDR	72.6dB
SFDR	98dB
THD	-92dB
Calibration	45sec
Active Area	2.3x1.7mm ²
Power	280mW (Analog)

Other Variations of Pipelined ADC

 

 
Time-interleaved N-path
Duplicate hardware for speed.
(Conroy, JSSC, April 1993)
Offset, gain, timing errors
One S/H for timing error.
May calibrate path offset and gain.
Still DNL errors show up
as time-varying spurious tones.



Opamp-sharing
Reuse hardware for low power.
(Nagaraj, JSSC, March 1997)
Opamp input is never reset.
Twice output worst-case settling.
Time-varying input capacitance
Opamp input switching makes it
sensitive to supply noise.

Pipelined ADC with $\Delta\Sigma$ Front-End


(Brooks, JSSC, Dec. 1997)

 

- $\Delta\Sigma$ modulator front-end coupled with pipeline rear-end.
- x8 oversampling, 89dB SNR @ 2.5MS/s.
- 0.6 μ CMOS, 55mW @ 5V, 5.7 x 6.2mm².

Two-Residue Pipelined ADC



(Mangelsdorf, ISSCC, 1993)

 

- Low gain, slow settling amplifier for zero crossings.
 - Suffer from reference error, offset and gain matching.


Pipelined Folding ADC

(Choe, JSSC, Dec. 2000)

  


- Achieves high folding degree without speed constraint.
- Further reduction in the number of comparators.
- Less accurate distributed interstage sampling.

Sampling Clock Jitter

 

 
$$\Delta t_{rms} = \frac{1}{2\pi f_{BW} 2^N} \sqrt{\frac{2}{3}}$$



- Worst-case RMS jitter < Q noise.
- Right signal at wrong time = Wrong signal at right time.
- Worst-case jitter should be < 80fsec for 15b @100MS/s.

Bottom-Plate S/H Design

(Li, JSSC, Dec. 1984)

 


- Minimize bottom switch on-resistance and watch its nonlinearity.

- Prevent output from wandering during sampling


- Turn off top switches early to reduce V_{th} -dependent nonlinear clock feed-through and fall time effect.

Low-Jitter Sampling Clock

 



- Use a low-jitter clock source, and minimize the clock delay.
- Square-wave clock is difficult to match impedance at a board level. Use a crystal filter for sinusoidal clock.

Bottom-Plate Switch Nonlinearity

 

- R_{on} nonlinearity is dominant in sampling.
- Reduce voltage drop across R_{on} , and keep R_{on} constant.

Nonlinearity of Bottom Switch

  



0.25μ process @2.5V

$$15\tau = 15(R_{on} + R)C < T/2$$

$$R \approx 10R_{on}, C = 0.5\text{pF}$$

Clock Boost for Low R_{on}

(Cho, JSSC, Mar. 1995)

  


$$R_{on} = \frac{1}{\mu C_{ox}(W/L)\Delta}$$

- R_{on} is lower, but nonlinear.

Clock Boost for Constant R_{on}


(Brooks, JSSC, Dec. 1997)

 


- R_{on} is relatively constant, but V_{th} is nonlinear.

Clock Boost with Variable V_{th}

(Pan, ISSCC 2000)

 


Another Clock Boost with Variable V_{th}

 


- Diode provides a voltage drop of V_{gs} .
- V_{in} should be low-impedance source to drive $|I_1 - I_2|$.

Considerations for Sampling

 


- kT/C and clock jitter
- $>10\%$ signal attenuation at Nyquist sampling if $RC \sim 1/20f_s$.
- Finite CMRR: $CMRR \times \Delta V_{cm}$.
- Low opamp gain is acceptable if transfer function is linear.
- At HF, switches are large, and S/D junction capacitors are nonlinear.
Dummy diode (?) may be effective to cancel nonlinearity.
- For reliability, limit V_{gs} , V_{gd} , and V_{ds} within V_{dd} (Abo, JSSC, May 1999).

Sampling in S/H and MDAC

 


Flash ADC for Sub-ADC (2b Case)

 

- Complexity and comparator offsets are limits.


Comparator with Double Latches

 


- Latch time constant is C/g_m set by process.
- Latch has a hysteresis of 10's of mV.
- Since latch input has large V_{GS} , watch for offset.
- With mV seed signal, latch flips in less than $\sim 0.2\text{ns}$.
- Additional digital latch is needed to avoid the meta-stable state.

Dynamic Comparator for 1.5b Case

Capacitor Divider
(Song, JSSC, May 1995)

 


Current Divider
(Cho, JSSC, Mar. 1995)

 


- For 1.5b comparator, no preamp is needed.
- No static power is consumed in dynamic latch.

Dynamic Latch Offset

Seed on Triode Input

 

Seed on Saturated Input


 


- Offset is large for triode input.
- By moving input pair to the middle, the input pair can be biased into saturation for lower offset.

Capacitor Matching Requirement

N bits/stage → Next stage can be (N-1) bits less accurate.


For example, to make 10b ADC;

  

$$\sqrt{2} \times \frac{\Delta C}{C} < \frac{1}{2^9} \rightarrow \frac{\Delta C}{C} < \frac{1}{\sqrt{2} \times 2^9}$$

$$\sqrt{16} \times \frac{\Delta C}{C} < \frac{1}{2^6} \rightarrow \frac{\Delta C}{C} < \frac{1}{2^8}$$

Opamp Gain Requirement

 

$$\left. \begin{array}{l} \text{Loop Gain} = A_o f = A_o \times \frac{C_2}{C_1 + C_2 + C_x} \\ \text{Gain Error} = \frac{C_1 + C_2 + C_x}{C_2} \times \frac{1}{A_o} \end{array} \right\}$$


- $C_1 = 0$ in S/H.
- $C_x = C_p + C_{gs} + (1+A) C_{gd}$

$$N=2: A_o > 2^9 \times \frac{C_1 + C_2 + C_x}{C_2} = 2^9 \left(2 + \frac{C_x}{C} \right) = 2^{10} \left(1 + \frac{C_x}{2C} \right)$$

$$N=5: A_o > 2^6 \times \frac{C_1 + C_2 + C_x}{C_2} = 2^6 \left(16 + \frac{C_x}{C} \right) = 2^{10} \left(1 + \frac{C_x}{16C} \right)$$

→ Gain requirement is less in the N=5 case.

Opamp Settling Requirement

 

$$f = \frac{C_2}{C_1 + C_2 + C_x}, \quad C_1 = 0 \text{ in S/H}$$

$$= \begin{cases} 1/(2 + \frac{C_x}{C}), & \text{if } N=2. \\ 1/(16 + \frac{C_x}{C}), & \text{if } N=5. \end{cases}$$

Compensated differently.

f factor of the N=2 case is more sensitive to the parasitics C_x .

Lower DC gain & Narrower BW.

$$A_o \times f > 2^{11-N},$$

$$e^{-T/2\tau} < \frac{1}{2^{11-N}},$$


$$\Phi_M = 90^\circ - \tan^{-1} \frac{\omega_{\text{unity}} \times f}{\omega_{p2}} > 60^\circ.$$

Then, settle with $\tau = \frac{1}{\omega_{\text{unity}} \times f}$
unless slew-limited.


How to Reduce Input Capacitance?

- High-speed design demands smaller sampling capacitance and larger input device for wider BW and faster settling.


Negative Cap.

 

Source Follower

 

Gain Stage

 


Normally-off 1/2 size dev. cancels input C_{gd} Miller cap.

Input cap. is driven by low imp. ($1/gm$) of the source follower.


Low gain but wide BW amp makes up gain loss.

Triple-Cascode Opamp

 


Capacitive CM Feedback

- No power consumption
- Fully balanced.

 

Folded-Cascode Opamp

 
- Centered CM input voltage, but slightly lower gain.
- Also more parasitic at 1st cascode node.





Gain-Boosted Cascode Opamp

- Cascode opamp settles fast, but has low gain.

 (Hosticka, JSSC, Dec. 1979, Bult, JSSC, Dec. 1990)



Gain-Boosted Opamp Stability

  


Doublet (pole-zero pair) slows down settling.


$$\rightarrow \omega_{\text{unity}} \times f < A_o \omega_p$$

If non-dominant pole, ω_{p2} , is lower than the boost-loop unity-gain frequency, $\Phi_M < 45^\circ$.
 
$$\rightarrow A_o \omega_p < \omega_{p2}$$




Two-Stage Opamp

 

- Larger signal swing than cascode.
- Cascode boosting can be used.
- Second pole is at g_{m2}/C_L .
- Right-half-plane zero at g_{m2}/C_c .

Design Considerations

 

Conclusions

- Minimize delay in the clock path for low jitter, and linearize bottom-plate switch for sampling.
- Optimize number of bits per stage to reduce capacitance matching and opamp gain requirement.
- Watch opamp gain, nonlinearity, input capacitance, and doublet effect in settling.
- Use tri-level thermometer-array capacitor MDAC, and shift comparator threshold by a half bit for minimum hardware.
- For higher resolution, use digital calibration.