 


Analog Design at 65 nm

Bob Lefferts, Navraj Nandra
Mixed-Signal IP
SNUG Israel 2007



•**CONFIDENTIAL INFORMATION**

•The following material is being disclosed to you pursuant to a non-disclosure agreement between you or your employer and Synopsys. Information disclosed in this presentation may be used only as permitted under such an agreement.

•**LEGAL NOTICE**

•Information contained in this presentation reflects Synopsys plans as of the date of this presentation. Such plans are subject to completion and are subject to change. Products may be offered and purchased only pursuant to an authorized quote and purchase order. Synopsys is not obligated to develop the software with the features and functionality discussed in the materials.

Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

Analog Versus Digital @ 65 nm

- Digital design
 - Significant density increase
 - Small, high speed, leaky devices
 - With lots of variation in timing.....
 - Effort focused on lower power techniques, SI effects, DFM
- Analog design
 - Increase in gate & off-state leakage
 - Decreased output impedance (poorer current sources)
 - Increased “Sources of Variation”
- Mixed signal design: using thin gate vs. thick gate circuits
 - Most analog designs use more than one gate oxide (core + I/O)
 - Analog device sizes set by precision, not minimum dimensions
 - “Same old” thick gate devices for slow speed analog circuits
 - *It is still possible to build high precision circuits*

Key Trends In Transistor Scaling

$$\frac{1}{\tau} = \frac{I_{ds}}{C \times V_{dd}} \sim \frac{\mu_{eff} \epsilon_{ox}}{\sum C} \frac{1}{L_g T_{ox}} \frac{(V_{dd} - V_t)^{1 \sim 2}}{V_{dd}}$$

Strained Si, high mobility channel $\rightarrow \mu_{eff}$
 High K $\rightarrow \epsilon_{ox}$
 Gate work function $\rightarrow (V_{dd} - V_t)^{1 \sim 2}$
 Intrinsic, parasitic interconnect $\rightarrow \sum C$
 Transistor scaling $\rightarrow L_g, T_{ox}$
 V_{dd}

Bottom-line: technology scaling hurts analog
Scaling effects not understood & modeled hurts SoC



Analog vs Digital Partitioning


- Move as much as possible into the digital domain
 - Digitally controlled PLL
 - PVT insensitive loop filter, loop dynamics
 - Digital control of simple analog function
- Digital access into analog domain – analog test bus
 - You need visibility into analog circuits to be able to verify device matching
- Use analog circuits (feedback) to remove normal variation
 - Examples:
 - PLL
 - Duty cycle correction
- Mixed Signal Design Example : DCC

Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary


Duty Cycle Correction : Clocks

 - Many systems use DDR (Double Data Rate) techniques where data transitions on BOTH edges of the clock
- PLL's can remove variation in period (frequency) but Duty Cycle variations show up as jitter with DDR




- Clock sources do not naturally produce exactly a 50% duty cycle
 - PMOS pulls up, NMOS pulls down
 - Difficult to “Dead Recon”
- Duty Cycle Correction
 - Actively force 50% duty cycle independent of the source clk

DCC Amp Schematic

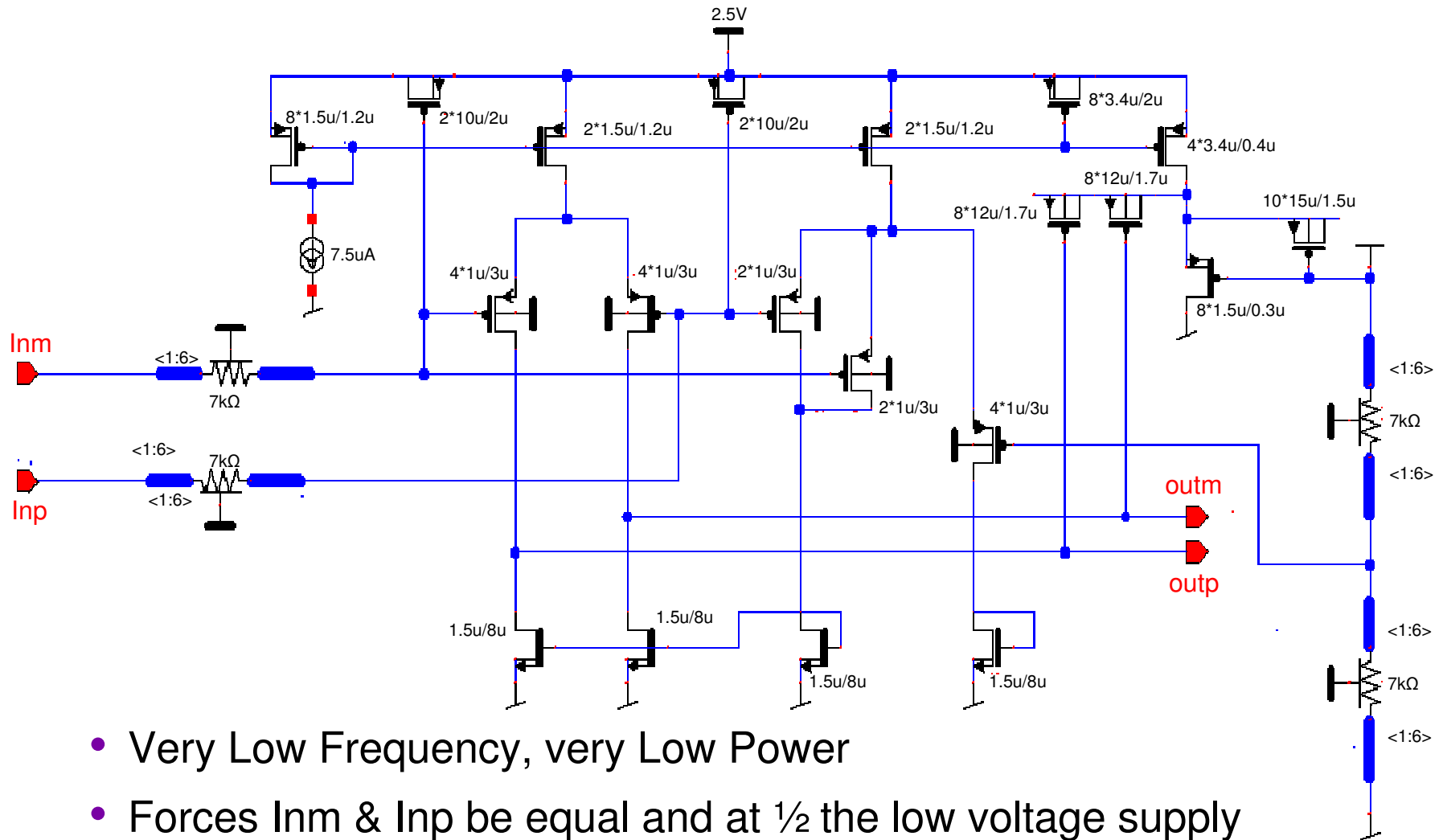


- Very Low Frequency, very Low Power
- Forces Inm & Inp be equal and at $\frac{1}{2}$ the low voltage supply

DCC Amp Schematic

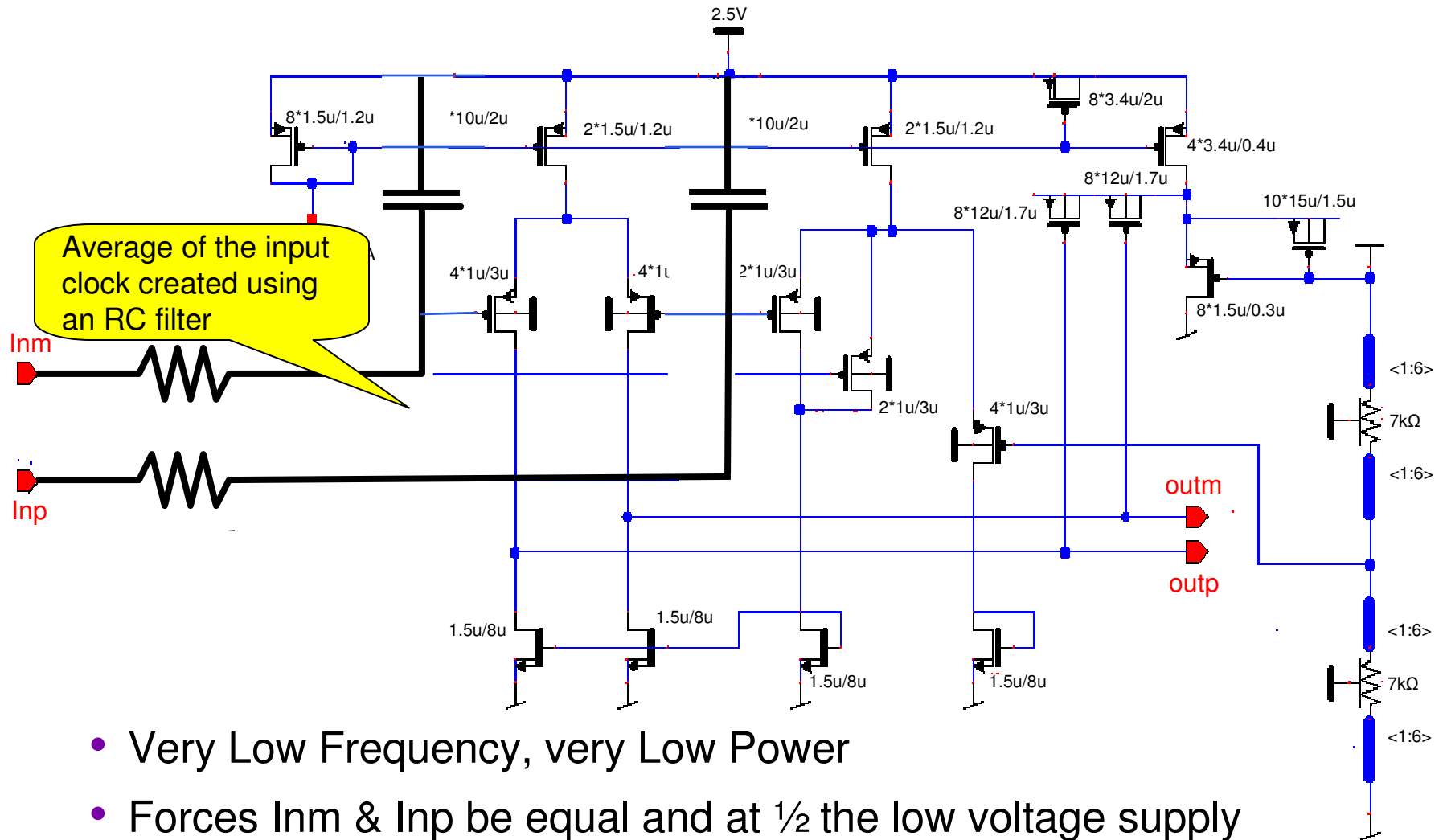


- Very Low Frequency, very Low Power
- Forces Inm & Inp be equal and at $\frac{1}{2}$ the low voltage supply

DCC Amp Schematic

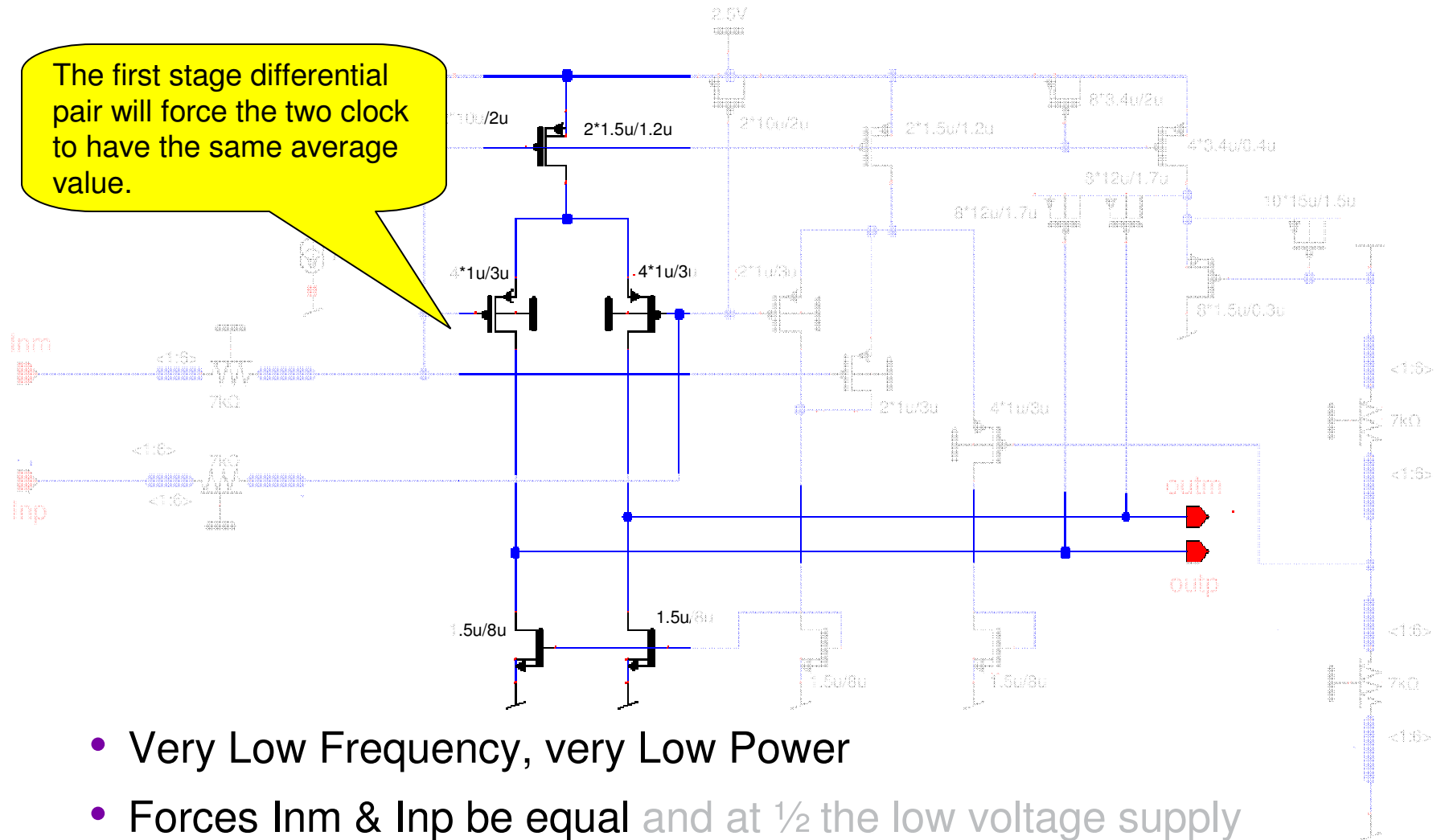



- Very Low Frequency, very Low Power
- Forces In_m & In_p be equal and at $\frac{1}{2}$ the low voltage supply

DCC Amp Schematic


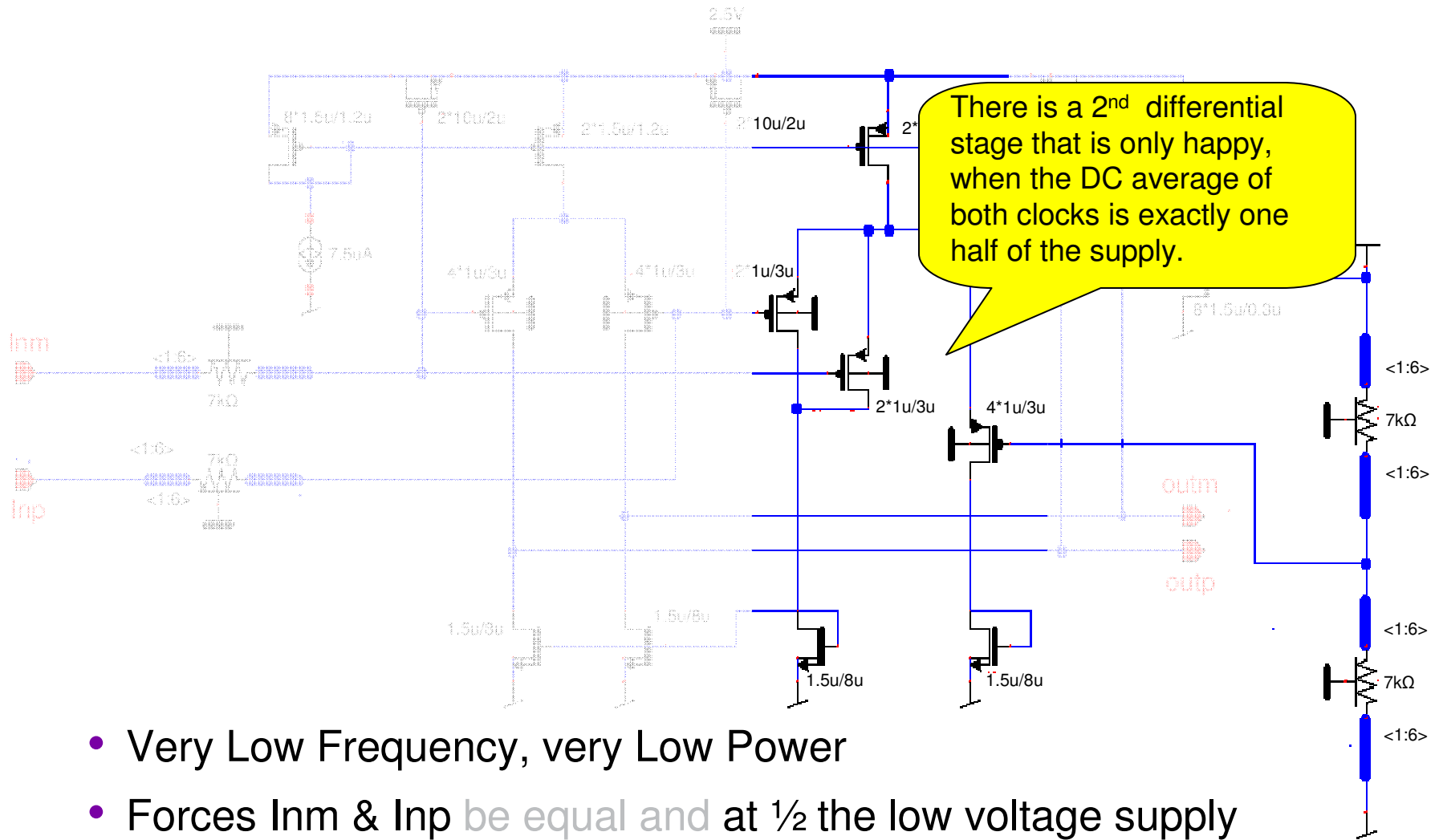


- Very Low Frequency, very Low Power
- Forces Inm & Inp be equal and at 1/2 the low voltage supply



Active Duty Cycle Correction : Results

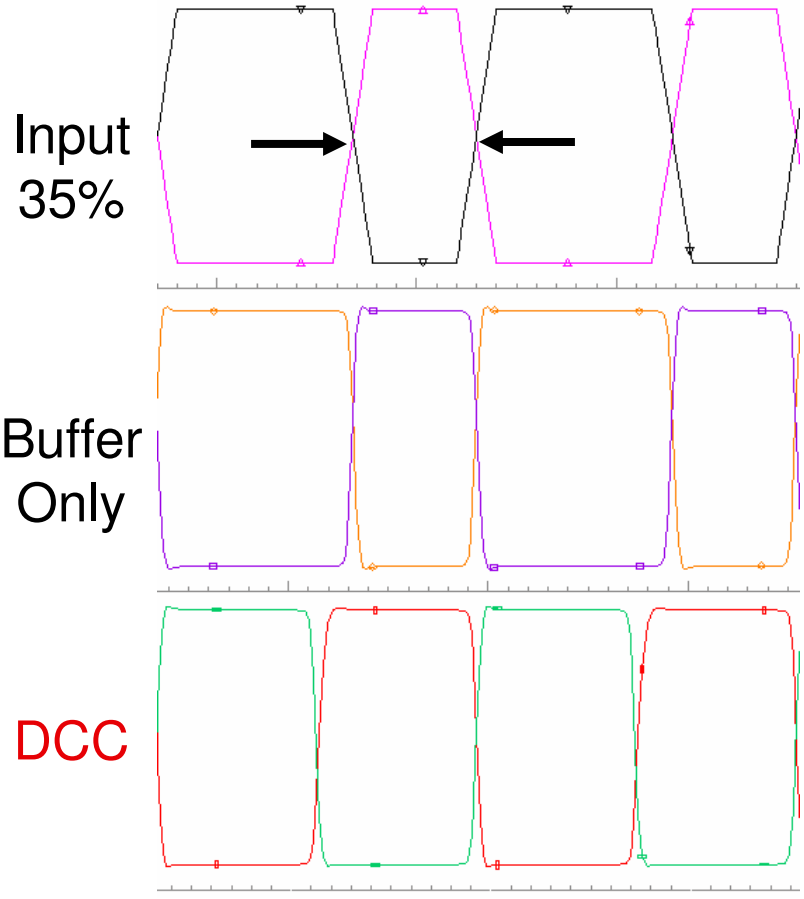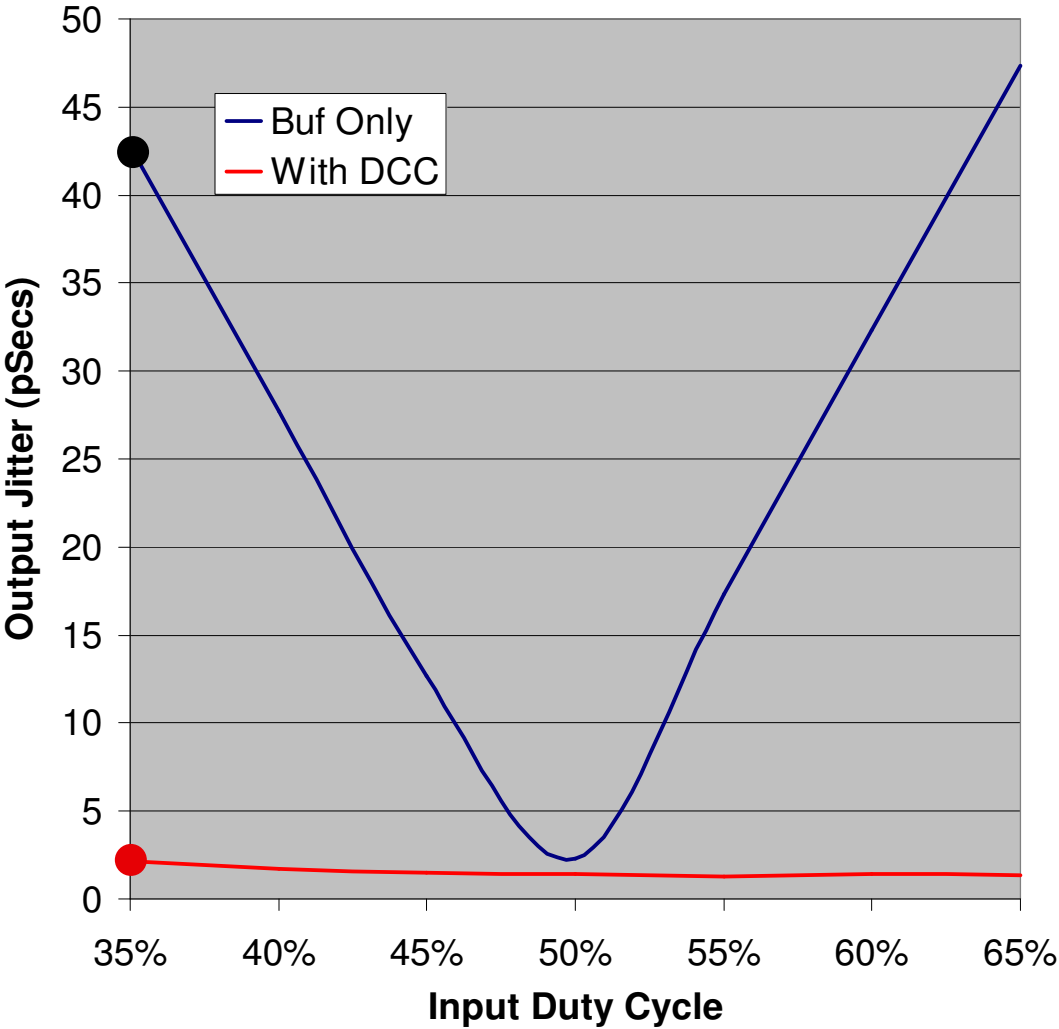



Active Duty Cycle Correction : Results

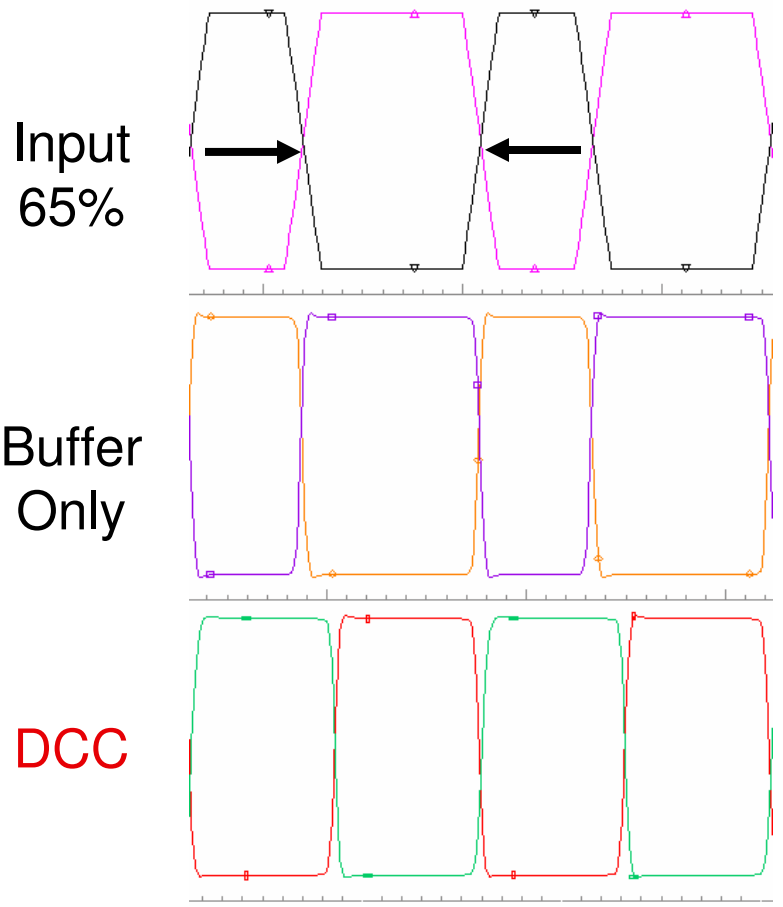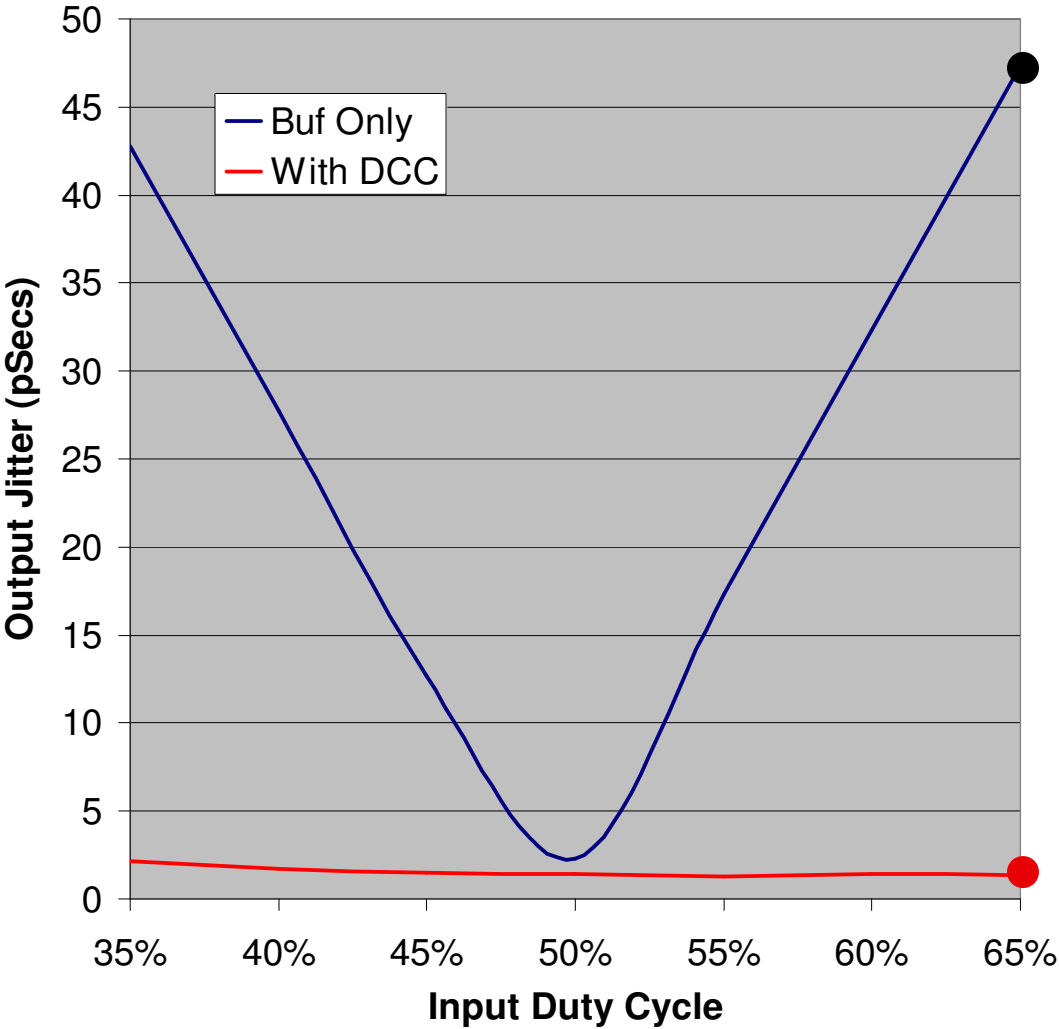

Active Duty Cycle Correction : Results

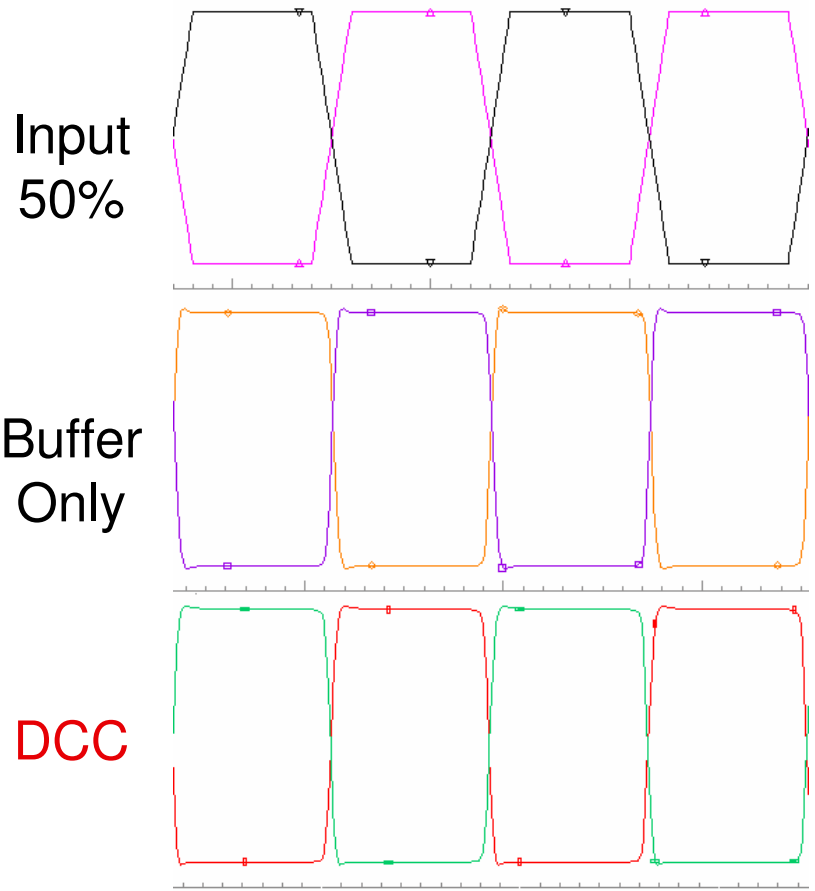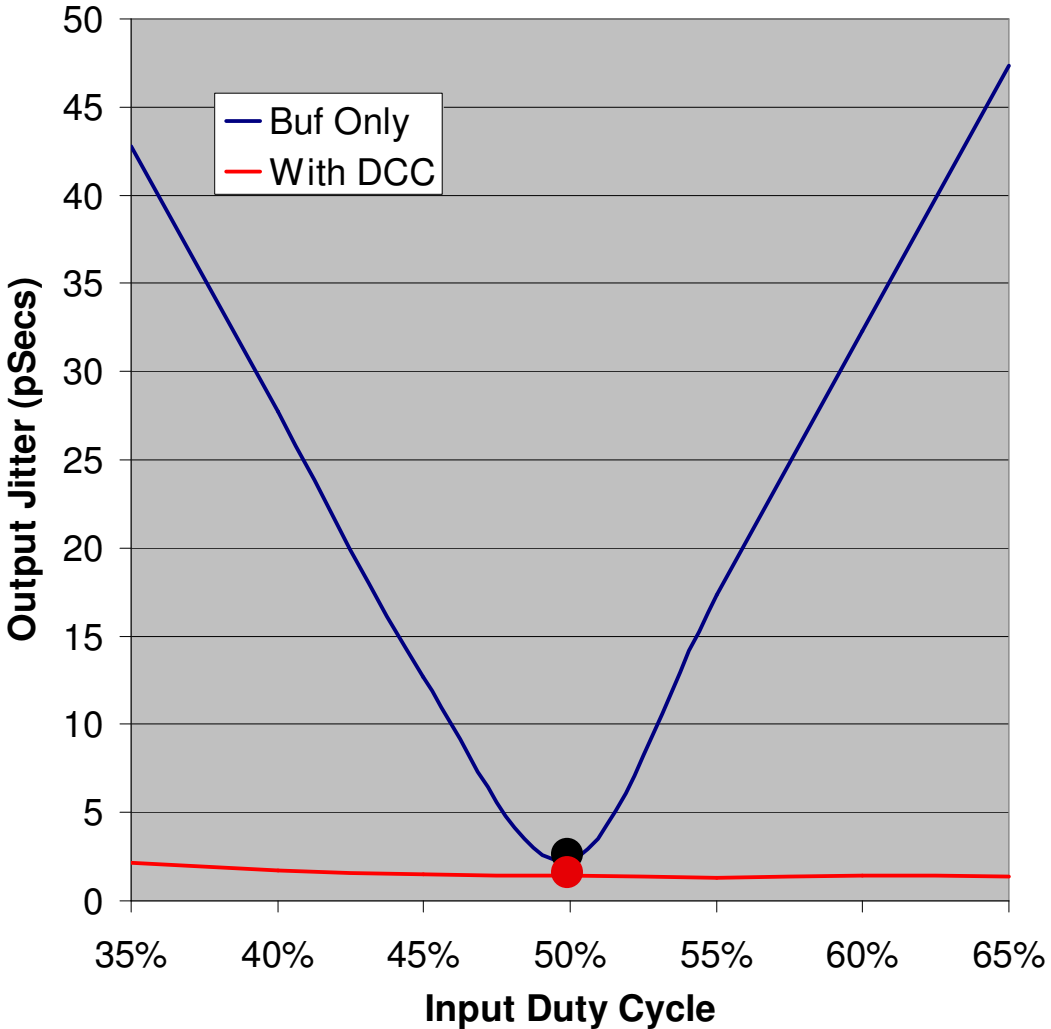

Active Duty Cycle Correction : Results

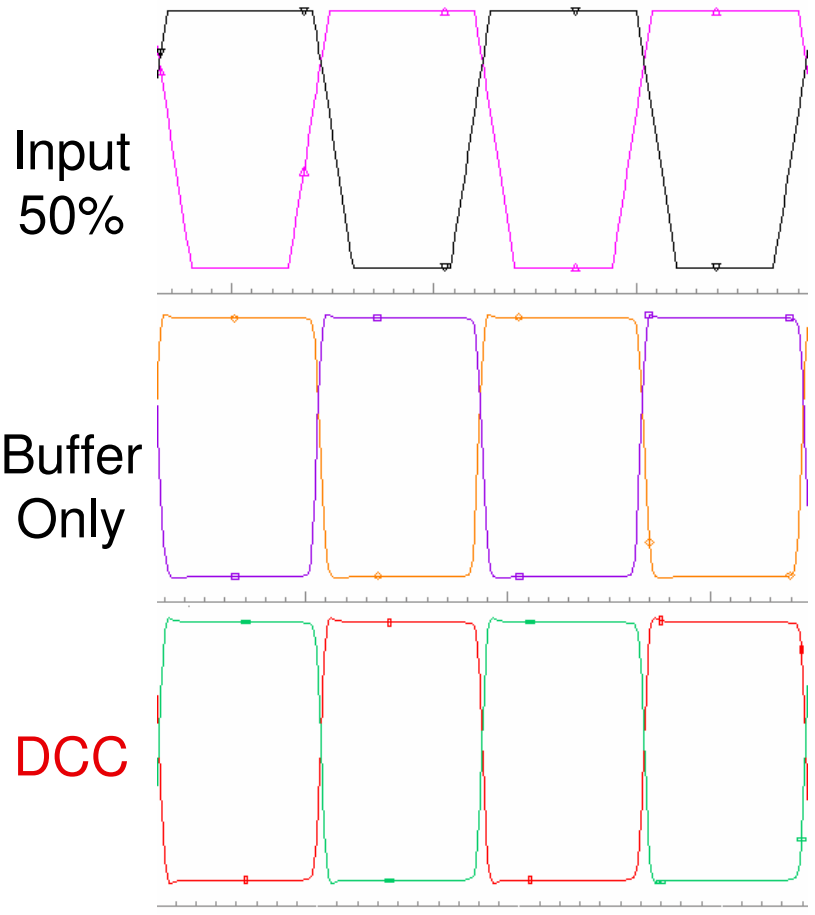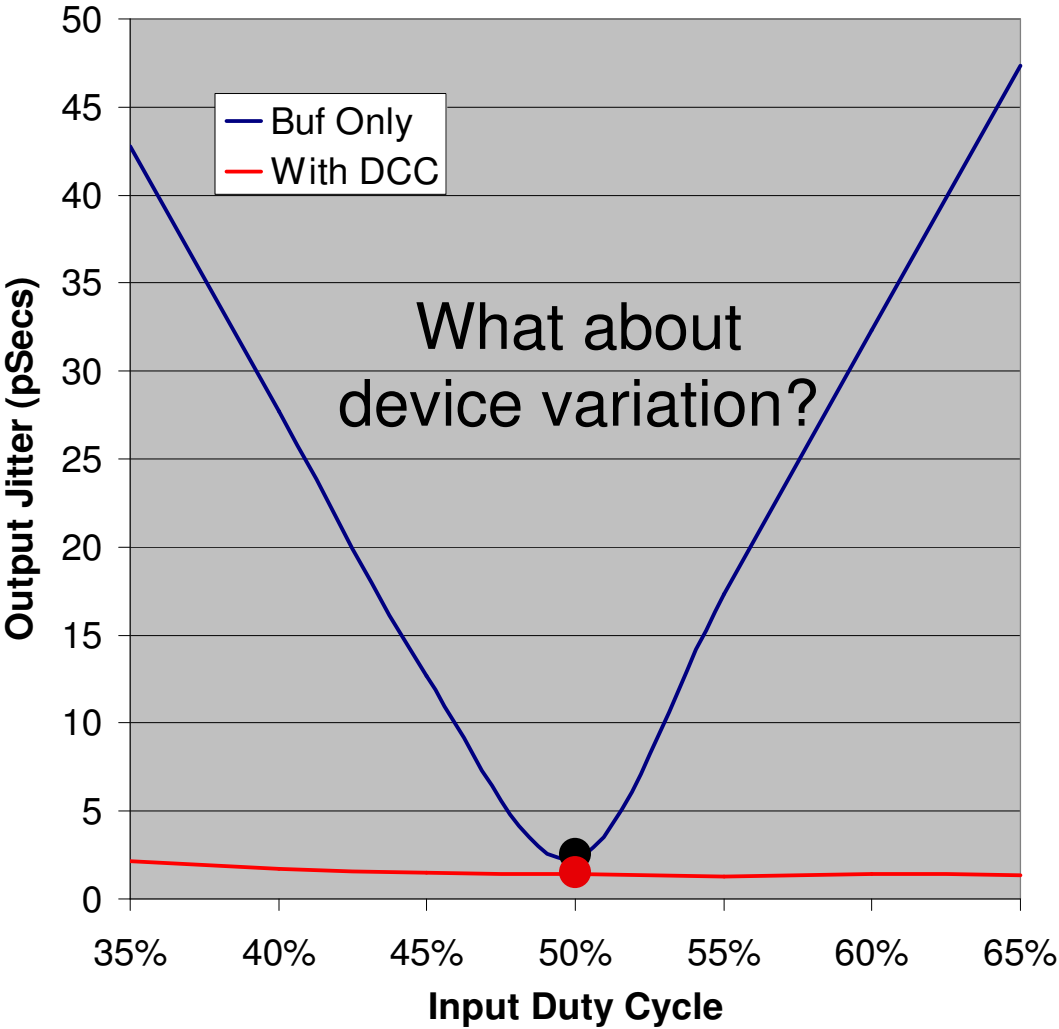


Variation due to device miss-match

- Buffer chain rise and fall times are dependent on the relative strengths of NMOS & PMOS.
- Variation in devices due to their small size causes variation in the output of a buffer chain


- 3σ I_{dsat} miss-match

$$\frac{\sim 3\%}{\sqrt{L \cdot W}}$$

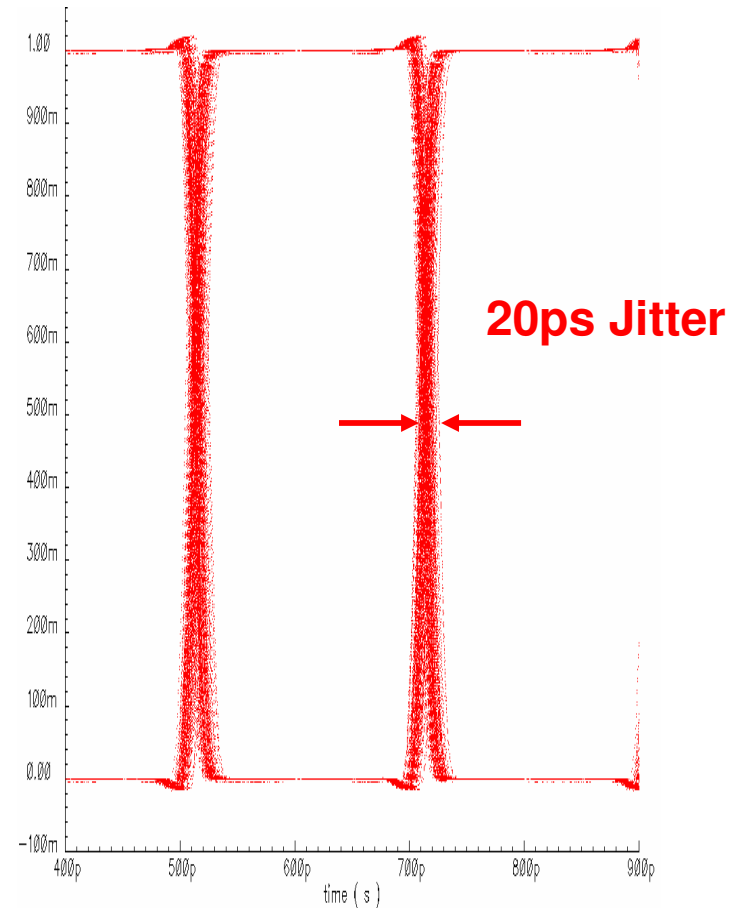- 0.5 X 0.065 device \rightarrow 16%
- Variation in the Op Amp changes the performance of the analog correction




DCC Amp Schematic

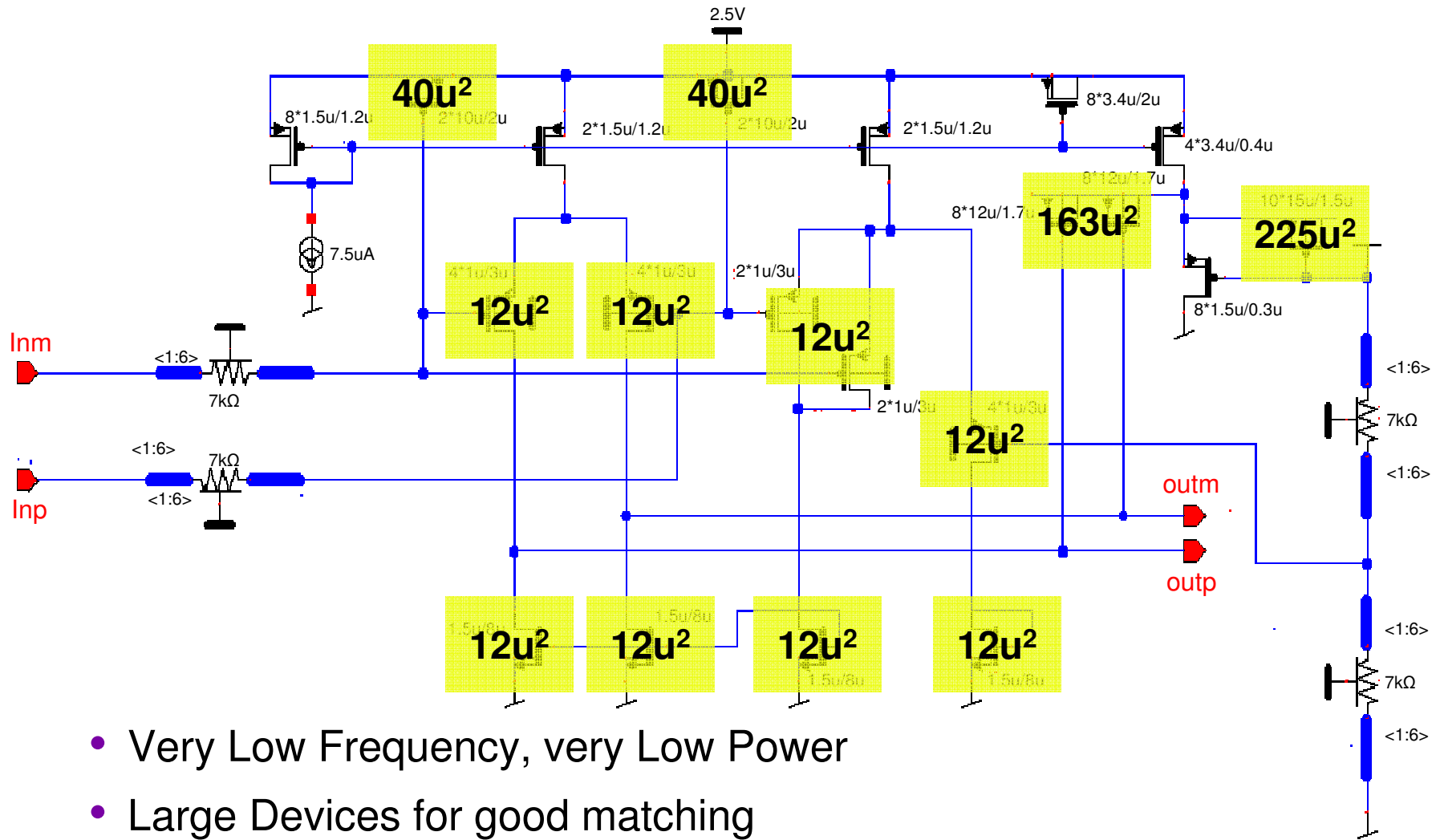


- Very Low Frequency, very Low Power
- Large Devices for good matching

Analog Functionality Depends on Device Matching

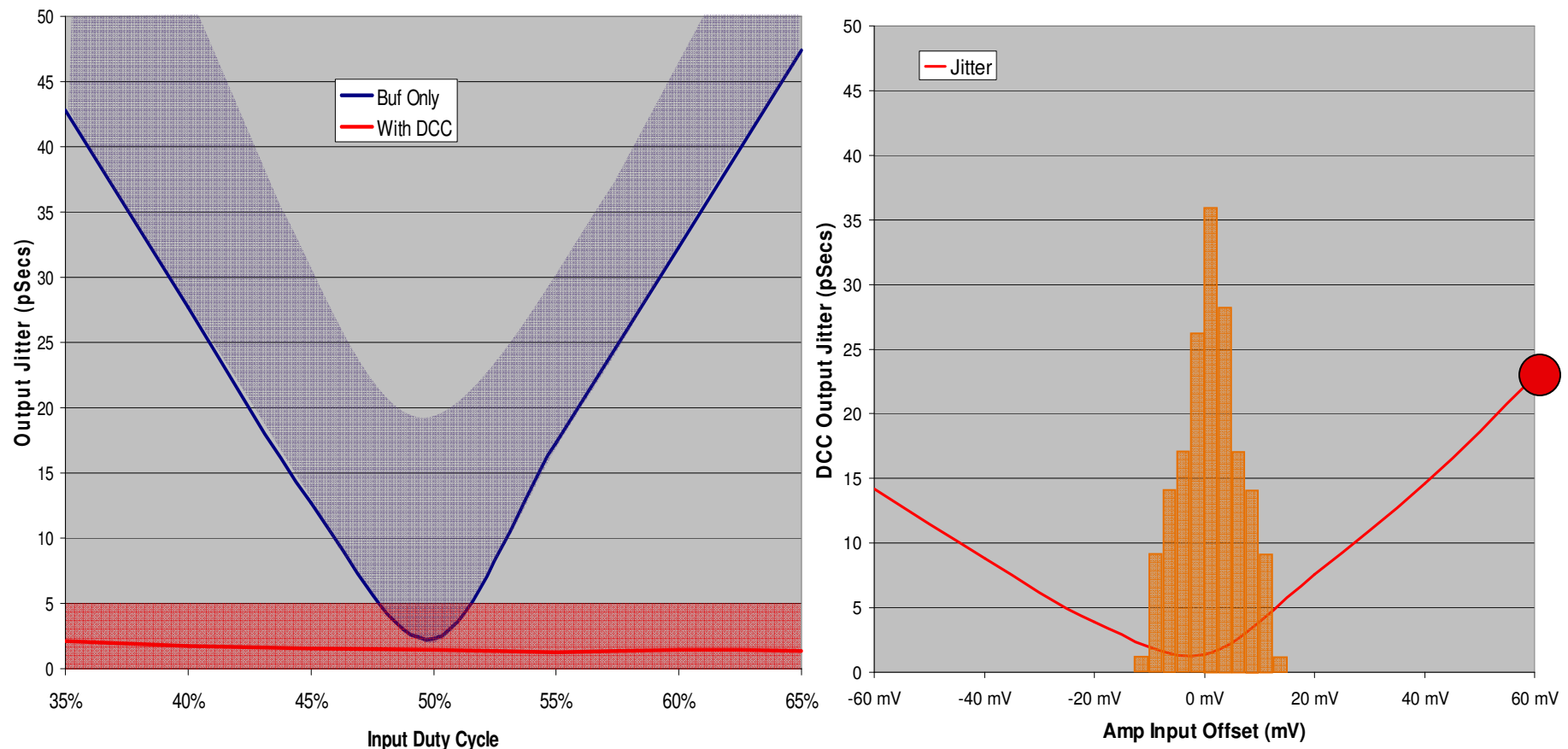
- Monte Carlo Simulations are mandatory in analog design
- **Systematic Offsets can Kill an Analog Circuit**



DCC Amp Layout @ 65nm

 


DCC Amp Layout

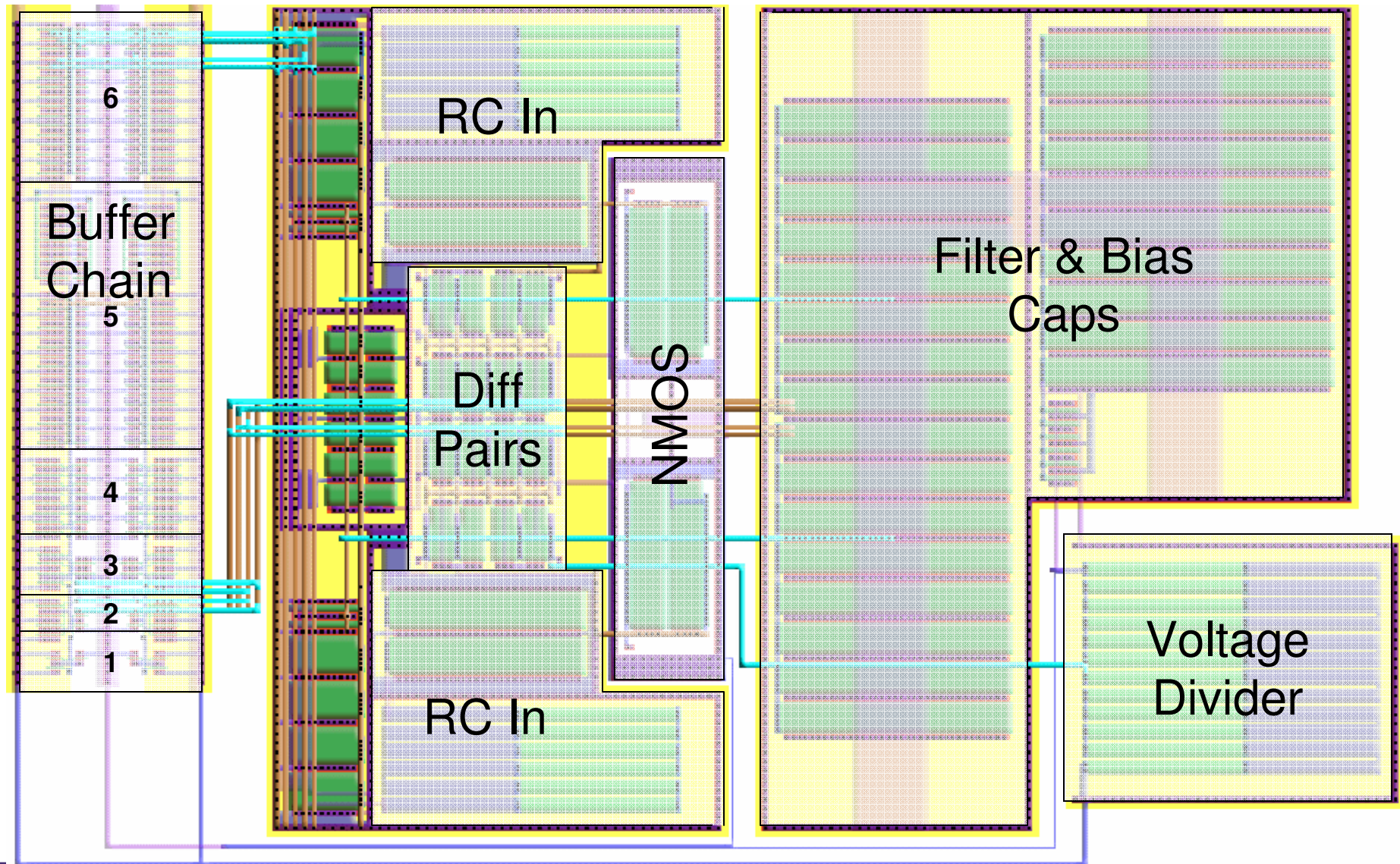


DCC Amp Layout – Good

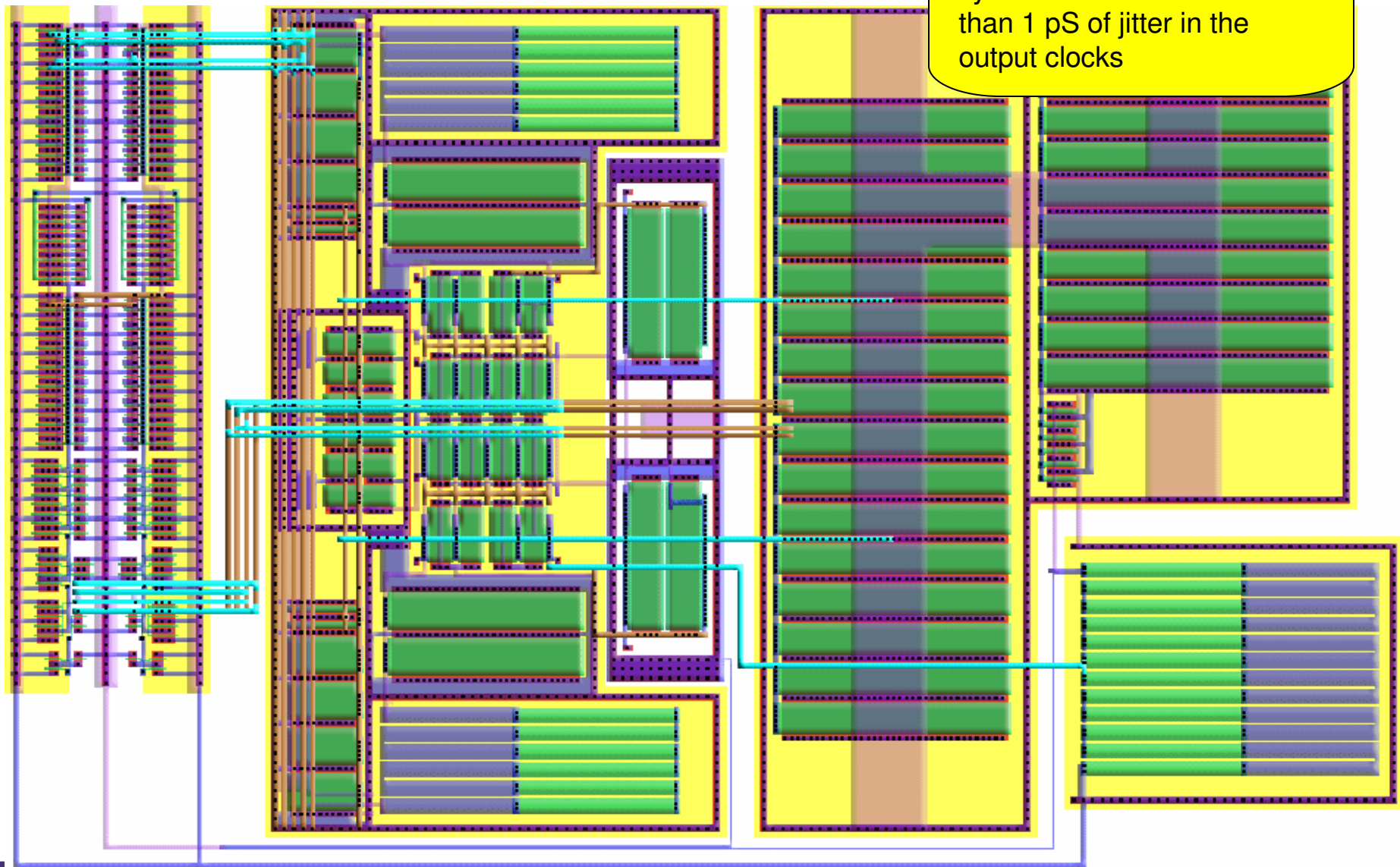This amplifier has <math><1\text{ mV}</math> of systematic offset and far less than



DCC Amp Layout – **BUSTED!**

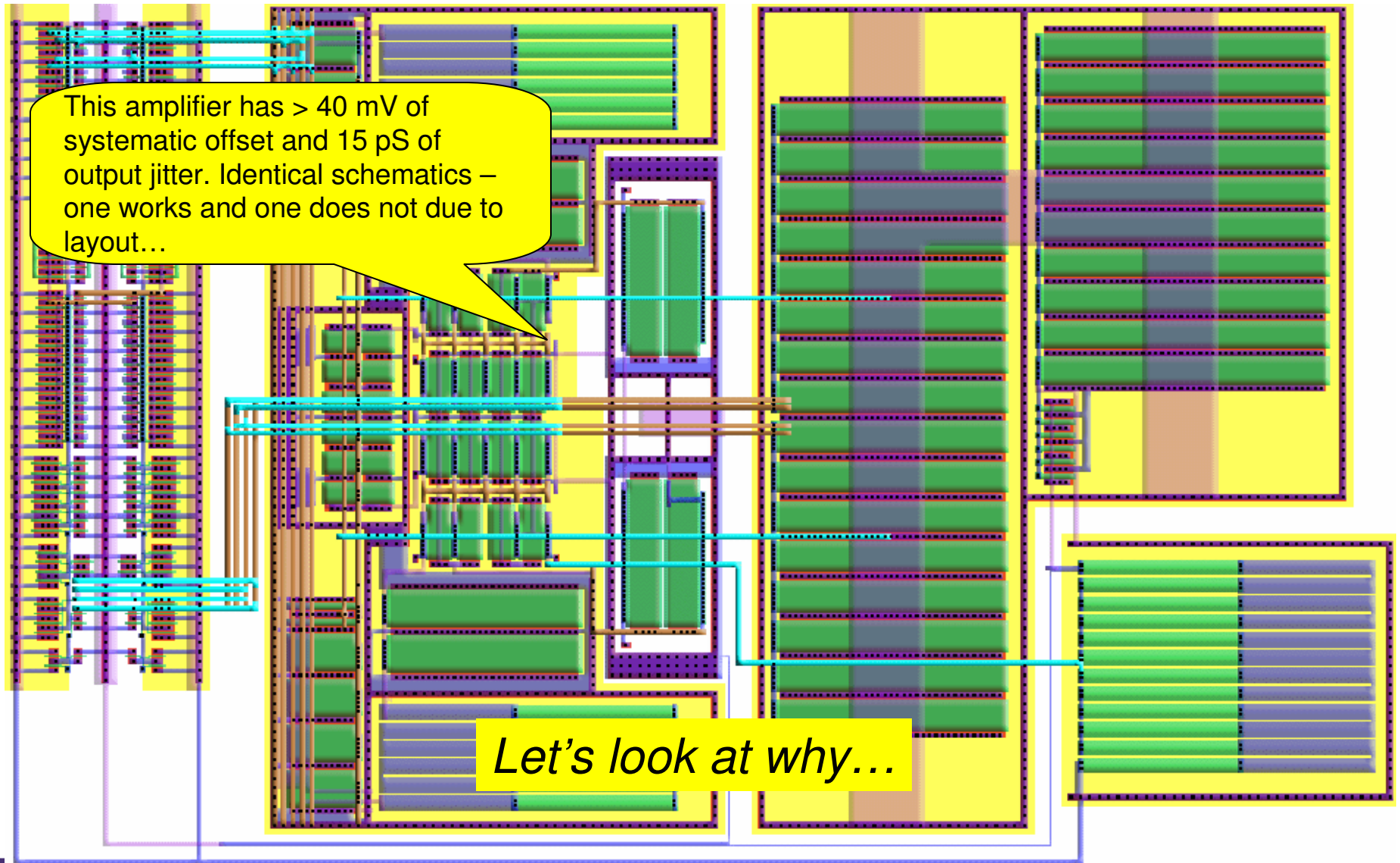

Outline


- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- **Killer sources of variation in analog design**
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - **Current mirror example**
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

Killer Sources of Variation


- Variation due to device size is well understood...
 - Monte Carlo simulations of V_t & I_{dsat} miss-match
- Systematic Variation based on Physical Changes to the device
 - STI Stress
 - Well Proximity
 - Contact Stress
 - OPC/PSM Variations
- Time Dependent Variation
 - NBTI
 - HCI

We are operating in a regime well beyond what would have been described as already broken 10 yrs ago!

 
Stress due to Shallow Trench Isolation (Modulates Mobility)




STI Stress

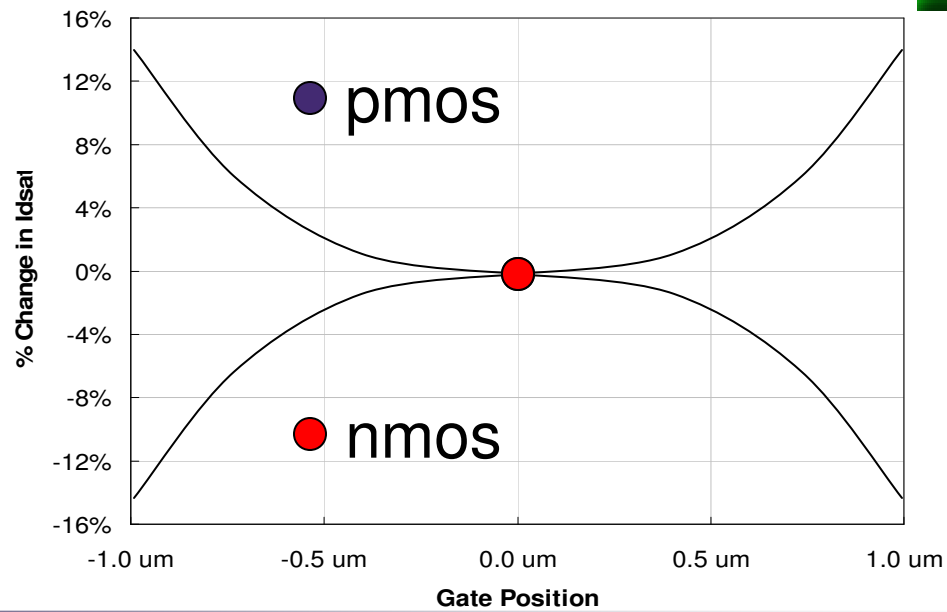

STI Stress

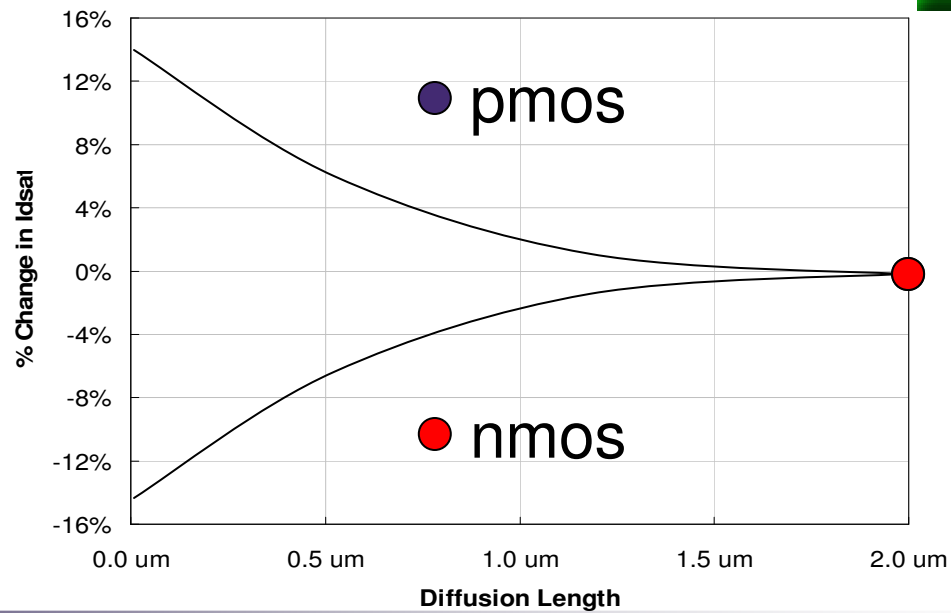


Device Matching and Current Scaling

 

- Every Poly Leg of a multi-fingered device becomes a separate SPICE model to account for placement inside the diffusion
- Current scaling errors of up to 60mV & 25% are possible due to STI

Ion Implantation : High Energy Well Implants Miss-Match due to Well Proximity


N-Well Implantation

 

Ion Implantation: High Energy Well Implants Miss-Match due to Well Proximity

N-Well Implantation

 
Well Proximity is observable
up to 1 μm from the well edge




Silicon

Well Proximity

 - 100 mV Threshold shift based on placement in a well
- Occurs for both N-Well and P-Well implants




Contact Stress

 


- If STI stress can change mobility – lets feature it
 - Add stress layers to increase device performance
 - Different stress for N & P Channel
- But contacts cut the stress layer & reduce the improvement
 - Device “On Current” becomes a function of contact density

65nm : Poly OPC/PSM Masks

 


Threshold Voltage vs. Time

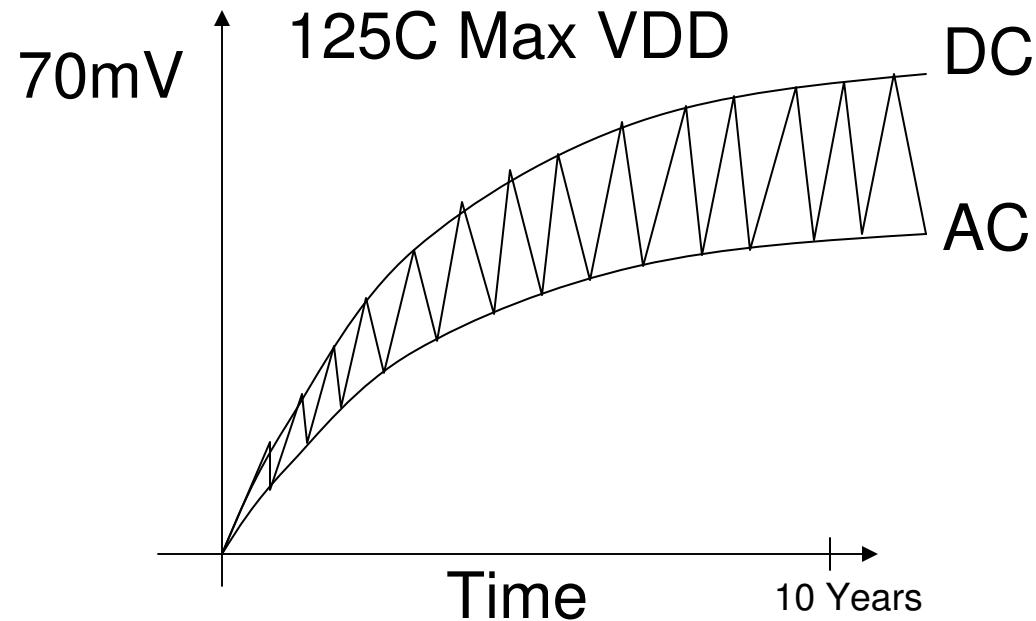

- NBTI has dramatic impact when matched PMOS devices do not have the same gate bias
 - This shows up more in power-down modes than in normal operation
- NBTI can be simulated using Verilog-A if you are clever
- Commercially available simulation capability will be released soon


NBTI Impact on Current Mirror (1)

- Simple mirror
- Used where high output resistance not needed
- As M1 and M2 undergo identical gate stress voltage, ΔV_t will vary identically for both of them. The output current follows the bias current for the range considered
- The variation in gate-to-source voltage for transistors M1 and M2 causes a further increase in stress voltages, which therefore must be taken into account for lifetime prediction

 


NBTI Impact on Current Mirror (2)

 - Cascode current mirror
- Higher output impedance




NBTI Impact on Current Mirror (3)

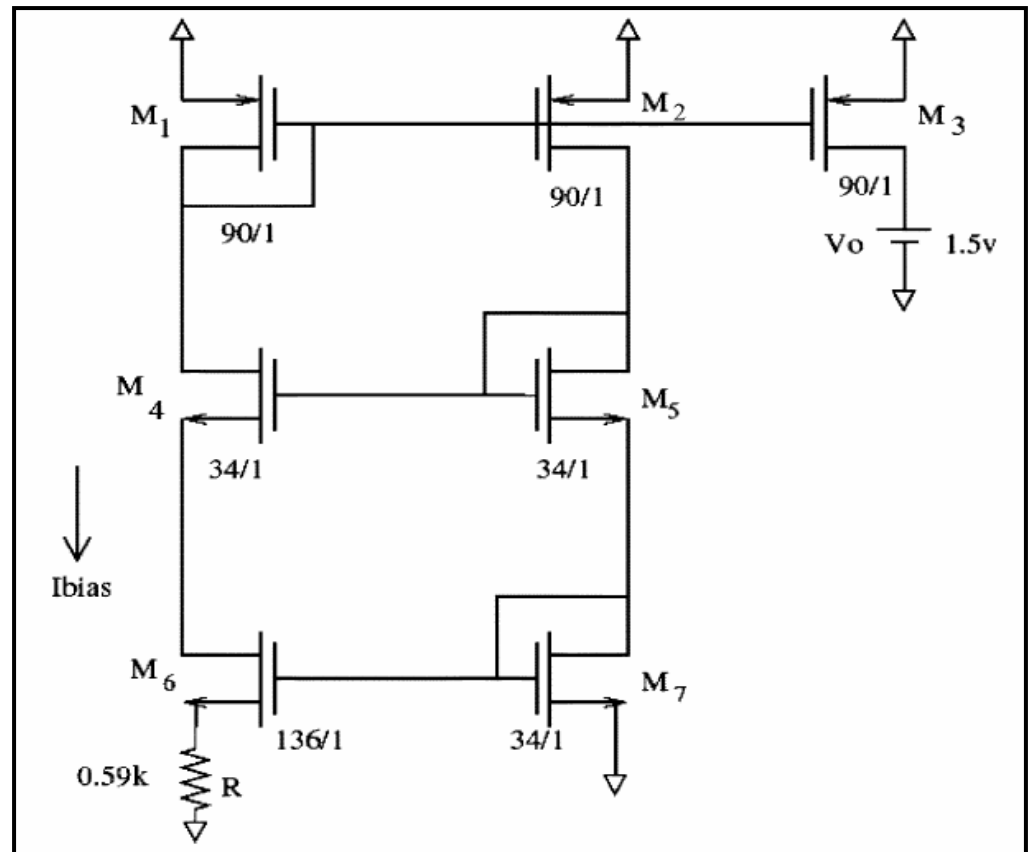- Constant biasing (g_m) circuit
- Applications where stable transconductances are required
- Positive feedback is always maintained to match all the g_m 's to the conductance of R
- Because of this reason, as long as R is constant, the bias currents are maintained at a constant value irrespective of PVT variations



Drift Current For Equal NBTI Induced ΔV_{th} Degradation

- Cascode current mirror shows the maximum drift (12.5%) in the output current for the same amount of NBTI-induced degradation
- Constant biasing mirror shows the least degradation (1%)
- The highest degradation in the cascode current mirror because there are two diode connected transistors in series and hence the change in voltage across the biasing resistor is a result of change in the V_{th} 's of M1, M3
- The least degradation observed in the constant gm biasing circuits a result of the positive feedback, which accounts for NBTI variation

 

"NBTI Degradation and Its Impact for Analog Circuit Reliability", Jha et al IEEE TRANSACTIONS ON ELECTRON DEVICES, VOL. 52, NO. 12, DECEMBER 2005

Current Mirror Summary

- Therefore it is clear that for the same amount of variation due to NBTI, different current mirror configurations behave differently and hence must be chosen depending on the application

Outline


- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- **Analog design trends @ 65 nm**
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

Trends: Fab/Design/EDA Cooperation

Circuit designers view

- Power dissipation constraints
- Analog design challenges
- Device variability/model accuracy
- Design methodology/tools
- Reliability

Process technologist's view

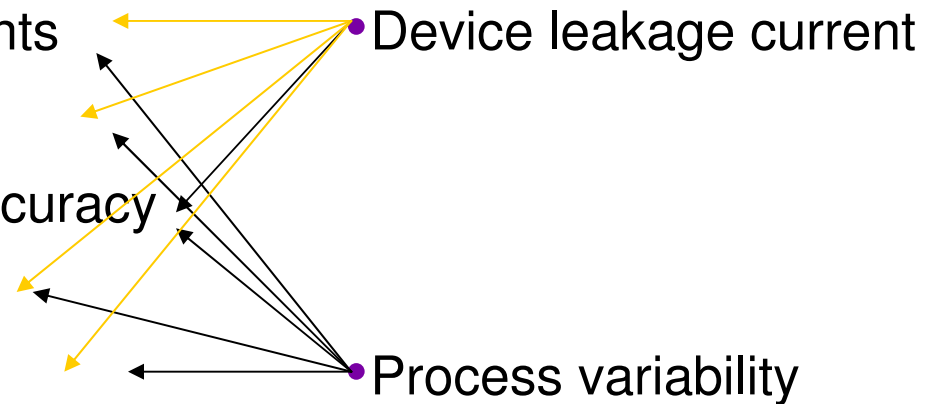

At ≤ 65 nm fab engineers need to work together with designers and EDA vendor to address power dissipation and process variability concerns

Analog design trends @ 65 nm



- SPICE model complexity
- Layout re-use
- Dual oxide partitioning
- On-chip voltage regulators
- On-chip RF components
 - Inductors **Cost**
 - Special Processing

Compact Device Models

- BSIM continues to be used
- Modern models formulated as a function of surface potential, rather than threshold voltage, in the channel and s/d edges
- Compact models at 65 nm require:
 - Scalability of sub-threshold currents and output resistance from short to long channels due to lateral doping non-uniformities
 - Dependence

Analog/Mixed Signal Design Methodology

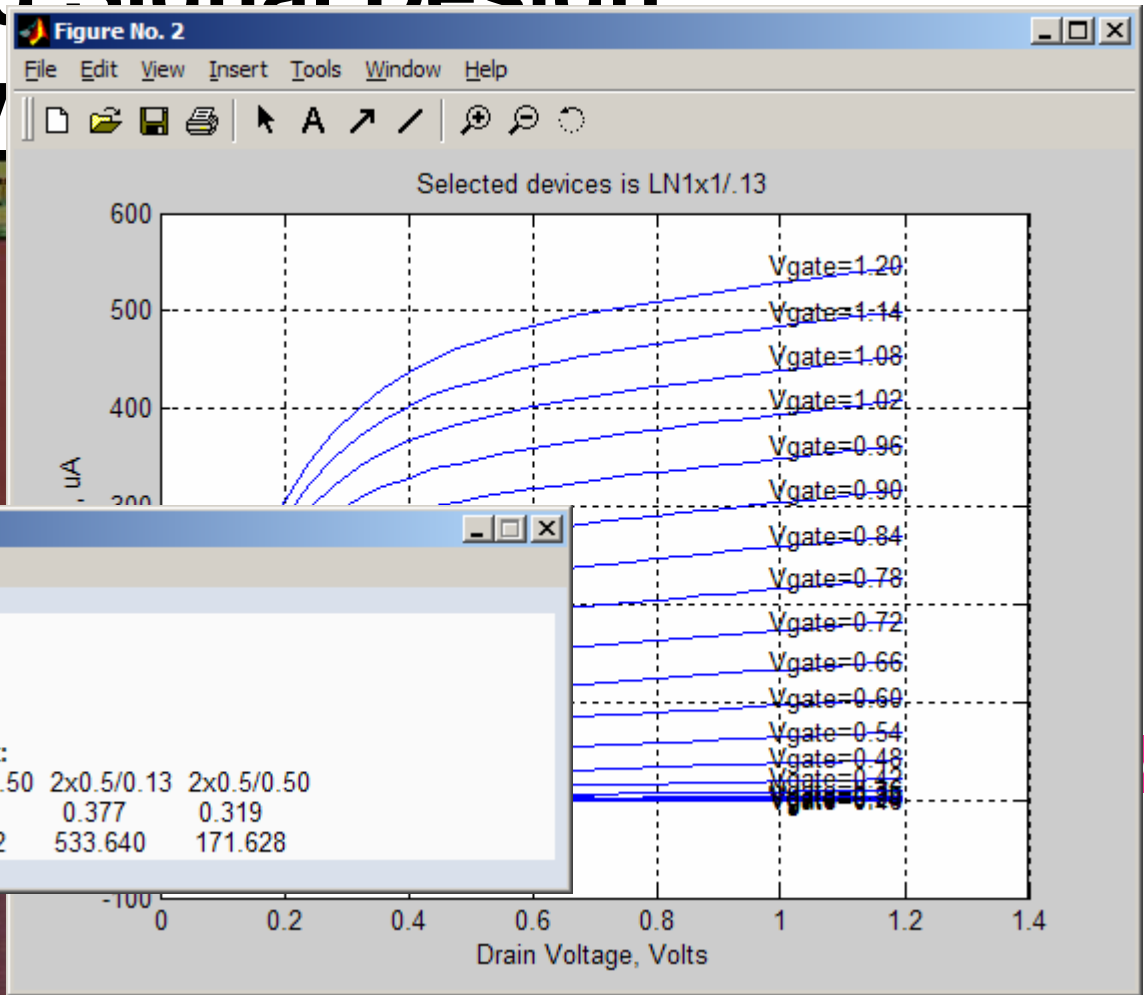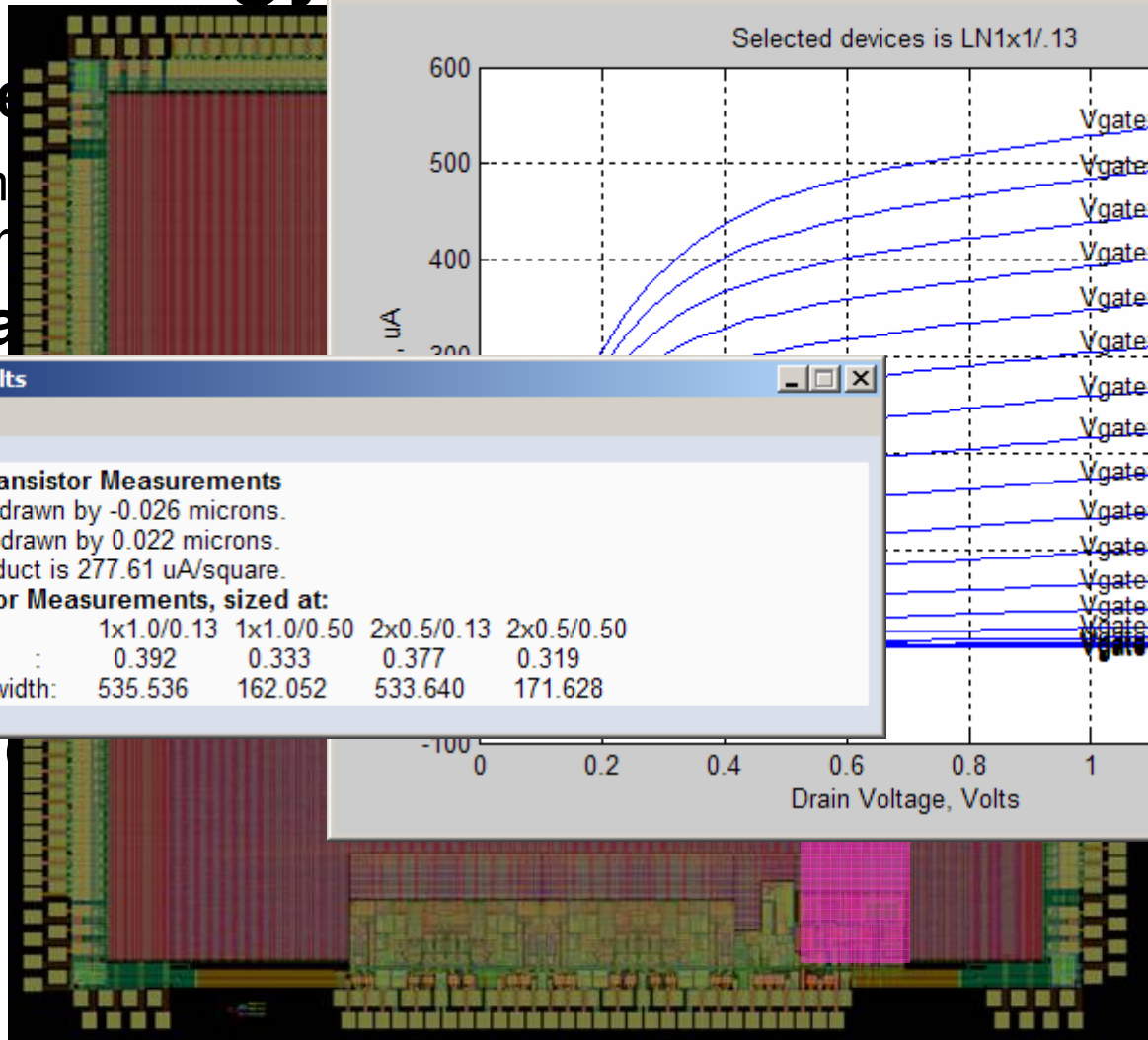- Architecture
 - Simulation
 - Simulation
- Simulation



Measurement Results

Nch Thinox (1V) Transistor Measurements

Leff is longer than drawn by -0.026 microns.
Weff is wider than drawn by 0.022 microns.
Mobility * Cox product is 277.61 uA/square.


Individual Transistor Measurements, sized at:

	1x1.0/0.13	1x1.0/0.50	2x0.5/0.13	2x0.5/0.50
Vthreshold, Volts	0.392	0.333	0.377	0.319
I _{dsat} , uA/micron_width	535.536	162.052	533.640	171.628


core

Analog Test-Bus

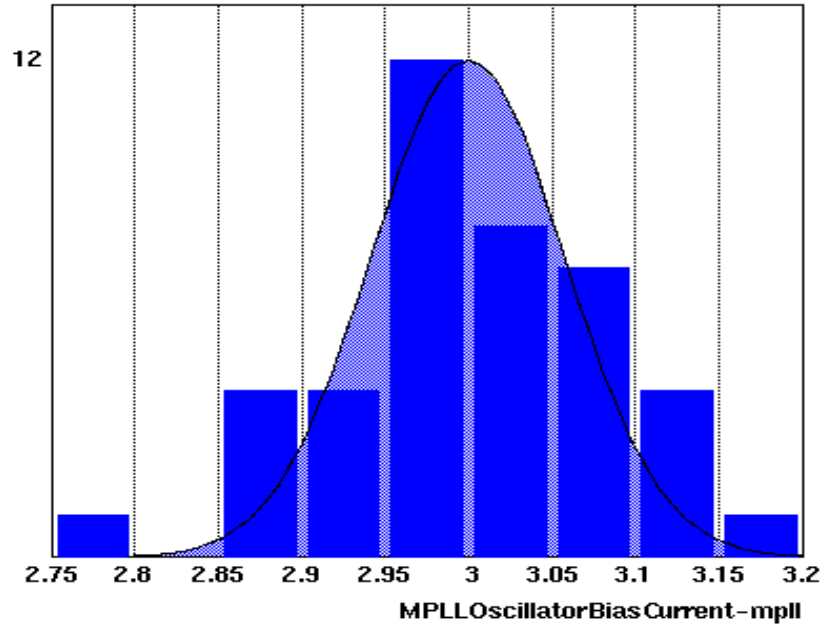
- Visibility into critical analog circuits - methodology allows analog voltages and currents to be measured



MPLLOscillatorBiasCurrent-mpil

 



1.2V_1cc_sleep_mA-icc

 

Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- **Low jitter PCI Express[®] PHY**
- Yield by design – USB 2.0 PHY
- Summary

Example: Low Jitter PCI Express[®] PHY

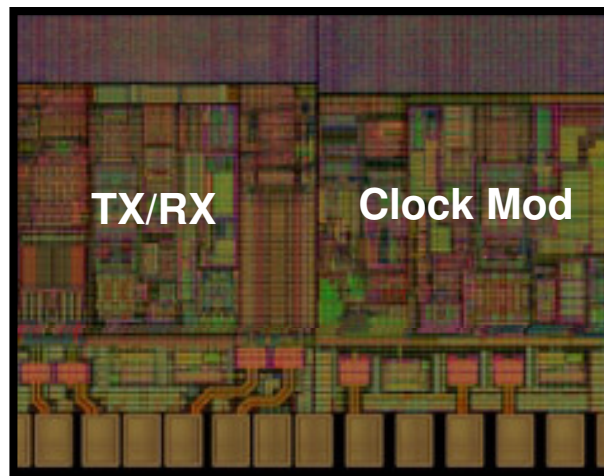 


Dedicated x1 configuration

High Performance PHY @ 65 nm...

- PSRR, Jitter
- Robustness
- Power
- Testability
- PVT invariance

→ **Need *digital* CDR**

Example PCIe PHY: Digital CDR

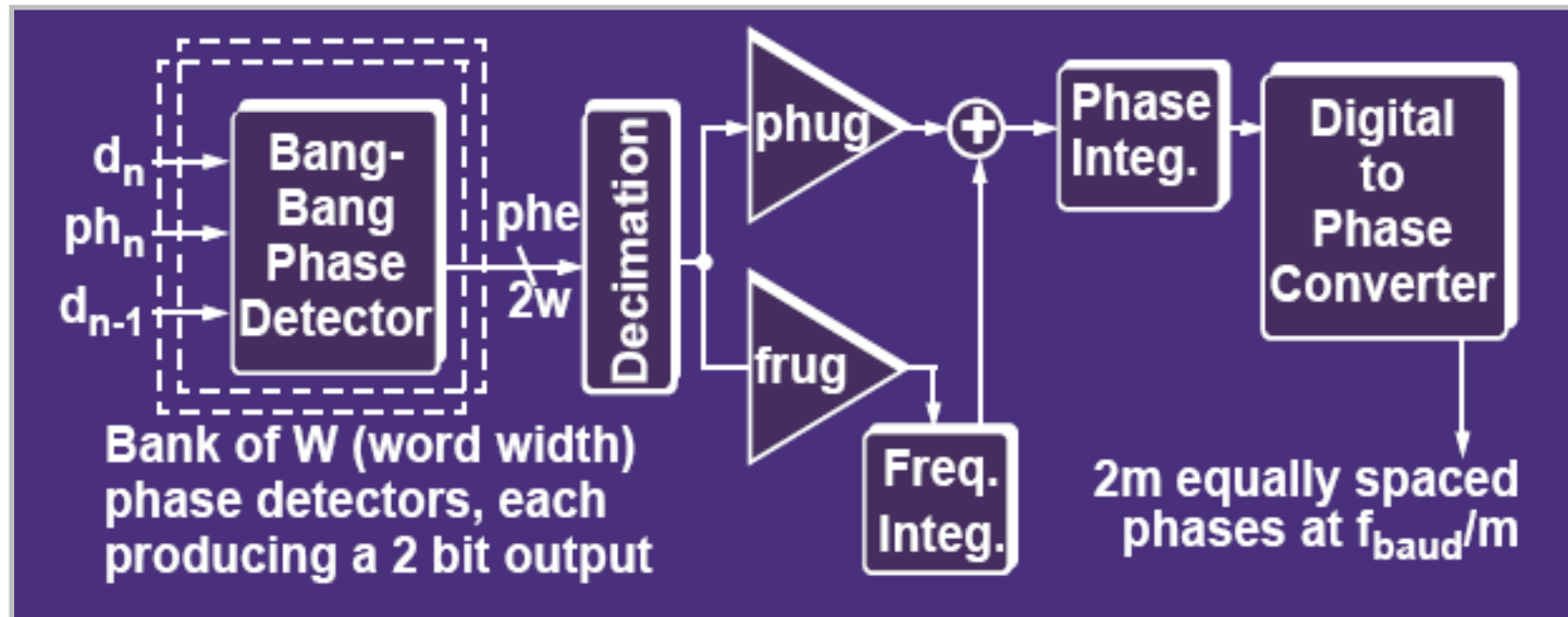

*“A Digital Clock and Data Recovery Architecture for Multi-Gigabit/s Binary Links”,
Jeff Sonntag and John Stonick Synopsys, Inc. CICC 2005*

Advantages Of Digital CDR

- PSRR, Jitter
 - Digital components
 - No PSRR
 - Jitter controlled by design resolution
 - Only analog component is DPC
 - May include high b/w PLL, always tracking reference clock
 - Tracking reference clock allows use of linear PFD and about 10 times the b/w of the CDR
 - High b/w effective at correcting power supply injected errors and thermally generated jitter

Advantages Of Digital CDR, cont.

- Robustness
 - False lock impossible
 - Tolerance of low transition densities
 - CDR is not integrating any noise when there are zero transitions as opposed to an analog CDR when you are always integrating → it is a perfect zero input!
- PVT invariance
 - K_{DPC} is not a function of PVT
 - Analog CDR depends on
 - K_{VCO} , R, C
 - Charge pump
 - Current
 - Up/down mismatch
 - leakage


Advantages Of Digital CDR, cont.

- Power
 - In order to achieve similar thermal jitter performance, the analog CDR would require much more power
- Testability
 - Standard digital SCAN techniques
 - Phase programmability can be used for margining purposes in vector-only ATE

Precision Is Possible

- Example: On-chip, per RX, sampling scope
 - Eye diagrams available through JTAG port
 - Synchronous and asynchronous operation supported
 - Measure channel pulse response, S21 insertion loss
 - Directly measure cross-talk in connectors, layout

On-Chip Sampling Scope per Lane

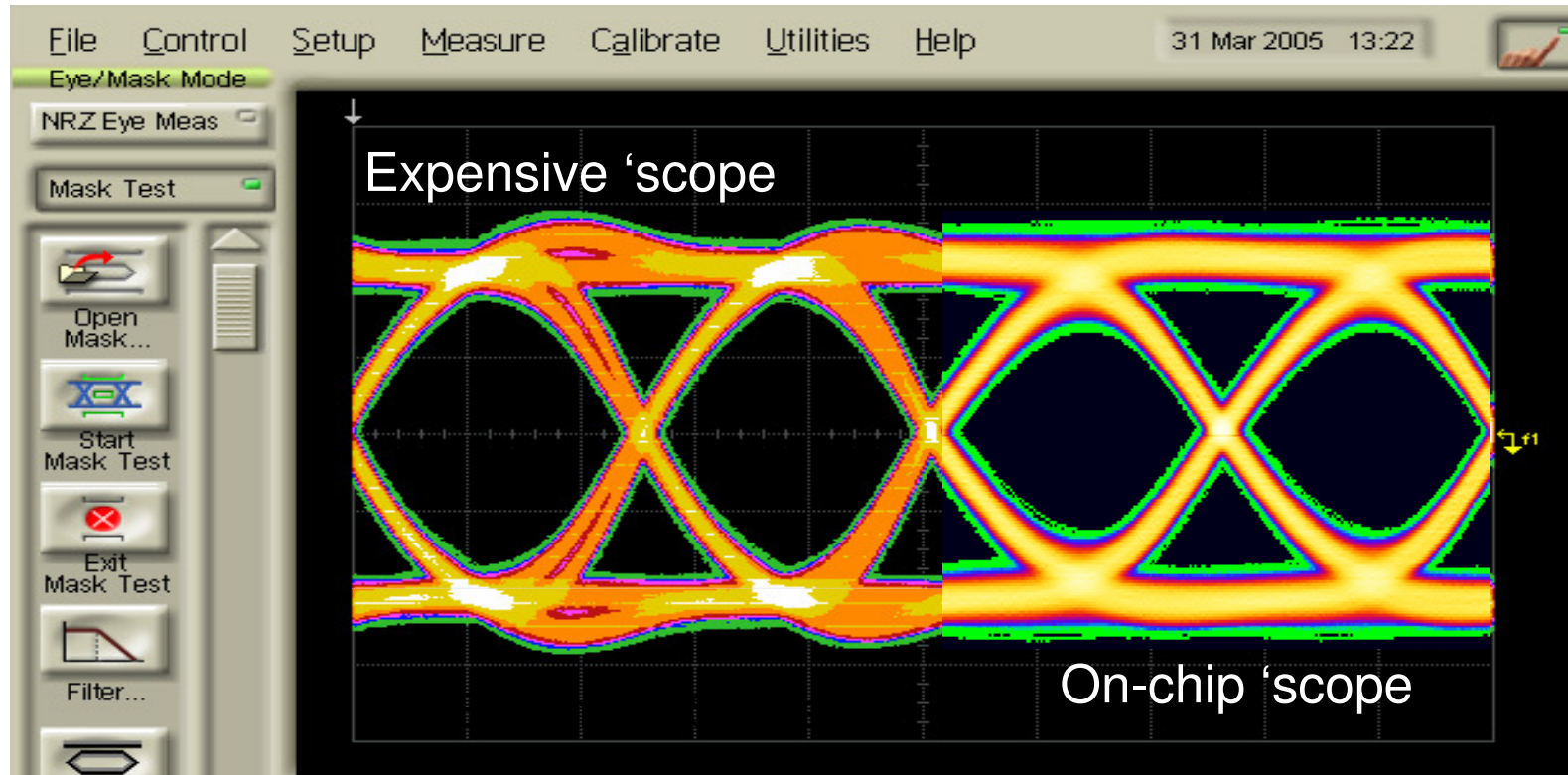

- Differences between external scope and internal diagnostics?
 - External Scope sees TX + Channel (16" FR4 + cables)
 - Internal scope sees TX + Channel + Bond Wires in the package
- Internal scope sees the high frequency filtering effects of the bond wires – and the actual RX eye!

413 bond wires on 4.5mm test chip

Bond wire layout for low cross-talk
Gnd-Signal-Signal-Gnd

Short wires for Gnd

Quad PCIe PHY


Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

USB 2.0 PHY “Yield By Design”

- Architecture optimizes parametric yields and minimize current consumption
- User controls many performance parameters to allow for various packages, systems and customization


USB 2.0 Compliance – Eye Diagram

 

Supply de-coupling removed

- Noisy power supplies can affect jitter
- Power supply filtering (decoupling) recommended


USB 2.0 Compliance – Eye Diagram

 

- Low HS DC levels
- Rise/fall shape not smooth
- High jitter
- Last bit transition violates eye

Excess board parasitics introduced

USB 2.0 Compliance – Eye Diagram

 

- ✓ HS DC levels
- ✓ Rise/fall shape
- ✓ Jitter
- ✓ Crossover voltage

Outline

- Analog versus digital design in sub-wave length technologies
- Design partitioning (Mixed-signal design)
- Mixed-signal design example: a duty cycle corrector
- Killer sources of variation in analog design
 - STI, WP, CS, OPC/PSM, NBTI, HCI
 - Current mirror example
- Analog design trends @ 65 nm
- Low jitter PCI Express[®] PHY
- Yield by design – USB 2.0 PHY
- Summary

Summary

- High performance analog/mixed-signal circuits are possible in standard deep sub-micron CMOS technologies
- A thorough understanding of the deep-submicron process effects must be made in order to produce working, robust production worthy analog/mixed-signal designs
- This requires close co-operation between the fab. process engineers, circuit designers and EDA vendor

SYNOPSYS[®]

Predictable Success