



Enabling Productivity



RTL Coding Guidelines

DEC, 1999



Professional Service Group
Synopsys, Inc. Asia Pacific Operations

**Disclosure of information shared to other than
those authorized, is strictly prohibited.**



Introductions

Enabling Productivity

- ❑ **A common set of problems facing everyone who is designing design-reuse ASICs:**
 - ☞ Time-to-market pressures demand rapid development
 - ☞ Quality of results, in performance and area, are keys to market success
 - ☞ Increasing chip complexity makes verification more difficult
 - ☞ The development team has different levels and areas of expertise
 - ☞ Design team members may have worked on similar designs in the past, but cannot reuse these designs because the design flow, tools, and guidelines have changed
- ❑ **The “Design Reuse Coding Style” offers design team members a collection of coding rules and guidelines.**
- ❑ **A high quality HDL code is a prerequisite for a high quality product.**



Agenda

Enabling Productivity

Presentation:

HDL Coding Style Guidelines

- General HDL Code Structure**
- Partitioning**
- Implying Logic Structure**
- Safe Coding & Avoiding Problems**
- Source Code Readability**
- Coding Style for Design Reuse**
- Design for Testability**
- Practices**



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL Coding Style Guidelines

- **General HDL Code Structure**
- **Partitioning**
- **Implying Logic Structure**
- **Safe Coding & Avoiding Problems**
- **Source Code Readability**
- **Coding Style for Design Reuse**
- **Design for Testability**
- **Practices**



General HDL Code Structure: Checklist Items

Enabling Productivity

- Standard File Headers (101)**
- File Naming Conventions (102)**
- Architecture Naming Conventions (103)**
- Signal Naming Conventions (104)**
- Use of Labels (105)**
- Linking in Verilog (106)**
- Clear & Meaningful Comments (107)**



Standard File Headers(101)

Enabling Productivity

- ❑ Make sure the code look familiar, no matter who writes the module.
- ❑ Make sure every file has a file header containing information on
 - file name or module function, author, creation date, abstract or summary, modification history
 - copyright, licensing agreement (if need)

```
////////////////////////////////////  
// FILE:  design.v  
// AUTHOR:  Brooke Tioga  
// $Id$ ←  
// ABSTRACT:  Description of the design object  
// KEYWORDS:  dsp, telecom, graphics  
// MODIFICATION HISTORY:  
// $Log$ ←  
//   Brooke          11/9/97  original  
//     Susie          3/3/98          revised as follows...  
//  
// (C) Copyright 1997 Synopsys Inc.  All rights reserved  
////////////////////////////////////
```

Used by RCS!



Headers for Major Constructs (101)

Enabling Productivity

```
////////////////////////////////////  
// FUNCTION:  double_trouble  
// AUTHOR:   Ornithal Shapiro  
// $Id$  
// ABSTRACT: to double throughput of filter  
// MODIFICATION HISTORY:  
// $Log$  
//      Ornithal      12/9/97      original  
//      Brooke        4/4/98      revised as follows...  
//      This function performs the interpolation of data ...  
////////////////////////////////////
```

- Use for each function and task**
- Use for each major section of code**




File Naming Conventions (102)

Enabling Productivity

- ❑ A consistent approach to naming files greatly improves communication among designers.
- ❑ Create individual files for each module:

Convention	Object	Example
design.v	Module	arbiter.v
tb_design.v	Verilog Testbench	tb_arbiter.v

 - ❑ Use module/function name as part of file name.





Architecture Naming Conventions (103)

Enabling Productivity

- ❑ **While the term “architecture” is a VHDL construct, it is used to categorize VHDL modules based on their level of abstraction.**
- ❑ **Keep the same file names for all architectures, and manage the design data with different file directories for each architecture.**



Signal Naming Conventions (104)

Enabling Productivity

- ❑ **Verilog reserved words (module, endmodule, wire, reg, always, begin, end, if, else, case, endcase, ...)**
 - ☞ must use lower case (Verilog requirement)
- ❑ **Names (module names, function names, block names, wires, regs, integers, ...)**
 - ☞ use lower case
- ❑ **Names (macro ...)**
 - ☞ use upper case
- ❑ **Names (Clock Signal)**
 - ☞ use clk1, clk2, or clk_interface
 - ☞ Use the same name for all clock signals that are driven from the same source.
- ❑ **Names (Reset Signal)**
 - ☞ use rst for reset signal



Signal Naming Conventions (104)

Enabling Productivity

- ❑ **Names (active low signal)**
 - ☞ end the signal name with an underscore followed by a lowercase character
 - ☞ example_b, example_n
- ❑ **Names (multibit-buses)**
 - ☞ use a consistent ordering of bits
 - ☞ for VHDL (y downto x) or (x to y)
 - ☞ for Verilog [x:0] or [0:x]
- ❑ **Names (meaningful)**
 - ☞ don't use ra for a RAM address, instead, use ram_addr
- ❑ **Check with your vendor for their name restrictions**
 - ☞ (e.g. case, length)
- ❑ **Noun/verb paradigm**
 - ☞ spot_run not run_spot
 - ☞ processor_interrupt not interrupt_processor



Signal Naming Conventions (104)

Enabling Productivity

- ❑ **For net names, use the same name throughout the hierarchy**
- ❑ **Consider dc_shell commands when choosing names:**
 - `set_input_delay 7.0 find(pin, "xi_pci*")`



Signal Naming Conventions (104)

Enabling Productivity

- ❑ Use naming conventions to indicate type of signal:

- ☞ input, output, register output, etc.

- ❑ Examples:

<code>clk_*</code>	Clock signal
<code>rst</code>	Reset signal
<code>*_n</code>	Negative logic (active low)
<code>*_r</code>	Output of a register
<code>*_a</code>	Asynchronous signal
<code>*_#n</code>	Signal used in the “n” phase
<code>*_nxt</code>	Data before being registered
<code>*_z</code>	Three-state internal signal
<code>xi_*</code>	Primary chip input
<code>xo_*</code>	Primary chip output
<code>xz_*</code>	Primary chip three state
<code>xb_*</code>	Primary chip bidirectional



Use of Labels (105)

Enabling Productivity

- ❑ Labels improve readability & debugging
- ❑ If labels are not specified, arbitrary labels are generated internal to simulation/synthesis tools
- ❑ Labeled *always@* facilitate repartitioning with the *group* command.

```
always@(posedge CLK)
  begin: CHT2BIT
    if (RESET == 1'b1)
      QOUT <= 2'b00;
    else
      QOUT <= QOUT + 1'b1;
  end
```

Use Labels at *begin*

```
dc_shell_script:
group -hdl_block CHT2BIT
```



Use Labels on *always@*, & function constructs



Linking Modules(106): Avoid Modules linked with `include`

Enabling Productivity

- ❑ Avoid modules linked with 'include'
- ❑ Reasons:
 - ☞ Locating the file
 - ⇒ The included file has to reside in the same directory from which the tool(simulation or synthesis) is invoked, or a path to the file must be specified in the source code.
 - ☞ Compilation
 - ⇒ The included file may complicate the design partitioning and may result in greater effort when developing a bottoms-up compile strategy.

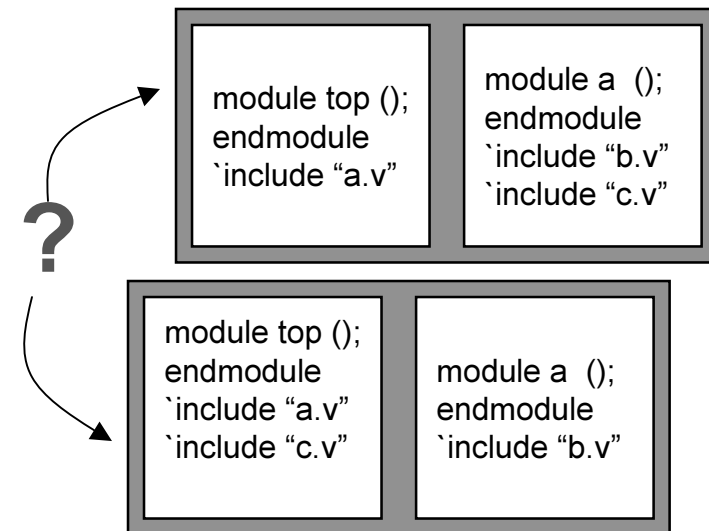 



Linking Modules (106): Avoid Multiple Modules in a Single File

Enabling Productivity

❑ Avoid multiple modules in single file.

❑ Reasons:

☞ Locating the file


⇒ Determining which files contain which modules cannot be inferred using the file name conventions.

☞ Compilation

⇒ Performing incremental compiles in DC due to small changes become more complex and timing consuming.

☞ Revision Control (RCS)

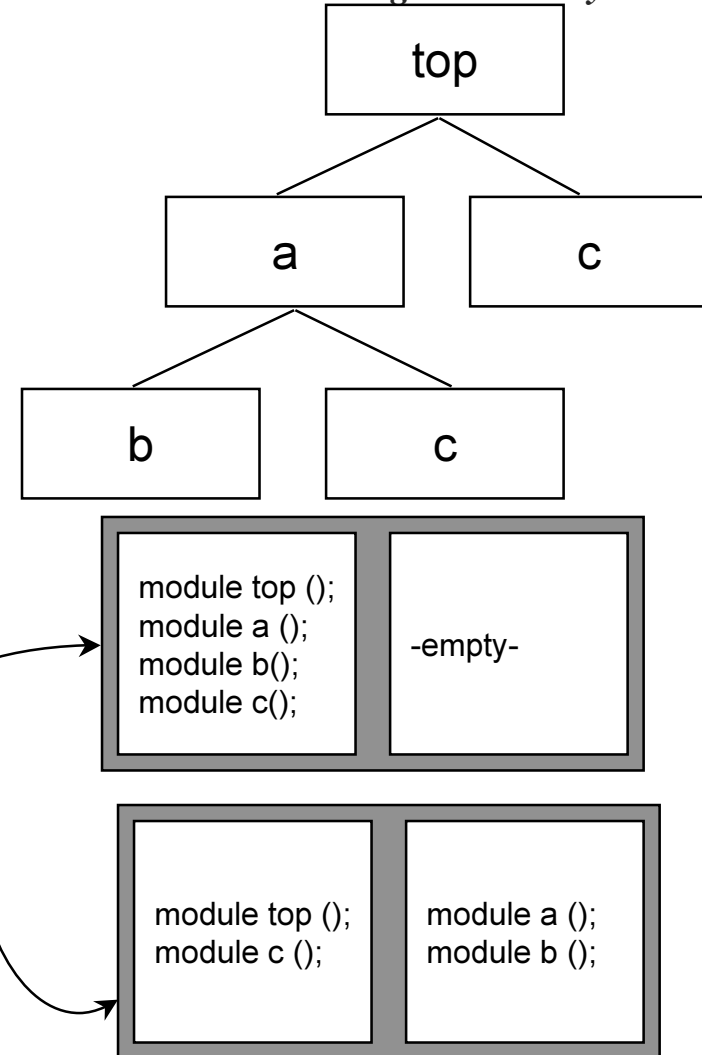⇒ Revision control and bug tracing become more complicated.





Linking Functions (106): Avoid Multiple Functions in a Single File


Enabling Productivity

❑ **Avoid: Multiple functions in single file**

❑ **Reasons:**

↳ **Revision Control (RCS)**

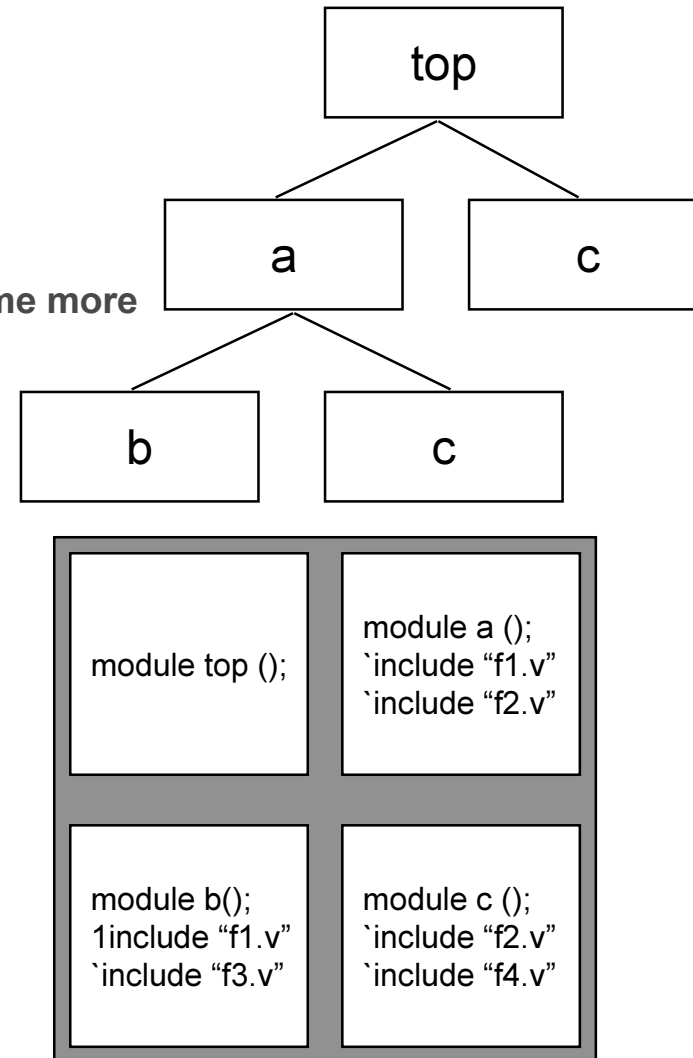⇒ Revision control and bug tracing become more complicated.





Clear Meaningful Comments (107)

Enabling Productivity

- ❑ **Improve readability, maintainability, ability to reuse, easy review, traceability**
- ❑ **Typical engineers response ...**

☞ *“I don’t have the time to comment now”*

☞ *When complete do you go back & comment or do you move on to the next assignment ?*



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure**
- Partitioning**
- Implying Logic Structure**
- Safe Coding & Avoiding Problems**
- Source Code Readability**
- Coding Style for Design Reuse**
- Design for Testability**
- Practices**



Partitioning Effects

Enabling Productivity

- ❑ **Partitioning is not just a functional issue. It can significantly affect the following process:**
 - **Synthesis Quality-of-Result (QOR)**
 - **Synthesis constraints**
 - **Synthesis scripts**
 - **Synthesis compile time**
 - **Static timing analysis**
 - **Floorplanning**
 - **Layout**



Partitioning Aims

Enabling Productivity

❑ **Physical Implementation Issues**

- ☞ **Keep related combinational logic together**
- ☞ **Combine shareable resource**
- ☞ **Merge user-defined resources and driven logic**
- ☞ **Partition based on design goals**

❑ **Partitioning to Speed Up the Compile Process**

- ☞ **Eliminate glue logic**
- ☞ **Maintain a reasonable gate size**
- ☞ **Maintain a reasonable number of levels**
- ☞ **Isolate point-to-point exceptions in the same module**



Partition Aims

Enabling Productivity

- ❑ **Partitioning to Simplify Scripts and Constraint Files**
 - ☞ Register all outputs
 - ☞ At chip-level create core logic, pad ring, and test hierarchy
- ❑ **Commands that Manipulate Hierarchy**
 - ☞ If artificial and suboptimal barriers exist in critical combinational logic path, you can rearrange the hierarchy to eliminate the suboptimal interface.
 - ⇒ DC command: group
 - ⇒ DC command: ungroup



Partitioning: Checklist Items

Enabling Productivity

- ❑ **Physical Implementation Issues**
 - ☞ **No snake paths in critical paths (201)**
 - ☞ **Combine sharable resources (202)**
 - ☞ **Merge User-Defined Resources with the logic they drive (203)**
 - ☞ **Separate logic with different synthesis goals**
 - ⇒ **area vs. speed sensitive (204)**
 - ⇒ **random vs. structured (205)**
 - ☞ **Separate Clock Generation Module (206)**
 - ☞ **Separate Asynchronous Logic (207)**
 - ☞ **Separate Finite State Machines (208)**



Partitioning: Checklist Items

Enabling Productivity


- ❑ **Partitioning to Speed Up the Compile Process**
 - ☞ **Eliminate glue logic (209)**
 - ☞ **Reasonable design size (210)**
 - ☞ **Reasonable hierarchy (211)**
 - ☞ **Isolate Point-to-Point Exceptions (212)**
- ❑ **Partitioning to Simplify Scripts and Constraints Files**
 - ☞ **Register the outputs (213)**
 - ☞ **Chip-Level Partitioning (214)**
- ❑ **Commands that Manipulate Hierarchy**
 - ☞ **Ungroup**
 - ☞ **Group**




Avoid Snake Paths (in critical path) (201)

Enabling Productivity

 - ❑ Design Compiler cannot move logic across hierarchical boundaries.
- ❑ Dividing related combinational logic into separate modules introduces artificial barriers restrict logic optimization



Poor Partitioning of Related Logic

 


Keep Related Logic in the Same Module



Avoid Snake Paths (in critical path) (201)

Enabling Productivity

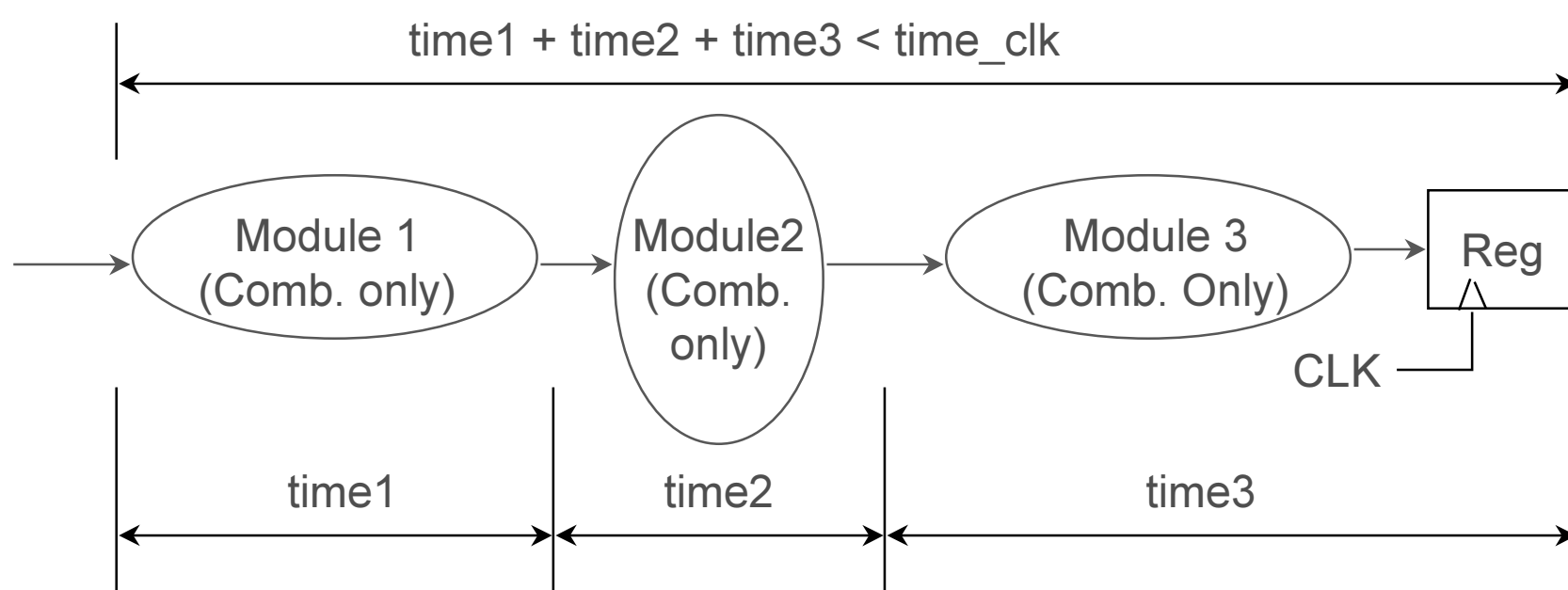- ❑ Snake Path - combinational logic path distributed over multiple modules
- ❑ DC does not allow cross boundary optimization & requires time budgeting






Combine Sharable Resources (202)

Enabling Productivity

- ❑ Resources (e.g. adders) can be shared if they are never used *at the same time*.
- ❑ For HDL Compiler to determine this, the resources **MUST** be in the same module and always@ block


BAD

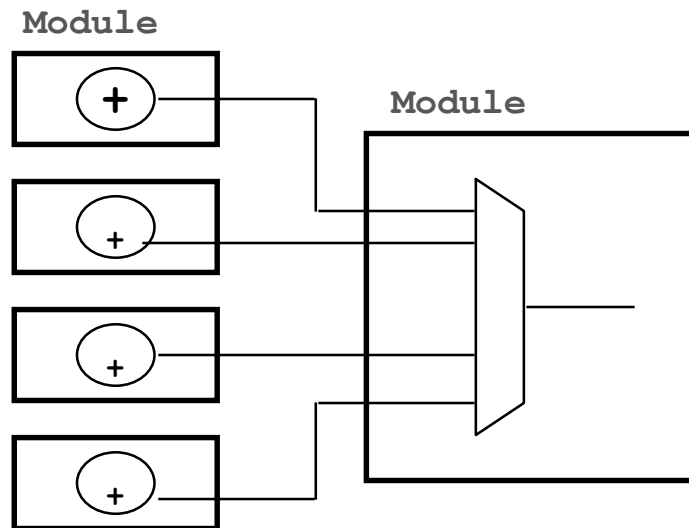

(Cannot Share
Across Modules)

GOOD
 
```
case (sel)
  2'b00 :Y = a + b;
  2'b01 :Y = c + d;
  2'b10 :Y = e + f;
  2'b11 :Y = g + h;
  default:Y = 8'bx;
endcase
```



SYNOPTIS[®]


Professional Service Group



Merge User-Defined Resources with the Logic They Drive(203)

Enabling Productivity

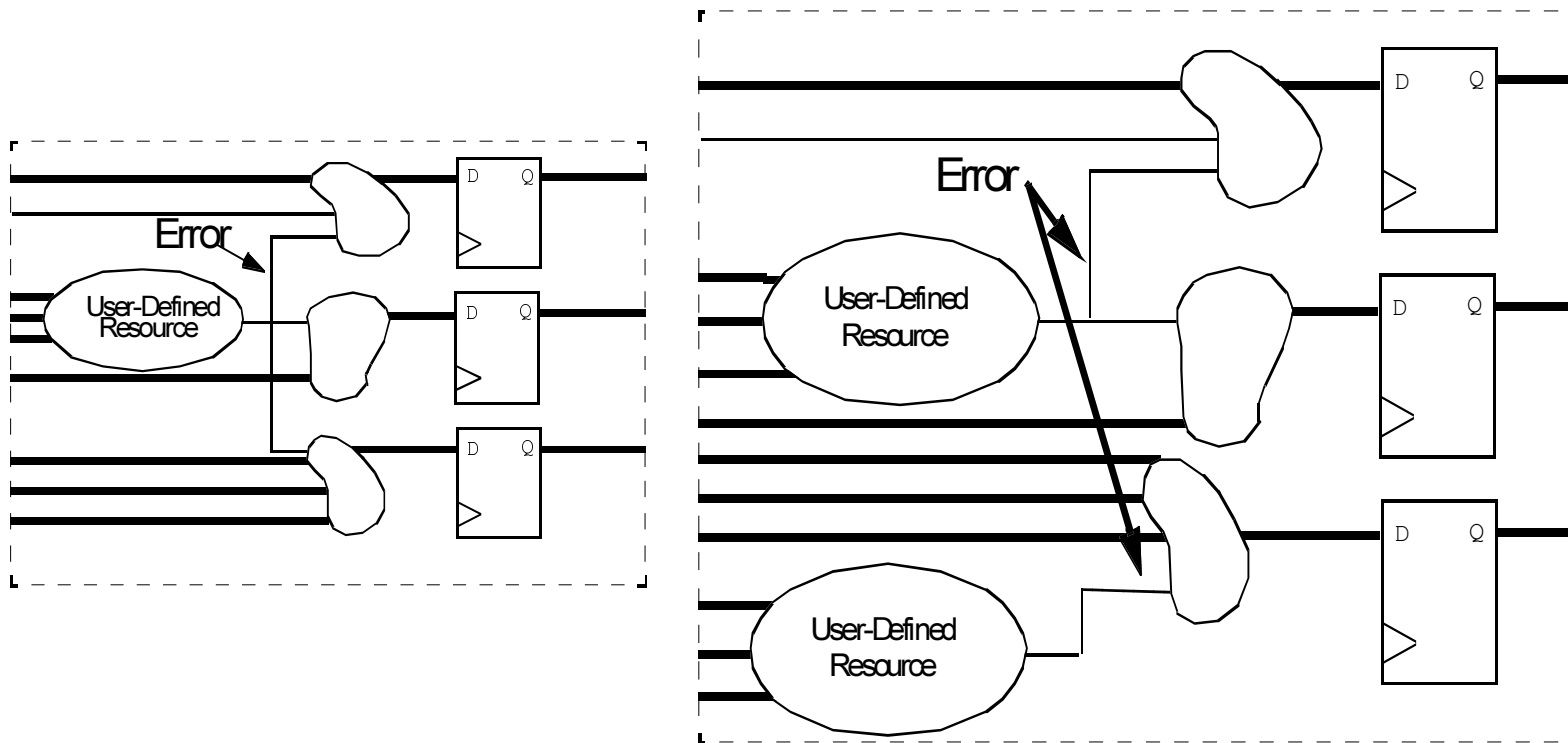- ❑ A user defined resource is any logic that drives a large fanout .
 - (e.g. mux-select for 100 muxes)
- ❑ You may want to replicate user defined resources to balance the load.
 - (e.g. 10 mux-selects to drive 10 muxes)






Merge User-Defined Resources with the Logic They Drive(203)

Enabling Productivity

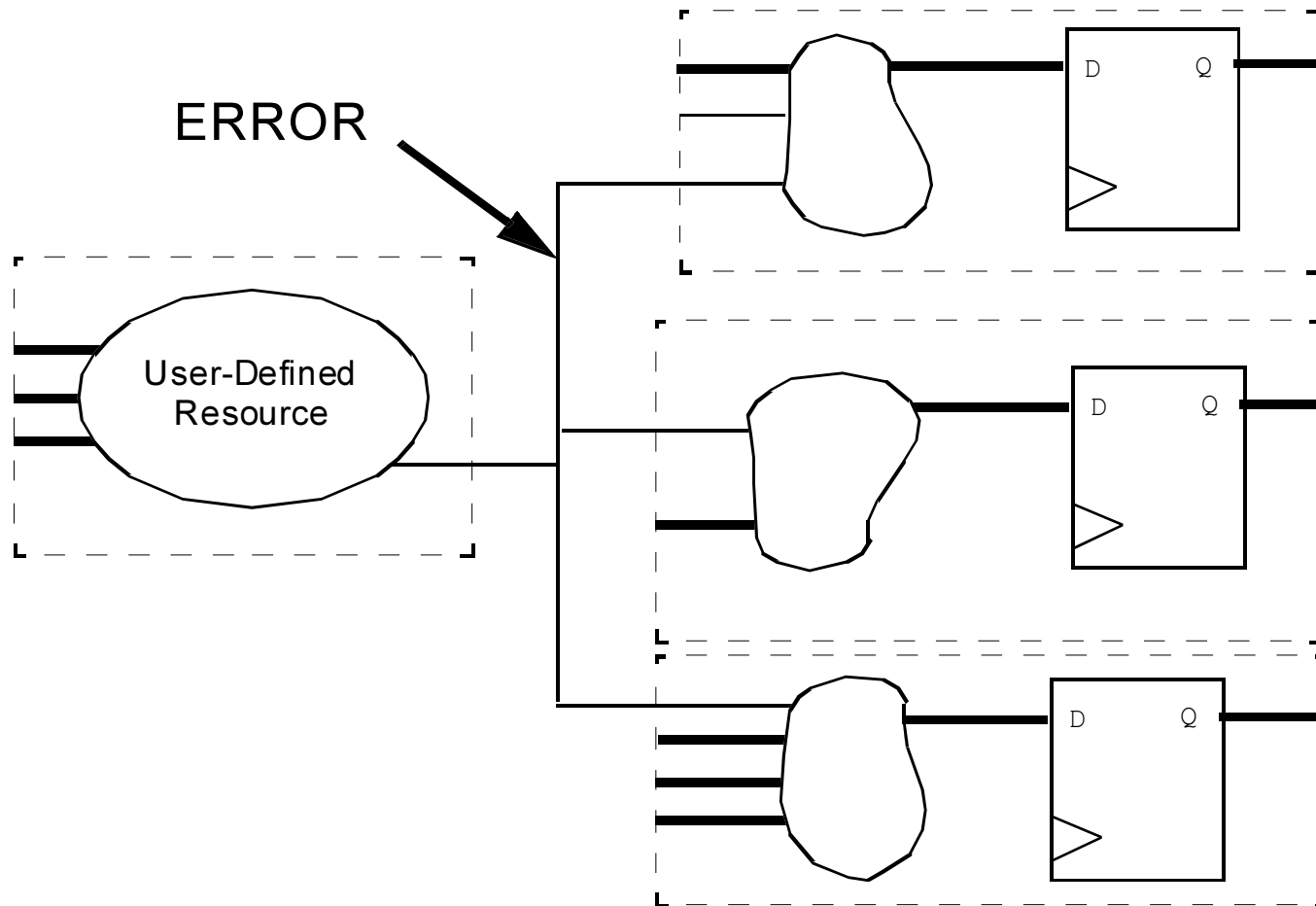- ❑ A poor partitioning might bring more synthesis and timing analysis problems.



SYNOPSYS[®]

Professional Service Group




Separate Area & Speed Logic (204)

Enabling Productivity

- ❑ Area and Speed Critical Logic are best optimized with different compile strategies
- ❑ Separate the logic so you can apply these strategies individually


BAD

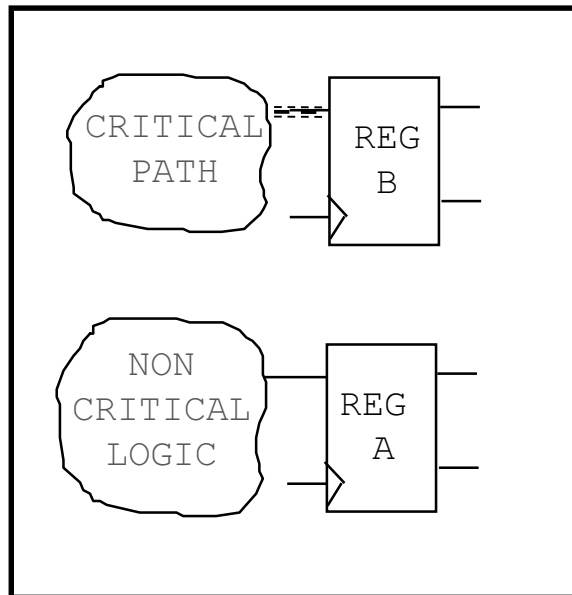

set_structure ???


GOOD

Speed Optimized

 

Might need to be flattened to make timing

Area Optimized

 

Should not be flattened




Separate Random & Structured Logic (205)

Enabling Productivity

- ❑ Random and Structured Logic are best optimized with different compile strategies.
- ❑ Separate logic so you can apply these strategies individually.


BAD

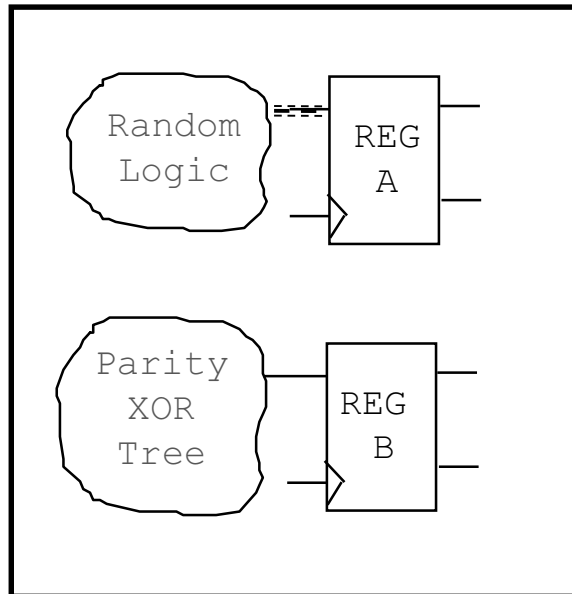

set_structure ???


GOOD

Contains random logic →

 

Might need to be flattened to make timing

Highly Structured →

 

Should not be flattened

SYNOPSYS[®]


Professional Service Group



Separate Clock Generation Module (206)

Enabling Productivity

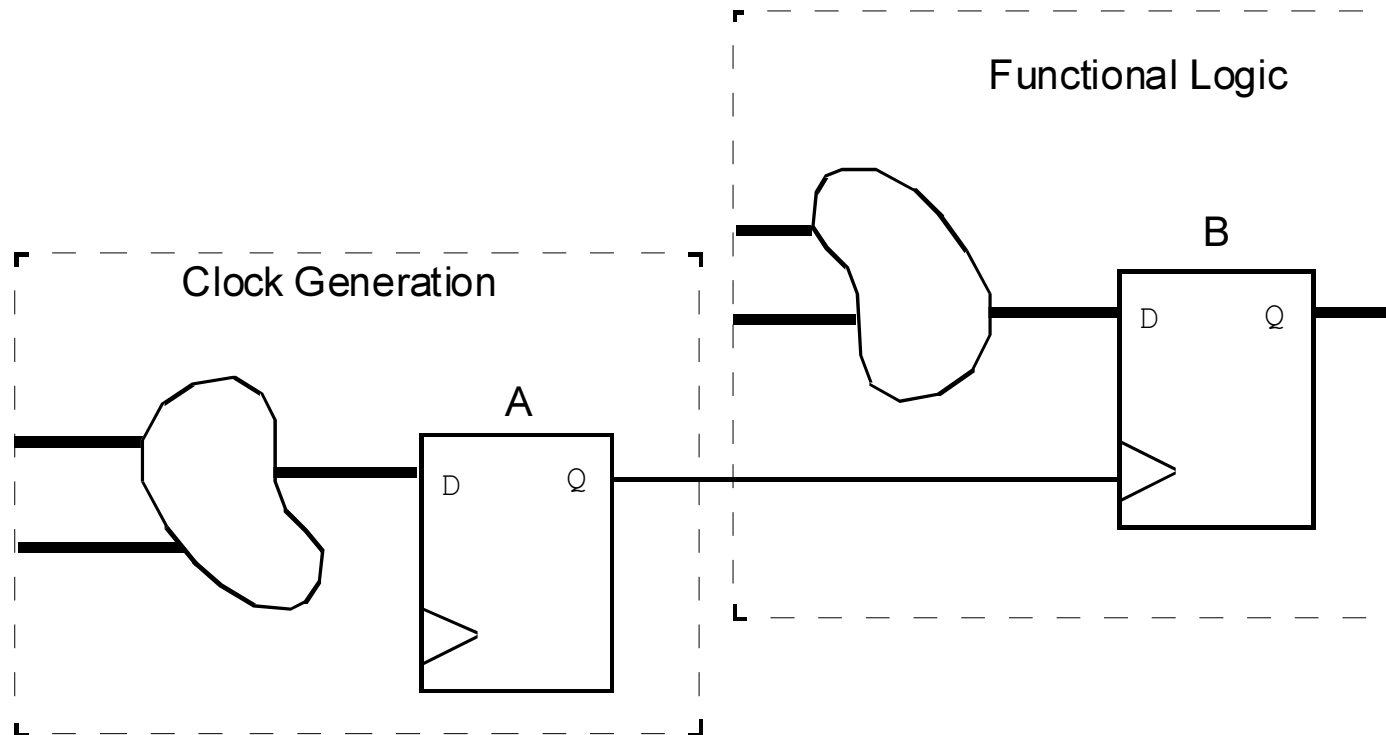- ❑ Clock generation logic is typically handcrafted and often requires special timing analysis.
- ❑ It is often recommended that clock generation logic be put into its own module.






Separate Asynchronous Logic (207)

Enabling Productivity

 - ❑ Asynchronous logic is sometimes technology-dependent, and typically requires gate-level instantiation and a special synthesis methodology.
- ❑ Asynchronous logic typically requires special test considerations and verification strategies.






Separate Finite State Machines (208)

Enabling Productivity

 - ❑ A state machine may benefit from the state machine compiler or from a flattening optimization strategy.
- ❑ Modules that contain only state machines simplify the state extraction and optimization process.






Eliminate Glue Logic (209)

Enabling Productivity

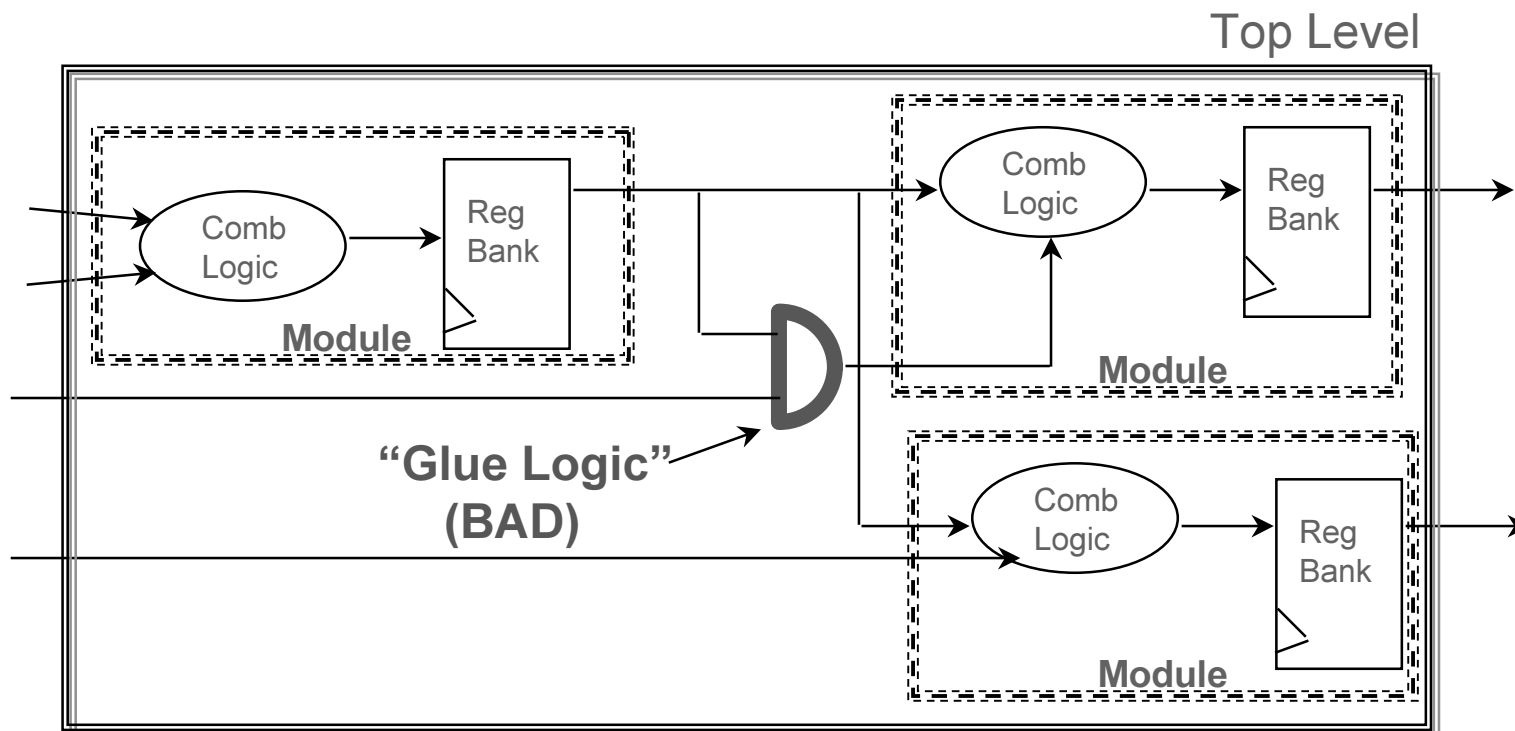- ❑ Design should only contain gates at the leaf level of the hierarchy tree
 - Reduces CPU time to compile small amounts of logic for glue.
 - Synthesis compile scripts are simplified when glue logic is removed.



SYNOPTYS®

Professional Service Group



Reasonable Design Size (210)

Enabling Productivity

- ❑ **Symptom: Too many lines of code in block**

- ❑ **Pitfalls:**
 - ☞ analyze / elaborate steps are slow
 - ☞ code is difficult to read / inspect

- ❑ **Recommendation:**
 - ☞ blocks should contain only clock
 - ☞ blocks should have few timing exceptions
 - ☞ add a new level of hierarchy



Reasonable Hierarchy (211)

Enabling Productivity

- ❑ **Use a reasonable number of levels in the hierarchy**

- ❑ **Pitfalls:**
 - ☞ reduced readability
 - ☞ longer compile times
 - ☞ more error prone (more places for error)


- ❑ **Recommend:**
 - ☞ Use 2-3 levels per major function block or algorithm,
 - ☞ Use no more than 8 levels per design.
 - ☞ A new level is introduced via DesignWare
(can be eliminated by ungroup)



Isolate Point-to-Point Exceptions (212)

Enabling Productivity

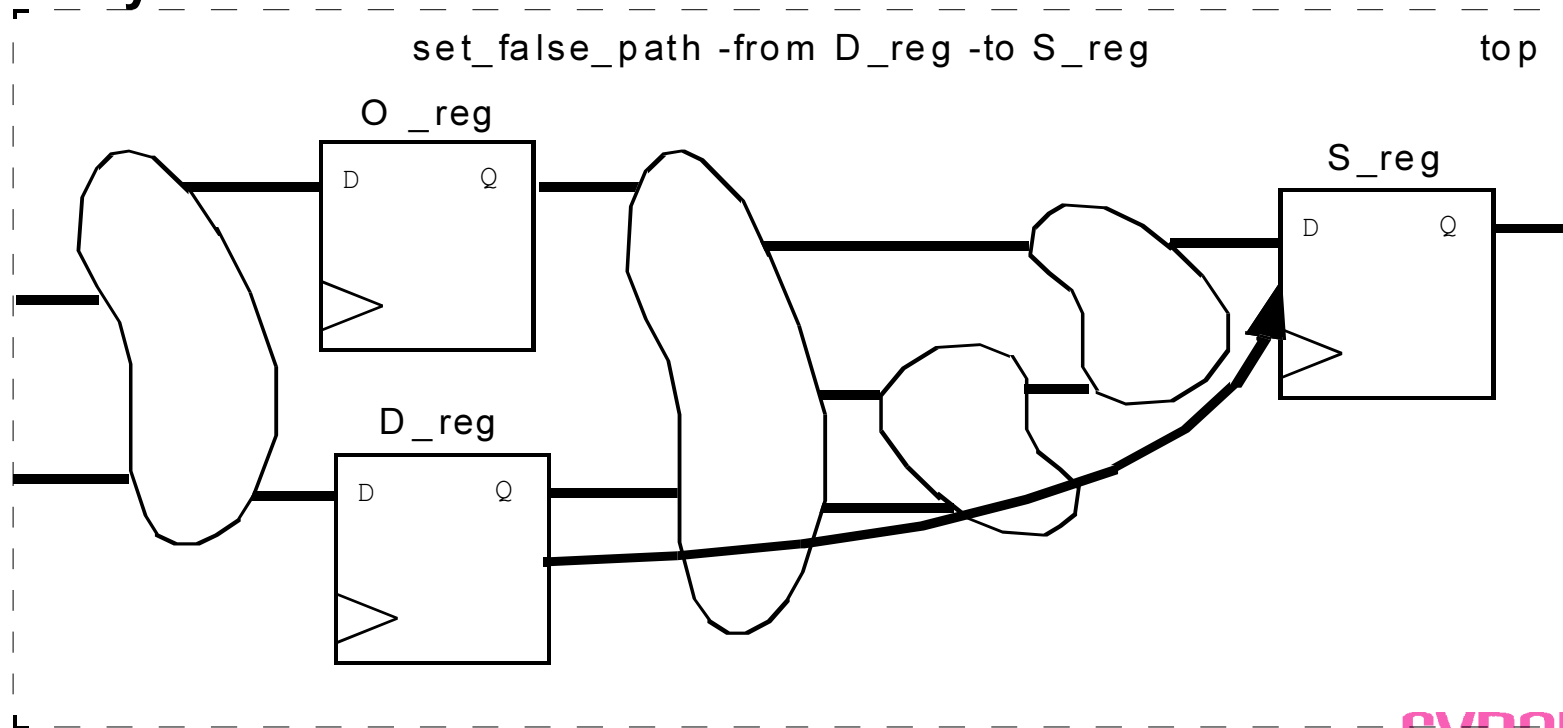- ❑ If a design contains point-to-point exceptions (false path/multiple cycles), keep those exceptions within a module.
- ❑ By containing the point-to-point exception within one module, execution-time in static timing analysis or synthesis is minimized.



SYNOPSYS[®]


Professional Service Group



Register the Outputs (213)

Enabling Productivity

 - ❑ To simplify the constraints and scripts process, register all outputs of a block.



```
set_drive drive_of <my_flop/Q> all_inputs  
set_input_delay 2 -clock CLK <input_port>
```


- ❑ The drive strength of the inputs is predictable.
- ❑ The input delays from the previous block are predictable.
- ❑ It speeds up simulation, since the process activate only once per clock cycle.



Chip-Level Partitioning (214)

Enabling Productivity

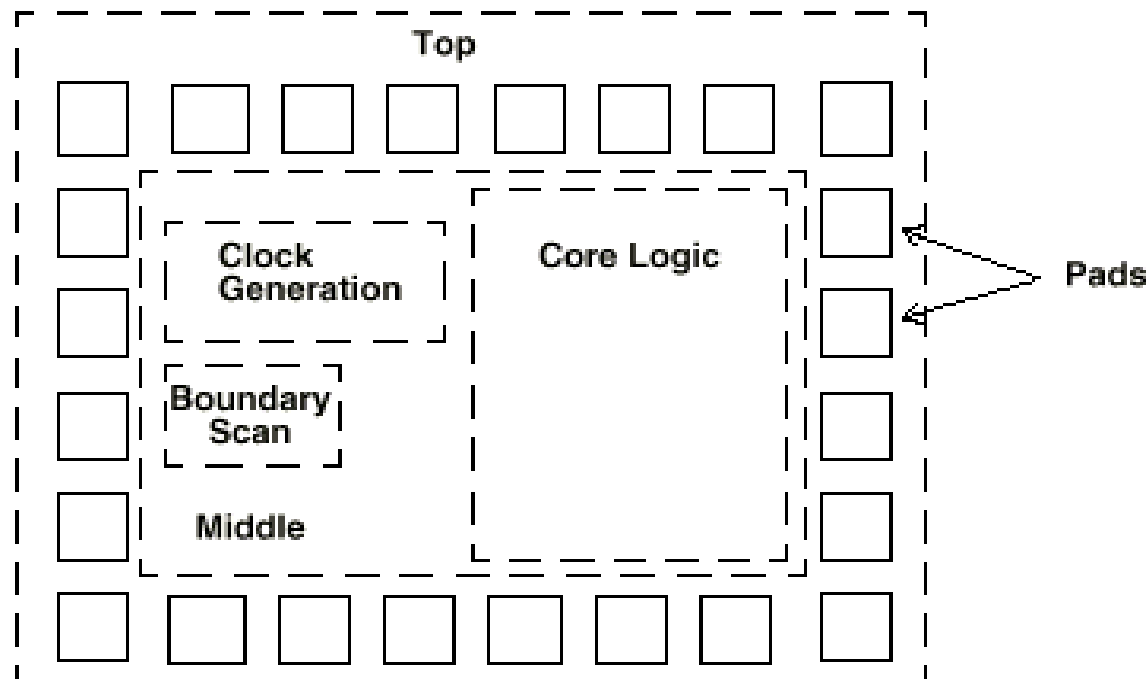- ❑ The partitioning recommendation for the top of an ASIC




- ❑ The clock generation circuitry is isolated from the rest of the design, since typically it is handcrafted and carefully simulated.



Ungrouping a Design Hierarchy

Enabling Productivity

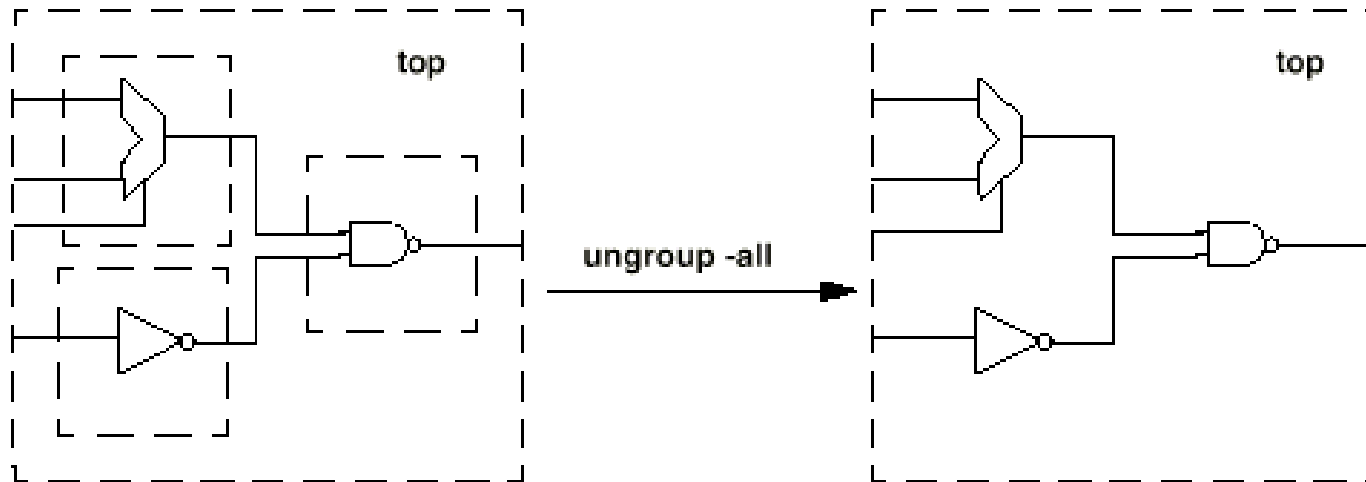- ❑ The ungroup command collapses hierarchy.






Group Cells into a Module

Enabling Productivity

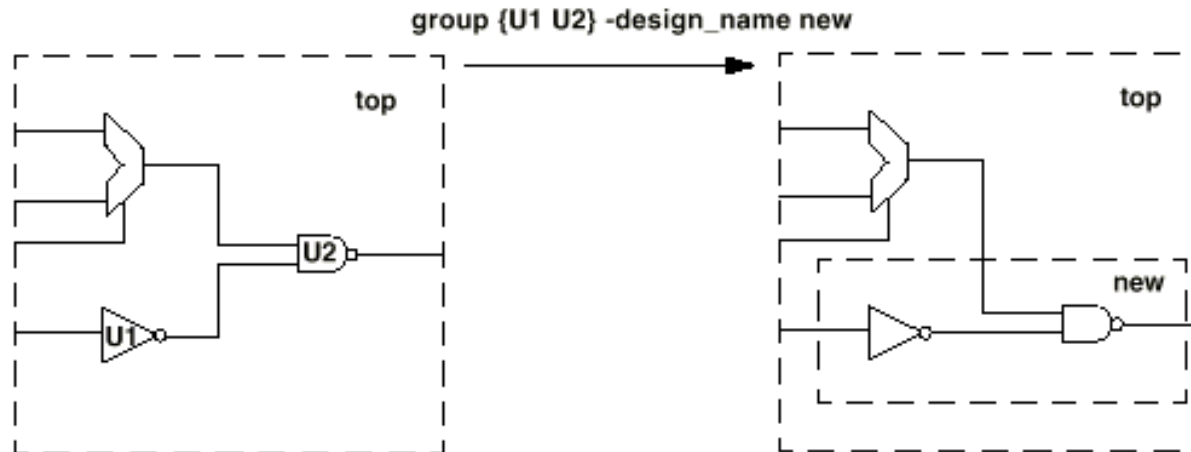- ❑ The group command allows you to create new levels of hierarchy from the objects at this level.






Group Cells into a Module

Enabling Productivity

- ❑ You can group individual HDL blocks with the `hdl_block` option of the `group` command.

Block label examples for Verilog source code
 
```
// This is a named always block
always @(A or B or C) begin: My_Process
.....
end
```



```
group -hdl_block My_Process -design My_Block
```



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure**
- Partitioning**
- Implying Logic Structure**
- Safe Coding & Avoiding Problems**
- Source Code Readability**
- Coding Style for Design Reuse**
- Design for Testability**
- Practices**



Implying Logic Structure: Checklist Items

Enabling Productivity

- Unintentional latches (301)**
- If vs. Case statement (302)**
- Code organization & optimization (303)**
- Resource sharing (304)**
- Finite Statement Machines (305)**
- Don't care inference (306)**
- Coding of repetitive structures (307)**
- Sharing Common Subexpression (308)**
- Avoid Redundant Logic and Subexpress. (309)**
- Inferring the Correct Register (310)**
- Structure for Minimum Delay (311)**
- Inferring Tri-State Drivers (312)**



Imply Structure

Enabling Productivity



- ❑ **Poor structure may never converge on the right results**
- ❑ **Poor structure usually means at least an increase in synthesis run times**
- ❑ **Designers imply lots of structure!**

You get what you write!




Unintentional Latches (301)

Enabling Productivity

An IF statement with outputs not fully specified synthesizes to a latch. Example:
 
```
module oops_latch ...  
  
  always @(GATE or A)  
  begin  
    if (GATE == 1)  
      Q = A;  
    end  
  
  endmodule
```



- ❑ `hdlin_check_no_latch = 'false'` is default. If set to "true" HDL Compiler will issue a warning if a latch is synthesized.




Unintentional Latches (301)

Enabling Productivity

A 'case' statement with paths that bypass reg assignment synthesizes to a latch. Example:

```
module oops_latch (bus_err, par_err, sys_err, irq_err, err_code);  
input bus_err, par_err, sys_err, irq_err;  
output [1:0] err_code;  
reg [1:0] err_code;  
  
always @(bus_err or par_err or sys_err or irq_err)  
begin  
    case ({bus_err, par_err, sys_err, irq_err})  
        4'b1000: err_code = 0;  
        4'b0100: err_code = 1;  
        4'b0010: err_code = 2;  
        4'b0001: err_code = 3;  
    endcase;  
end  
  
endmodule
```

 

Assign a value under all conditions. Assign value to all variables. Use a 'default' clause. Use 'full_case' directive.



If vs. Case Statements (302)

Enabling Productivity

- Priority Encoder :

```
if (sel[0])
    z = dat[0];
else if (sel[1])
    z = dat[1];
else if (sel[2])
    z = dat[2];
else
    z = dat[3];
```

If HDL compiler cannot statically determine that branches are parallel, it synthesizes hardware that include a priority encode.

- Simple “One Hot”Encoder:

```
case (1'b1) // synopsys parallel_case
    sel[0] : z = dat[0];
    sel[1] : z = dat[1];
    sel[2] : z = dat[2];
    sel[3] : z = dat[3];
endcase;
```

Parallel_case: no cases overlap

Is synopsys directive needed ?



Code Organization & Optimization (303)

Enabling Productivity

- ❑ **Organize code such that the latest arriving (design speed) or most frequent (simulation speed) event is evaluated first:**

```
if (often)
    ....
else if (rare)

case (state)
    often: ...
    lessoften: ...
    rare: ....
```


- ❑ **This approach speeds up design speed since the latest arriving signal is further down the logic cone**
- ❑ **This approach speeds simulation since the first condition evaluated is usually true eliminating the need for further processing.**



Resource Sharing (304)

Enabling Productivity

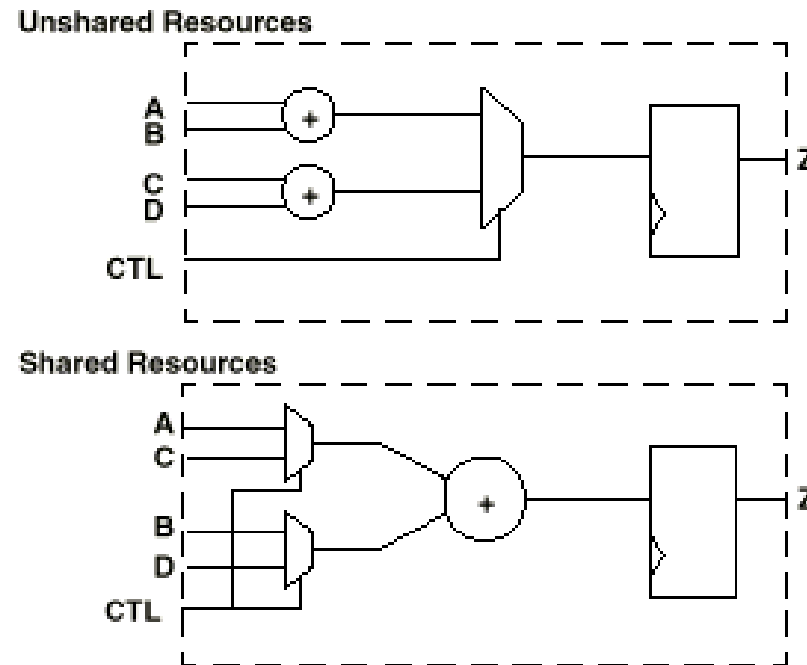- ❑ Design Compiler can share resources like adders or multipliers.
- ❑ Resource sharing can only occur if the resource allocation do not violate the limitations of scope and restrictions.





Resource Sharing (304)

Enabling Productivity

Resource Sharing =

Resource Allocation

+

Implementation Selection



Resource Allocation (304)

Enabling Productivity

- ❑ Resource Allocation is the process of determining the number of resources in your design.

```
// Depending upon adder_control,  
// select correct inputs.  
  
if (adder_control)  
    adder_output = busa + busb;  
else  
    adder_output = busc + busd;
```

One adder
or two?






Implementation Selection (304)

Enabling Productivity

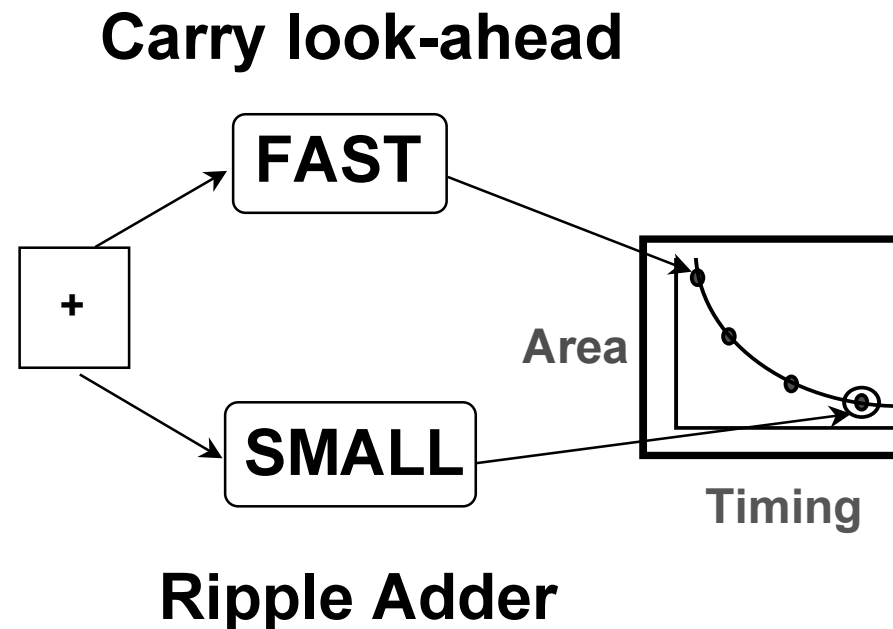- ❑ Implementation selection is the process of choosing the correct DesignWare architecture according to your constraints.





Limitations of Resource Sharing (304)

Enabling Productivity

- ❑ **Not all operations in your design can be shared. The following operators can be shared.**
 - ☞ *****, **+**, and **-**
 - ☞ **>**, **>=**, **<**, and **<=**

- ❑ **Operations can be shared only if they lie in the same always block.**

- ❑ **Two operations can be shared only if no execution path exists from the start of the block to the end of the block that reaches both operations. (Control Flow Conflicts)**

- ❑ **Operations cannot be shared if doing so cause a combinational feedback loop. (Data Flow Conflicts)**



Resource Sharing (304): Scope

Enabling Productivity

```

always @(A1 or B1 or C1 or D1 or COND_1) always @(A2 or B2 or C2 or D2 or COND_2)
begin
begin
  if (COND_1)
  if (COND_2)
    Z1 = A1 + B1;
    Z2 = A2 + B2;
  else
  else
    Z1 = C1 + D1;
    Z2 = C2 + D2;
end
end process P2;
end

```

Allowed & Disallowed Sharing

	A1+B1	C1+D1	A2+B2	C2+D2
A1+B1	-	yes	no	no
C1+D1	yes	-	no	no
A2+B2	no	no	-	yes
C2+D2	no	no	yes	-

Only Operators in the same always@ block can be SHARED !



Resource Sharing (304): Control Flow Conflicts

Enabling Productivity

```

always @ (A or B or C or D or E or F or G
         or H or I or J or OP)
begin: ADDER_SELECT
  Z1 = A + B;
  case (OP)
    2'b00 : Z2 = C + D;
    2'b01 : Z2 = E + F;
    2'b10 : Z2 = G + H;
    2'b11 : Z2 = I + J;
  endcase;
end

```

Allowed & Disallowed Sharings

	A+B	C+D	E+F	G+H	I+J
A+B	-	no	no	no	no
C+D	no	-	yes	yes	yes
E+F	no	yes	-	yes	yes
G+H	no	yes	yes	-	yes
I+J	no	yes	yes	yes	-

Disable resource sharing only if logic is in CRITICAL PATH



Resource Sharing (304): Control Flow Conflicts

Enabling Productivity

- ❑ **Operations in separate branches of a ?: (conditional) construct cannot share the same hardware.**
- ❑ **Consider the following line of code where expressions_n represents any expressions.**

`z = expression_1 ? expression_2 : expression_3;`

HDL Compiler interprets this code as

```
temp_1 = expression_1;  
temp_2 = expression_2;  
temp_3 = expression_3;  
  
z = temp_1 ? temp_2 : temp_3;
```

HDL Compiler evaluates both expression_2 and expression_3, regardless of the value of the conditional.

Therefore, operations in expression_2 cannot share the same resource as operations expression_3.



Resource Sharing (304): Data Flow Conflicts

Enabling Productivity

- ❑ To understand how sharing can cause a feedback loop, consider the following example.

```
//Data Flow Conflict
always @(A or B or C or D or E or F or Z or ADD_B)
begin
  if(ADD_B) begin
    TEMP_1 = A + B;
    Z = TEMP_1 + C;
  end
  else begin
    TEMP_2 = D + E;
    Z = TEMP_2 + F;
  end
end
```


When the A+B addition is shared with the TEMP_2+F addition on an adder call R1 and the D+E addition is shared with the TEMP_1+C addition on an adder called R2, a feedback loop results



Resource Sharing (304): Data Flow Conflicts

Enabling Productivity

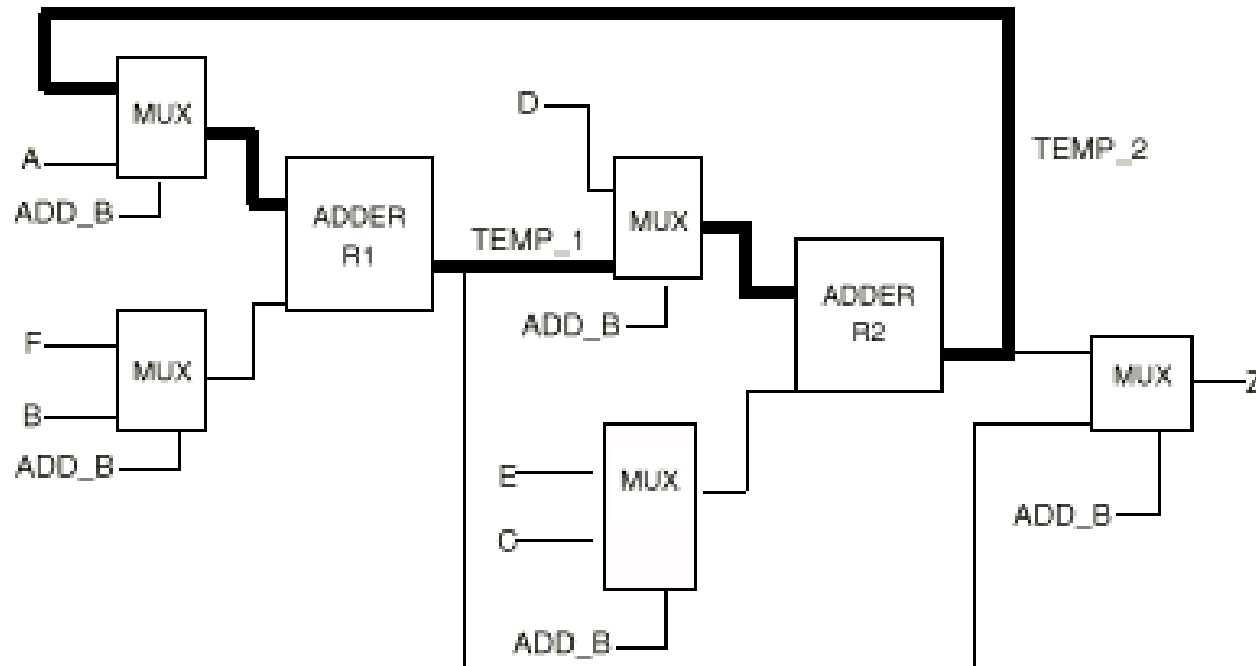- ❑ Feedback Loop For the previous example.



HDL Compiler resource sharing mechanism does not allow combinational feedback paths to be created because most timing verifiers cannot handle them properly.



Critical Path Considerations...(304)

Enabling Productivity

- ❑ To enable automatic sharing for all designs, set the `dc_shell` variable as shown before you execute the compile command.

```
dc_shell> hlo_resource_allocation = constraint_driven
```

- ❑ The default value for this variable is *constraint_driven*.

- ❑ To disable automatic sharing for uncompiled designs, and enable resource sharing only for selected designs, enter the following commands:

```
dc_shell> hlo_resource_allocation = none
```


```
dc_shell> current_design = MY_DESIGN
```

```
dc_shell> set_resource_allocation constraint_driven
```



Finite State Machines (305): Extracting


Enabling Productivity

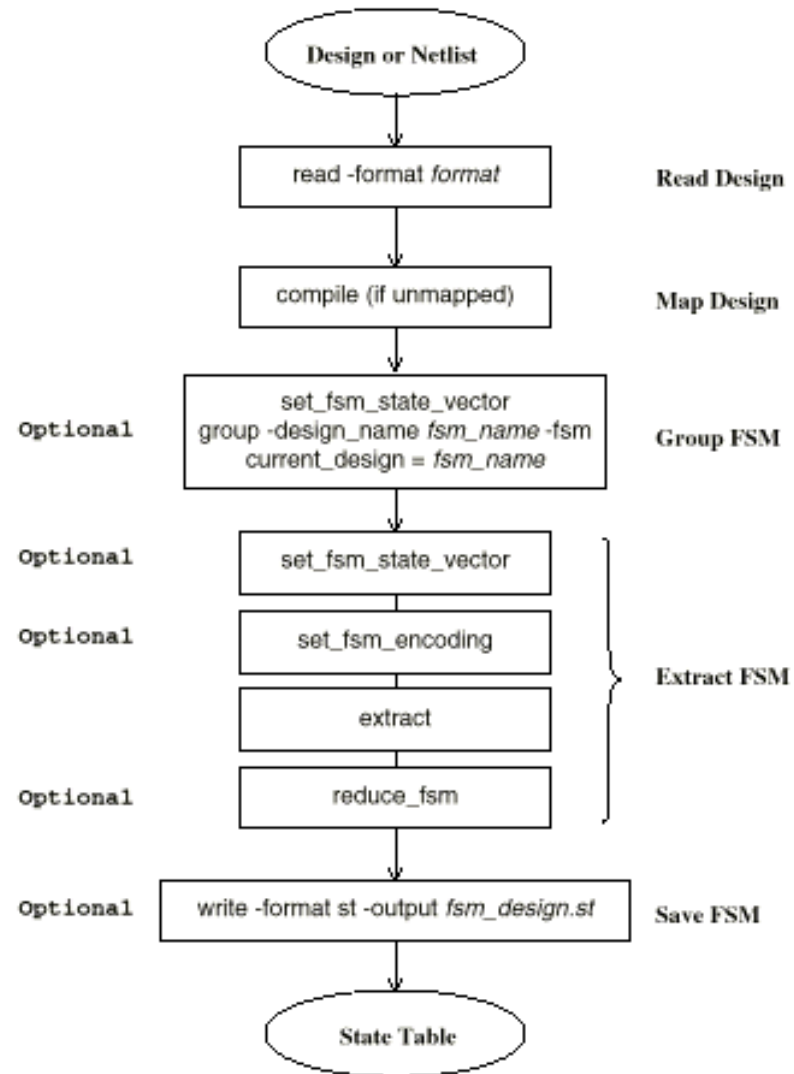



Finite State Machines (305): Compile

Enabling Productivity

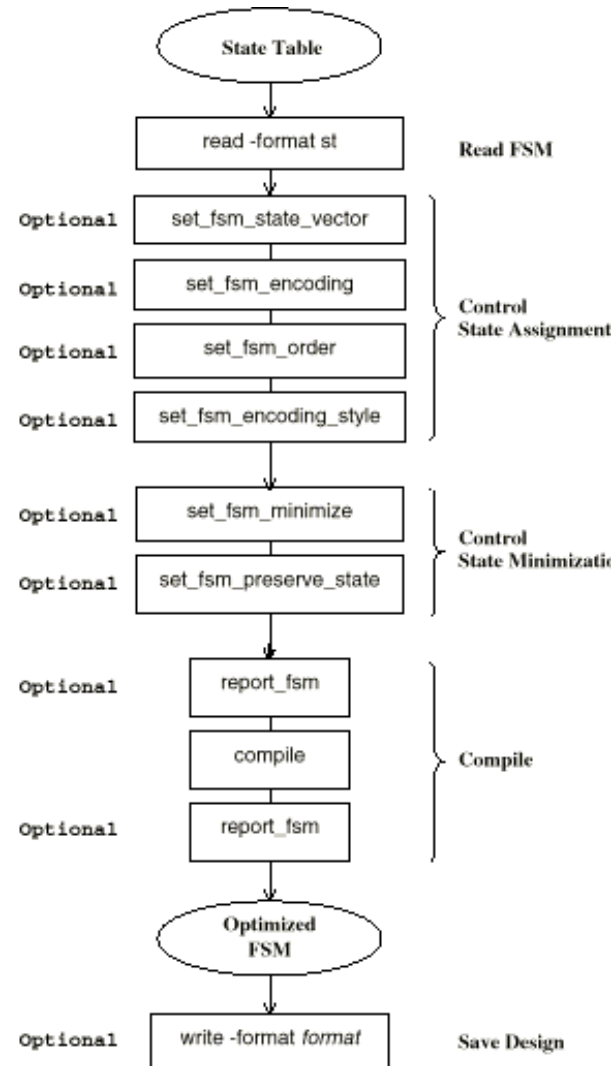



Finite State Machines (305)

Enabling Productivity

- ❑ **Design Compiler uses logic and gate-level optimization techniques for synthesis.**

- ❑ **Two additional techniques are available for FSMs:**
 - ***State Minimization***
removal of redundant states

 - ***State Assignment***
encoding styles (e.g. binary, gray, one-hot)

- ❑ **Technique: (1) read in design, (2) map to gates, and (3) extract FSM**



State Machine Extraction (305)

Enabling Productivity

- ❑ **Extract out the state machine when:**
 - ☞ **Number of states is from 15-32**
AND
 - ☞ **States and surrounding logic are random**
AND
 - ☞ **Best state ordering and number of bits is unpredictable**
AND
 - ☞ **Constraints are a mix of timing and area**



State Machine Syntax (305)

Enabling Productivity

- ❑ **Use Synopsys' directives and style if you wish to extract out a state machine.**

- ❑ **Synopsys Style:**
 - **Separate state machine into two processes**
 - **Create an enumerated type for the state vector**
 - **Drive FSM with embedded Synopsys directives**
 - **Read HDL Compiler for Verilog manual for detailed information**

After FSM extraction and optimization, back-annotate states into HDL code - but do not routinely flow through the extraction process.



FSM Verilog Example (305)

Enabling Productivity

```
// This finite-state machine (Mealy type) reads 1 bit  
// per cycle and detects 3 or more consecutive 1s.
```

```
module enum2_V(signal, clock, detect);  
input signal, clock;  
output detect;  
reg detect;
```

```
// Declare the symbolic names for states  
parameter [1:0]//synopsys enum state_info  
    NO_ONES = 2'h0,  
    ONE_ONE = 2'h1,  
    TWO_ONES = 2'h2,  
    AT_LEAST_THREE_ONES = 2'h3;
```

```
// Declare current state and next state variables.  
reg [1:0] /* synopsys enum state_info */ cs;  
reg [1:0] /* synopsys enum state_info */ ns;
```

```
// synopsys state_vector cs  
always @ (cs or signal)  
begin  
    detect = 0;// default values  
    if (signal == 0)  
        ns = NO_ONES;  
    else  
        case (cs) // synopsys full_case  
            NO_ONES: ns = ONE_ONE;  
            ONE_ONE: ns = TWO_ONES;  
            TWO_ONES,  
            AT_LEAST_THREE_ONES:  
                begin  
                    ns =  
AT_LEAST_THREE_ONES;  
                    detect = 1;  
                end  
            endcase  
        end  
    end  
always @ (posedge clock) begin  
    cs = ns;  
end  
endmodule
```



Example Synopsys (Non Verilog) FSM Code

Enabling Productivity

```
# Soft drink machine -- Price is 15 cents
.design    soft_drink_machine
# Inputs:  clock and reset signals;
#         nickel, dime, and quarter input signals
.inputnames  clk reset nickel_in dime_in quarter_in
# Outputs: nickel change, dime change, dispense drink
.outputnames nickel_out dime_out dispense
# Clock signal name and type
.clock clk rising_edge
# Asynchronous reset signal, type, and reset state
.asynchronous_reset reset rising IDLE
# State table
100 IDLE    FIVE    000
010 IDLE    TEN     000
...
%%% OWE_DIME  IDLE    010
# Wait in current state until money is deposited
000 IDLE    IDLE    000
000 FIVE    FIVE    000
000 TEN     TEN     000
```

Refer to the Design Compiler Family Reference Manual 's appendix for more information regarding Synopsys FSM Code



Don't Care Inference (306)

Enabling Productivity

- ❑ You can greatly reduce circuit area with don't-cares in your design.
 - ☞ Use x, z, ? in case items of the casex statement to infer don't-care conditions.
 - ☞ Use z, ? In case items of the casez statement to infer don't-care conditions.

```
module decoder8_c(A, Z);
parameter N = 8;
parameter log2N = 3;
input [N-1:0] A;
output [log2N-1:0] Z;
reg [log2N-1:0] Z;

always @(A) begin: encode
  casex (A) // synopsys full_case parallel_case
    8 0000001 : Z = 3 000;
    8 000001x : Z = 3 001;
    8 000001xx : Z = 3 010;
    8 00001xxx : Z = 3 011;
    8 0001xxxx : Z = 3 100;
    8 001xxxxx : Z = 3 101;
    8 01xxxxxx : Z = 3 110;
    8 1xxxxxxx : Z = 3 111;
  endcase
end
endmodule
```



Coding of Repetitive Structures (307)

Enabling Productivity

```
module foo (j, k, l, z);
input  [3:0] j, k, l;
output [3:0] z;
reg    [3:0] z;

integer i;

always @(j or k or l)
begin
    z[0] = (j[0] + k[0]) ^ l[0];
    z[1] = (j[1] + k[1]) ^ l[1];
    z[2] = (j[2] + k[2]) ^ l[2];
    z[3] = (j[3] + k[3]) ^ l[3];
    z[4] = (j[4] + k[4]) ^ l[4];
    z[5] = (j[5] + k[5]) ^ l[5];
    z[6] = (j[6] + k[6]) ^ l[6];
    z[7] = (j[7] + k[7]) ^ l[7];
end

endmodule
```

```
module foo (j, k, l, z);
input  [7:0] j, k, l;
output [7:0] z;
reg    [7:0] z;

integer i;

always @(j or k or l)
begin
    for (i=0; i <=7; i=i+1)
        z[i] = (j[i] + k[i]) ^ l[i];
    end
endmodule
```



Sharing Common subexpressions (308)

Enabling Productivity

- ❑ **Sharing common subexpressions might reduce the area of your circuit.**
- ❑ **You can manually force common subexpressions to be shared by declaring a temporary variable to store the subexpression, then use the temporary variable where you want to repeat the subexpressions.**

// Simple Additions with a Common Subexpression

```
temp = a + b;  
x = temp;  
y = temp + c;
```



Sharing Common subexpressions (308)


Enabling Productivity

- ❑ You can let Design Compiler automatically determine whether sharing common subexpressions improves your circuit; however, there are some limitations that you should know.

// Unidentified Command Subexpression


Y = A + B + C;

Z = D + A + B

 

The parser does not recognize A+B as a common subexpression, because the second equation as (D+A).

 You can force the parser to recognize the common subexpression by rewriting the second assignment statements.



Z = A + B + D;

or

Z = D + (A + B)



Avoid Redundant Logic and subexpressions (309)

Enabling Productivity

❑ Minimize redundant recalculation

```
// Bad - Will synthesize four adders
```

```
X = A + B + C;
```

```
Y = D + C + A;
```

```
// Better - Will only synthesize three adders
```

```
T = A + C;
```

```
X = T + B;
```

```
Y = T + D;
```

```
// Bad - Will synthesize 4 multipliers and 3 adders
```

```
Z = A*C + A*D + B*C + B*D;
```

```
// Better - Will synthesize 1 multiplier and 2  
adders
```

```
Z = (A + B) * (C + D);
```



Avoid Redundant Logic and subexpressions (309)

Enabling Productivity

- ❑ Don't include statements in loops when their values don't change!

```
for (i=0; i<=7; i=i+1)
begin
    proc_data = pci_data;
    fifo(i) = cache(i-1);
end
```

```
proc_data = pci_data;
for (i=0; i<=7; i=i+1)
begin
    fifo(i) = cache(i-1);
end
```

Better



```
if (flag)
begin
    proc_data = pci_data;
    proc_add = cache_add;
end
else
begin
    proc_data = pci_data;
    proc_add = int_add;
end
```

```
proc_data = pci_data;
if (flag)
begin
    proc_add = cache_add;
end
else
begin
    proc_add = int_add;
end
```




Inferring the Correct Register - Synchronous Resets (310)

Enabling Productivity

- An attribute is needed to guide DC in inferring synchronous sets or resets in a design.
 
```
module dff_sync_reset (data, clk, s_reset, q);  
  input data, clk, s_reset;  
  output q;  
  reg q;  
  
  // synopsys sync_set_reset "s_reset"  
  
  always @(posedge clk)  
    if (s_reset)  
      q = 1'b0;  
    else  
      q = data;  
  
endmodule
```



Check Your Technology Library For Sync Set/Reset Cells




Inferring the Correct Register - Asynchronous Resets (310)

Enabling Productivity

- ❑ No attribute is needed to guide DC in inferring asynchronous sets or resets in a design. (Guidance is via coding style)
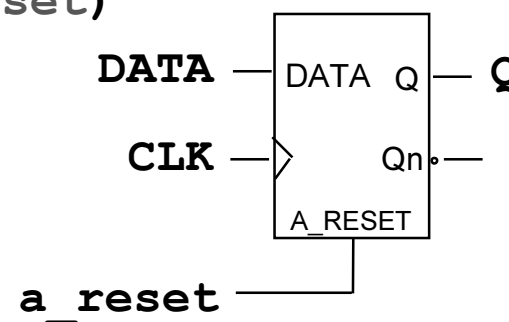
```
module dff_async_reset (data, clk, a_reset, q);  
  input data, clk, a_reset;  
  output q;  
  reg q;  
  
  always @(posedge clk or posedge a_reset)  
    if (a_reset)  
      q = 1'b0;  
    else  
      q = data;  
  
endmodule
```



Check Your Technology Library For Async. Set/Reset Cells



Check Inference Report

Enabling Productivity

- During Elaboration an Inference report is produced:

```
dc_shell> elaborate top_level -arch rtl -lib WORK > elaborate.output
           or
dc_shell> read -format verilog top.v > elaborate.output
```

Sample Inference Report:

Inferred memory devices in process 'synchronizer_reg' in routine m68k line 334 in file '/home/design/syn/try8/hdl/m68k.v'.

```
=====
```

Register Name	Type	Width	Bus	AR	AS	SR	SS	ST
asn_d_reg	Flip-flop	1	-	N	N	N	Y	N
asn_s_reg	Flip-flop	1	-	N	N	N	Y	N
ldsn_d_reg	Flip-flop	1	-	N	N	N	Y	N
ldsn_s_reg	Flip-flop	1	-	N	N	N	Y	N
mrwn_d_reg	Flip-flop	1	-	N	N	N	Y	N
mrwn_s_reg	Flip-flop	1	-	N	N	N	Y	N
udsn_d_reg	Flip-flop	1	-	N	N	N	Y	N
udsn_s_reg	Flip-flop	1	-	N	N	N	Y	N

```
=====
```



Environment Var's for FF Inference

Enabling Productivity

❑ `hdlin_ff_always_sync_set_reset = 'true'`

Each object in the reference design is interpreted as if `sync_set_reset` attribute/directive is present

❑ `hdlin_check_no_latch = 'true'`

Used to generate a warning message during elaborate if a memory element is inferred in reference design.



See Synthesis Reference Manual for Others



Structure for Minimum Delay (311)

Enabling Productivity

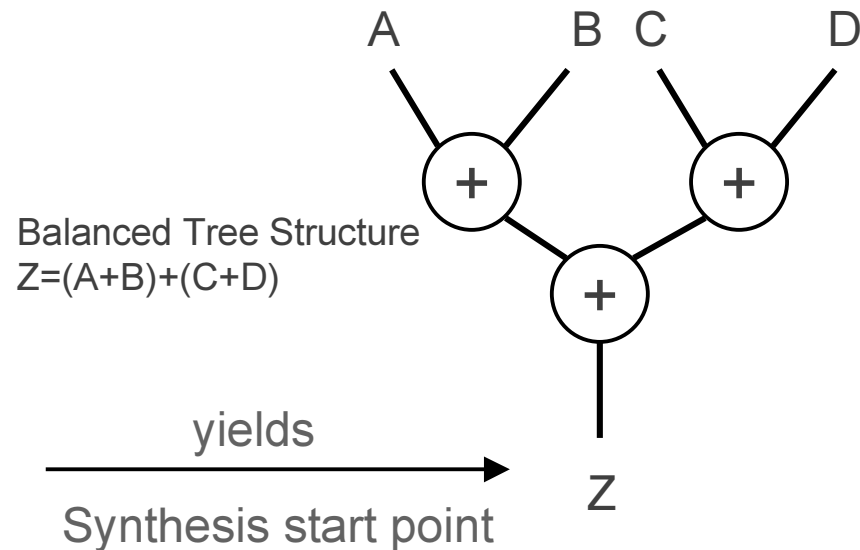 - ❑ You can define the synthesis structure starting point and possibly obtains better quality of results.






Structure for Minimum Delay (311)

Enabling Productivity

❑ Consider the signal arrival times.


// Expression Tree with Minimum Delay
// Signal A arrives Last

$$Z = ((B + C) + D) + A;$$

 

// Expression Tree with Minimum Delay
// Same Arrival Times for All Signals

$$Z = (A + B) + (C + D);$$

 




Inferring Tri-State Drivers (312)

Enabling Productivity

- ❑ Tri-state logic is synthesized on the output driver when the output signal is assigned “Z”.
- ❑ It's important to know that each always block can generate only one Tri-state buffer as an output driver.

```
always @(from_table or enable)
begin: DRIVE_OUTPUT
  if (enable)
    to_bus = from_table;
  else
    to_bus = 8'bz;
end
```
 
```
always @(SELA or SELB or A or B) begin:
  T=1'bz;
  if (SELA)
    T = A;
  if(SELB)
    T = B;
end
```





Inferring Tri-State Drivers - Multiple Tri-state Drive Inference (312)

Enabling Productivity

```
module tristate_a ( a, b, sela, selb, out1);
input a, b, sela, selb;
output out1;
reg out1;
    always @(slea or a)
        out1 = (sela) ? a : 1'bz;

    always @(selb or b) begin
        if (selb)
            out1=b;
        else
            out1=1'bz;
    end
endmodule
```

```
module tristate_a ( a, b, sela, selb, out1);
input a, b, sela, selb;
output out1;
wire out1;

    assign out1= (sela) ? a : 1'bz;
    assign out1= (selb) ? b : 1'bz;

endmodule
```



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure
- Partitioning
- Implying Logic Structure
- Safe Coding & Avoiding Problems**
- Source Code Readability
- Coding Style for Design Reuse
- Design for Testability
- Practices



Safe Coding & Problems: Checklist Items

Enabling Productivity

- One clock per module (401)**
- Separate Sequential & Combination Processes (402)**
- Proper sensitivity lists (403)**
- Blocking Statement vs. Non-blocking Statement (404)**
- Named association (405)**
- Instantiation of Sensitive or Asynch Circuits (406)**
- Avoid Continuous Signal Assignments (407)**
- Reset Strategy Consistency and properly coded (408)**
- Instantiation of black-box (no timing) cells (409)**
- Avoid Initialization (410)**
- Avoid Mixed-Edge Sensitivity (411)**
- Constant Propagation (412)**



One Clock per Module (401)

Enabling Productivity

- ❑ **Synthesis was designed to optimize combinational logic clocked by a register driven from a single clock source**
- ❑ **Synthesis script development becomes much more complex with multiple clocks**
- ❑ **Asynchronous logic is often introduced as a result of logic with clock interfaces**
- ❑ **However it's sometimes unavoidable. If more than one clock in a module then:**
 - ↳ **Estimate impact on testability**
 - ↳ **Estimate impact on synthesis**
 - ↳ **Estimate impact on mixed clocks timing analysis**



Separate Sequential & Combination Processes (402)

Enabling Productivity

```
module count (CLOCK, RESET, RESULT);  
    input CLOCK, RESET;  
    output RESULT;  
    reg RESULT, AND_BITS, OR_BITS, XOR_BITS;  
    reg [2:0] COUNT;
```

```
always @(posedge CLOCK) begin : BAD_EXAMPLE
```

```
    if (RESET) begin
```

```
        COUNT <= 0;
```

```
        RESULT <= 0;
```

```
    end
```

```
    else begin
```

```
        COUNT <= COUNT + 1;
```

```
        AND_BITS <= & COUNT; // AND_BITS gets a Flip Flop
```

```
        OR_BITS <= | COUNT; // OR_BITS gets Flip Flop
```

```
        XOR_BITS <= ^ COUNT; // XOR_BITS get a Flip Flop
```


```
        RESULT <= AND_BITS & OR_BITS & XOR_BITS;
```

```
    end
```

```
end // BAD_EXAMPLE
```

```
endmodule
```

 Code That Implies Extra
Unwanted Registers





Separate Sequential & Combination Processes *(402)*

Enabling Productivity

```
module count (CLOCK, RESET, RESULT);
input CLOCK, RESET;
output RESULT;
reg RESULT, AND_BITS, OR_BITS, XOR_BITS;
reg [2:0] COUNT;

always @(posedge CLOCK) begin : SEQ_BLK
    if (RESET) begin
        COUNT <= 0;
        RESULT <= 0;
    end
    else begin
        COUNT <= COUNT + 1;
        RESULT <= AND_BITS & OR_BITS & XOR_BITS;
    end
end // SEQ_BLK

always @(COUNT) begin : COMB_BLK
    AND_BITS = & COUNT;
    OR_BITS = | COUNT;
    XOR_BITS = ^ COUNT;
end // COMB_BLK

endmodule
```


Code Without Implying
Extra Registers



Proper Sensitivity Lists (403)

Enabling Productivity

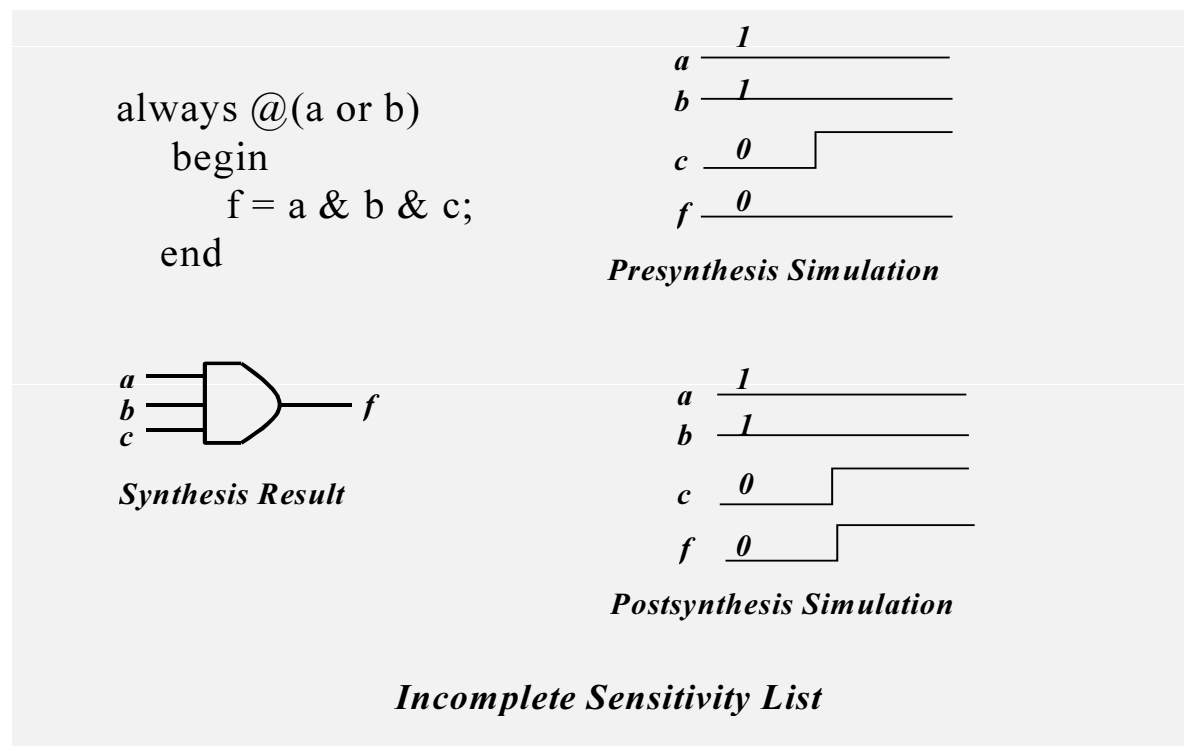- ❑ **Pitfall: gate-level simulation mismatch**
- ❑ **Symptoms:**
 - ☞ Warnings during DC read/elaborate
 - ☞ Inconsistent behavior with slight change in stimulus





Blocking vs. Non-blocking Assignments (404)

Enabling Productivity

- ❑ **Blocking procedural assignments are more like S/W**
 - **reg changes immediately**
 - **Sensitive to dependence**
 - **Sensitive to assignment order**
 - **Simulation speed improvement**

- ❑ **Non-blocking procedural assignments are more like H/W**
 - **reg changes scheduled**
 - **Insensitive to dependence**
 - **Insensitive to assignment order**



Blocking vs. Non-blocking Assignments (404)

Enabling Productivity

❑ **Example of Blocking vs. Non-blocking**

```
always @(a or b or sel) begin : My_Mux
  if ( sel == 1'b0)
    out = a;
  else
    out = b;
end
```

Blocking Assignment

```
always @(posedge CLK) begin :
Shift_reg
  st1_reg <= data_in;
  st2_reg <= st1_reg;
  out_reg <= st2_reg;
end
```


Non-blocking Assignment




Blocking vs. Non-blocking Assignments (404)

Enabling Productivity

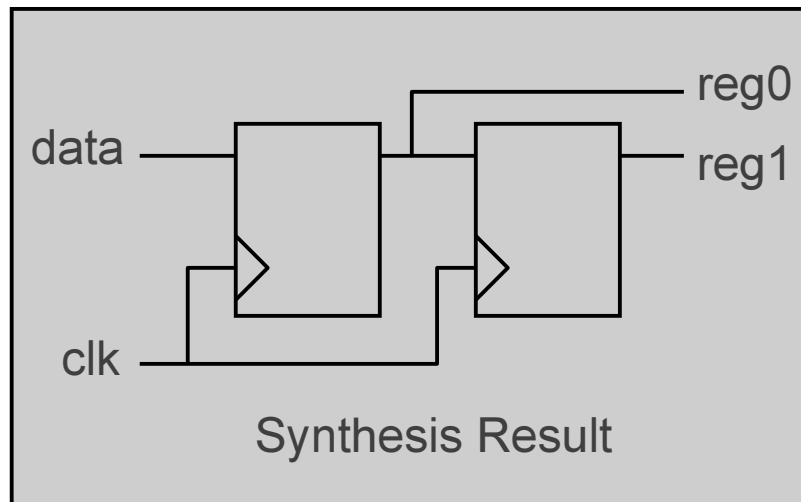- ❑ Proper Use of Blocking and Non-blocking assignment in the sequential always block.


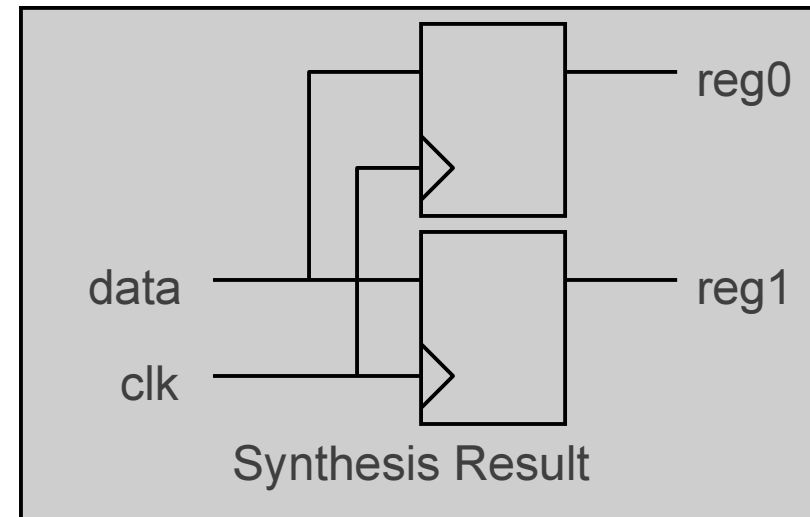
```
//Proper use of Non-blocking assignment  
always @(posedge clk) begin  
    reg0 <= data;  
    reg1 <= reg0;  
end
```



```
//Improper use of Blocking assignment  
always @(posedge clk) begin  
    reg0 = data;  
    reg1 = reg0;  
end
```



Blocking vs. Non-blocking Assignments (404)

Enabling Productivity

- ❑ Improper use of blocking assignment might cause race condition.
- ❑ Potential Race
 - ☞ The intention here is that **a** is shifted to **b** and **b** is shifted to **c** on the positive edge of the clock. However, since Verilog HDL does not specify the order where the always blocks are scheduled, the simulator may schedule that statement **b=a** before the statement **c=b**.

```
//Potential Race
always @(posedge clk)
    c=b;

always @(posedge clk)
    b=a;
```



Named Association (405)

Enabling Productivity

❑ Instantiation port connection via order (implicit)

```
my_adder U1 (base, offset, eff);  
    - is not equivalent to -  
my_adder U1 (base, eff, offset);
```

❑ Instantiation port connection via name (explicit)

```
my_adder U1 (.A(base), .B(offset), .SUM(eff));  
    - is equivalent to -  
my_adder U1 (.SUM(eff), .B(offset), .A(base));
```


Recommend: Always use name based port association.



Instantiation of Sensitive or Asynchronous Circuits (406)

Enabling Productivity

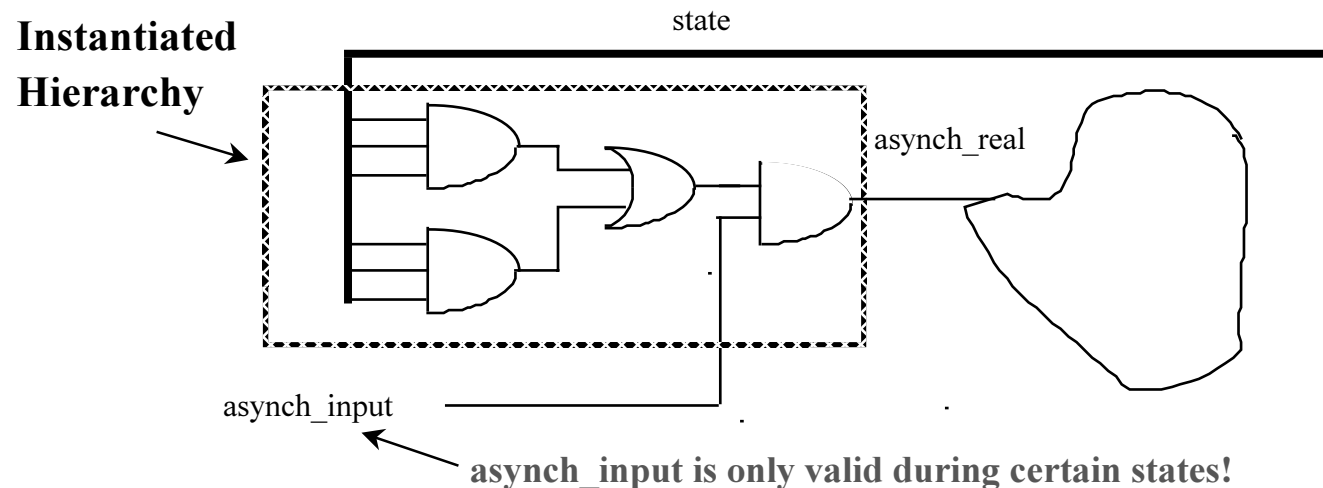- ❑ **Asynchronous logic is difficult to describe in an HDL or to time accurately through static timing analysis.**



INSTANTIATION and GATE SIMULATION is the correct methodology for asynchronous logic.



Avoid Continuous Signal Assignment (407)

Enabling Productivity

- ❑ **Continuous assignment are executed in no defined order and synthesize to combinational logic.**
- ❑ **To facilitate the option to repartition in synthesis, and to improve code readability, you should place the logic in a combinational always block instead.**

```
// Continuous Assignment Example -- Not Recommended
assign sum = a_in ^ b_in ^ c_in;
assign c_out = (a_in & b_in) | (b_in & c_in) | (a_in & c_in);
```

```
// Combinational process -- Recommended
always @(a_in or b_in or c_in) begin: Full_Adder
    sum = a_in ^ b_in ^ c_in;
    c_out = (a_in & b_in) | (b_in & c_in) | (a_in & c_in);
end // Full_Adder
```



Reset Strategy Consistency (408)

Enabling Productivity

- ❑ **Synchronous or asynchronous external reset ?**
- ❑ **What FF cells are available in the library ?**
 - ☞ **Sync set/reset**
 - ☞ **Async set/reset**
- ❑ **Which strategy does the ASIC vendor prefer ?**
- ❑ **What attributes should I set in source code?**
- ❑ **How can I audit proper inference of registers ?**

Plan a Reset Strategy & Then Use it Consistently




Reset Strategy Consistency (408)

Enabling Productivity

❑ Example: Synchronous Reset
 
```
// synopsys sync_set_reset "RESET"  
always @(posedge CLK)  
begin  
    if (RESET)  
        Q = 1'b0;  
    else  
        Q = DATA;  
end
```






Reset Strategy Consistency (408)

Enabling Productivity

❑ Example: Asynchronous Reset
 
```
always @(posedge CLK or posedge RESET)
begin
  if (RESET)
    Q <= 1'b0;
  else
    Q <= DATA;
end
```





Reset Strategy Consistency (408)

Enabling Productivity

- ❑ **Apply a consistent reset strategy, synchronous or asynchronous.**
 - ☞ **Simplify Synthesis, DFT...efforts.**
- ❑ **Infer minimum area D flip-flop cells only when the designer is 100 percent certain that the circuit will self-initialize with no ambiguity.**
- ❑ **Make sure that the circuit will self-initialize.**
 - ☞ **Simulate the gate level design before logic implementation.**



Instantiation of Black-Box Cells (409)

Enabling Productivity

- ❑ **Timing-Driven Synthesis Requires Timing to be Defined for all Components**
- ❑ **Static-Timing Analysis is also Dependent on Full Timing**
- ❑ **Synthesis Timing Models:**
 - ↳ **Vendor Supplied (ie. LSI RAM Model)**
 - ↳ **Designer Created with Library Compiler Constructs**
 - ⇒ **No Special Library License Required (cell's don't have function statements - thus cannot be inferred)**



Example Synthesis-Timing Model (409)

Enabling Productivity

```
library (RAM_LIBRARY) {  
  
  cell(RAM_64x8) {  
    area : 0;  
    pin(WE) {  
      direction : input;  
      capacitance : 1;  
    }  
    bus (A) {  
      bus_type : BUS6 ;  
      direction : input;  
      capacitance : 1;  
    }  
  }  
}
```



Ex. Synthesis-Timing Model-cntd (409)

Enabling Productivity

```
bus (D_IN) {
  bus_type : BUS8 ;
  direction : input;
  capacitance : 1;
}
bus (D_OUT) {
  bus_type : BUS8 ;
  direction : output ;
  pin(D_OUT[0]) {
    timing () {
      intrinsic_rise : 25.0;
      intrinsic_fall : 25.0;
      related_pin : "A[5] A[4] A[3] A[2] A[1] A[0] D_IN[0] WE" ;}
  }
}
```



Avoid Initialization (410)

Enabling Productivity

- ❑ **Do not initialize; synthesis will ignore !**

```
initial
  begin
    count = 0;
  end

always @ (posedge CLK)
  begin
    count = count + 1;
  end
```

What will synthesis produce?




Avoid Mixed-Edge Sensitivity (411)

Enabling Productivity

```
always @(posedge CLK or negedge CLK)
begin
  if (CLK)
    countA = countA + 1;
  else if (!CLK)
    countA = countA + 2;
end
```

```
always
begin
  @(posedge CLK);
  countB = countB + 1;
  @(negedge CLK);
  countB = countB + 2;
end
```

Mixing Clock Edges Example

 


1. The duty cycle of the clock becomes a critical issue in timing analysis, in addition to the clock frequency itself.
2. Most scan-based testing methodologies requires separate handling of positive and negative edge triggered flops.



Constant Propagation -1 (412)

Enabling Productivity

 

- ❑ **Tie-off pins on subdesigns at the lowest level and don't propagate as a primary port if not necessary**
- ❑ **This will help avoid:**
 - **problems with constant propagation**
 - **possible unconnected port issues**
 - **netlist translation issues (VHDL, Verilog, EDIF, etc.)**

DC can't eliminate redundant logic across boundaries when connected to ports

SYNOPTSYS[®]

Professional Service Group



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure
- Partitioning
- Implying Logic Structure
- Safe Coding & Avoiding Problems
- Source Code Readability**
- Coding Style for Design Reuse
- Design for Testability
- Practices



Readability: Checklist Items

Enabling Productivity

- Meaningful embedded comments (501)**

- Use of Loops & Arrays (502)**

- Use of Constants (503)**

- Reduction Operators (504)**

- Proper use of 'define & parameter' (505)**



Meaningful Embedded Comments (501)

Enabling Productivity

- Improve readability, maintainability, ability to reuse, easy review, trace-ability to spec, etc.**

- Typical engineers response ...**

“I don’t have the time to comment now”

- When complete do you go back & comment or do you move on to the next assignment ?**



Use of Arrays and Loops (502)

Enabling Productivity

- ❑ **Use Higher-Level Looping Constructs**
 - ↳ For Loop & While Loop

- ❑ **For Verilog: use 'defines**

- ❑ **Use Arrays instead of group of bits (see example next)**



Example of Register Bank (502)

Enabling Productivity

```
module RGBANK (CLK, WE, ADDR, DATA_IN, DATA_OUT);
input          CLK, WE;
input  [1:0]  ADDR;
input  [7:0]  DATA_IN;
output [7:0]  DATA_OUT;
reg    [7:0]  DATA_OUT;

reg [7:0] RG_0, RG_1, RG_2, RG_3;

always @(ADDR or RG_0 or RG_1 or RG_2 or RG_3)
begin
    DATA_OUT = 0;
    case (ADDR)
        0: DATA_OUT = RG_0;
        1: DATA_OUT = RG_1;
        2: DATA_OUT = RG_2;
        3: DATA_OUT = RG_3;
    endcase;
end

always @(posedge CLK)
begin
    if (WE)
        case (ADDR)
            0: RG_0 = DATA_IN;
            1: RG_1 = DATA_IN;
            2: RG_2 = DATA_IN;
            3: RG_3 = DATA_IN;
        endcase;
    end
endmodule // RGBANK
```



Register Bank Using Arrays (502)

Enabling Productivity

```
module RGBANK (CLK, WE, ADDR, DATA_IN, DATA_OUT);
input          CLK, WE;
input  [3:0]   ADDR;
input  [7:0]   DATA_IN;
output [7:0]   DATA_OUT;

reg [7:0] RG[3:0];

assign DATA_OUT = RG[ADDR];

always @(posedge CLK)
begin
    if (WE)
        RG[ADDR] = DATA_IN;
    end
endmodule // RGBANK
```



Use of Constants (503)

Enabling Productivity

- ❑ **Constants are a very simple way of improving Verilog source code readability and code quality by eliminating typographical errors.**
- ❑ **Sometimes, if the architecture changes, only the constants need to be updated.**

```
// in a header file, declare all constants shared by more than
// one module
`define INTBUS_WIDTH 16
`define EXTBUS_WIDTH 32
...
`define DEVICE_ID 16'h0007
`define REVISION_ID 16'h0002
```




Use of Constants (503)

Enabling Productivity

```
// within module files, declare all local constants
`define CONTROL_OFFSET = 3'b000
`define STATUS_OFFSET = 3'b001
`define MASK_OFFSET = 3'b010
`define INT_OFFSET = 3'b011
...
// Register Read Mux
case (addr)
    `CONTROL_OFFSET : data_out = control_reg;
    `STATUS_OFFSET  : data_out = status_reg;
    `MASK_OFFSET    : data_out = mask_reg;
    `INT_OFFSET     : data_out = int_reg;
```



Use of Reduction Operators (504)

Enabling Productivity

These verbosity...

```
AND      z = a[0] & a[1] & a[2];
OR       z = a[0] | a[1] | a[2];
XOR      z = a[0] ^ a[1] ^ a[2];
NAND     z = ~(a[0] & a[1] & a[2]);
NOR      z = ~(a[0] | a[1] | a[2]);
XNOR     z = ~(a[0] ^ a[1] ^ a[2]);
```

... become these concise statements.

```
AND      z = &a;
OR       z = |a;
XOR      z = ^a;
NAND     z = ~&a;
NOR      z = ~|a;
XNOR     z = ~^a;
```



Use of Reduction Operators (506)

Enabling Productivity

□ Parity Logic:

```
EVEN_PARITY = ^DATA[7:0];  
ODD_PARITY  = ~^DATA[7:0];
```

-or-

```
EVEN_PARITY = DATA[7] ^ DATA[6] ^ DATA[5] ^ DATA[4]  
             ^ DATA[3] ^ DATA[2] ^ DATA[1] ^ DATA[0];  
ODD_PARITY  = DATA[7] ~^ DATA[6] ~^ DATA[5] ~^ DATA[4]  
             ~^ DATA[3] ~^ DATA[2] ~^ DATA[1] ~^ DATA[0];
```



Proper Use of `defines & parameters (505)

Enabling Productivity

- **`define**
 - ↳ Text substitution
 - ↳ Typical uses include
 - ⇒ constants
 - ⇒ readability improvement

- **parameter**
 - ↳ Represents constants
 - ↳ Can be modified at compile time
 - ↳ Modified via
 - ⇒ defparam statement
 - ⇒ module instance statement
 - ↳ Typical uses include
 - ⇒ delay specification
 - ⇒ width of variables



Proper Use of `defines & parameters (505)

Enabling Productivity

pc_defines.v

```
`define SERIAL_CS 16'h1050  
`define PARALLEL_CS 16'h23ff  
`define FLOPPY_CS 16'h4b80
```

Do you have a preference?

io_control.v

```
`include "pc_defines.v"  
...  
...  
  
if (ADDR == `SERIAL_CS)  
    ...  
else if (ADDR == `PARALLEL_CS)  
    ...  
else if (ADDR == `FLOPPY_CS)  
    ...
```

```
...  
...  
...  
  
if (ADDR == 16'h1050)  
    ...  
else if (ADDR == 16'h23ff)  
    ...  
else if (ADDR == 16'h4b80)  
    ...
```



Proper Use of `defines & parameters (505)

Enabling Productivity

```
module regbank (clk, data_in, data_out);  
parameter size = 8, delay = 1;  
input  [size-1:0] data_in;  
output [size-1:0] data_out;  
reg    [size-1:0] data_out;  
  
always @(posedge clk)  
    data_out = #delay data_in;  
  
endmodule
```

```
module top;  
reg clk;  
reg [15:0] inA;  
reg [3:0]  inB;  
wire [15:0] outA; // need delay of 3  
wire [3:0]  outB; // need delay of 2  
  
regbank #(16, 3) U1 (clk, inA, outA);  
regbank U2 (clk, inB, outB);  
  
endmodule
```

```
module annotate;  
  
defparam  
    top.U2.size = 4,  
    top.U2.delay = 2;  
  
endmodule
```



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure
- Partitioning
- Implying Logic Structure
- Safe Coding & Avoiding Problems
- Source Code Readability
- Coding Style for Design Reuse**
- Design for Testability
- Practices



Code Reuse: Checklist Items

Enabling Productivity

- Don't Embed Synthesis scripts in source code (601)**

- Maintain technology independence (602)**

- Use GTECH for simple cell instantiation (603)**

- Databook Quality Description (604)**

- Parameterize modules (605)**



Code Reuse Principal

Enabling Productivity

- ❑ **Design reuse is the action of utilizing objects in the form of macros, subsystems, and systems in the development of new systems**
- ❑ **Design object - with it's associated views (interface, functional spec, etc.) is intended for use in an "object oriented" way**
- ❑ **For example, an implementation of CCITT H.261 (Video Compression Std) should be implemented such that it can be reused in other systems with minimal effort**
- ❑ **Other examples: PCI bus, ADPCM, MPEG decoder, JPEG, etc.**



Levels of Code Reuse

Enabling Productivity

- ❑ **Reuse by the individual**
 - Commonly done, but limited
 - For example: Counter, Mux, RAM Model, etc.
- ❑ **Reuse within a group**
 - Short lifetime, but improved
 - For example: Adaptive Equalizer
- ❑ **Reuse by department/lab**
 - Reasonable lifetime, significant productivity benefits
 - For example: MPEG Decoder
- ❑ **Reuse across enterprise Highest level of reuse**
 - Significant competitive advantage



Don't Embed Synthesis Scripts in Source Code(601)

Enabling Productivity

- ❑ **Example of embedded dc_shell script:**

```
// synopsys dc_script_begin
// set_max_area 2500.0
// set_drive -rise 1 port_b
// synopsys dc_script_end
```

- ❑ **Or hiding simulation constructs or other (e.g. FPGA) from synthesis compiler**

```
-- translate_off
initial
. . .
-- translate_on

-- then set hdlin_translate_off_skip_text = false
to have DC analyze and elaborate the module
```



Maintain Technology Independence (602)

Enabling Productivity

- ❑ **Use DesignWare components**
 - DesignWare components are pre-verified for synthesis and can save you time coding and testing your design.
 - Using DesignWare components can also improve your quality of results.

- ❑ **The DesignWare Library is extensive and is broken down into five families:**
 - Standard Family(adder, subtractor, multiplier, comparator, etc)
 - ALU Family(barrel, shifter, incrementer/decrementer, etc)
 - Advanced Math Family(advanced multiplier, vector add/subtract, etc)
 - Sequential Family(FIFOs, Gray-Scale counters, stack, etc)
 - Fault Tolerant Family(parity checker, CRC generator, etc)
 - Refer to DesignWare Library documentation for detailed information.



Synthetic Parts: Using DesignWare (602)

Enabling Productivity

Through HDL inference

```

...
if (OPCODE_1) then
  mult_output <= busa * busb;


```

Through HDL instantiation

```

// instantiate DW02_MULT
DW02_MULT #(wordlength1, wordlength2)
U1 (in1, in2, control, product)

```

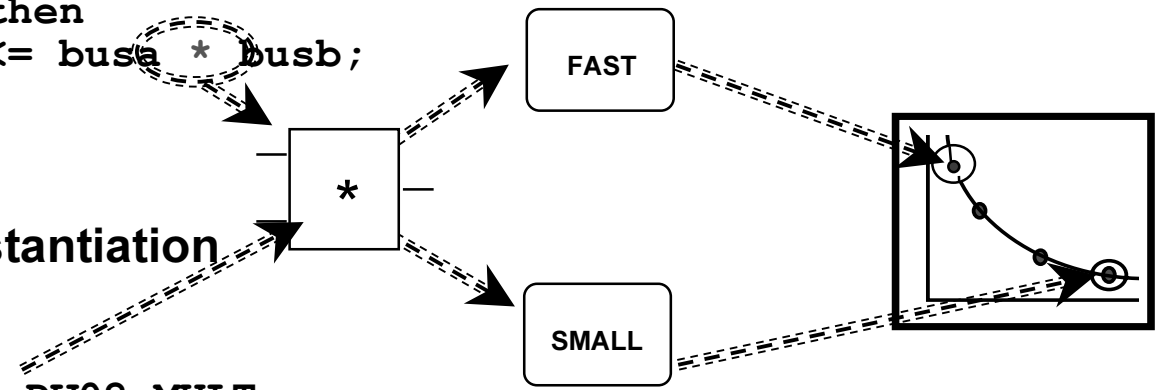

Reference Design

Synthesis Binds to Synthetic Module

Synthesis Selects Proper Implementation

Implementation Optimized for Context



Use GTECH for simple cell instantiation (603)

Enabling Productivity

❑ **When necessary to instantiate ... use GTECH !**

- Provides technology independence
- Typical GTECH cells (AND, NAND, OR, NOR, XOR, FA, HA, FF, LATCH, AOI, MUX, etc.)
- Use *map_only* attribute to prevent DC from *ungrouping* or
- In *dc_shell*:

```
set_map_only { find(reference "my_gtech_cell" }
```



Using GTECH - verilog (603)

Enabling Productivity

```
`include "<SYNOPTSYS_ROOT>/packages/gtech/src_ver/gtech_lib.v"

module top (...);
...
...

GTECH_AND2  U1 (.A(in1), .B(in2), .Z(out1));
GTECH_NAND2 U2 (in3, in4, out2);

...
...
endmodule
```

GTECH instantiation allows a technology independent HDL description.



Databook Quality Description (604)

Enabling Productivity

- ❑ **Databook-like quality implies published quality documentation.**
- ❑ **It's worth spending the effort to produce databook-like comments and consider the following characteristics:**
 - ☞ **Readable Documentation**
 - ☞ **Traceability to Specification**
 - **Block diagrams**
 - **Functional specification**
 - **Description of parameters and their use**
 - **Interface signal descriptions**
 - **Timing diagrams and requirements**
 - **Verification strategy**
 - **Synthesis constraints**



Databook Quality Description (604)

Enabling Productivity

☐ **Continue...**

- ☞ **Useful Examples of How To Use the Module**
- ☞ **A complete Testbench for the Module**
 - **Verification reports (what was tested)**
 - **Technology used**



Parameterize Modules (605)

Enabling Productivity

- ❑ The use of the parameter construct improve the ability to reuse this module because of the parameterization provided by the parameter statement.

```
module FIFO (CLK, WRITE_ENABLE, WRITE_SELECT, READ_SELECT,  
            DATA_IN, DATA_OUT);
```

```
parameter SELECT_WIDTH = 3;  
parameter DATA_WIDTH = 8;  
parameter FIFO_DEPTH = 8;
```

```
input CLK, WRITE_ENABLE;  
input [SELECT_WIDTH-1:0] READ_SELECT, WRITE_SELECT;  
input [DATA_WIDTH-1:0] DATA_IN;
```

You can change the parameter value in a module during instantiation or elaborating designs in synthesis.

module_name #(parameter_value,.....) instance_name(port list)
or
elaborate design_name -parameters parameter_list



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines


- General HDL Code Structure
- Partitioning
- Implying Logic Structure
- Safe Coding & Avoiding Problems
- Source Code Readability
- Coding Style for Design Reuse
- Design for Testability**
- Practices



Why Design for Test?

Enabling Productivity

Test Dev. Time
Total Design Time
%

 

Controllability & Observability as Percentage of Circuit

Source of Graph: "ASIC Testing Upgraded", by Marc Levitt, IEEE Spectrum, May 1992, pp26-29

SYNOPSYS[®]

Professional Service Group



Use Synchronous Design Style

Enabling Productivity

- Avoid One Shots
- Avoid Asynchronous State Machines
- Isolate Asynchronous Logic

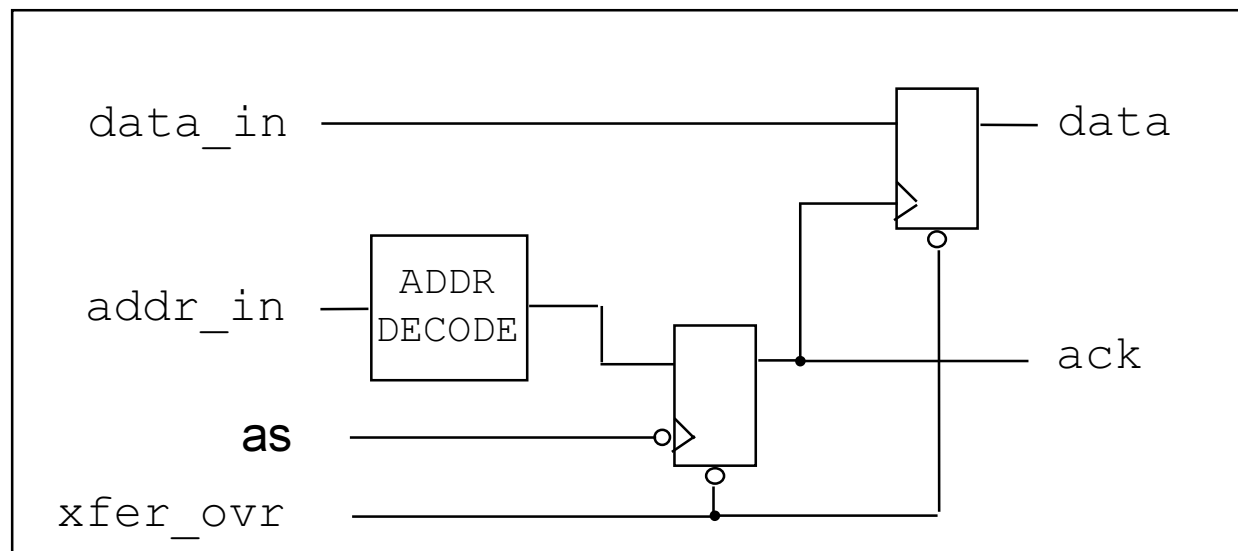


Fig. 1 Example Asynchronous Bus Interface



Exercise: Make Asyn. Xface Testable

Enabling Productivity


```
module bus_xface (data_in, addr_in, as, xfer_ovr, ack,data);
input [3:0] data_in;
input [3:0] addr_in;
input as, xfer_ovr;
output [3:0] data;
output ack;

reg [3:0] data;
reg ack;

always @ (negedge as or negedge xfer_ovr)
if(~xfer_ovr)
ack <= 1'b0;
else
ack <= addr_dec;

ADDR_DECODE U1(addr_in, addr_dec);

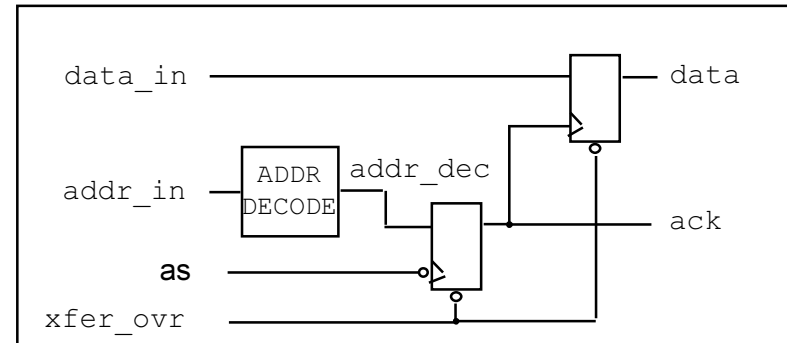always @ (posedge ack or negedge xfer_ovr)
if(~xfer_ovr)
data <= 4'b0000;
else
data <= data_in;
endmodule
```





Bypass Internally Created Clock

Enabling Productivity

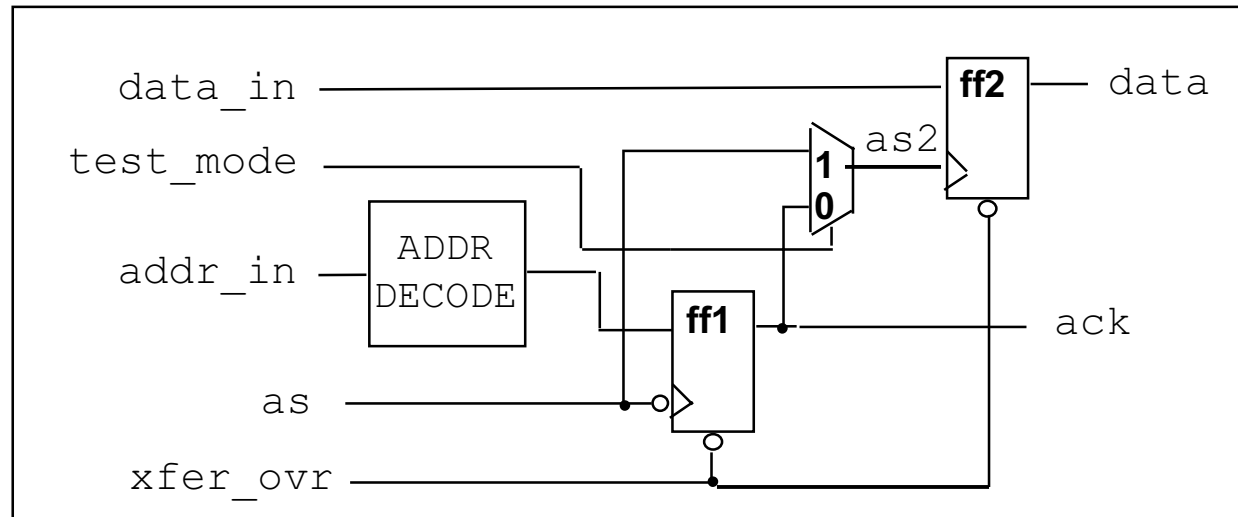


Fig 2. Testable “Asynchronous” Xface with Controlled Clock Ckt.

- Internal clock is not controllable: bypass it during test.
- Two phases of clock used: route scan chain ff1 to ff2 to prevent “shoot thru”.
- Assume “as” is available at chip I/O and synchronous relative to other clocks during test.



Verilog Code for Bypassed Asyn Ckt

Enabling Productivity

```
module bus_xface (data_in, addr_in, as, xfer_ovr, ack,data,test_mode);
input [3:0] data_in;
input [3:0] addr_in;
input as, xfer_ovr; test_mode;
output [3:0] data;
output ack;

reg addr_dec;
reg [3:0] data;
reg ack;
wire as2;

assign as2 = test_mode ? as : ack;

always @ (negedge as or negedge xfer_over)
if(~xfer_over)
ack <= 1'b0;
else
ack <= addr_dec;

ADDR_DECODE U1(addr_in, addr_dec);

always @ (posedge a or negedge xfer_over)
if(~xfer_over)
data <= 4'b0000;
else
data <= data_in;
endmodule
```




Avoid Internal Three State Buses

Enabling Productivity

 


Fig. 3 Example Three-State Circuit

Rule: Cannot have multiple drivers active at the same time.

- Can potentially cause bus contention and a power sink, if the values driven by the drivers are different.

Rule: Must have at least one driver active at all times.

- Cannot test enable signal, if disabling drivers causes bus to float.




Exercise: Make 3 States Testable

Enabling Productivity

```
module tri_state (en,d1,d2,tribus);
input d1, d2;
input [1:0] en;
output tribus;
reg tribus;

 always @(d1 or en)
  if (en)
    tribus = d1;
  else
    tribus = 1'bz;
always @(d2 or en)
  if (en)
    tribus = d2;
  else
    tribus = 1'bz
endmodule
```





Use Pull-Ups & Muxed Enables

Enabling Productivity

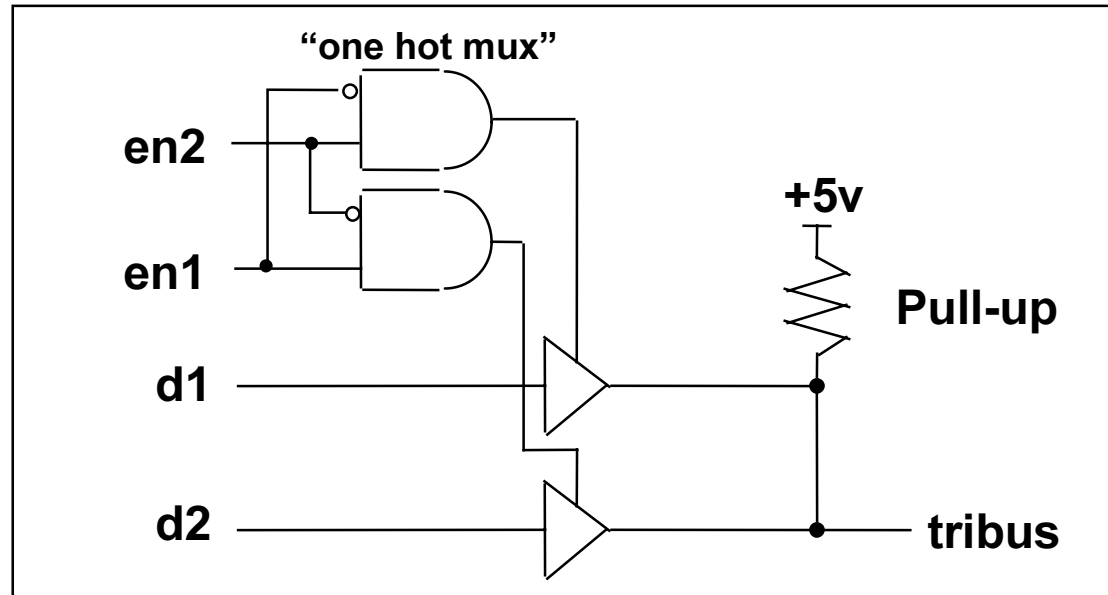


Fig. 4 Example Three-State w/ Pull-ups & Multiplexed Enables

- All tri-state controls are preferably fully decoded to ensure one active driver



Verilog Code for Pull-ups & 3-States

Enabling Productivity

```
module tri_state (en1, en2,d1,d2,tribus);
input d1, d2;
input en1,en2;
output tribus;
reg tribus;

always @(d1 or en1 or en2)
  if (en1 & ~en2)
    tribus = d2;
  else
    tribus = 1'bz;

always @(d2 or en1 or en2)
  if (~en1 & en2)
    tribus = d1;
  else
    tribus = 1'bz;

pullup (tribus); // not synthesizable

endmodule
```

- Pull-ups can ONLY be instantiated, not inferred in Verilog code.



Use Mux Instead of Three -State

Enabling Productivity

 


Fig. 5 Example Multiplexed Bus

- Simpler to code.
- No possibility of bus contention

```
module mux_example (en,d1,d2,tribus);
input d1, d2;
input en;
output tribus;
reg tribus;

always @(d1 or d2 or en)
    if (en)
        tribus = d1;
    else
        tribus = d2;
endmodule
```



Avoid Uncontrollable Clocks

Enabling Productivity

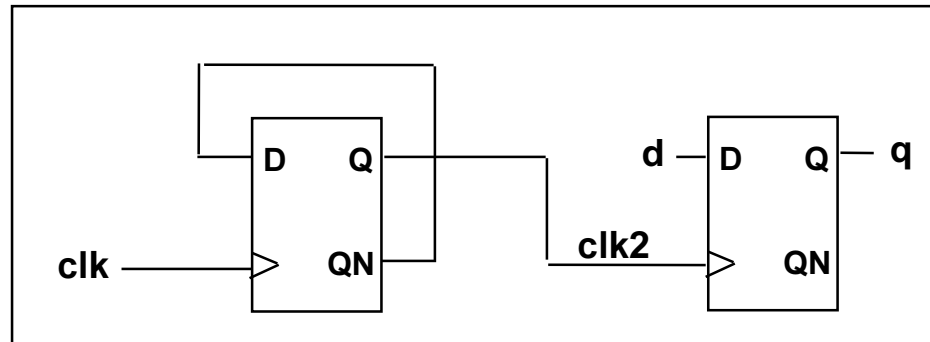


Fig. 6 Example Clock Divider Circuit

Rule: All clocks must be controllable and accessible from top level ports.


- Chip tester would require multiple tester cycles per serial scan chain data item.
- Clock dividers inherently untestable, belong to asynchronous circuit category.



 Exercise: Make Clk2 Controllable

Enabling Productivity

```
module clk_gen (d, clk, q);  
input clk, d;  
output q;  
  
reg clk2;  
  
always @ (posedge clk)  
    clk2 <= ~clk2;  
  
always @ (posedge clk2)  
    q <= d;  
  
endmodule
```





Bypass Bad Clocks During Test

Enabling Productivity

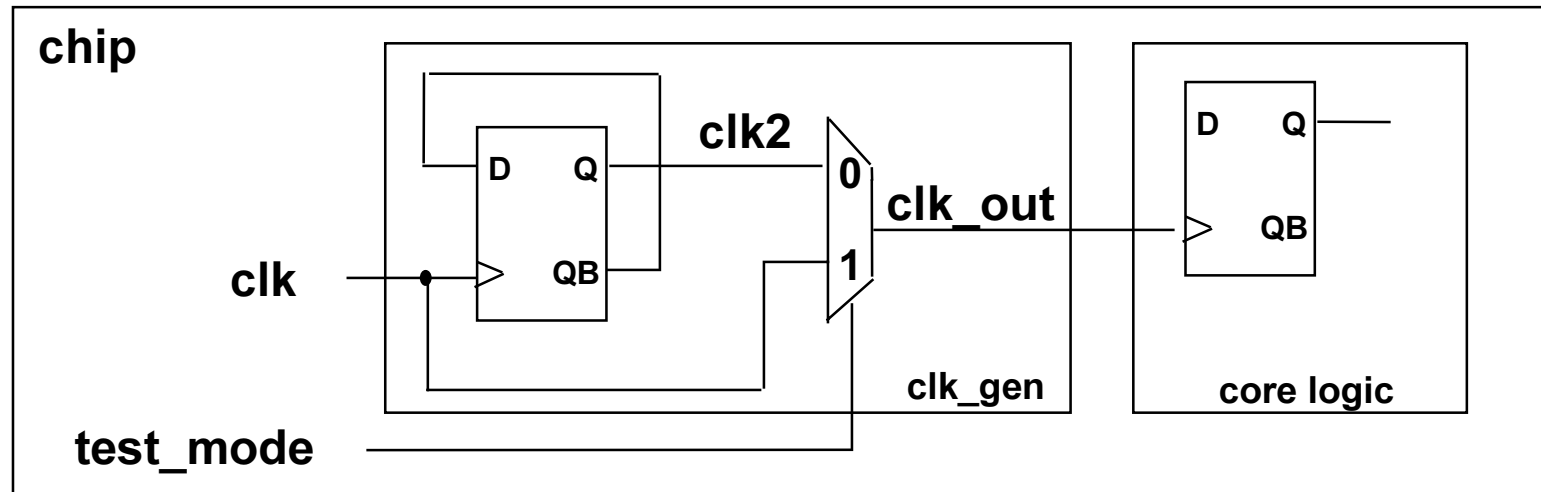


Fig. 7 Example Asynchronous Clock Generator Bypass

- Bypass circuitry added to source code by designer.
- During test: use chip level clock, during regular operation: use derived clock.
- TEST_MODE signal is active high during test, and requires a dedicated port.



Verilog Code for Clock Bypass Logic

Enabling Productivity

- General Rule: Isolate clock generation circuit into its own level of hierarchy.

```
module clk_gen (d, clk, test_mode, q, clk_out);
input clk, d, test_mode;
output q, clk_out;

reg clk2, clk_out;

always @ (posedge clk)
  clk2 <= ~clk2;

always @ (posedge clk_out)
  q <= d;

always @ (test_mode or clk or clk2)
  if (test_mode)
    clk_out = clk;
  else
    clk_out = clk2;

endmodule
```

```
module chip (clk, test_mode, data_in, instr_in, data_out);
input clk, test_mode;
input [31:0] data_in;
input [7:0] instr_in;
output [15:0] data_out;

wire [15:0] data_out;
wire clk_inner;

clk_gen clk_gen_0(clk, test_mode, clk_inner);

core_logic core_logic_0(clk_inner, data_in, instr_in, data_out);

endmodule
```



Avoid Using Clocks as Data Inputs

Enabling Productivity

 


Fig. 8 Example Set - Reset Latch

Rule: DO NOT Use Clocks as Data Inputs.


- Race condition could exist between the enable and data of the latch.
- Even if race condition fixed - it's very difficult to detect and correct such problems.
- Falls under category of asynchronous logic.



Exercise: Make Clock Testable

Enabling Productivity

```
module s_r_latch(set, reset, q);  
input set, reset;  
output q  
  
reg q;  
  
always @ (set or reset)  
if(set |reset)  
q <= set;  
  
endmodule
```

 



Use a S-R Flip-flop

Enabling Productivity

 


Fig. 9 Example S-R FF

```
module s_r_ff ( set, reset, clk, q);
input set, reset, clk;
output q;

reg q;

// synopsys sync_set_reset "set, reset"
always @ (posedge clk)
  if (set)
    q <= 1'b1;
  else if (reset)
    q <= 1'b0;

endmodule
```



Uncontrollable Asynchronous Resets

Enabling Productivity

 


Fig. 10 Example Uncontrollable Reset During Test

Rule: All asynchronous reset / set signals should be controllable through a chip level port.

- The integrity of data scanned through the register during scan shifting must be upheld.
- Uncontrolled reset/set signals could overwrite/erase parts of the scan chain data



Exercise: Fix Uncontrollable Reset

Enabling Productivity


```
module asyn_reset (clk,d1,d2, reset,qout);
input d1, d2, clk, reset;
output qout;

reg ar;

always @ (posedge clk or negedge reset)
if (~reset)
  ar <= 1'b0;
else
  ar <= d1;

always @ (posedge clk or negedge ar)
if (~ar)
  qout <= 1'b0;
else
  qout <= d2;

endmodule
```

 



Controlling Asynchronous Resets

Enabling Productivity

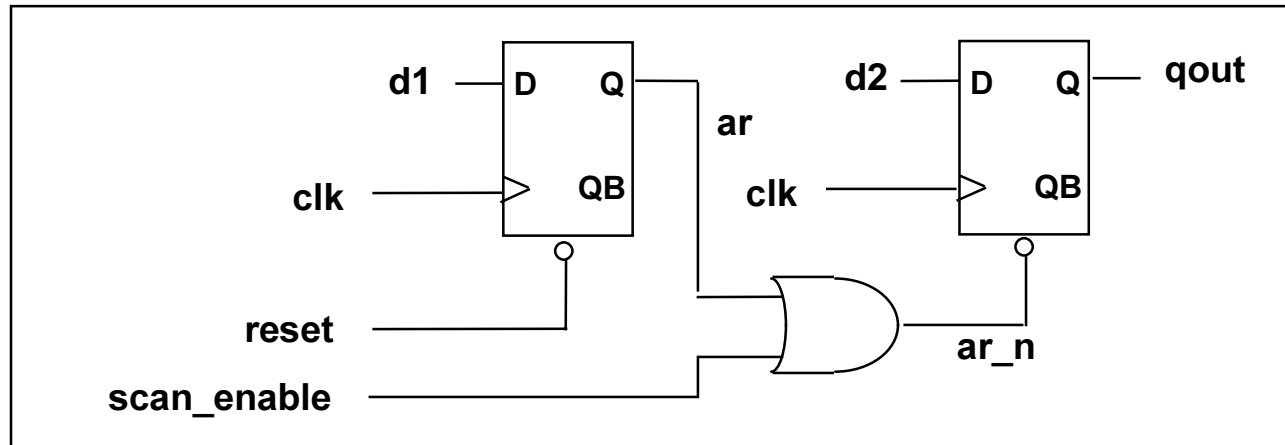


Fig. 11 Example Test Override of Asynchronous Reset

- During scan shift operation, reset held inactive, scan data integrity upheld.
- During capture cycle of test, `scan_enable` is low and thus asynchronous reset signal can be tested.



Vevilog Code to Control Asynch. Reset

Enabling Productivity

- Internal reset signal “gated” within asynchronous reset description

```
module asyn_reset (clk, d1, d2, reset, scan_enable, qout);
input d1, d2, clk, reset, scan_enable;
output qout;

reg ar;

always @ (posedge clk or negedge reset)
if (~reset)
    ar <= 1'b0;
else
    ar <= d1;

wire ar_n = ar | scan_enable;

always @ (posedge clk or negedge ar_n)
if (~ar_n)
    qout <= 1'b0;
else
    qout <= d2;

endmodule
```




Verilog Code for Reset Synchronizer

Enabling Productivity

```
Module syn_reset(clk,asyn_reset,scan_enable,int_reset_n);
input clk, asyn_reset, scan_enable;
output int_reset_n;

reg q1, q2;

always @ (posedge clk or negedge asyn_reset)
  if (~asyn_reset)
    q1 <= 1'b0;
  else
    q1 <= 1'b1;

....
....
....

always @ (posedge clk)
  q2 <= q1;

wire int_reset_n = scan_enable | d1;

endmodule
```



Avoid Combinational Feedback Loops

Enabling Productivity

 


Fig. 13 Example S-R Latch


Rule: Do not have combinational feedback loops in design.

- Introduces states in the design which cannot be synchronously controlled.
- Faults within the logic of the combinational feedback loop may not be testable.
- Asynchronous feedback loops cause problems with synthesis.



Exercise: Make S-R Latch Testable

Enabling Productivity

 

```
module s_r_latch ( set, reset, q);  
input set, reset;  
output q;  
  
wire tmp;  
  
nor (q, reset, tmp);  
nor (tmp, set, q);  
  
endmodule
```



Model S-R Latch as a Leaf Cell

Enabling Productivity

 


Fig.14 Example s_r_latch as a leaf cell

- If SR Latch is modelled as a leaf cell in the technology library, then internal feedback loop not visible to the test generation software.
- Should not be a problem IF a scannable equivalent of the cell exists in the library.
- Otherwise must treat latch as you treat other latches in your design (latches discussed in Test Schemes).



Bi-di Pads Introduce Feedback Loops

Enabling Productivity

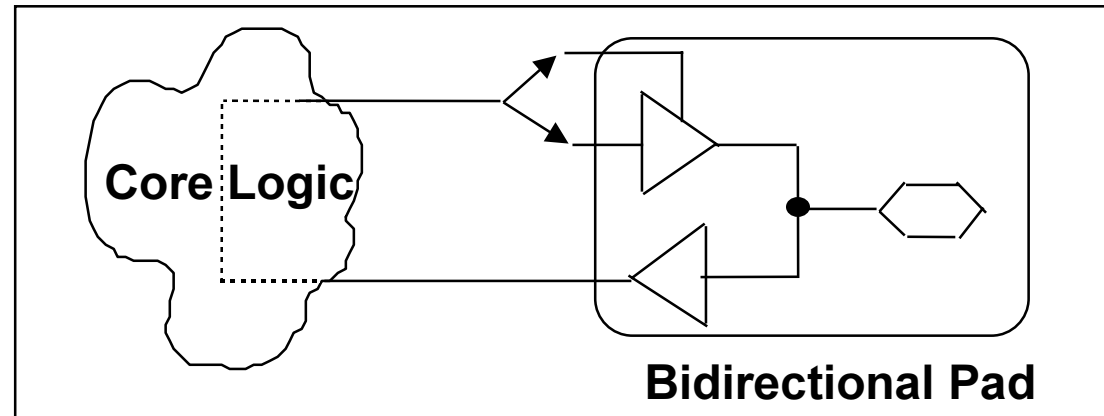


Fig. 15 Example of Feedback Loop w/Bi-Directional Pad

- Combinational feedback path might exist from the input driver thru the internal core logic to the enable or data pin of the output driver.
- Feedback is evident only when the pad is in “output mode”.
- Feedback may or may not be detected by test design rule checker.
- Feedback loop might have to be explicitly broken. Best practice: eliminate loops altogether from design.



Design for Test Rules Summary

Enabling Productivity

- Use Synchronous design styles.
- Avoid Asynchronous designs
- Asynchronous: Isolate Asynchronous logic
- Avoid Three-State Drivers
- 3States: Cannot have more than one driver active at a time
- 3States: Must have at least one driver active at all times (or use a pullup)
- All clocks must be controllable and accessible from top level ports.
- Do NOT use clocks as data inputs.
- All asynchronous reset/set signals must be controllable thru top level port
- Do not have combinational feedback loops in the design.



Test Schemes

Enabling Productivity

- **Latches in Flip-flop Based Designs**
- **Improving Control & Observability**
- **Techniques for Testing RAMs**



Latches in Flip-flop Based Designs

Enabling Productivity

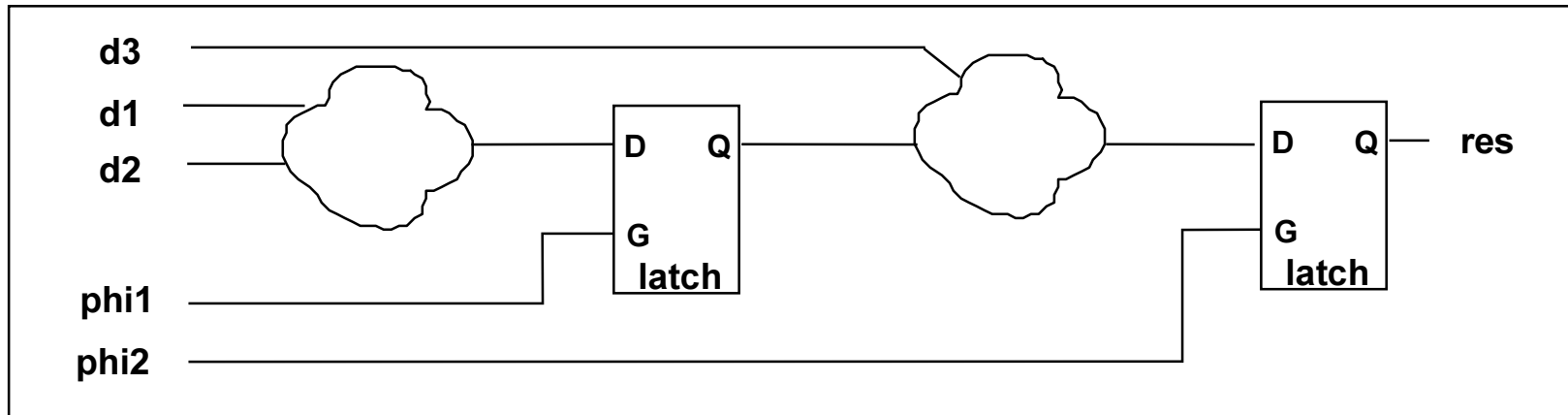


Fig. 16 Example Latches in a Design

You can:

- Leave them as is - let test tool deal with them.
- Replace them with a scannable equivalent (for example use a LSSD cell).
- Model them as black boxes, with the resultant loss of fault coverage
- Hold them transparent during test (watch out for combinational feedback loops!)



Making Latches Transparent

Enabling Productivity

 


Fig. 17 Example Transparent Model for a Latch

- Latch is modelled as a combinational circuit which represents a latch in active (pass thru) mode.
- Lose some fault coverage on enable pin of latch.
- Treat enable pin as data, do not “hook” it up to clock source.
- This treatment of latches is tool specific (ie. beyond Verilog coding style).



Improving Control & Observability

Enabling Productivity

- Given: Scan chains improve testability by providing access to internal registers.
- You can make a design more observable and/or controllable and thus better for test by adding flip-flops at crucial points.

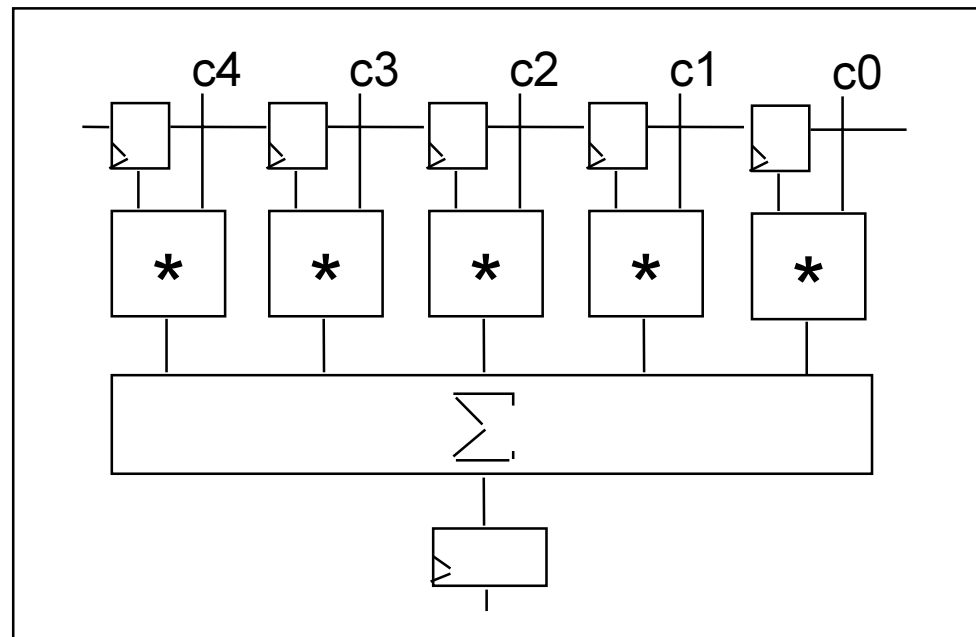


Fig.18 Example “Difficult to Test” Circuit



Adding FF's to Improve Controllability

Enabling Productivity

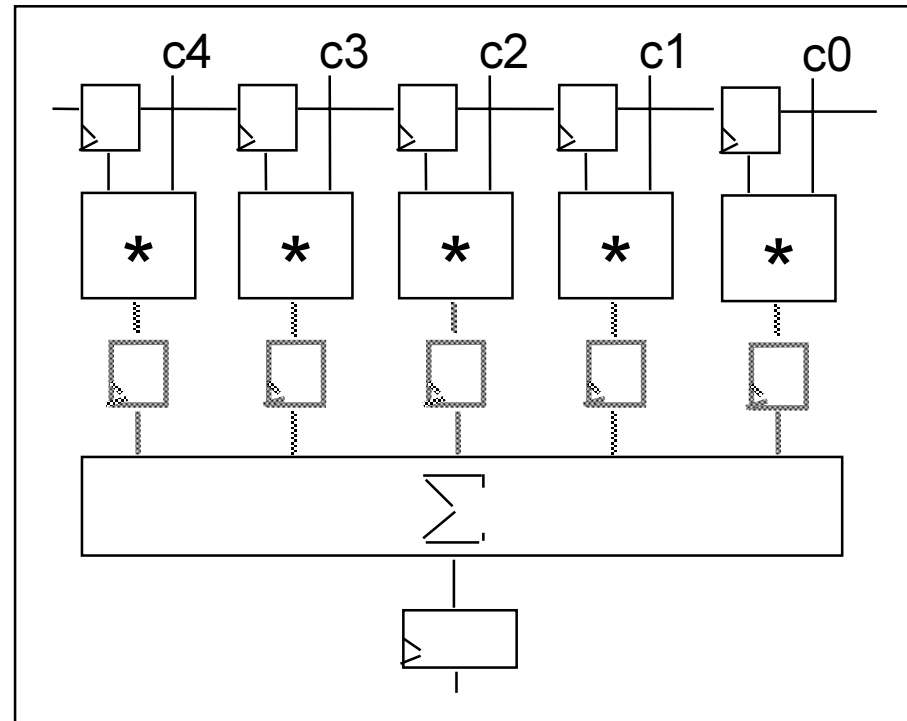


Fig.19 Example Design with Improved Testability

- Simplifies the timing constraints of the design (increases latency, decreases critical paths).
- Can test adder without adding primary input/outputs to the multipliers.



Partitioning to Improve Testability

Enabling Productivity

Rule: Do not allow hierarchical boundaries in combinational paths.

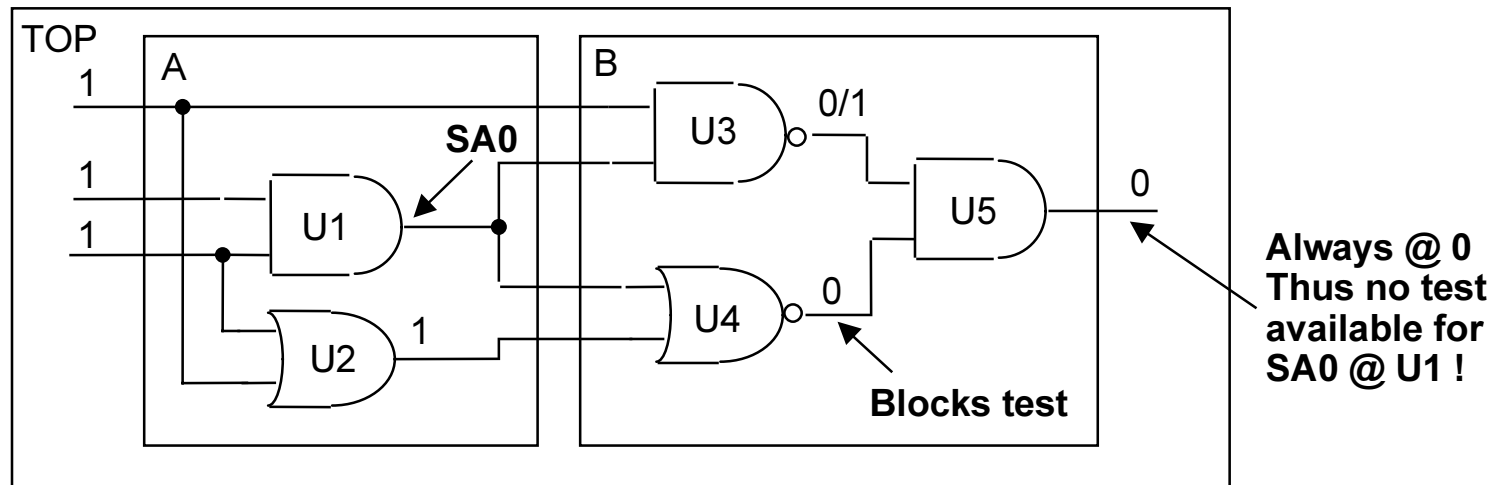


Fig. 20 Testing for a Stuck-At-0 Fault with a Reconvergent Fanout Design

Reconvergent fanout : different paths from the same signal converge again at the same component downstream in the logic.



Techniques for Testing RAMs

Enabling Productivity

- Multiplexed I/O
- Register Bounding
- Transparent RAMs
- Built-In-Self-Test (BIST)

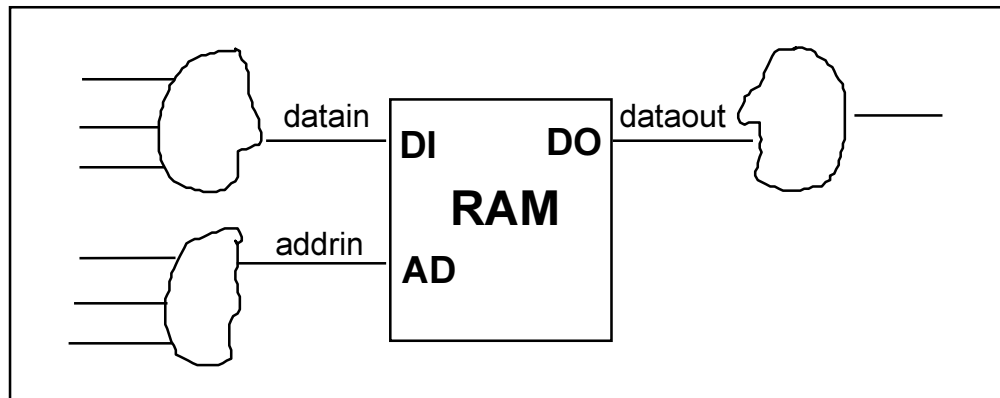


Fig.21 Example RAM with surrounding logic



Multiplexed I/O for RAMs

Enabling Productivity

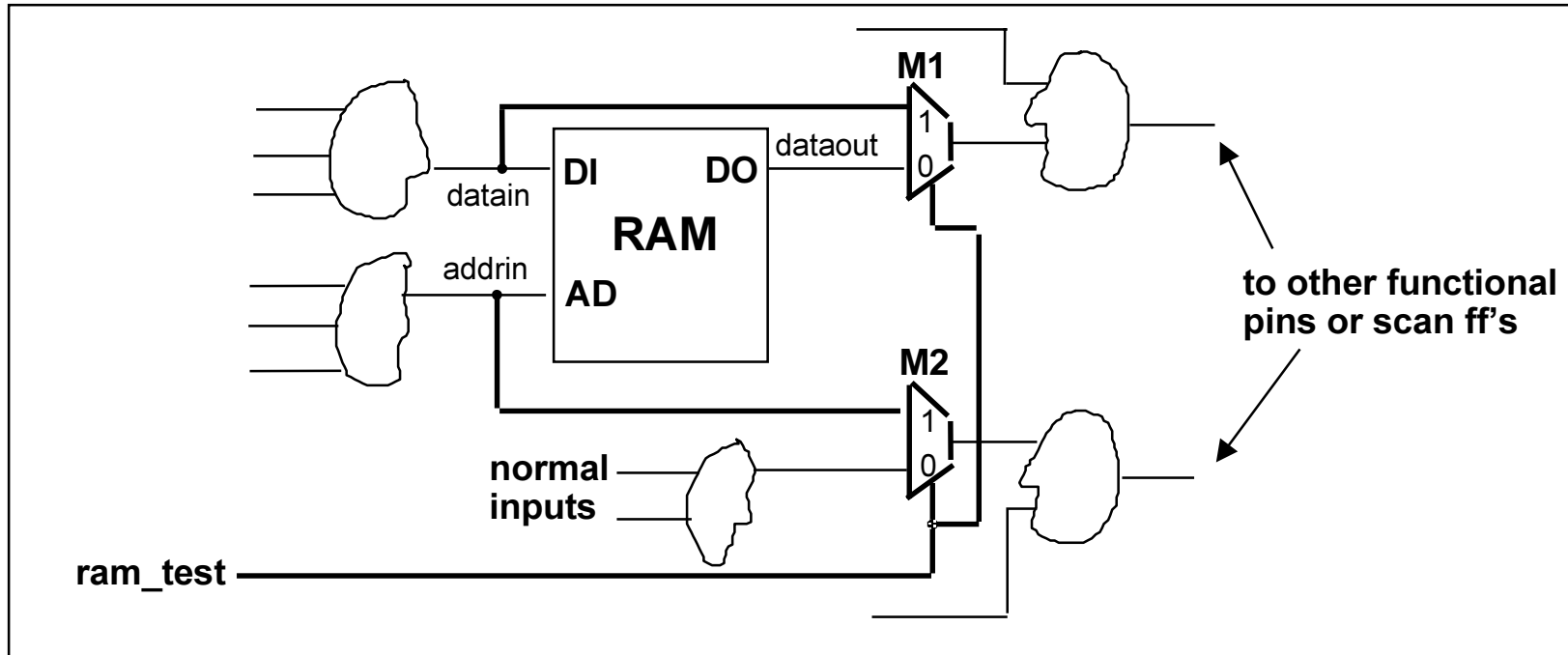


Fig.22 Example Multiplexed I/O Test Scheme applied



Multiplexed I/O Test Scheme

Enabling Productivity

- Increases the observability of the data input to the RAM.
- Increases the controllability of the data output by the RAM.
- Increases the observability of the address driving the RAM.
- If the RAM has a known state during test, then output mux is not needed.



Register Bounding for RAMs

Enabling Productivity

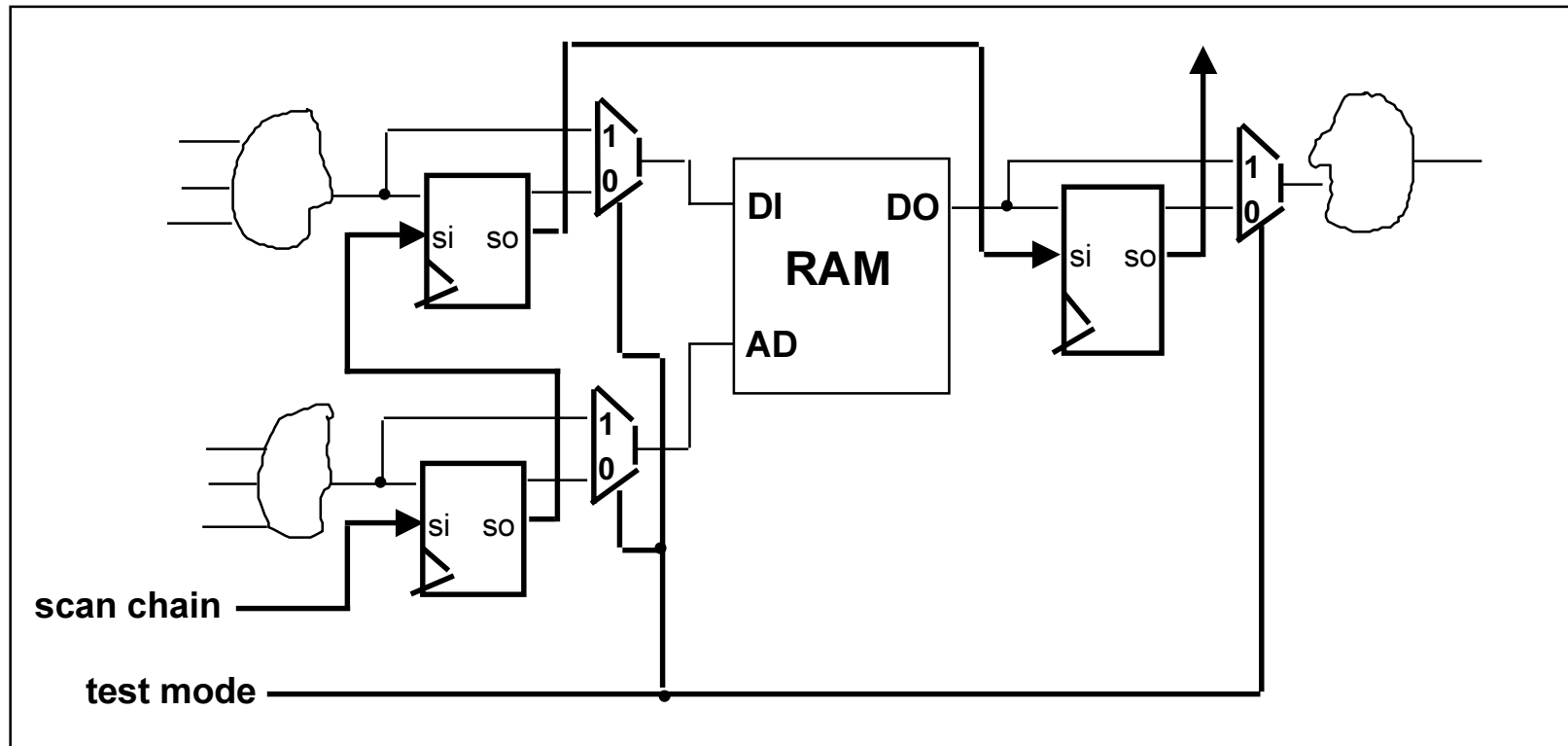


Fig.23 Example Register Bounding Scheme applied to RAM



Register Bounding Scheme

Enabling Productivity

- In normal mode, the bounding registers are bypassed.
- The rest of the ASIC is isolated from the memory and can be tested independently.
- Bounding registers can be used to access & test RAM array.
- All memory arrays to be tested are usually connected into one scan chain.
- Not appropriate for memory arrays more than 1K words.
- Muxes only necessary if combo logic in between internal registers and RAM pins.
- RAM read/write control might need to be controlled by scan_enable signal.



Transparent RAMs

Enabling Productivity

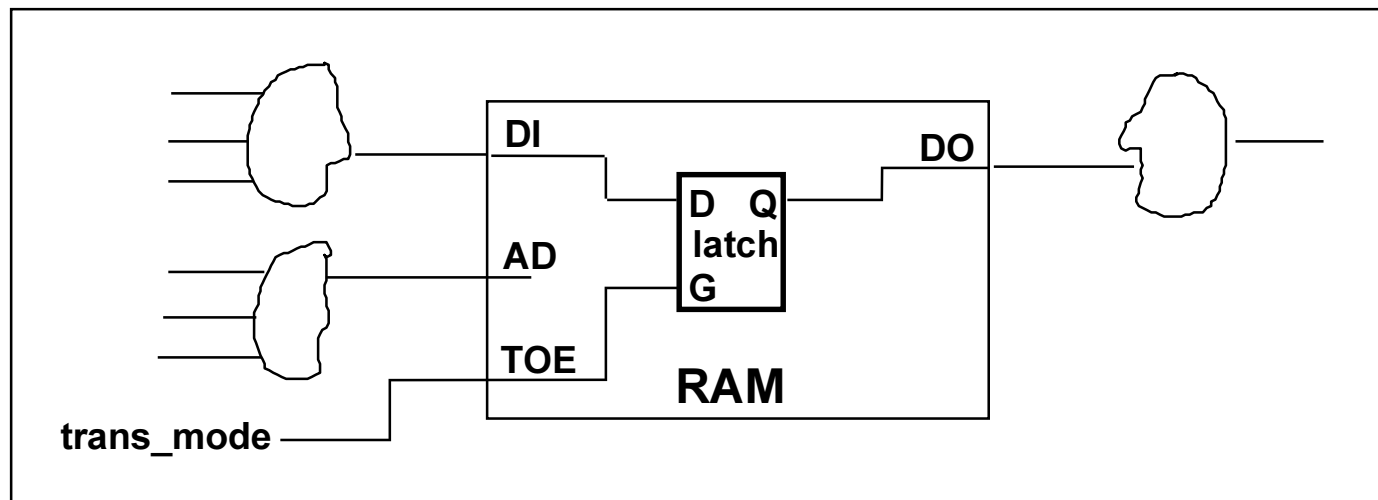


Fig.24 Example Transparent RAM



Transparent RAM Scheme

Enabling Productivity

- Treats the RAM array as if it consists of an array of latches.
- Meant to allow observability of data inputs at data output.
- Must have technology library support from vendor.
- Does not test address inputs or RAM array.



Comparison of RAM Test Schemes

Enabling Productivity

Test Method	Coverage & Ease	Implementation Limitations	Comments
Multiplexed I/O	Easiest Tests Logic Only	Adds mux delay to paths	
Register Bounding	Tests Logic & RAM	Mux if combo logic; Arrays < 1K words	
Transparent Mode	No Additional Muxes Tests Logic Only	Additional Test Protocol	Limited ASIC Library Support
BIST	Tests RAM only Comprehensive	Additional real-estate	Limited by available S/W tools

Table 1 Comparison of RAM Test Schemes



Recommended Test Schemes for RAMs

Enabling Productivity

- If the address, datain, and dataout pins of the RAM are connected directly to internal registers with no combinational logic in between, then *use register bounding* (ie. make surrounding registers part of a scan chain).
- If combinational logic exists between internal registers and the address & data pins of the RAM, consider the following in the order given:

Small / Medium Arrays	Large Arrays
Register Bounding	BIST
Multiplexed I/O	Register Bounding
BIST	Multiplexed I/O

Table 2: Test Schemes For Combo Logic Surrounding RAM



Test Scheme Summary

Enabling Productivity

- Hold Latches in transparent mode.
- Add flip-flops to a design to increase controllability & observability
- Do not partition a combinational logic path across hierarchical boundaries.
- Use register bounding to test RAMs (as a first choice).



Test Methodology Summary

Enabling Productivity

- Test is a *design methodology*. It has its own testability rules, created to insure that scan chains can be added to a design, with the ultimate goal of using an Automated Test Pattern Generator (ATPG) to create test patterns for the chip.
- Most problems associated with test can be avoided or anticipated and corrected up front, during the INITIAL synthesis of the source Verilog code to gates.



HDL for Synthesis Guidelines

Enabling Productivity

Presentation:

HDL for Synthesis Guidelines

- General HDL Code Structure
- Partitioning
- Implying Logic Structure
- Safe Coding & Avoiding Problems
- Source Code Readability
- Coding Style for Design Reuse
- Design for Testability
- Practices**



Practices

Enabling Productivity

- Unsupported Verilog Language Constructs**
- Limitations of Blocking and Non-blocking Assignments**
- Limitations of D Flip-Flop Inferences**
- while Loops Limitations**
- forever Loops Limitations**
- Handling Comparisons to X and Z**
- Limitations of Using Delay Specification**
- Limitations of Tri-State Inferences**
- Limitations of Arithmetic Operators**
- Limitations of casex and casez Statement**
- Case Statement usage**
- Register Inferring**



Unsupported Verilog Language Constructs

Enabling Productivity

❑ **Unsupported Definitions and Declarations**

- ☞ **time declaration**
- ☞ **event declaration**
- ☞ **triand, trior, tri1, tri0, and trireg net types**
- ☞ **Ranges and arrays for integers**

❑ **Unsupported operators**

- ☞ **Case equality and inequality operators (=== and !==)**
- ☞ **Division and modulus operators for variables**

❑ **Unsupported gate-level constructs**

- ☞ **nmos, pmos, cmos, rpmos, rcmos, pullup, pulldown, tranif0, tranif1, rtran, rtranif0, and rtranif1 gate types**



Unsupported Verilog Language Constructs

Enabling Productivity

❑ **Unsupported Statements**

- **defparam statement**
- **initial statement**
- **repeat statement**
- **delay control**
- **event control**
- **wait statement**
- **fork statement**
- **deassign statement**
- **force statement**
- **release statement**
- **procedural continuous assignment**



Limitations of Blocking and Non-blocking Assignments

Enabling Productivity

- ❑ A variable can follow only one assignment method and cannot be the target of both Blocking and Non-blocking assignments.

```
// Unsynthesizable Example
always @(posedge clk or negedge reset)
begin
  if ( !reset ) begin
    a = 0;
    b = 0;
  end
  else begin
    a <= data;
    b <= a;
  end
end
end
```

Mixing Blocking and Non-Blocking assignments



Limitations of Blocking and Non-blocking Assignments

Enabling Productivity

- ❑ RTL assignments are allowed only when no blocking delays are used
 - ☞ #1 a<=b ---- unsynthesizable
- ❑ If variables in two always blocks having dependencies are used in mixing Blocking and Non-blocking statements, they might case the design unsynthesizable.

```
always @(posedge clk or negedge reset)
begin
  if ( !reset ) begin
    a = #1 0;
    ...
  end
  else begin
    a = #1 data1;
    ...
  end
end
```

synthesizable

```
always @(posedge clk or negedge reset)
begin
  if ( !reset ) begin
    d <= #1 0;
    ...
  end
  else begin
    d <= #1 c;
    ...
  end
end
```

synthesizable

```
wire c=a & b ....;
```

A blocking delay is implied here.

But DC reports:
Error :RTL assignments are allowed only when no blocking delays are used.



Limitations of D Flip-Flop Inferences

Enabling Productivity

- The signal in an edge expression cannot be an indexed expression.**

- Set and reset conditions must be single-bit variables.**

- Set and reset conditions cannot use complex expressions.**

- An if statement must occur at the top level of the always block.**



Limitations of D Flip-Flop Inferences

Enabling Productivity

// Unsynthesizable Examples

```
always @(posedge clk[1])
```

Invalid: it uses an indexed expression

```
always @(posedge clk and negedge reset_bus)
```

```
if (!reset_bus[1])
```

Invalid: it uses a bused variable

```
always @(posedge clk and negedge reset)
```

```
if (reset == (1-1))
```

Invalid: it uses a complex expression

```
always @(posedge clk or posedge reset) begin
```

```
# 1;
```

```
if (reset)
```

Invalid: the if statements does not occur at the top level



while Loops Limitations

Enabling Productivity

- ❑ **A while loop creates a conditional branch that must be broken by one of the following statements to prevent combinational feedback.**

- `@(posedge clock)`

- `@(negedge clock)`

```
// Unsupported while loop
always
  while ( x < y )
    x = x + z;
```

```
// Supported while loop
always begin
  begin @(posedge clock)
    while ( x < y )
      begin
        @(posedge clock)
          x = x + z;
      end
  end
end
```



forever Loops Limitations

Enabling Productivity

- ❑ **Infinite loops in Verilog use the keyword forever.**
- ❑ **You must break up an infinite loop with the following statements to prevent combinational feedback.**
 - ☞ **@(posedge clock)**
 - ☞ **@(negedge clock)**

```
//Supported forever Loop
always
  forever
  begin
    @(posedge clock);
    x = x + z;
  end
```



Handling Comparison to X and Z

Enabling Productivity

- ❑ **Comparison to an X or a Z, a warning message is displayed in DC indicating that the comparison always evaluated to false, which might cause simulation to disagree with synthesis.**

```
// Comparison to X Ignored
always begin
    if ( A === 1'bx )
        B = 0;
    else
        B = 1;
end
```



Handling Comparison to X and Z


Enabling Productivity

- ❑ Improper using of case statement might cause synthesis not to agree with simulation.

```
module case_withxz(q, a, b, c, d, sel);  
input a, b, c, d;  
input [1:0] sel;  
output q;  
reg q;
```

```
always @(sel or a or b or c or d)  
case(sel)  
2'b00: q=a;  
2'b0x: q=b;  
2'b10: q=c;  
2'b11: q=d;  
endcase
```

```
endmodule
```

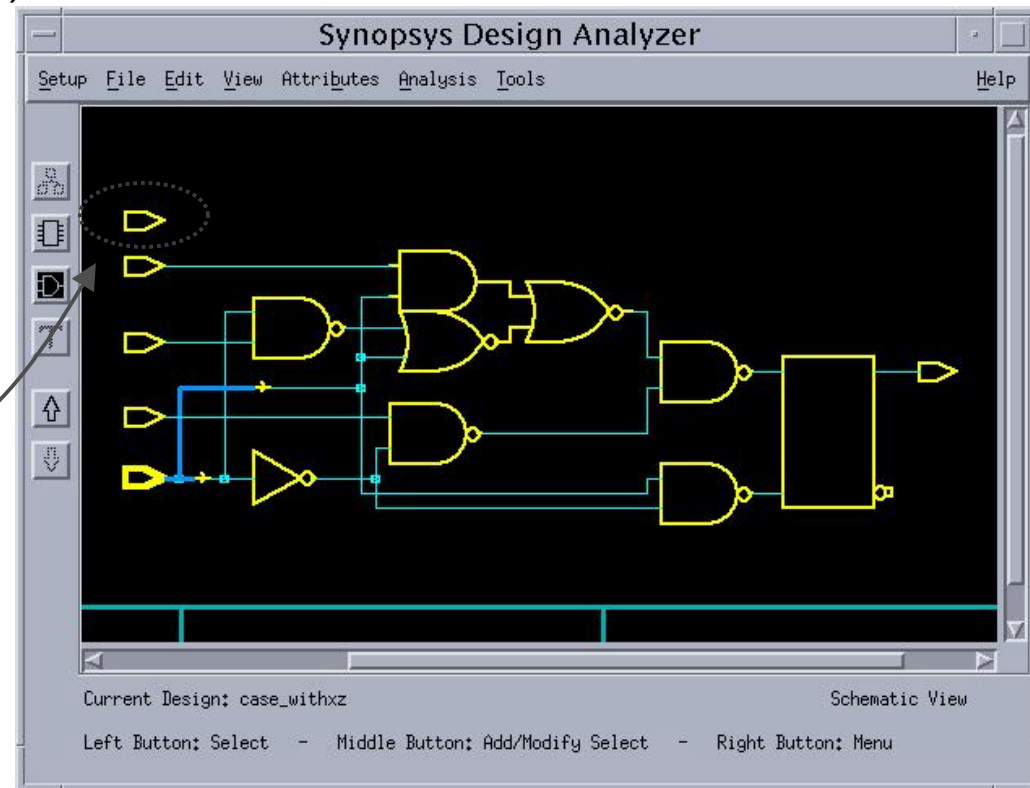



Limitations of Using Delay Specification

Enabling Productivity

- ❑ **You can use delay specification information for modeling, but Design Compiler ignores delay information.**
- ❑ **If the functionality of your circuit depends on the delay information, Design Compiler might create logic whose behavior does not agree with the behavior of the simulated circuit.**

```
module top(a, c, d, clk);  
  reg b;...
```

```
  flip_flop F1(a, clk, c);  
  flip_flop F2(b, clk, d);
```

```
  always @(a or c or d or clk)  
  begin  
    b <= #100 a;  
  end  
endmodule
```




Limitations of Tri-State Inferences

Enabling Productivity

- ❑ **When a variable is registered in the same block in which it is three-stated, HDL Compiler also registers the enable of this type of code.**
 
```
// Three-State Driver with Enable
module ff_3state (DATA, CLK, THREE_STATE, OUT1);
input DATA, CLK, THREE_STATE;
output OUT1;
reg OUT1;
  always @ (posedge CLK) begin
    if (THREE_STATE)
      OUT1 = 1'bz;
    else
      OUT1 = DATA;
  end
endmodule
```






Limitations of Tri-State Inferences

Enabling Productivity

❑ An example for Three-State Driver without Registered Enable

```
// Three-State Driver without Registered Enable
module ff_3state (DATA, CLK, THREE_STATE, OUT1);
input DATA, CLK, THREE_STATE;
output OUT1;
reg OUT1;
reg TEMP;
always @(posedge CLK)
    TEMP = DATA;

 always @(THREE_STATE or TE
    if (THREE_STATE)
        OUT1 = TEMP;
    else
        OUT1 = 1'bz;
endmodule
```





Limitations of Arithmetic Operators

Enabling Productivity

- ❑ **Arithmetic operators perform simple arithmetic on operands. The Verilog arithmetic operators are**
 - **Addition (+)**
 - **Subtraction (-)**
 - **Multiplication (*)**
 - **Division (/)**
 - **Modules (%)**
- ❑ **HDL Compiler requires that / and % operators have constant-valued operands.**



Limitations of casex and casez Statements

Enabling Productivity

- ❑ HDL Compiler allows ?, z, x bits in casex items in a casex statement, but not in casex expressions.
- ❑ HDL Compiler allows ?, z in casez items in a casez statements, but not in casez expressions.

```
// Invalid casex Expression  
express = 3'bxz?;  
...  
//illegal testing of an expression  
casex (express)  
...  
Endcase
```

```
// Invalid casez Expression  
express = 1'bz;  
...  
//illegal testing of an expression  
casez (express)  
...  
Endcase
```



Case Statement: Full Case


Enabling Productivity

- ❑ A case statement is full if all possible branches are specified.
- ❑ A full case statement does not infer latches.

```
module casetest1(q, a, b, c, d, sel);  
input a, b, c, d;  
input [1:0] sel;  
output q;  
reg q;
```

```
always @(sel or a or b or c or d)  
  case(sel)  
    2'b00: q=a;  
    2'b01: q=b;  
    2'b10: q=c;  
    2'b11: q=d;  
  endcase
```

```
endmodule
```

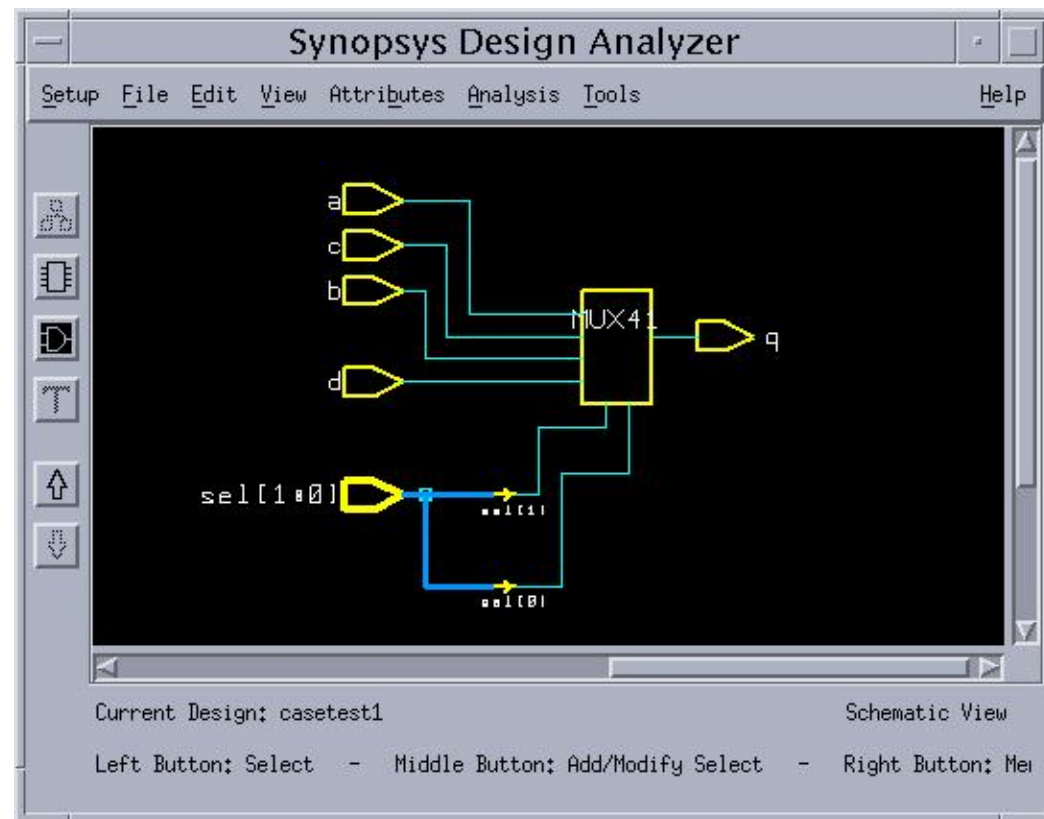




Case Statement: No-full Case

Enabling Productivity

- ❑ A case statement that is not full case infers latches.
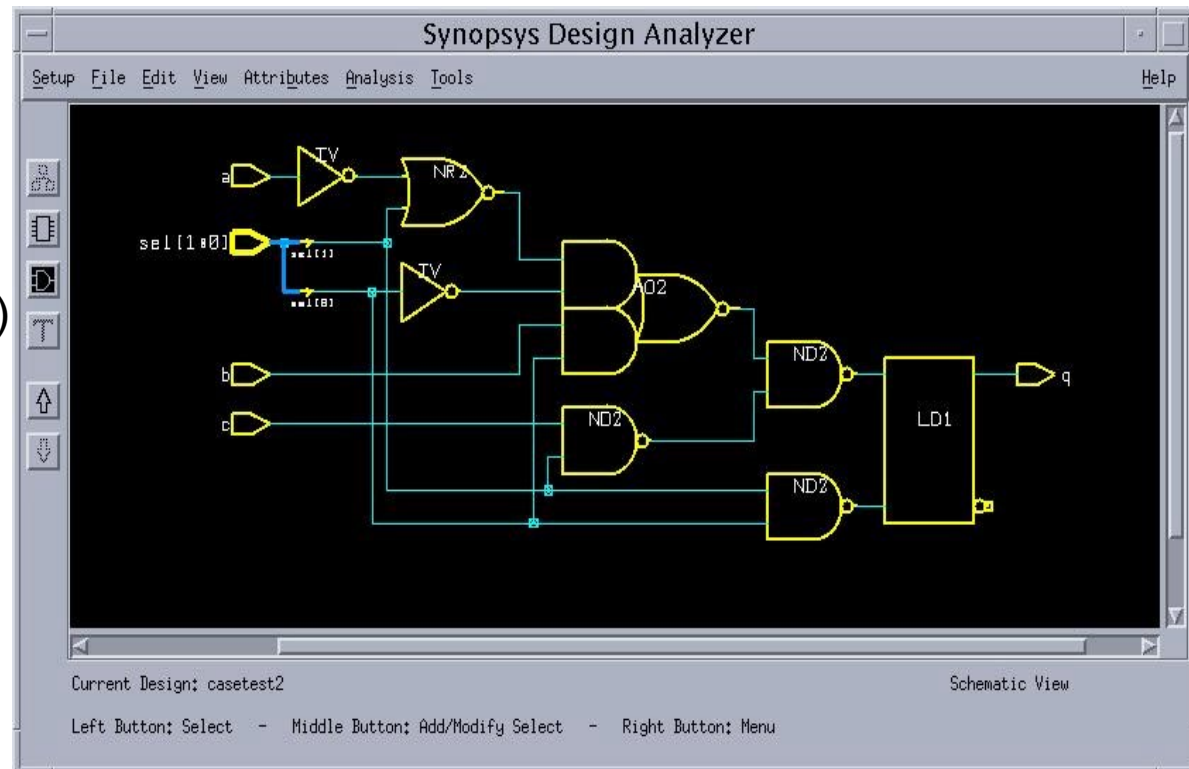
```
module casetest2(q, a, b, c, sel);  
input a, b, c;  
input [1:0] sel;  
output q;  
reg q;  
  
always @(sel or a or b or c)  
case(sel)  
2'b00: q=a;  
2'b01: q=b;  
2'b10: q=c;  
endcase  
  
endmodule
```





Case Statement: Compile Directive


Enabling Productivity

- ❑ A compile directive “`synopsys full_case`” guides Design Compiler not to synthesize latches.

```
module casetest3(q, a, b, c, sel);  
input a, b, c;  
input [1:0] sel;  
output q;  
reg q;
```

```
always @(sel or a or b or c)  
  case(sel) //synopsys full_case  
    2'b00: q=a;  
    2'b01: q=b;  
    2'b10: q=c;  
  endcase
```

```
endmodule
```

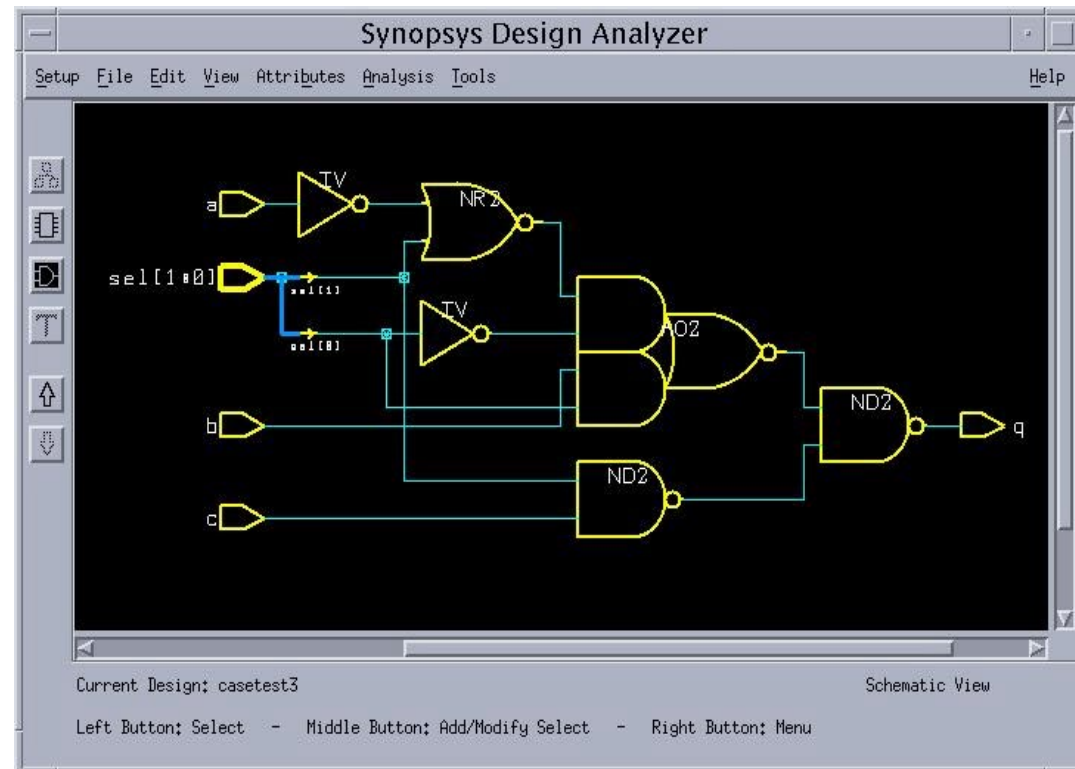



Case Statement: Default Clause


Enabling Productivity

- ❑ A case statement that is not full case with the default clause does not infer latches.

```
module casetest4(q, a, b, c, sel);  
input a, b, c;  
input [1:0] sel;  
output q;  
reg q;
```

```
always @(sel or a or b or c)  
case(sel)  
2'b00: q=a;  
2'b01: q=b;  
2'b10: q=c;  
default: q=a;  
endcase
```

```
endmodule
```

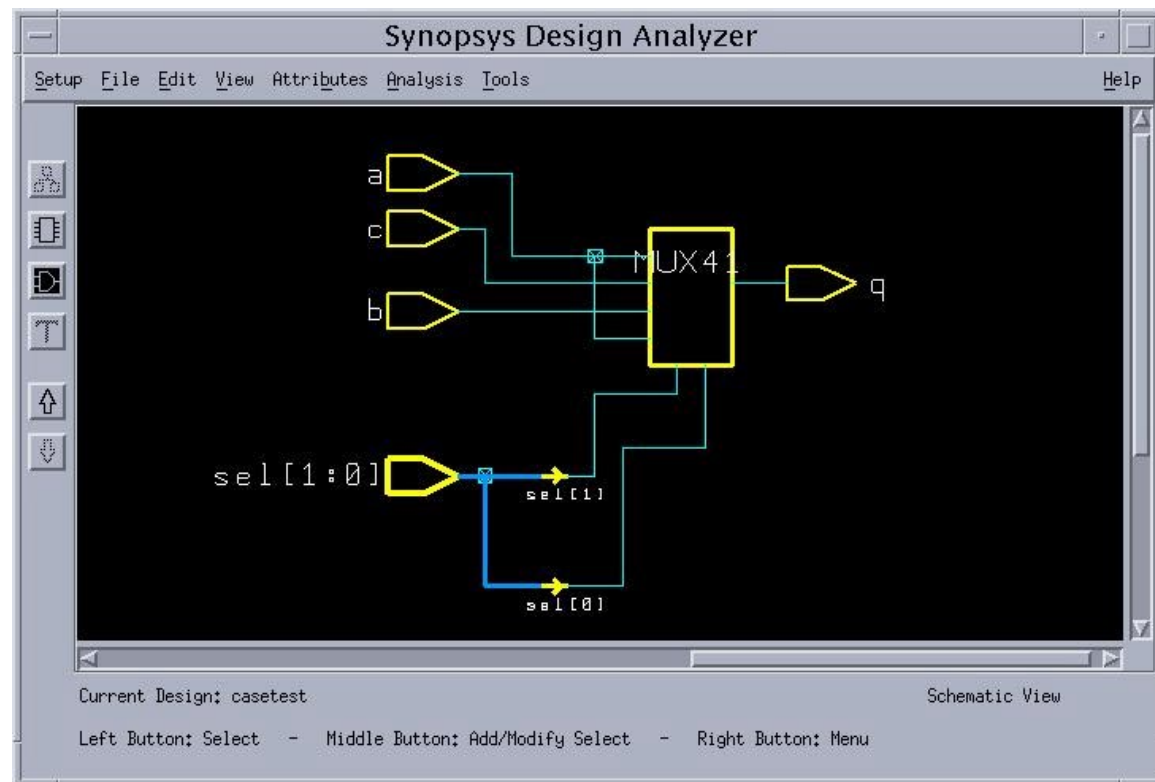



Case Statement: with Priority Encoder


Enabling Productivity

- ❑ A case statement is parallel case if no case items overlap.
- ❑ In the following example, a priority encoder is synthesized.

```
module casetest5(q, a, b);  
input [1:0] a, b;  
output [1:0] q;  
reg [1:0] q;
```

```
always @(a or b)  
case(2'b10)  
a: q = 2'b10;  
b: q = 2'b01;  
endcase
```

```
endmodule
```

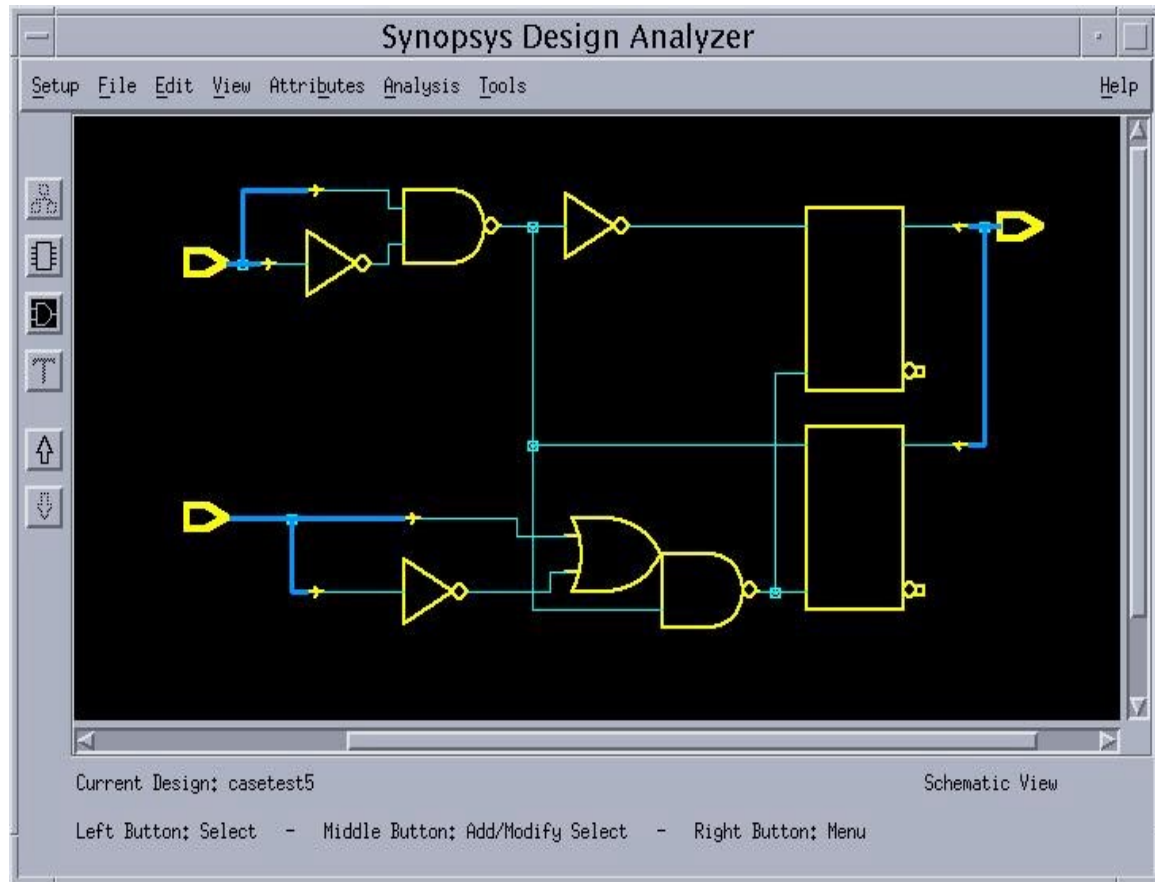




Case Statement: without Priority Encoder

Enabling Productivity

- ❑ A compiler directive “synopsys parallel_case” guides Design Compiler not to synthesize a priority encoder.
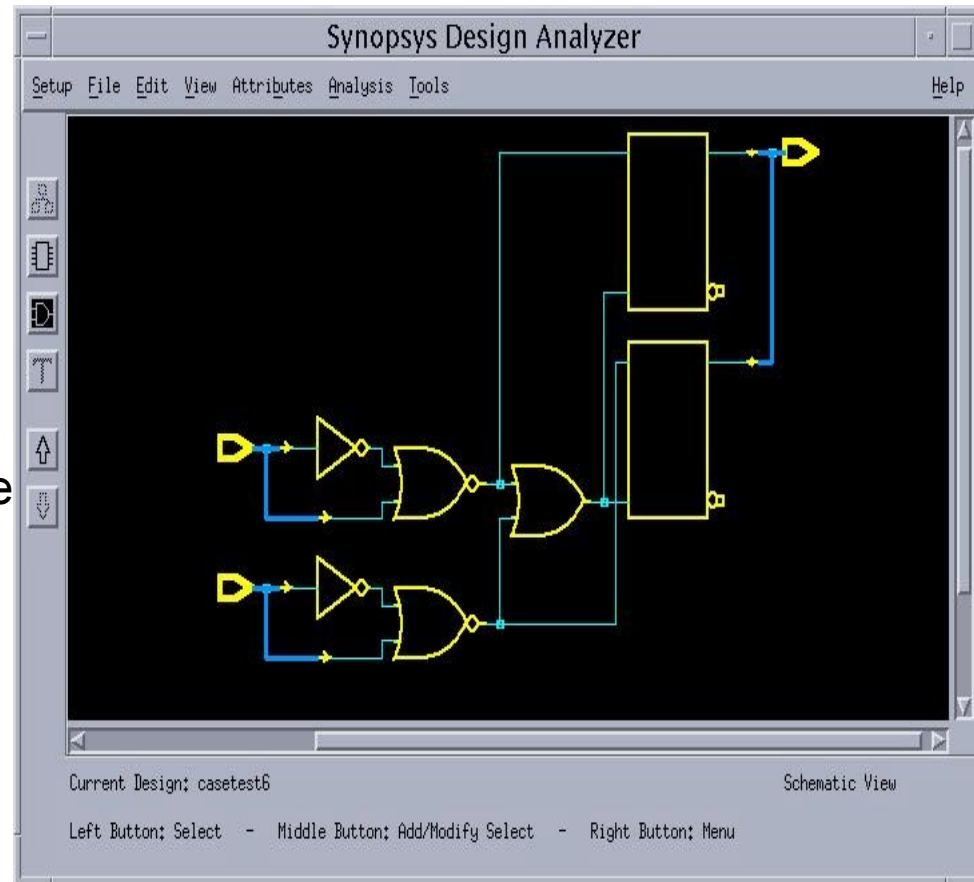
```
module casetest6(q, a, b);  
input [1:0] a, b;  
output [1:0] q;  
reg [1:0] q;  
  
always @(a or b)  
  case(2'b10) //synopsys parallel_case  
    a: q = 2'b10;  
    b: q = 2'b01;  
  endcase  
  
endmodule
```






SR Latch

Enabling Productivity
 
```
module sr_latch (SET, RESET, Q);  
input SET, RESET;  
output Q;  
reg Q;  
  
//synopsys async_set_reset "SET, RESET"  
always @(RESET or SET)  
    if (~RESET)  
        Q = 0;  
    else if (~SET)  
        Q = 1;  
  
endmodule
```






Latch Inference Using an if Statement

Enabling Productivity

```
// Latch Inference Using an if Statement
always @ (DATA or GATE) begin
  if (GATE) begin
    Q = DATA;
  end
end
```

```
// Avoiding Latch Inference
always @ (DATA, GATE) begin
  Q = 0;
  if (GATE)
    Q = DATA;
end
```
 
```
// Another Way to Avoid Latch Inference
always @ (DATA, GATE) begin
  if (GATE)
    Q = DATA;
  else
    Q = 0;
end
```



D Latch




D Latch with Asynchronous Set

Enabling Productivity

```
// D Latch with Asynchronous Set
module d_latch_async_set (GATE, DATA, SET, Q);
input GATE, DATA, SET;
output Q;
reg Q;

 //synopsys async_set_reset "SET"
always @(GATE or DATA or SET)
  if (~SET)
    Q = 1'b1;
  else if (GATE)
    Q = DATA;
endmodule
```



Ps. Because the target technology library does not contain a latch with an asynchronous set, Design Compiler synthesizes the set logic, using combinational logic.




D Latch with Asynchronous Reset

Enabling Productivity

```
// D Latch with Asynchronous Reset
module d_latch_async_reset (RESET, GATE, DATA,
Q);
input RESET, GATE, DATA;
output Q;
reg Q;

 //synopsys async_set_reset "RESET"
always @ (RESET or GATE or DATA)
  if (~RESET)
    Q <= 1'b0;
  else if (GATE)
    Q <= DATA;
endmodule
```






D Latch with Asynchronous Set and Reset

Enabling Productivity

```
// D Latch with Asynchronous Set and Reset
module d_latch_async (GATE, DATA, RESET, SET, Q);
input GATE, DATA, RESET, SET;
output Q;
reg Q;

 // synopsys async_set_reset "RESET, SET"
// synopsys one_cold "RESET, SET"
always @ (GATE or DATA or RESET or SET)
begin : infer
  if (!SET)
    Q <= 1'b1;
  else if (!RESET)
    Q <= 1'b0;
  else if (GATE)
    Q <= DATA;
end
```






Simple D Flip-Flop

Enabling Productivity


```
// Positive Edge-Triggered D Flip-Flop
module dff_pos (DATA, CLK, Q);
input DATA, CLK;
output Q;
reg Q;

 always @(posedge CLK)
    Q <= DATA;
endmodule
```



```
// Negative Edge-Triggered D Flip-Flop
module dff_neg (DATA, CLK, Q);
input DATA, CLK;
output Q;
reg Q;

 always @(negedge CLK)
    Q <= DATA;
endmodule
```






D Flip-Flop with Asynchronous Set

Enabling Productivity

```
// D Flip-Flop with Asynchronous Set
module dff_async_set (DATA, CLK, SET, Q);
input DATA, CLK, SET;
output Q;
reg Q;

 always @(posedge CLK or negedge SET)
  if (~SET)
    Q <= 1'b1;
  else
    Q <= DATA;
endmodule
```






D Flip-Flop with Asynchronous Reset

Enabling Productivity

```
// D Flip-Flop with Asynchronous Reset
module dff_async_reset (DATA, CLK, RESET, Q);
input DATA, CLK, RESET;
output Q;
reg Q;

 always @(posedge CLK or posedge RESET)
  if (RESET)
    Q <= 1'b0;
  else
    Q <= DATA;
endmodule
```






D Flip-Flop with Asynchronous Set and Reset

Enabling Productivity

```
// D Flip-Flop with Asynchronous Set and Reset
module dff_async (RESET, SET, DATA, Q, CLK);
input CLK;
input RESET, SET, DATA;
output Q;
reg Q;

 // synopsys one_hot "RESET, SET"
always @(posedge CLK or posedge RESET or posedge SET)
  if (RESET)
    Q <= 1'b0;
  else if (SET)
    Q <= 1'b1;
  else
    Q <= DATA;
endmodule
```






D Flip-Flop with Synchronous Set

Enabling Productivity

```
// D Flip-Flop with Synchronous Set
module dff_sync_set (DATA, CLK, SET, Q);
input DATA, CLK, SET;
output Q;
reg Q;

 //synopsys sync_set_reset "SET"
always @(posedge CLK)
  if (SET)
    Q <= 1'b1;
  else
    Q <= DATA;
endmodule
```






D Flip-Flop with Synchronous Reset

Enabling Productivity

```
// D Flip-Flop with Synchronous Reset
module dff_sync_reset (DATA, CLK, RESET, Q);
input DATA, CLK, RESET;
output Q;
reg Q;

 //synopsys sync_set_reset "RESET"
always @(posedge CLK)
  if (~RESET)
    Q <= 1'b0;
  else
    Q <= DATA;
endmodule
```





D Flip-Flop with Synchronous and Asynchronous Load

Enabling Productivity

```
// D Flip-Flop with Synchronous and Asynchronous Load
module dff_a_s_load (ALOAD, SLOAD, ADATA, SDATA, CLK, Q);
input ALOAD, ADATA, SLOAD, SDATA, CLK;
output Q;
reg Q;

always @ (posedge CLK or posedge ALOAD)
  if (ALOAD)
    Q <= ADATA;
  else if (SLOAD)
    Q <= SDATA;
endmodule
```

