

Low-Power DFE Design

Sameh Ibrahim and Behzad Razavi
Electrical Engineering Department
University of California, Los Angeles
(JSSC, June 2011)

Outline


- **Motivation**
- **Background**
- **Scaling limits of DFEs**
- **Proposed architecture**
- **Design of building blocks**
- **Experimental results**

Equalizer Categories



- TX vs. RX Equalization




- Digital vs. Analog

 

- Linear vs. Non-Linear

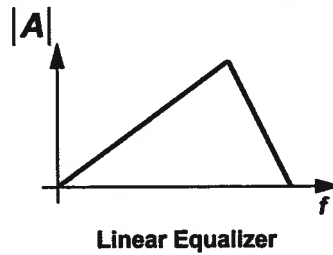 

Linear Equalizer

 


3

Prior Art

Reference	Bit Rate	CMOS	Loss	Topology
[ChenISCC09]	10 Gb/s	32 nm	10 dB	4-Taps integrating DFE
[LiuISCC09]	10 Gb/s	65 nm	23.2 dB	DFE-IIR
[HidakaISCC09]	10.3 Gb/s	90 nm	35.8 dB	Linear equalizer + 1-Tap Speculative DFE
[BulzacchelliISCC09]	11.1 Gb/s	65 nm	16 dB	1-Tap speculative DFE + 4-Tap DFE
[LiaoISCC08]	40 Gb/s	90 nm	10 dB	Linear Equalizer
[LuVLSI08]	40 Gb/s	0.13 μ m	14 dB	Linear Equalizer
[LeeJSSC06]	20 Gb/s	0.13 μ m	20 dB	Linear Equalizer
[SunagaISCC09]	18 Gb/s	90 nm	14 dB	4-Taps DFE, 1 st tap assisted by CDR
[TurkerVLSI09]	19 Gb/s	90 nm	11 dB	1-Tap speculative DFE
[WangVLSI09]	21 Gb/s	65 nm	11.7 dB	Linear equalizer + 1-Tap DFE

4

Decision Feedback Equalizer

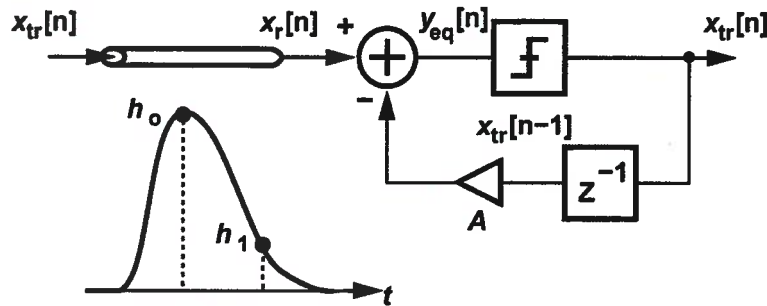

$$x_r[n] = h_0 x_{tr}[n] + h_1 x_{tr}[n-1]$$

$$y_{eq}[n] = x_r[n] - A x_{tr}[n-1]$$


$$= h_0 x_{tr}[n] + h_1 x_{tr}[n-1] - A x_{tr}[n-1]$$

- ☺ Corrects both loss and reflections
- ☹ High power (especially, digital)
- ☺ Does not increase cross-talk
- ☹ Tight timing constraints

5


Comparison of Linear Eq. and DFE

Linear Equalizer

 

- No feedback → high speed
- But cannot compensate for notches in freq. response.
- Amplifies noise and crosstalk.

DFE

 

- Cancels tail of impulse response.
- But feedback delay limits the speed.
- Clips noise and crosstalk.


→ Use ~5-10 dB of linear equalization followed by a DFE.

6

- Direct Full-Rate DFE
- Unrolled Full-Rate DFE
- Direct Half-Rate DFE
- Multiplexed-Half-Rate DFE
- Unrolled Half-Rate DFE


7

Direct and Unrolled Full-Rate DFEs

 


8

Direct and MUXed Half-Rate DFE

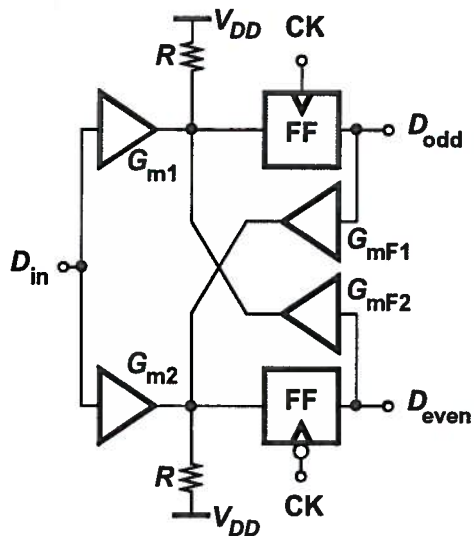

$$t_{cq} + t_{setup} + t_{FB} < UI$$

 


$$t_{cq,FF} + t_{setup} + t_{p,MUX} + t_{FB} < UI$$

[Payne, JSSC, Dec.05]

9

Half-Rate Unrolled DFE


 


$$t_{cq,FF} + t_{setup} + t_{cq,MUX} < UI$$

[Bulzacchelli, JSSC, Dec.06]

10

  - How far can we reduce the power dissipation of a DFE?
- How do we systematically scale without degrading:
 - Speed
 - Voltage Headroom
 - Gain
- Can't apply reverse scaling:





[Gondi & Razavi, JSSC, Sep. 07]

11


Scaling Methodology

  - Scale:
 - Transistor Widths by M
 - Bias Currents by M
 - Load Resistors and Inductors by 1/M.
- As a result,
- Speed relatively constant if load stage (e. g., CDR) can be driven.
 - Voltage headroom and gain are constant.
 - Power dissipation falls by 1/M.



12

Linear Scaling Limitations

 

- Electronic Noise
- Offset Voltage
- Flipflop Sensitivity

13

Effect of Noise on BER



- With only noise present:

$$BER = Q \left(\frac{V_{pp,eq}}{2\sqrt{V_{n,eq}^2}} \right)$$


- For $BER = 10^{-14}$

$$V_{pp,eq}/2\sqrt{V_{n,eq}^2} = 7.6$$

What happens if the circuit has offset?

  

14

 

- Half of the bits see an effective peak swing of $V_{pp,eq}/2 - V_{os}$ and the other half $V_{pp,eq}/2 + V_{os}$

$$BER = \frac{1}{2}Q\left(\frac{V_{pp,eq}/2 - V_{os}}{\sqrt{V_{n,eq}^2}}\right) + \frac{1}{2}Q\left(\frac{V_{pp,eq}/2 + V_{os}}{\sqrt{V_{n,eq}^2}}\right) \approx \frac{1}{2}Q\left(\frac{V_{pp,eq}/2 - V_{os}}{\sqrt{V_{n,eq}^2}}\right)$$


15

Effect of FF Sensitivity

- Sensitivity is defined as the minimum input voltage that guarantees regeneration to approximately 80% of the full latch output swing in half clock cycle.

$$V_{sens} = \frac{0.8I_{SS}}{G_{m1}} \exp\left(-\frac{G_{m3}R_D - 1}{2R_DC_Lf_{CK}}\right)$$

 - What happens if the peak input swing is equal to V_{sens} ?




$$BER = \frac{1}{2}Q\left(\frac{V_{pp,eq}/2 - V_{os} - V_{sens}}{\sqrt{V_{n,eq}^2}}\right)$$


$$V_{pp,eq} \geq 15\sqrt{V_{n,eq}^2} + 2(V_{os} + V_{sens})$$

16

Latch Offset: Definition

 


 - Input offset voltage is the voltage that produces no regeneration (i.e., keeps the latch metastable).



17

Latch offset: Abrupt Clock Edge

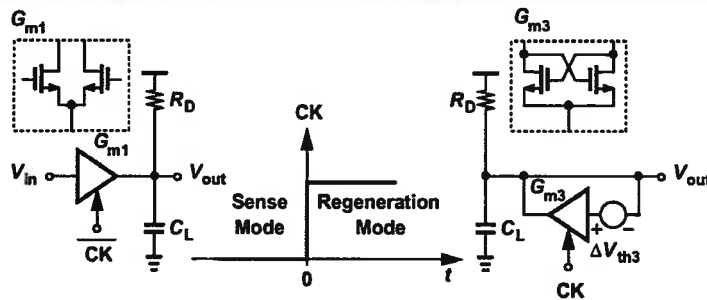

- At the end of sense mode: $V_{out}(0) = G_{m1}R_D V_{in}$

- During regeneration:


$$G_{m3}(V_{out} + \Delta V_{TH3}) = \frac{V_{out}}{R_D} + C_L \frac{dV_{out}}{dt}$$

$$V_{out}(t) = \frac{G_{m3}R_D\Delta V_{TH3}}{G_{m3}R_D - 1} \left(\exp \frac{G_{m3}t}{C_L} \exp \frac{-t}{R_DC_L} - 1 \right) + G_{m1}R_D V_{in} \exp \frac{G_{m3}t}{C_L} \exp \frac{-t}{R_DC_L}$$

- For no regeneration: $\frac{G_{m3}R_D}{G_{m3}R_D - 1} \Delta V_{TH3} = -G_{m1}R_D V_{in} \Rightarrow V_{in} = \frac{-\Delta V_{TH3}}{G_{m1}R_D - \frac{G_{m1}}{G_{m3}}}$

18


Latch Offset: Gradual Clock Edge

 

$$g_{m1}(t) = G_{m1} \sqrt{1 - \frac{\alpha t}{t_r}}$$

$$g_{m3}(t) = G_{m3} \sqrt{\frac{\alpha t}{t_r}}$$

 
$$\alpha = V_{CK,pp}/(\sqrt{2}V_{ov,CK})$$



$$\Rightarrow G_{m3} \sqrt{\frac{\alpha t}{t_r}} (V_{out} + \Delta V_{TH3}) + G_{m1} \sqrt{1 - \frac{\alpha t}{t_r}} V_{in} = \frac{V_{out}}{R_D} + C_L \frac{dV_{out}}{dt}$$

- No closed-form solution
- Use a correction factor:
 
$$V_{in} = \frac{-\Delta V_{TH3}}{G_{m1} R_D - \frac{G_{m1}}{G_{m3}} \exp \frac{(G_{m3} R_D - 2)t_r}{2\alpha R_D C_L}}$$



19

Overall Latch Offset

$$I_1 = \begin{cases} \frac{G_{m1} \Delta V_{TH1}}{G_{m1} \frac{(V_{GS} - V_{TH})_2 \Delta \beta_1}{2 \beta_1}} \\ \frac{I_{SS} \Delta R_D}{2 R_D} \end{cases}$$

$$V_{OS,L}^2 = (\Delta V_{TH1})^2 + \frac{(V_{GS} - V_{TH})_1^2}{4} \left(\frac{\Delta \beta_1}{\beta_1} \right)^2$$

$$+ \frac{\Delta V_{TH3}^2 + \frac{(V_{GS} - V_{TH})_3^2}{4} \left(\frac{\Delta \beta_3}{\beta_3} \right)^2}{\left[G_{m1} R_D - \frac{G_{m1}}{G_{m3}} \exp \frac{(G_{m3} R_D - 2)t_r}{2\alpha R_D C_L} \right]^2}$$

$$+ \left(\frac{\Delta R_D}{R_D} \right)^2 \frac{(V_{GS} - V_{TH})_3^2}{4 \left[G_{m1} R_D - \frac{G_{m1}}{G_{m3}} \exp \frac{(G_{m3} R_D - 2)t_r}{2\alpha R_D C_L} \right]^2}$$


$$+ \left(\frac{\Delta R_D}{R_D} \right)^2 \frac{(V_{GS} - V_{TH})_1^2}{4}$$

$$I_2 = \begin{cases} \frac{G_{m3} \Delta V_{TH3}}{G_{m3} \frac{(V_{GS} - V_{TH})_3 \Delta \beta_3}{2 \beta_3}} \\ \frac{I_{SS} \Delta R_D}{2 R_D} \end{cases}$$

- Analysis applicable to both offset and noise

20

Overall Latch Noise

 




- Input noise voltage is that **random voltage waveform** that keeps the latch metastable.

$$\overline{V_{n,in}^2} = \frac{8kT\gamma B_n}{g_{m1}} + \frac{\frac{8kT\gamma B_n}{g_{m3}} + 8kTR_D B_n}{\left[g_{m1}R_D - \frac{g_{m1}}{g_{m3}} \exp\left(\frac{(g_{m3}R_D - 2)t_r}{2\alpha R_D C_L}\right) \right]^2}$$


21

Scaling Example in 90-nm CMOS

   Reference Design:
10-Gb/s 1-Tap Full-Rate DFE



22

 

- Offset cancellation can help but it also slows down the critical path.
- Drive capability still good.



23

Outline

- Motivation
- Background
- Scaling limits of DFEs
- **Proposed architecture**
- **Design of building blocks**
- **Measurement results**



24

Begin with Two Half-Rate Architectures

  

25

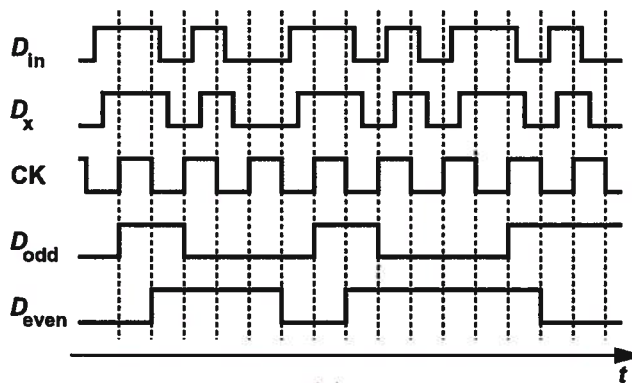 Multiplexed Unrolled Half-Rate (MUHR) Arch.



- Two FFs sample D_x on opposite CK edges.
- MUX2 reproduces full-rate data and selects one of MUX1 inputs.


$$t_{cq,FF} + t_{setup} + t_{cq,MUX1} + t_{p,MUX2} < UI$$

26

- Stack the MUX's.
- Replace flipflops by latches.
- Add gain stage before MUX.
- Use inductive peaking.

27


MUX Stacking

 

- ☺ Removes the delay of one MUX
- ☺ Reduces power consumption and number of inductors.

28

Feedback Simplification

 


☺ Reduces delay of critical path to:

$$t_{D,latch} + t_{d,SMUX} < UI$$


29

Addition of Gain Stages

 


- ☺ Larger swings → Faster current steering
- ☺ Still a better trade-off even with higher taps

30

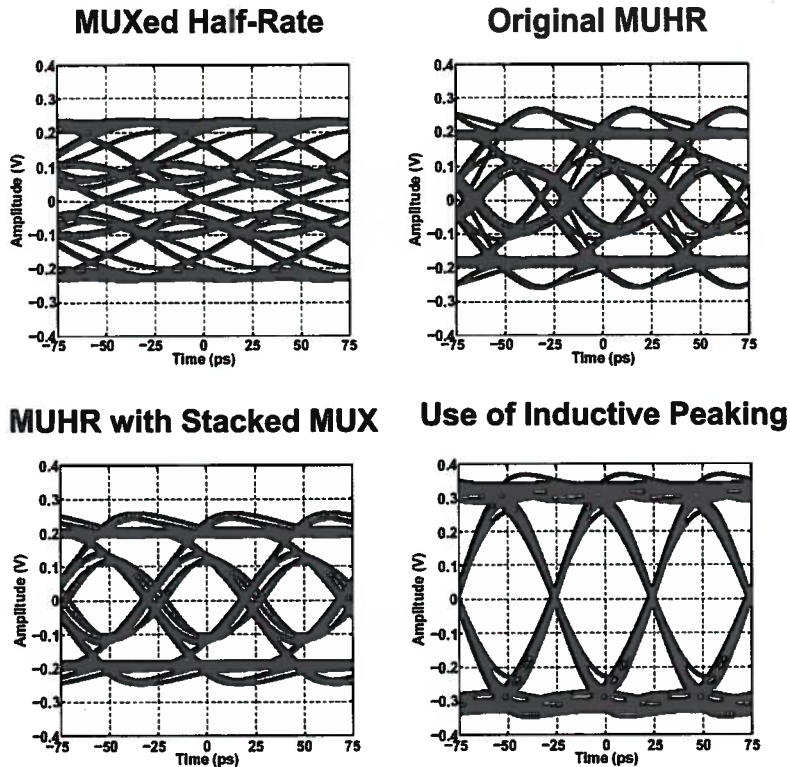

31



Overall Equalizer Architecture

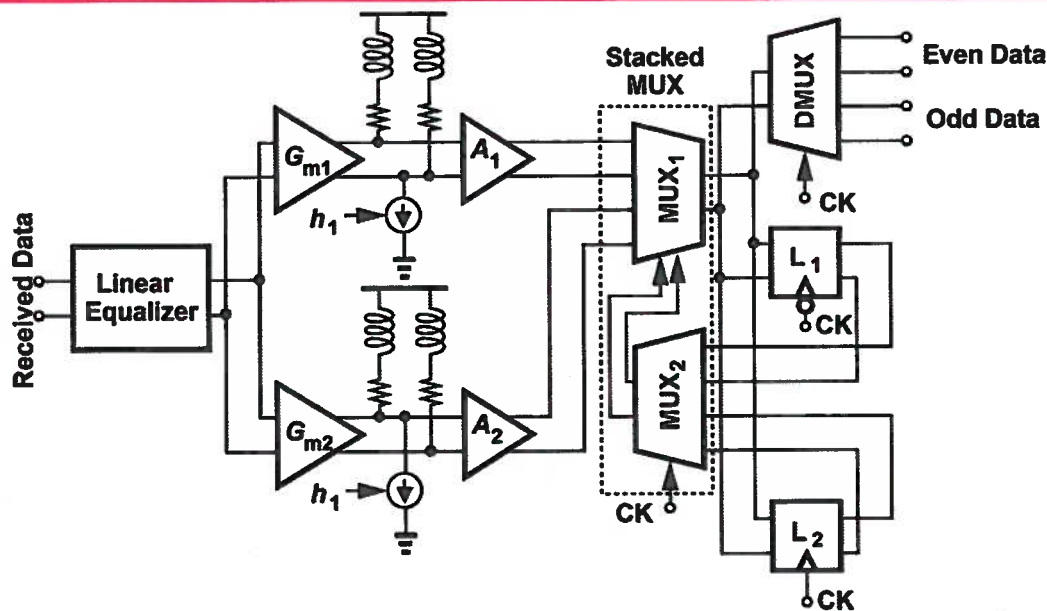

- ☺ Inductive peaking improves speed at summing nodes and latches.
 - ☺ Linear equalizer assists equalization (9 dB of boost required).
- [Ibrahim&Razavi, ISSCC, Feb.10]


32

Linear Equalizer

  


33

Multiplexer and Feedback Latch

 


- Class-AB Clocking
- Inductive Peaking

 


- Class-AB Clocking
- R_1 to shift output CM

34

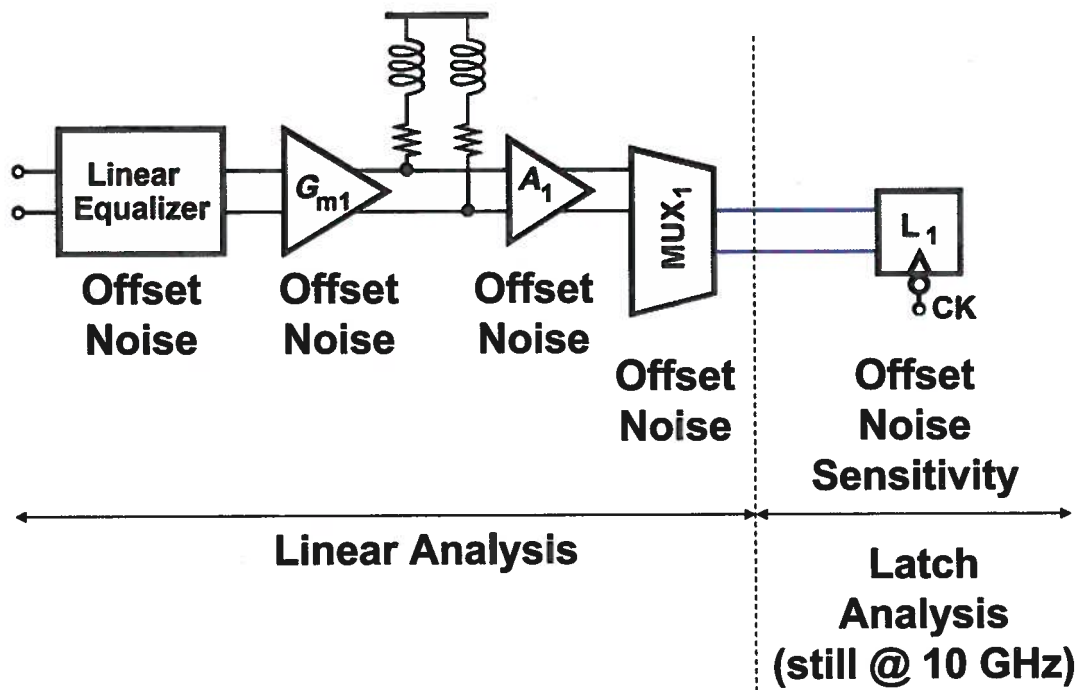



35

Required Eye Opening

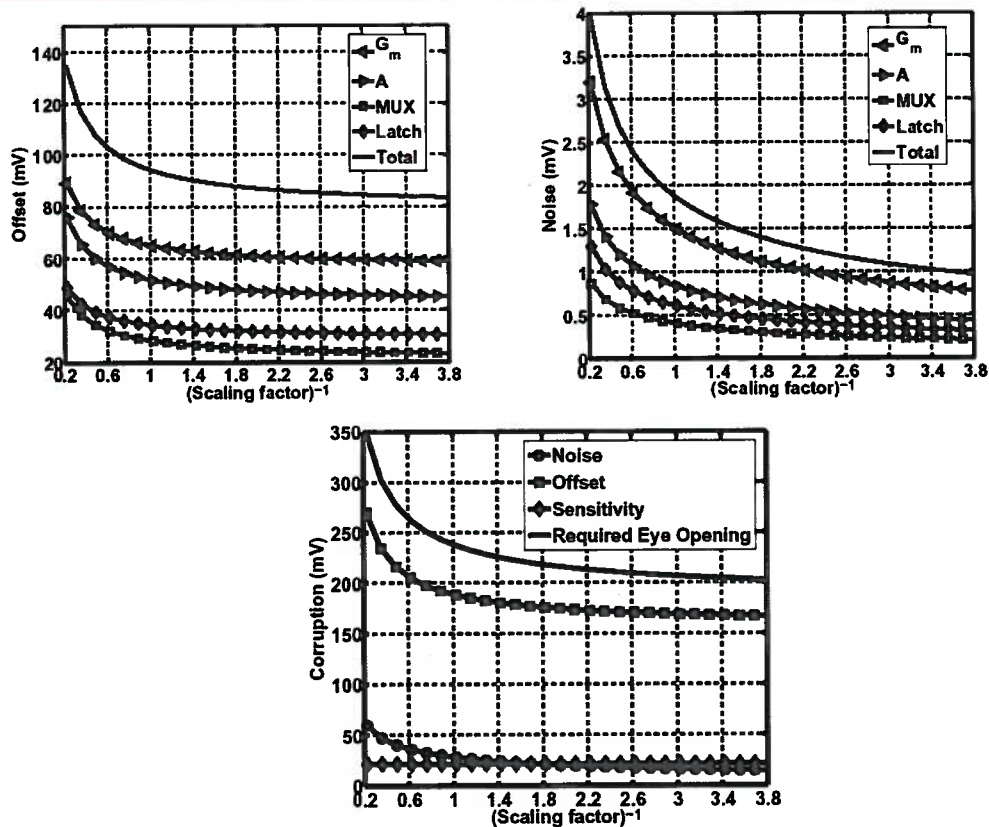


36

Effect of Scaling on Inductors

  


37

Die Photo

 



Fabricated in TSMC 90-nm CMOS technology

38

 

39


Channel Input & Output

  

Horizontal scale: 20 ps/div
Vertical scale: 100 mV/div
20-Gb/s PRBS7 data
18-inch FR4 trace
10-ps input jitter (pp)

40


DMUX Output Eye

 

Horizontal scale: 20 ps/div
Vertical scale: 50 mV/div
20-Gb/s PRBS7 input – 10-Gb/s output

41

Bathtub Curves

 

20-Gb/s PRBS7 data
0.44 UI eye opening for 6-inch FR4 trace
0.36 UI eye opening for 18-inch FR4 trace

42

Block	Power	Delay
Linear Equalizer	5 mW	
Transconductor	$3 \text{ mW} \times 2 = 6 \text{ mW}$	
Tap	$30 \text{ } \mu\text{W} \times \text{digital word}$	
Amplifier	$4 \text{ mW} \times 2 = 8 \text{ mW}$	5 ps
SMUX	5 mW	10 ps
Latch	$5 \text{ mW} \times 2 = 10 \text{ mW}$	17 ps
DMUX	20 mW	

43


BER Estimation

Need to consider:

- Additive Noise
- ISI
- CDR Skew
- Jitter

44

Effect of Noise and ISI

 

• ISI Distribution:

$$g_{ISI}(y) = \frac{1}{2(V_{RX} - V_S)} \quad V_S < y < V_{RX},$$

$$= 0 \quad y < V_S \text{ or } y > V_{RX}$$

• Noise Distribution:

$$g_n(y) = \frac{1}{\sqrt{2\pi}\sigma_n} \exp\left(-\frac{y^2}{2\sigma_n^2}\right)$$

• Probability of Error:

$$P_e = \int_{V_S}^{V_{RX}} g_{ISI}(y) \left[\int_y^{\infty} g_n(v) dv \right] dy$$

$$P_e \approx \frac{\sigma_n}{V_{RX} - V_S} \left(0.0284 \left[Q\left(\frac{V_S}{\sigma_n}\right) - Q\left(\frac{V_{RX}}{\sigma_n}\right) \right] \right.$$


$$+ 0.0118 \left[\frac{V_S}{\sigma_n} \exp\left(\frac{-V_S^2}{2\sigma_n^2}\right) - \frac{V_{RX}}{\sigma_n} \exp\left(\frac{-V_{RX}^2}{2\sigma_n^2}\right) \right]$$

$$\left. + 0.1023 \left[\exp\left(\frac{-V_{RX}^2}{2\sigma_n^2}\right) - \exp\left(\frac{-V_S^2}{2\sigma_n^2}\right) \right] \right).$$


[Gondi,
JSSC, Sep. 07]

45

Effect of Clock Skew

 

$$V_{S,eff} = V_S[-(t/T_1)^2 + 1]$$


 


[Gondi,
JSSC, Sep. 07]

46

- Weight P_e according to clock jitter distribution, $g_{CK}(T_s)$:

$$g_{err}(T_s) = P_e|_{V_S(T_s)} \cdot g_{CK}(T_s)$$

  

[Gondi,
JSSC, Sep. 07]